

AMPLIFIERS


Bipolar Junction Transistors

- It can be use as amplifier and logic switches.
- BJT consists of three terminal:
 - collector : C
 - base : B
 - emitter : E
- Two types of BJT : pnp and npn


TRANSISTOR CONSTRUCTION

- 3 layer semiconductor device consisting:
 - 2 n- and 1 p-type layers of material
→ npn transistor
 - 2 p- and 1 n-type layers of material
→ pnp transistor
- The term bipolar reflects the fact that holes and electrons participate in the injection process into the oppositely polarized material

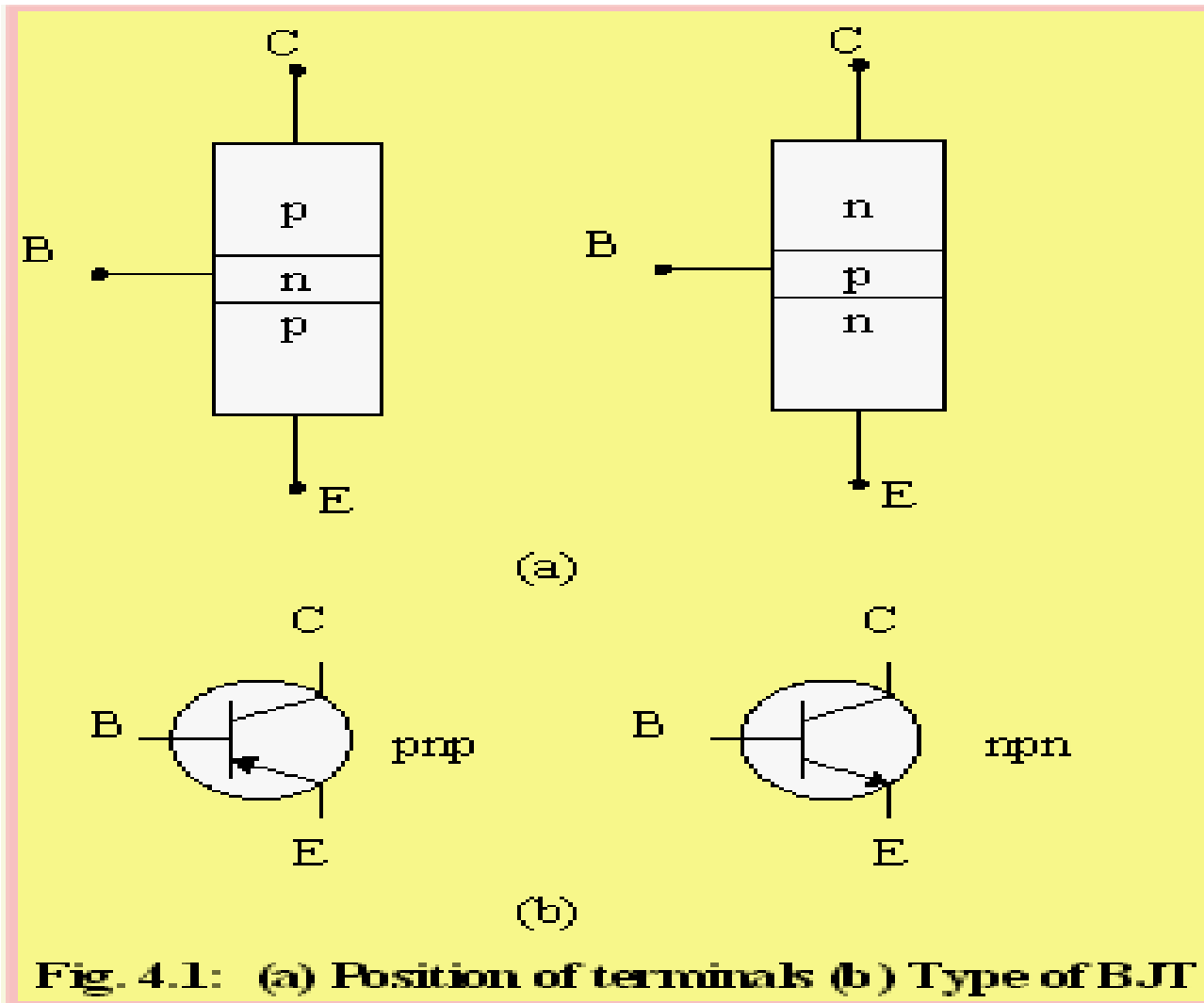Position of the terminals and symbol of BJT.



TRANSISTOR CURRENTS

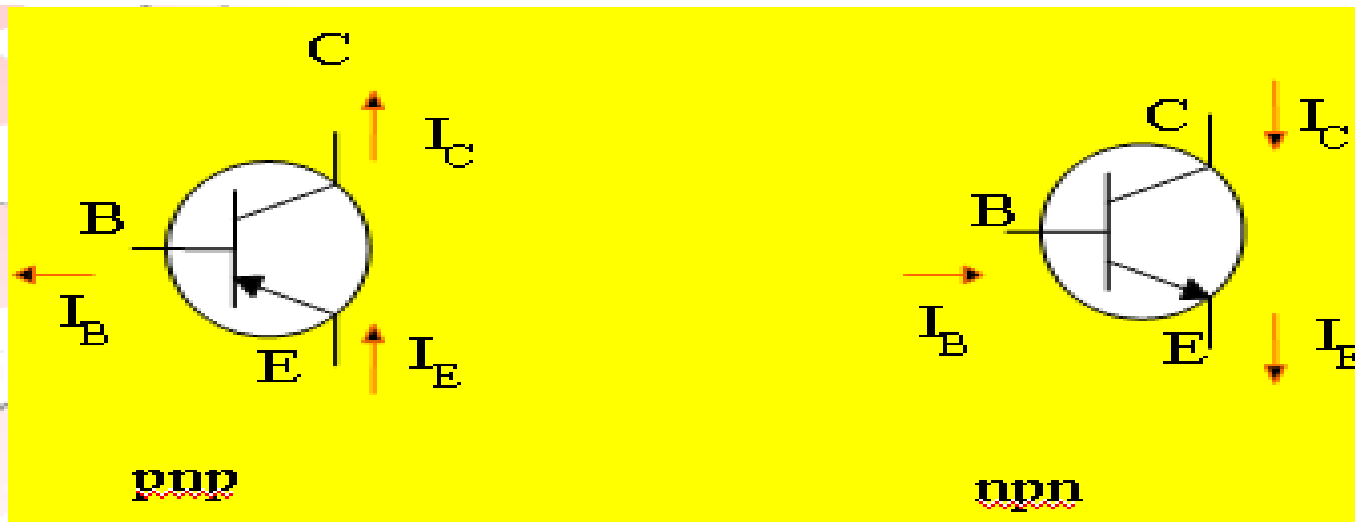

I_C = the collector current

I_B = the base current

I_E = the emitter current


-The arrow indicates the direction of the emitter current:

pnp: E → B


npn: B → E

TRANSISTOR OPERATION

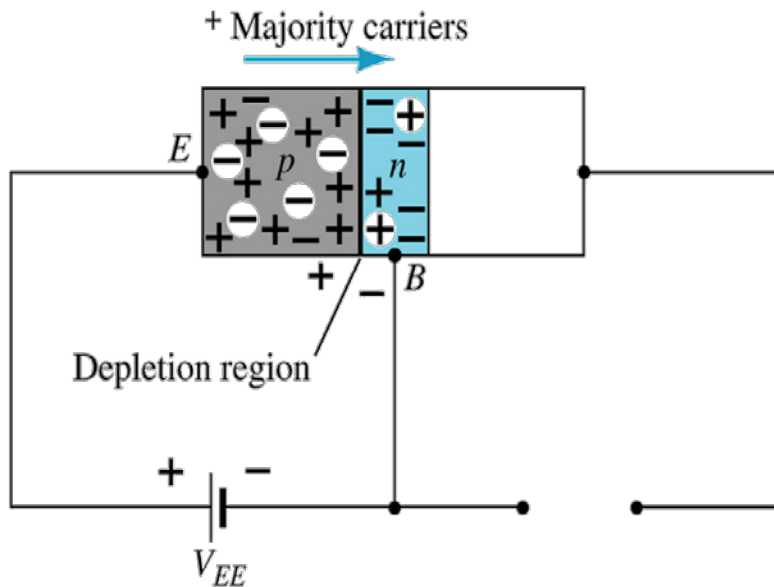
- One p-n junction of a transistor is reverse-biased, whereas the other is forward-biased.



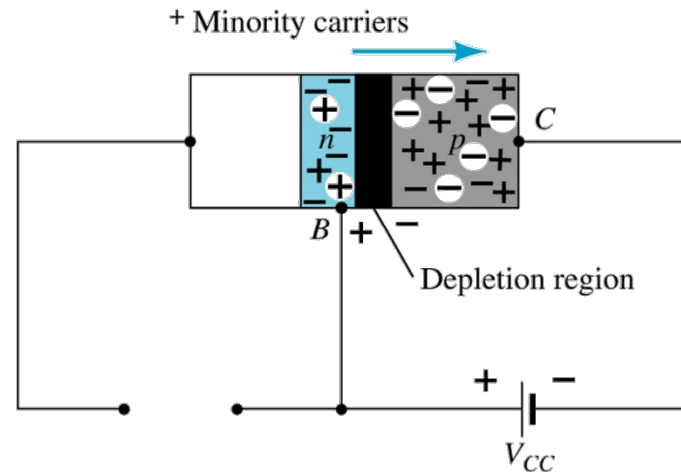**Forward-biased
junction
of a pnp transistor**



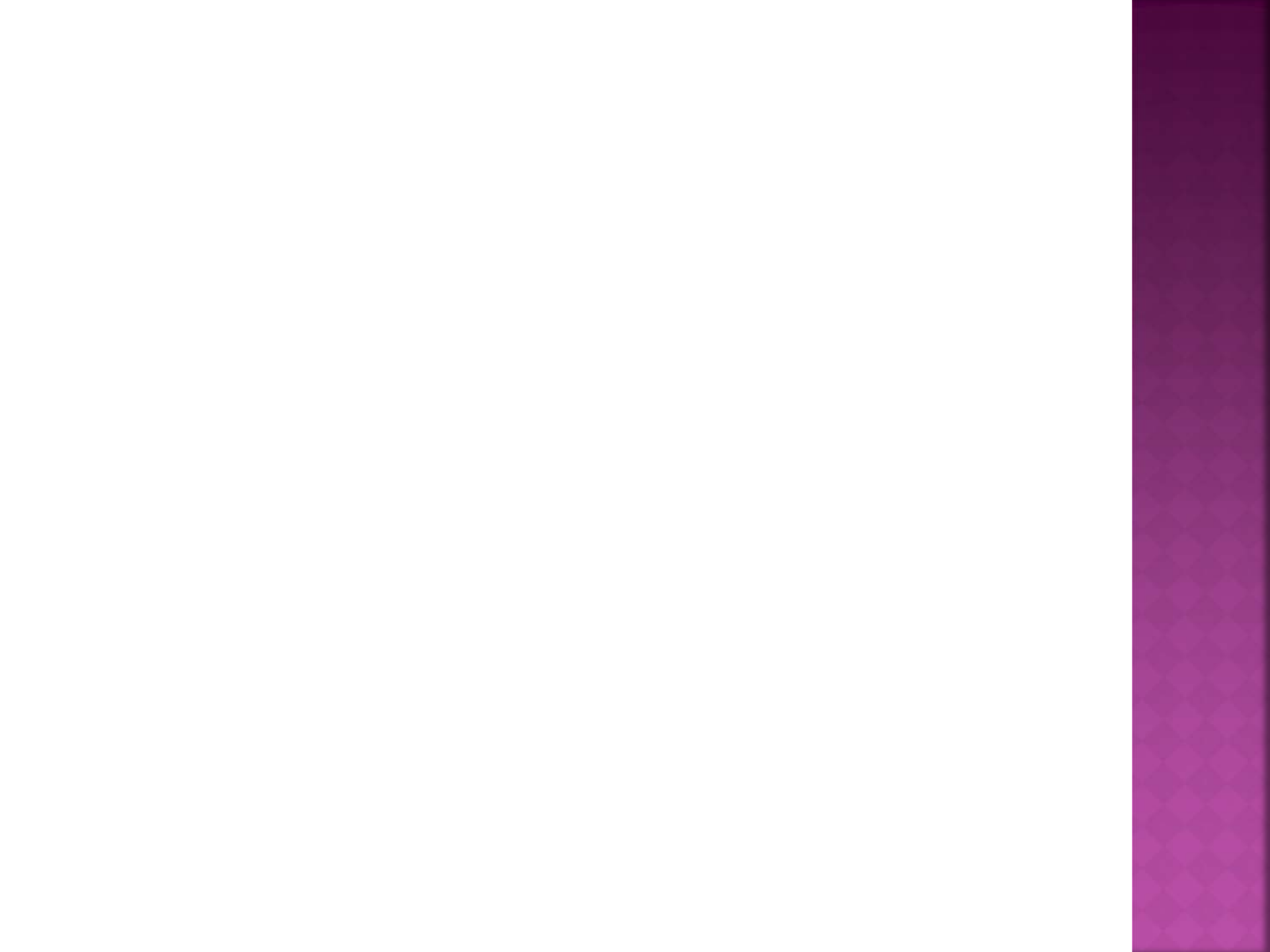**Reverse-biased
junction
of a pnp transistor**


















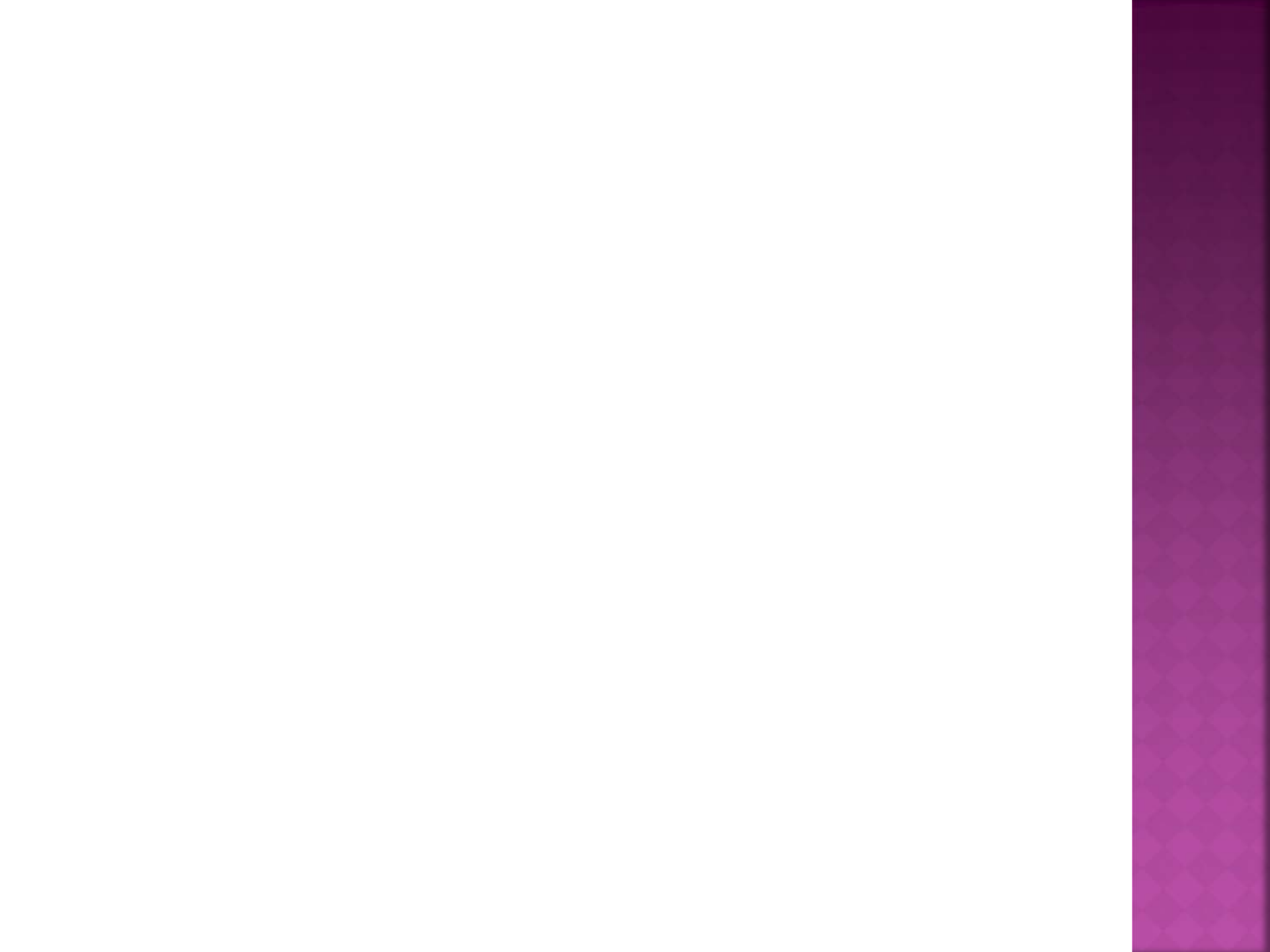
















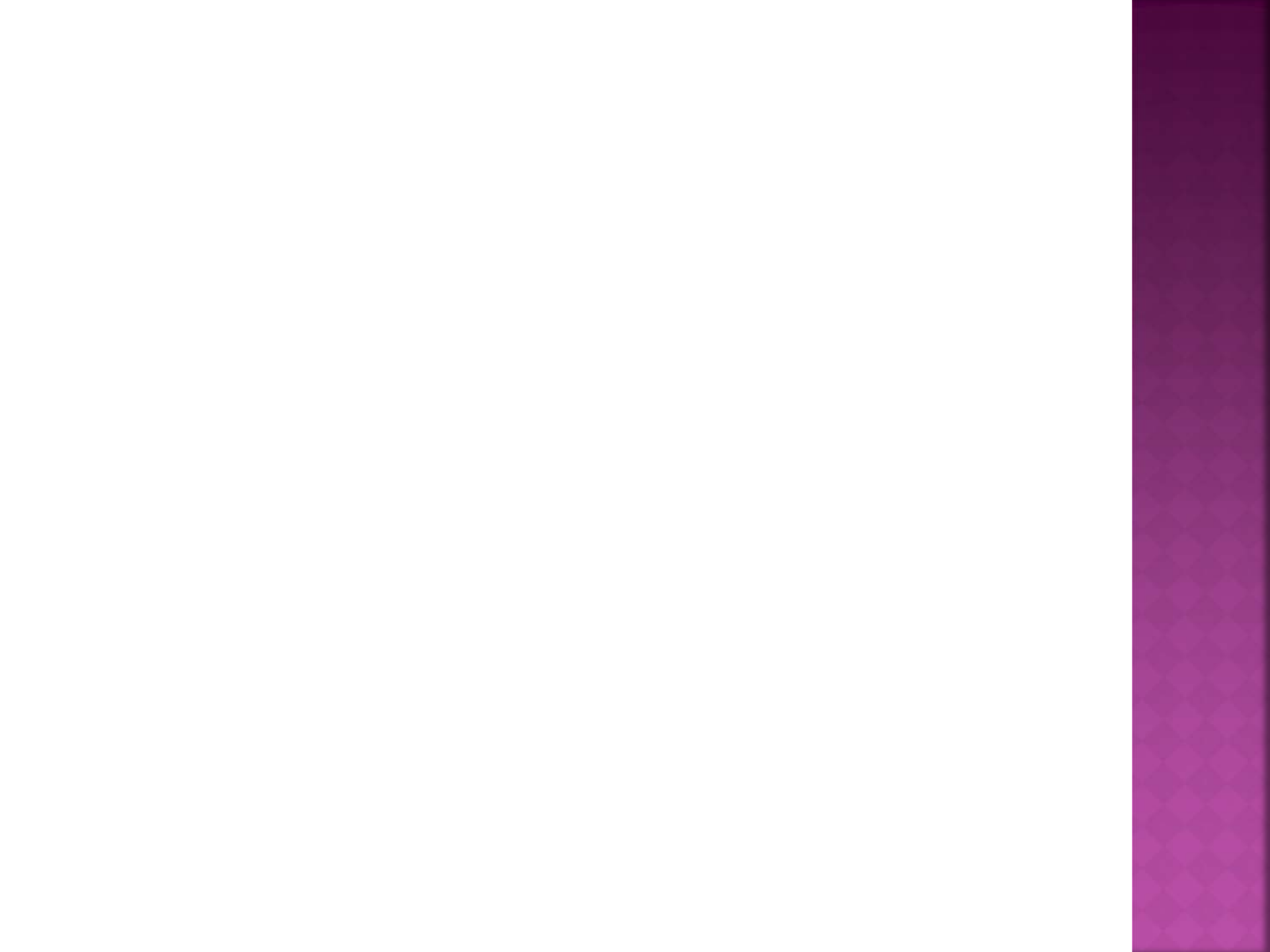
















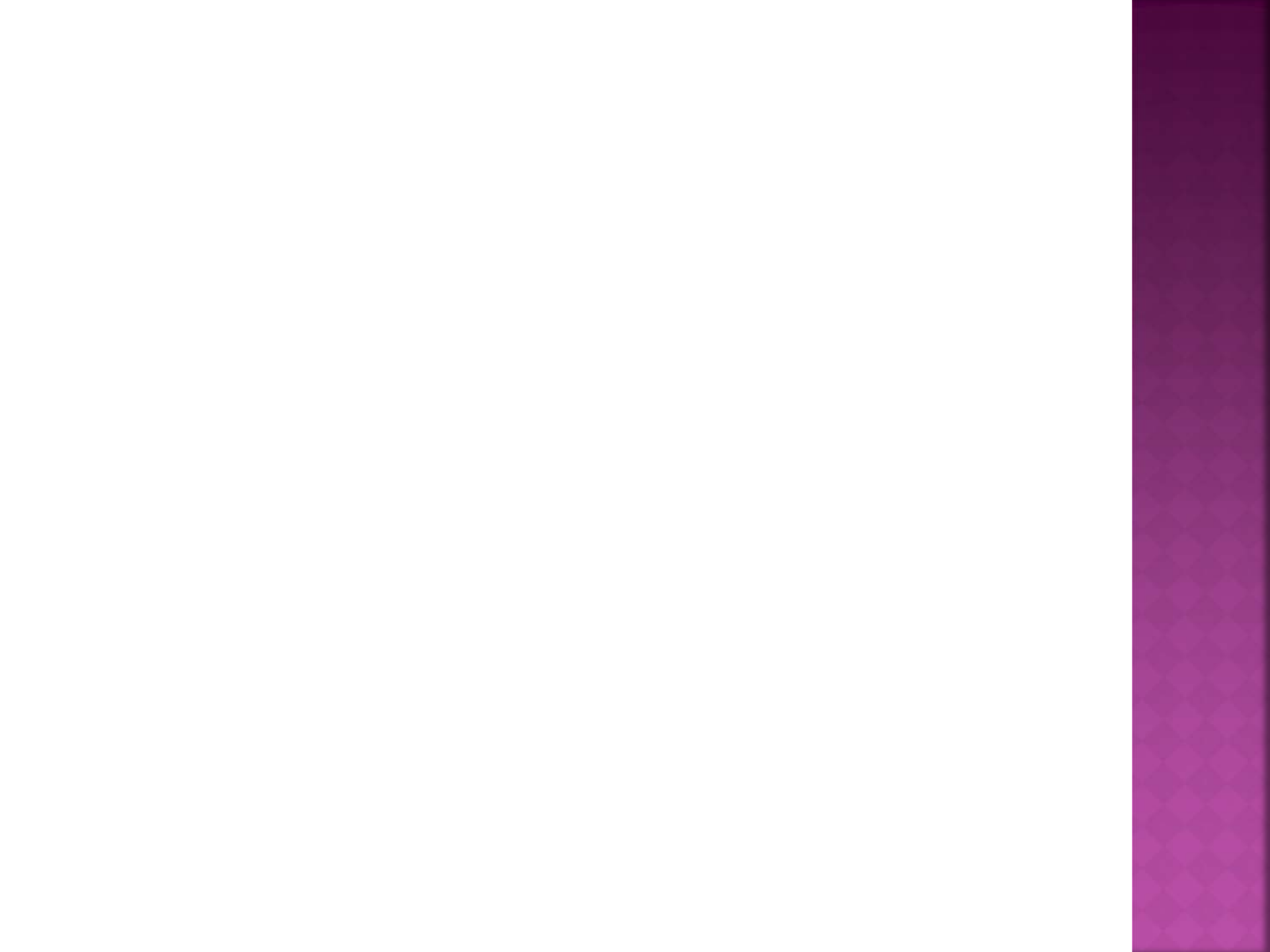
















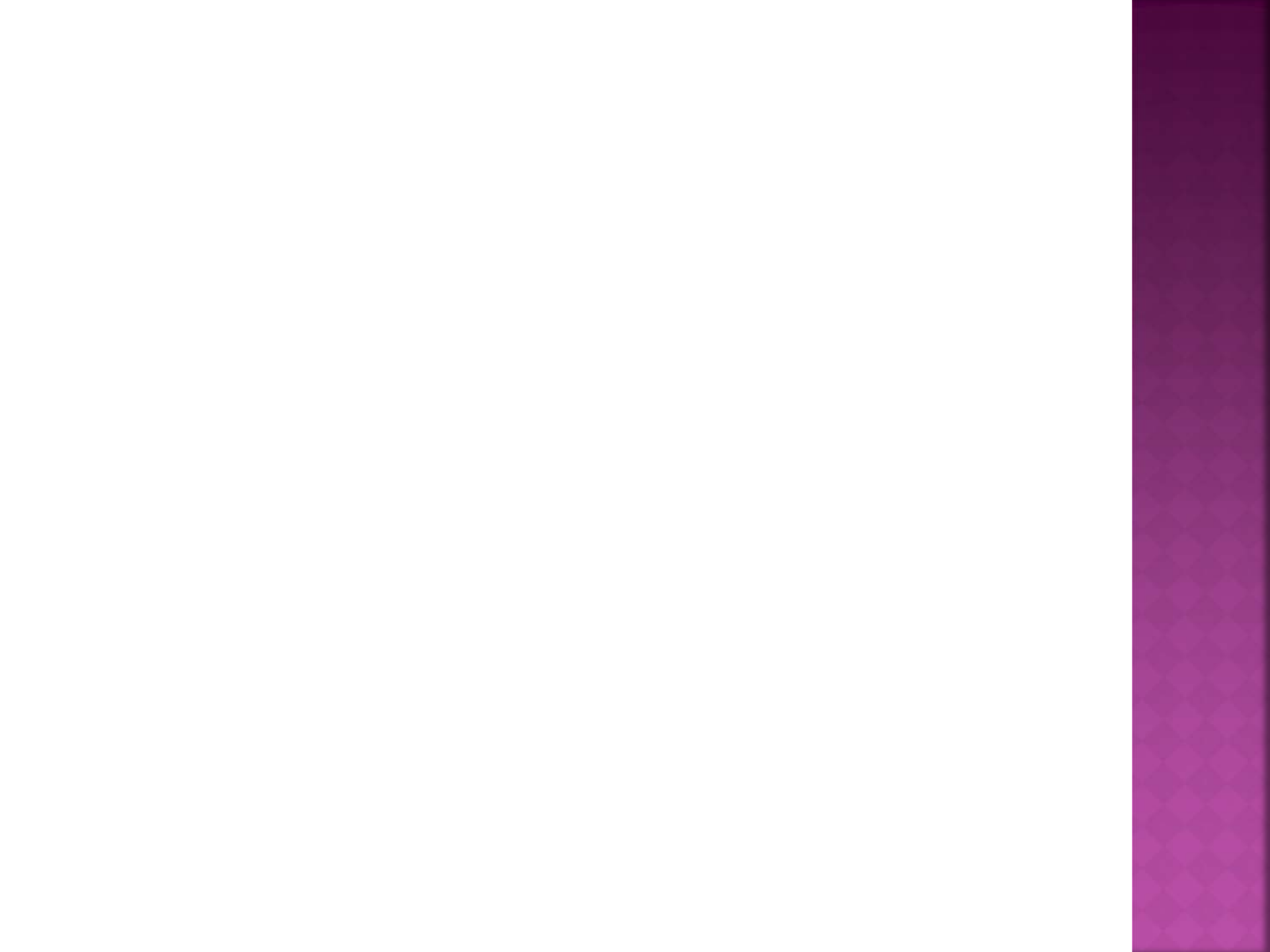
















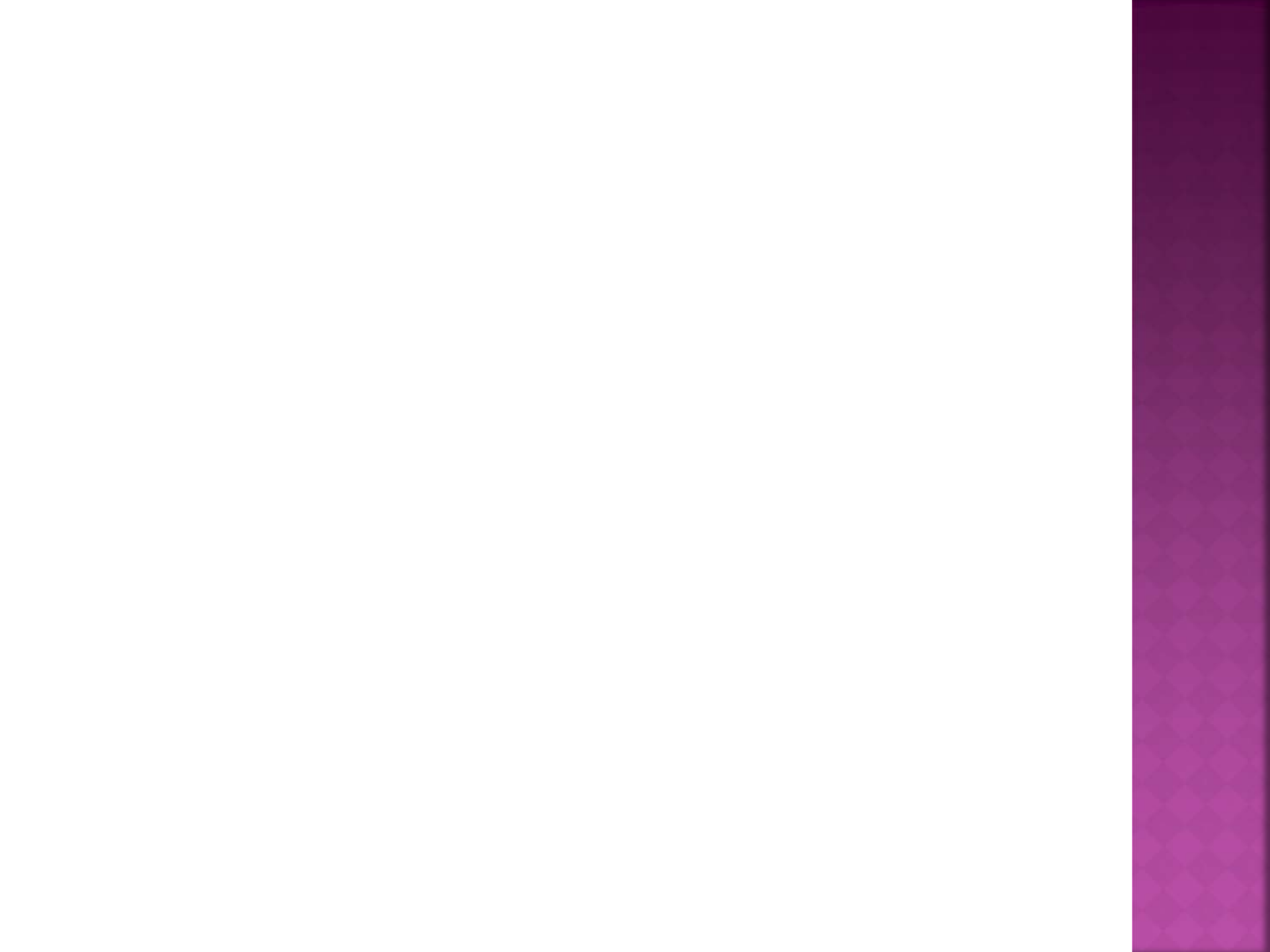
















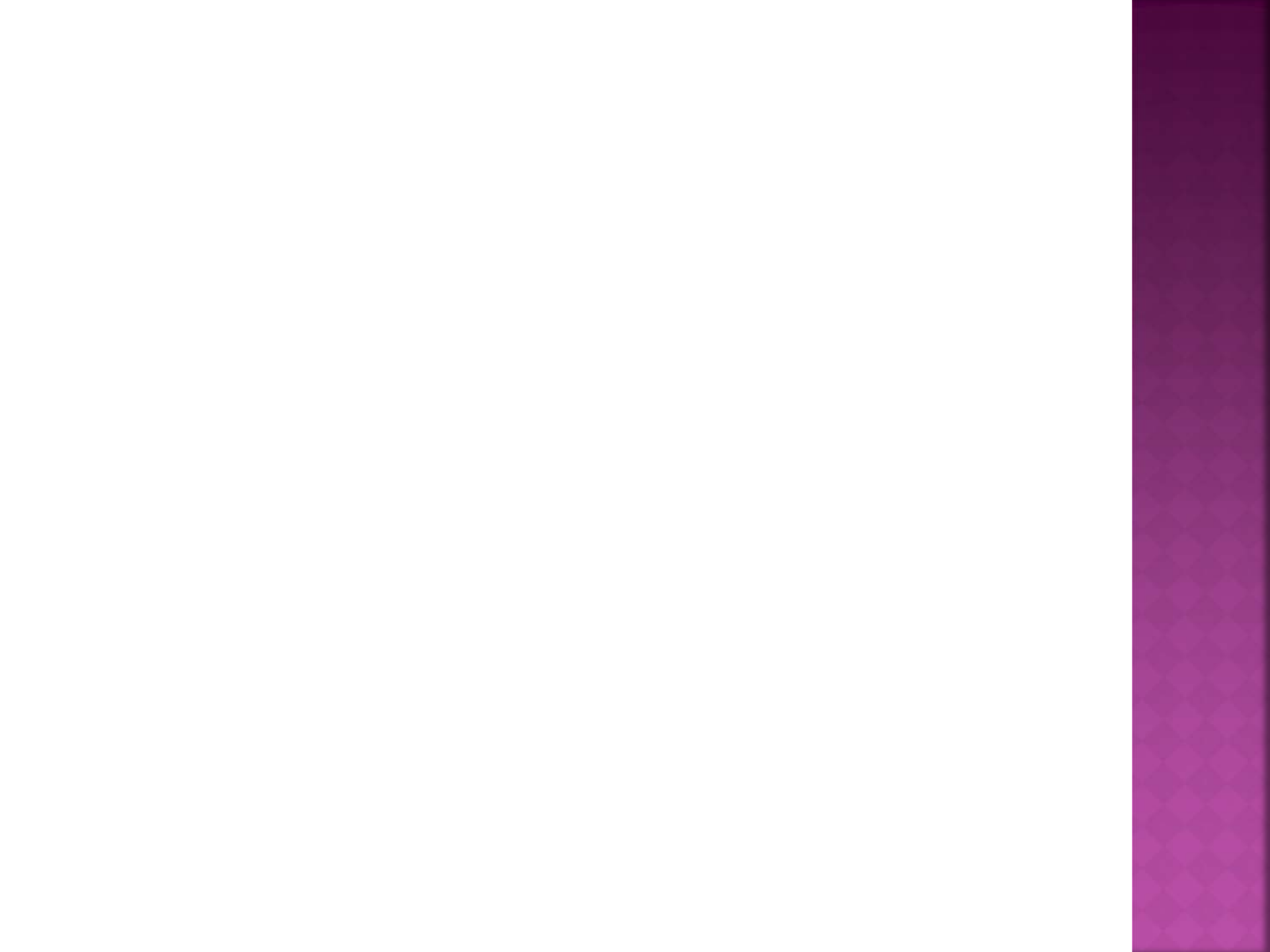
















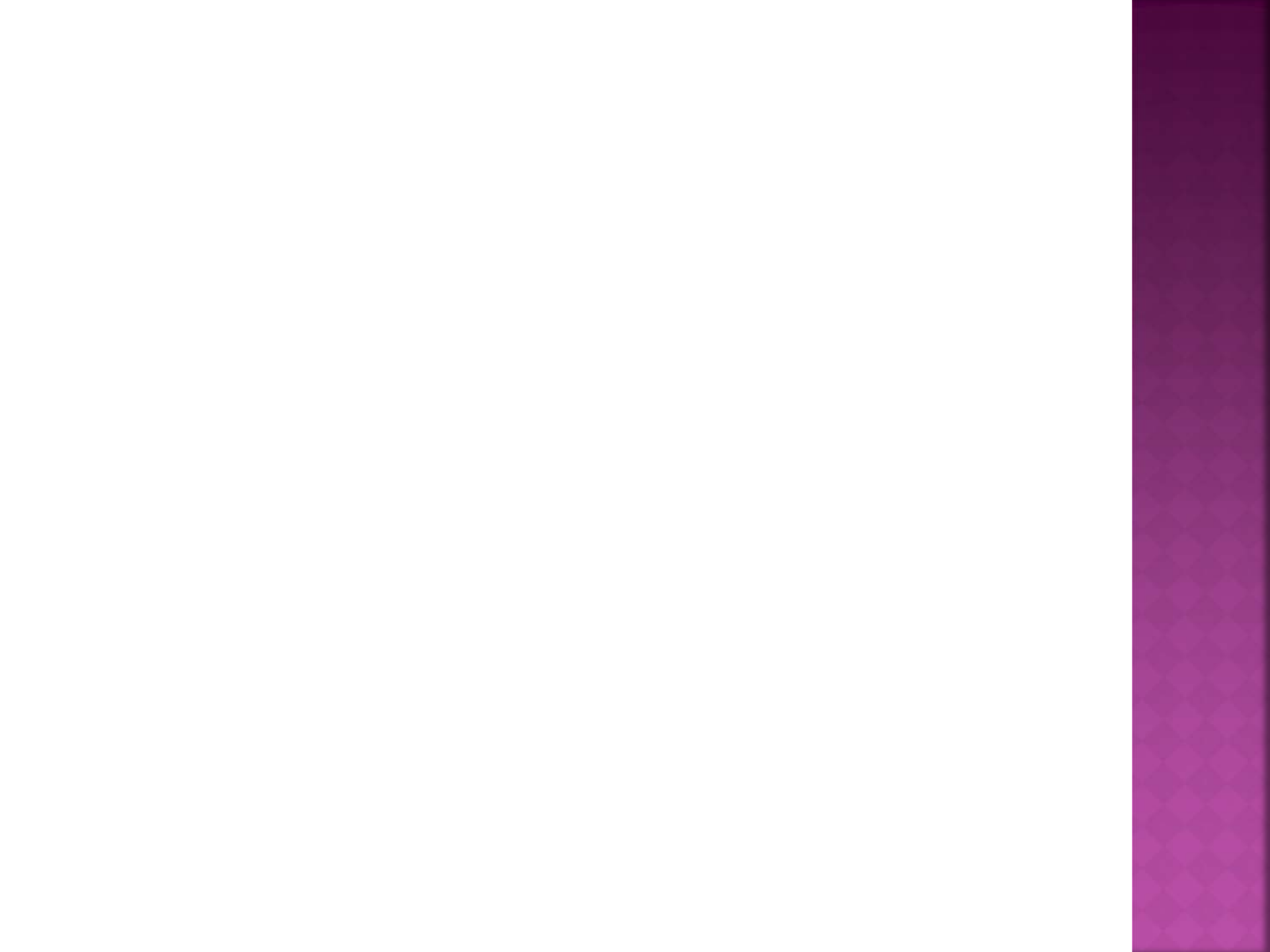
















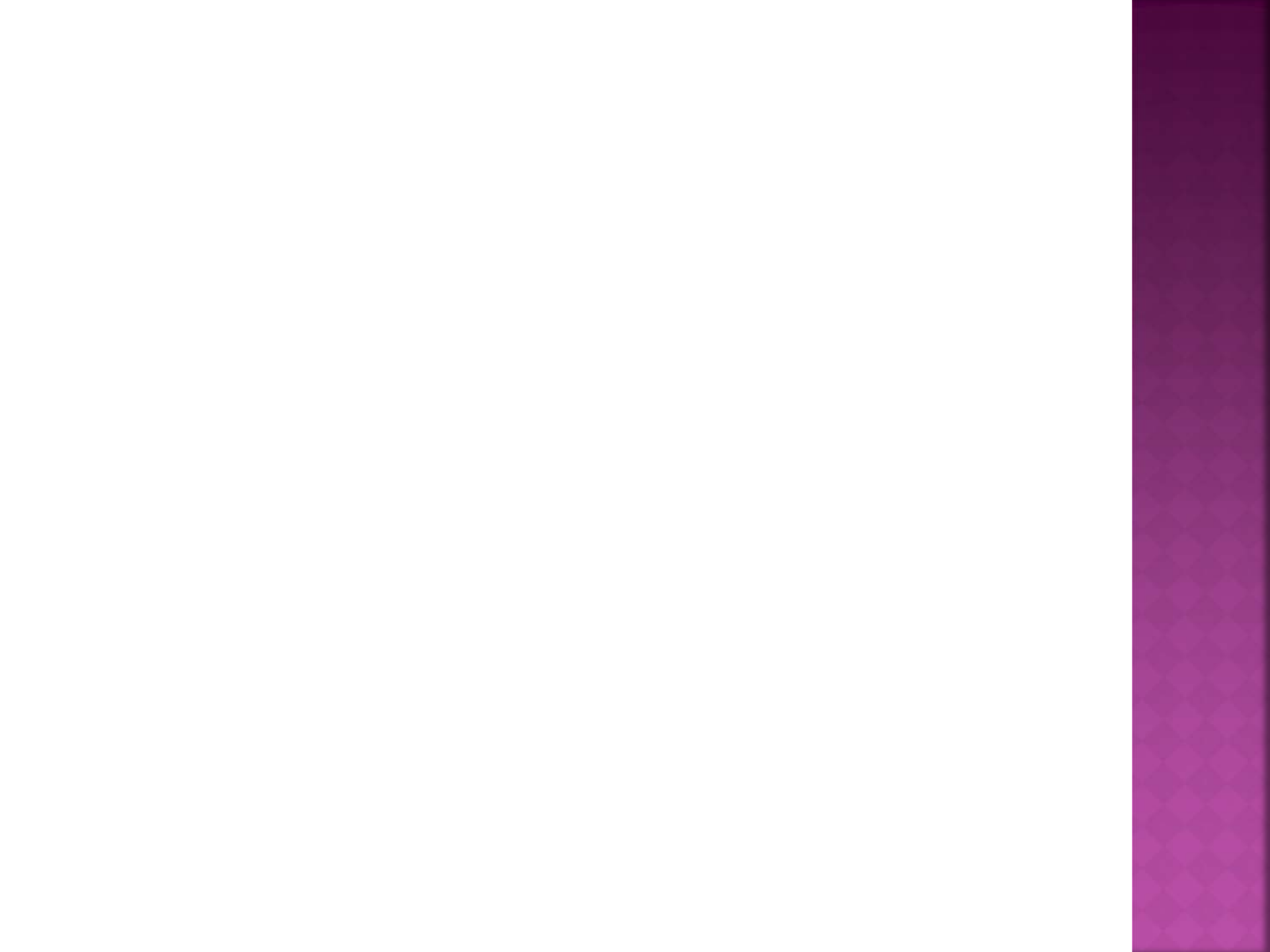
















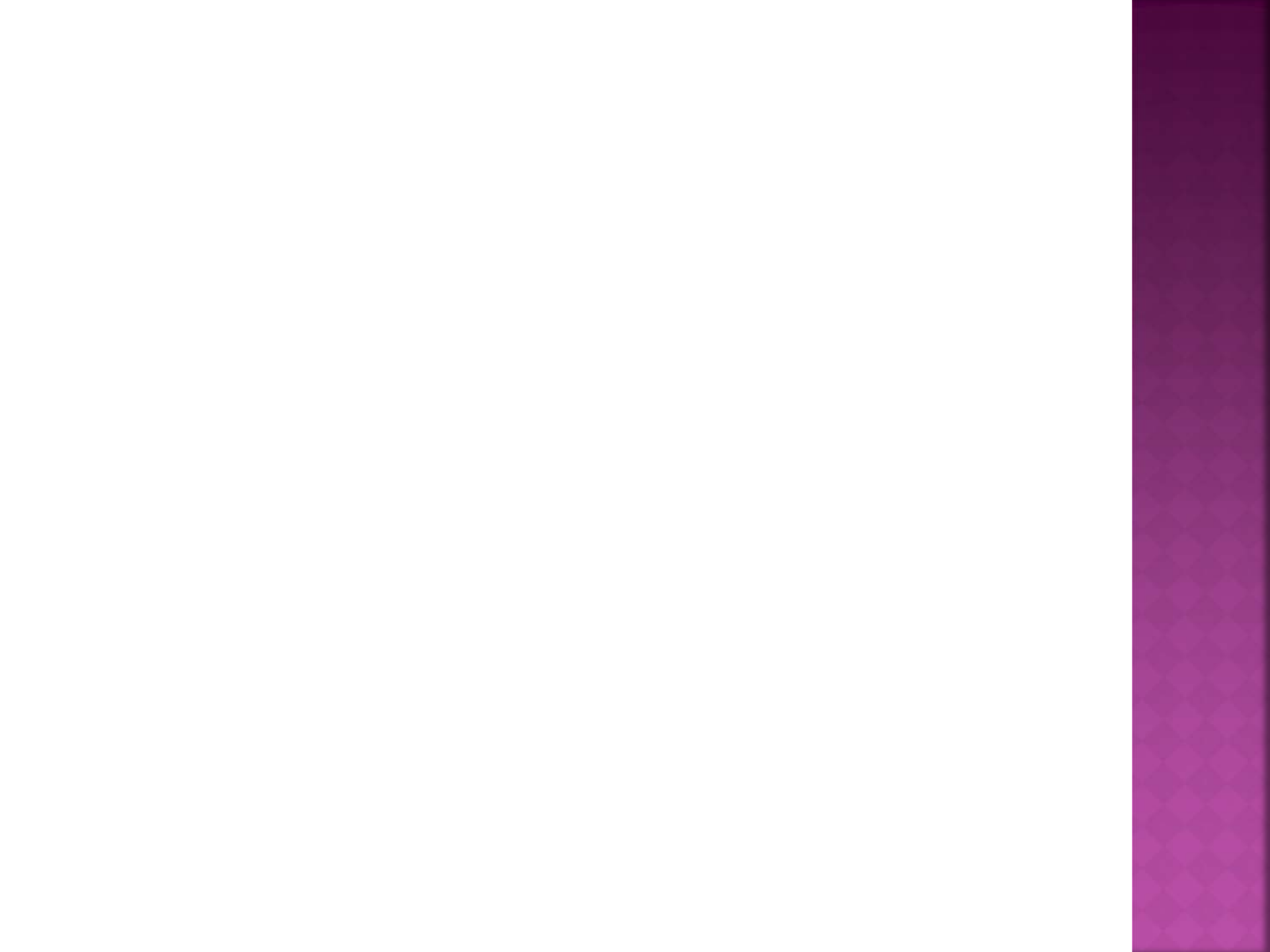
















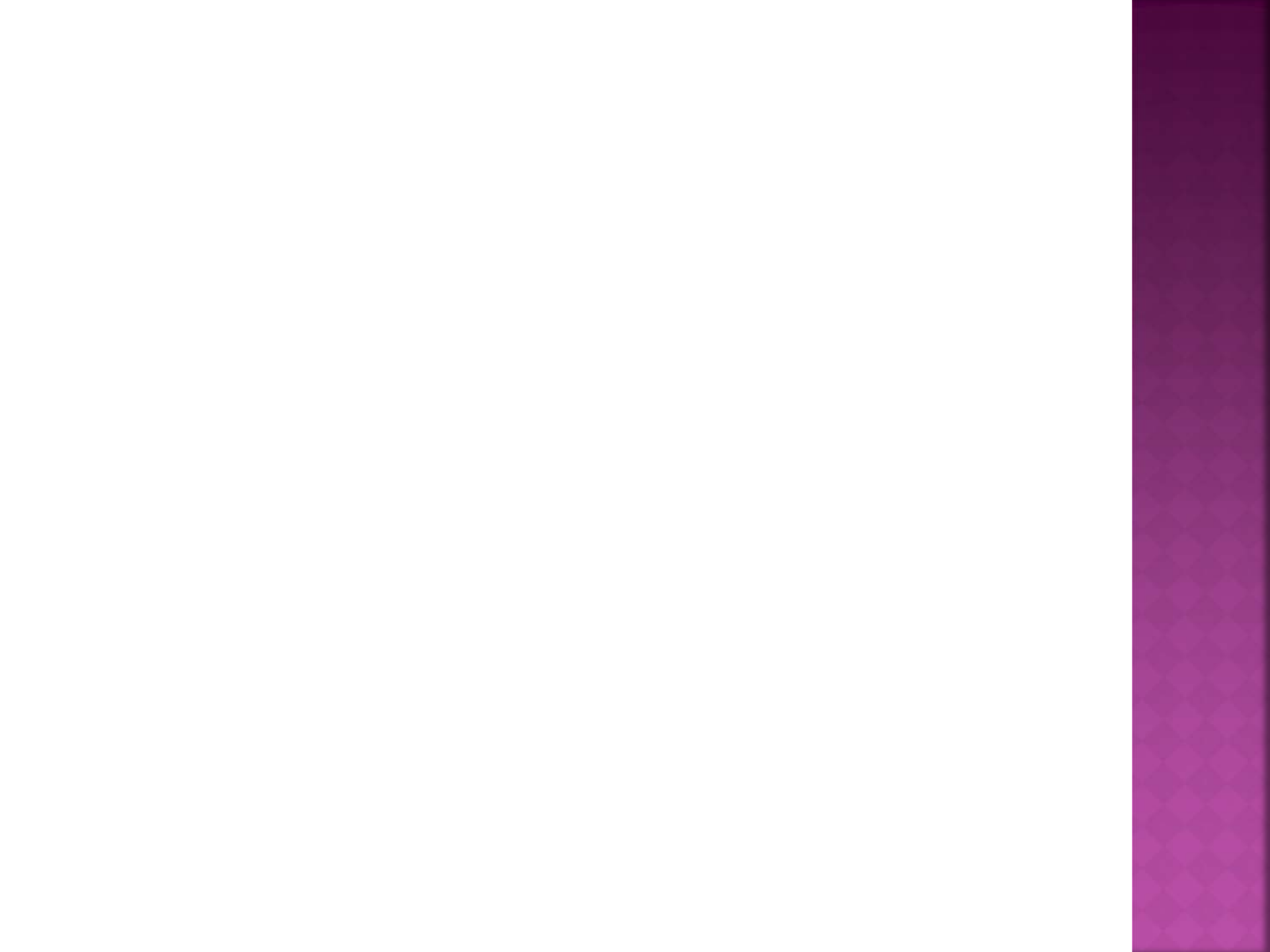














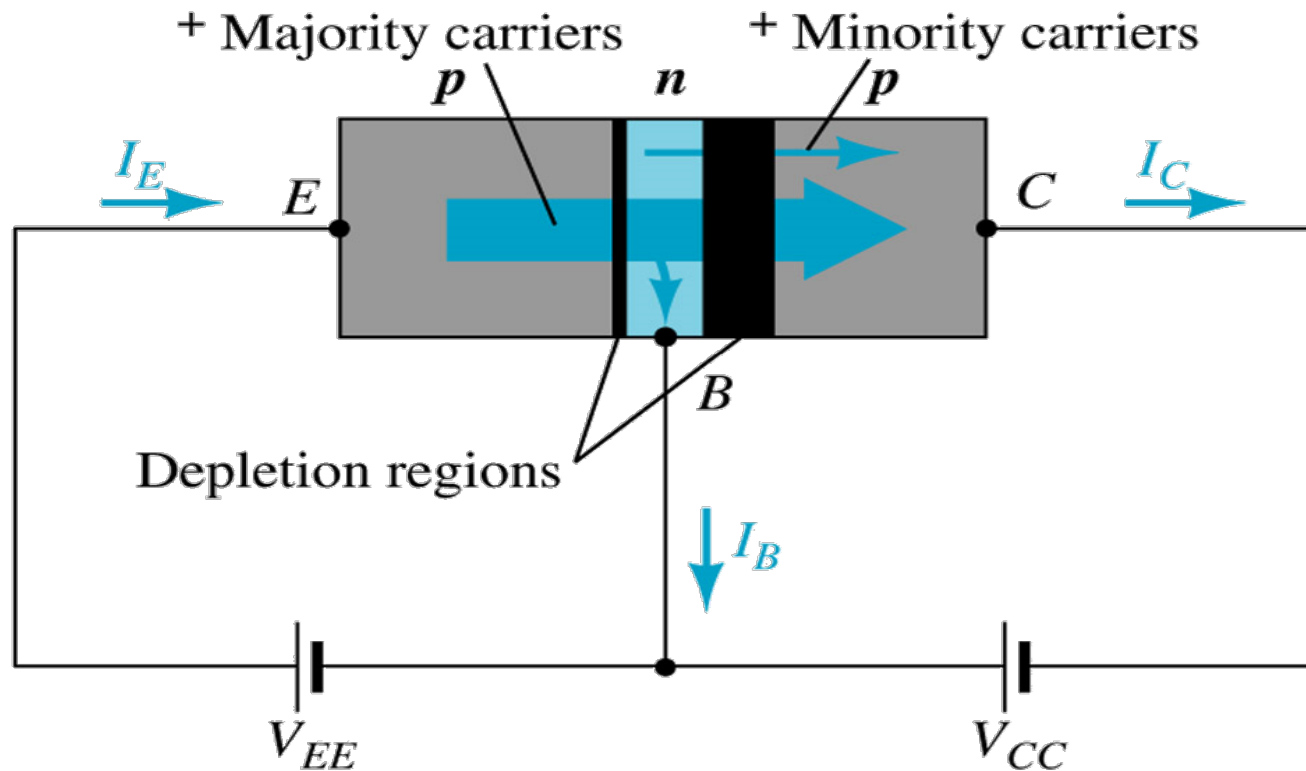

- Both biasing potentials have been applied to a pnp transistor and resulting majority and minority carrier flows indicated.

- ◉ Majority carriers can cross the reverse-biased junction because the injected majority carriers will appear as minority carriers in the n-type material.
- ◉ Applying KCL to the transistor :

$$I_E = I_C + I_B$$

The I_C comprises of two components – the majority and minority carriers

$$I_C = I_{Cmajority} + I_{Cminority}$$





I_{CO} – I_C current with emitter terminal open and is called leakage current.

ASSGINMENT QUESTION:


- ⦿ Explain transistor as an amplifier.
- ⦿ Why common emitter configuration is mostly used?

COMMON-BASE CONFIGURATION

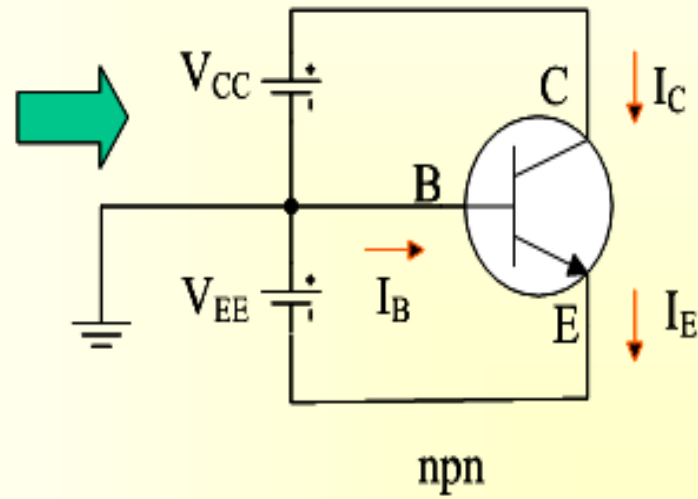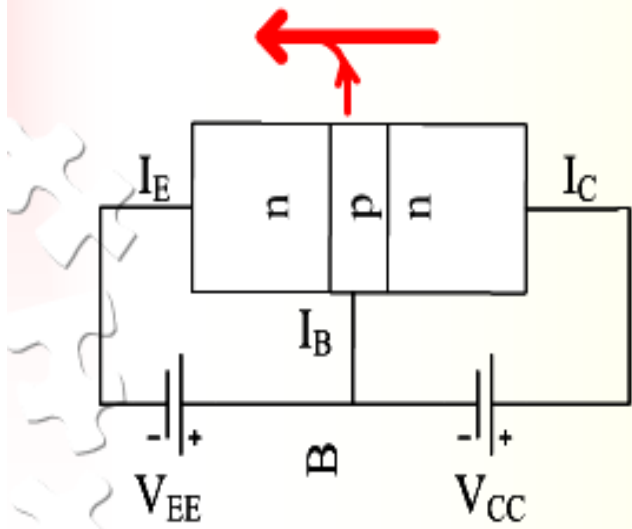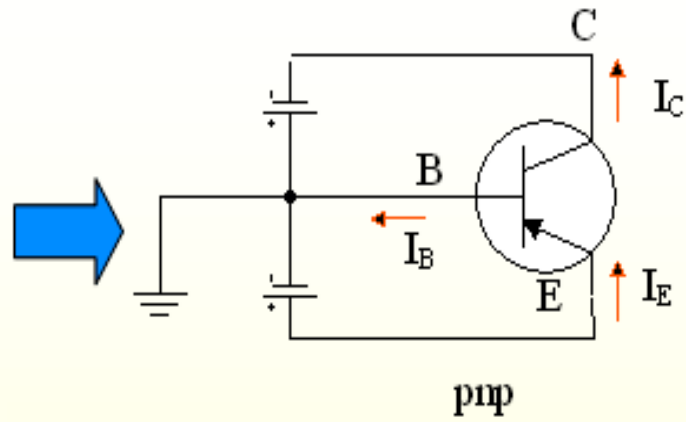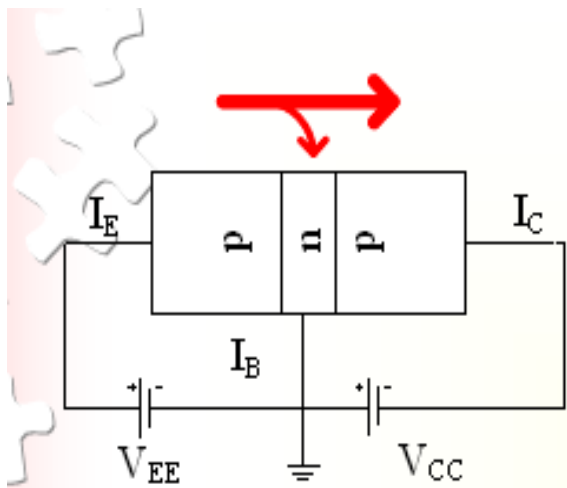
- ◉ Common-base terminology is derived from the fact that the :
 - base is common to both input and output of the configuration.
- ◉ All current directions will refer to **conventional** (hole) flow and the arrows in all electronic symbols have a direction defined by this convention.



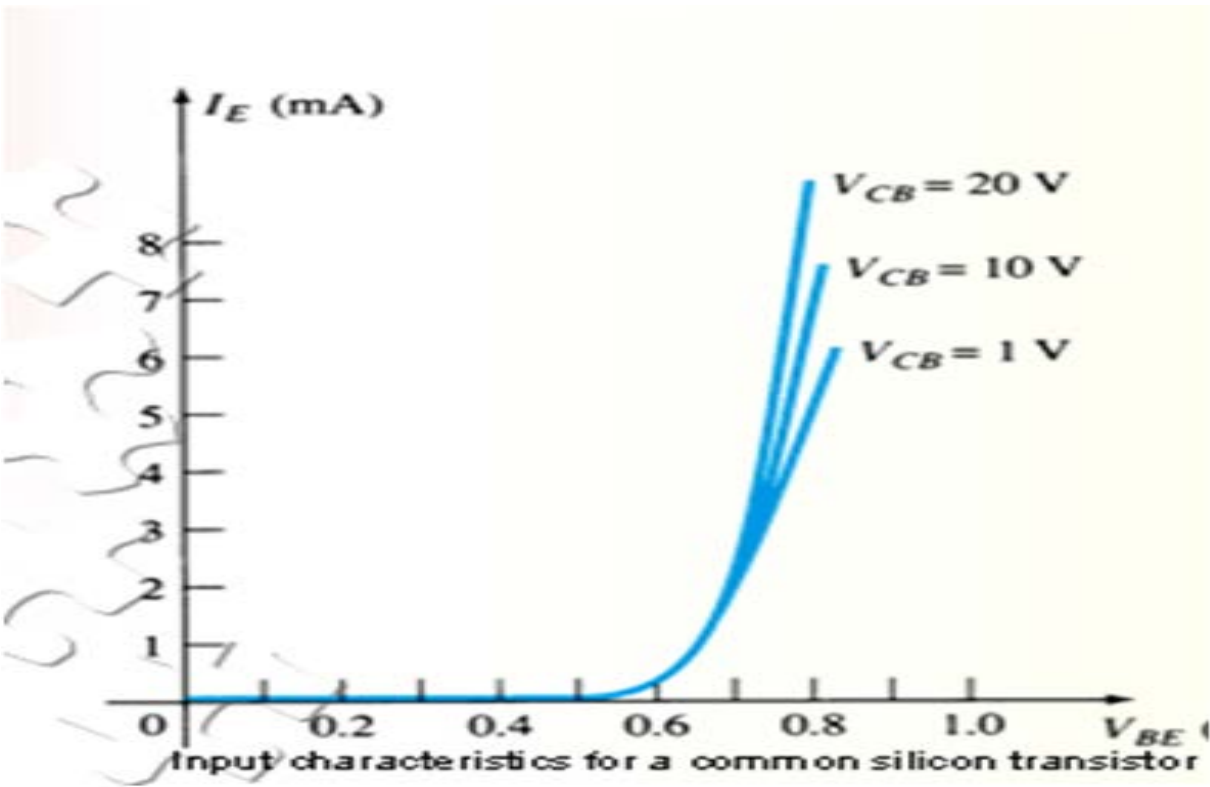- ◉ To describe the behavior of common-base amplifiers requires two set of characteristics:
 - Input or driving point characteristics.
 - Output or collector characteristics



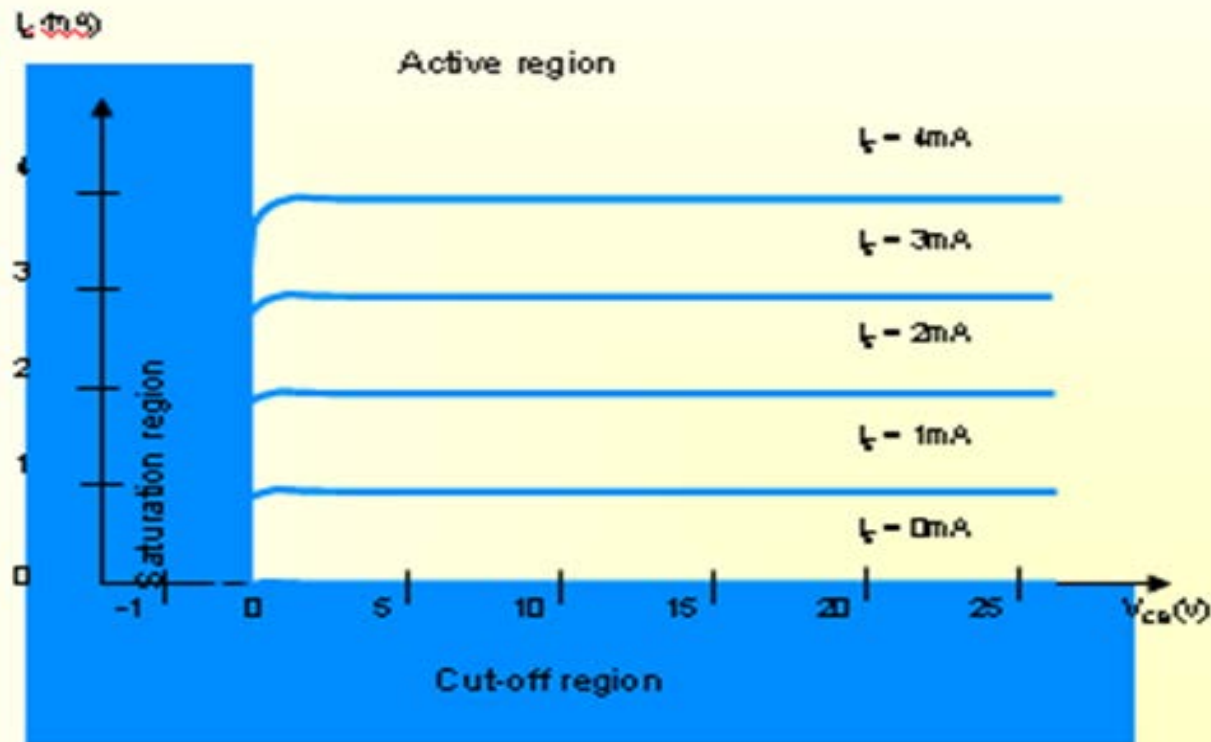The output characteristics has 3 basic regions:



(V) Output of collector characteristics for common-base transistor amplifier

Active region

- I_E increased, I_C increased
- BE junction forward bias and CB junction reverse bias
- Refer to the graf, $I_C \approx I_E$
- I_C not depends on V_{CB}
- Suitable region for the transistor working as amplifier

Saturation region

- BE and CB junction is forward bias
- Small changes in V_{CB} will cause big different to I_C
- The allocation for this region is to the left of $V_{CB} = 0$ V.

Cut-off region

- Region below the line of $I_E = 0$ A
- BE and CB is reverse bias
- no current flow at collector, only leakage current

- In the dc mode the level of I_C and I_E due to the majority carriers are related by a quantity called alpha

$$\alpha = \frac{I_C}{I_E}$$



$$I_C = \alpha I_E + I_{CBO}$$

- It can then be summarize to $I_C = \alpha I_E$ (ignore I_{CBO} due to small value)
- For ac situations where the point of operation moves on the characteristics curve, an ac alpha defined by


$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

BIASING

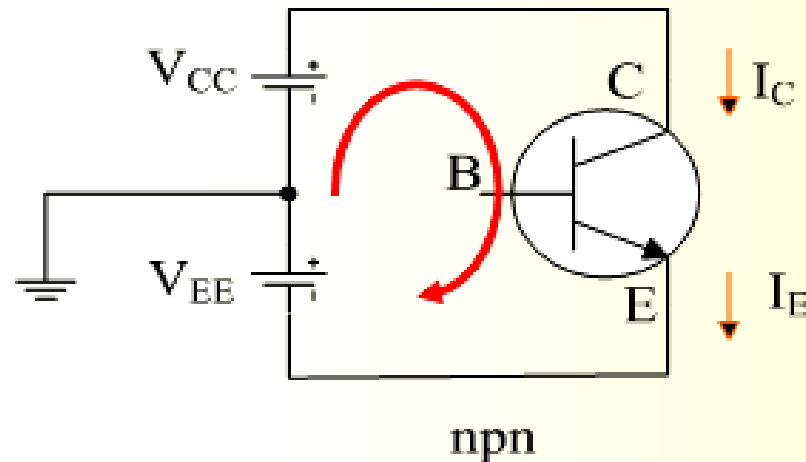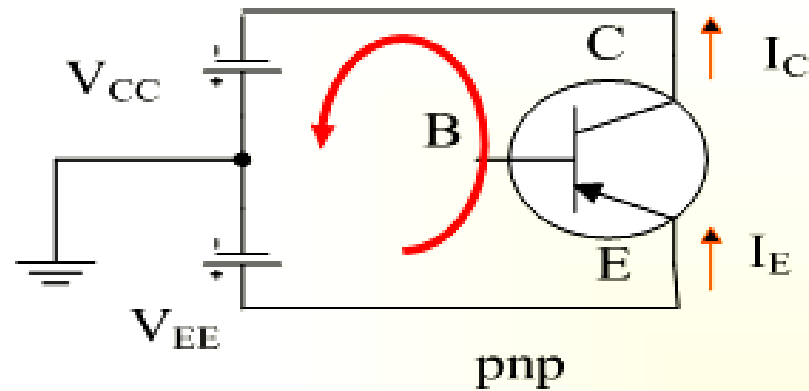- Proper biasing CB configuration in active region by approximation $I_C \approx I_E$ ($I_B \approx 0 \mu A$)




TRANSISTOR AS AN AMPLIFIER

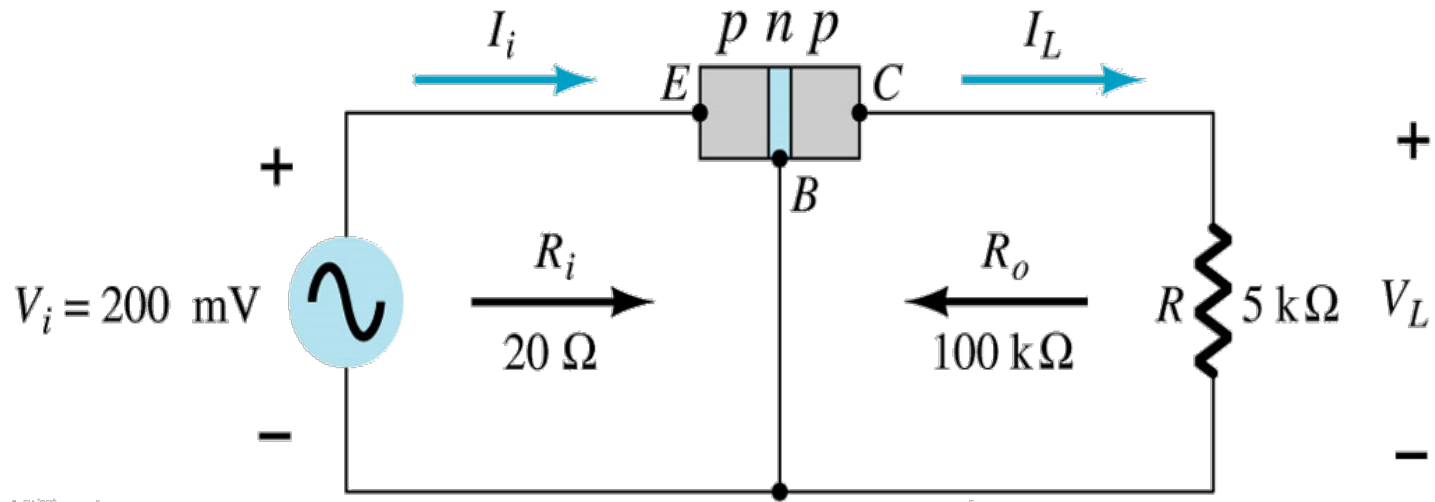


COMMON-EMITTER CONFIGURATION

- ◉ It is called common-emitter configuration since :
 - emitter is common or reference to both input and output terminals.
 - emitter is usually the terminal closest to or at ground

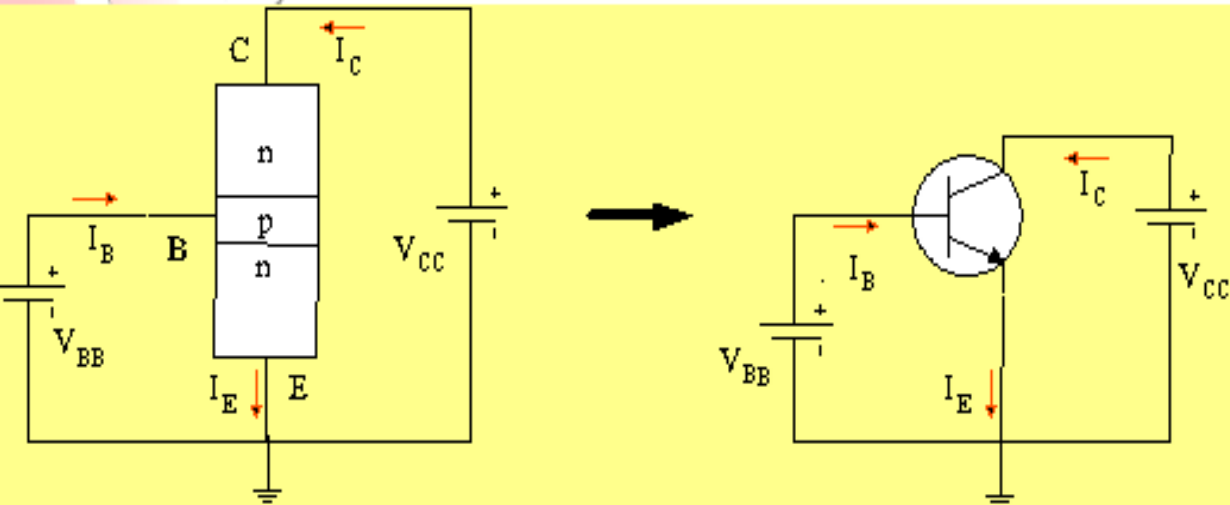Proper Biasing common-emitter configuration in active region




(a) npn transistor configuration

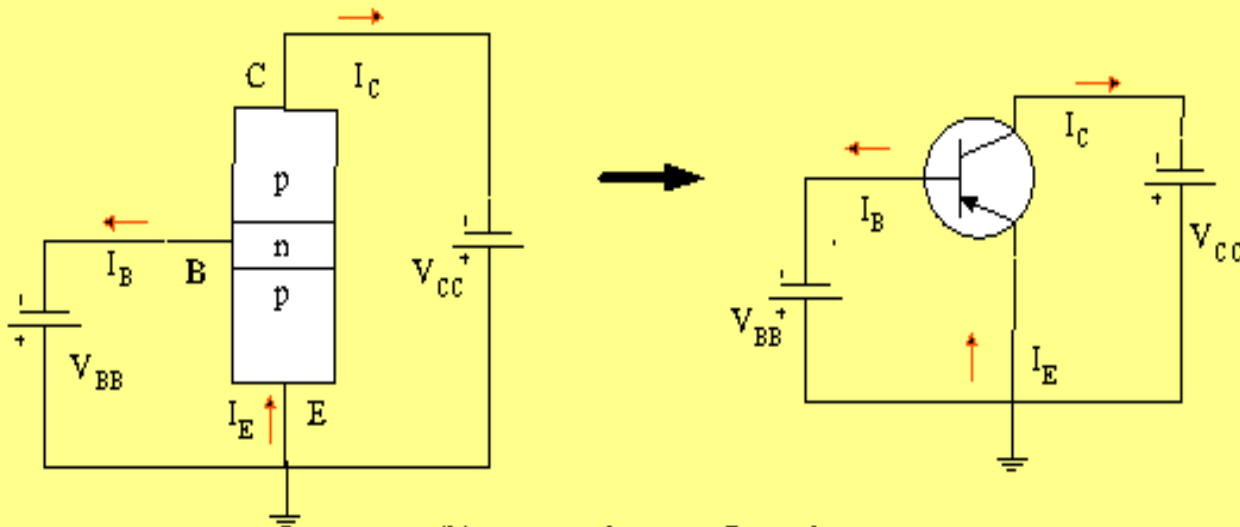

(b) pnp transistor configuration


$$I_E = I_C + I_B$$

Fig 4.7 : Common-emitter configuration

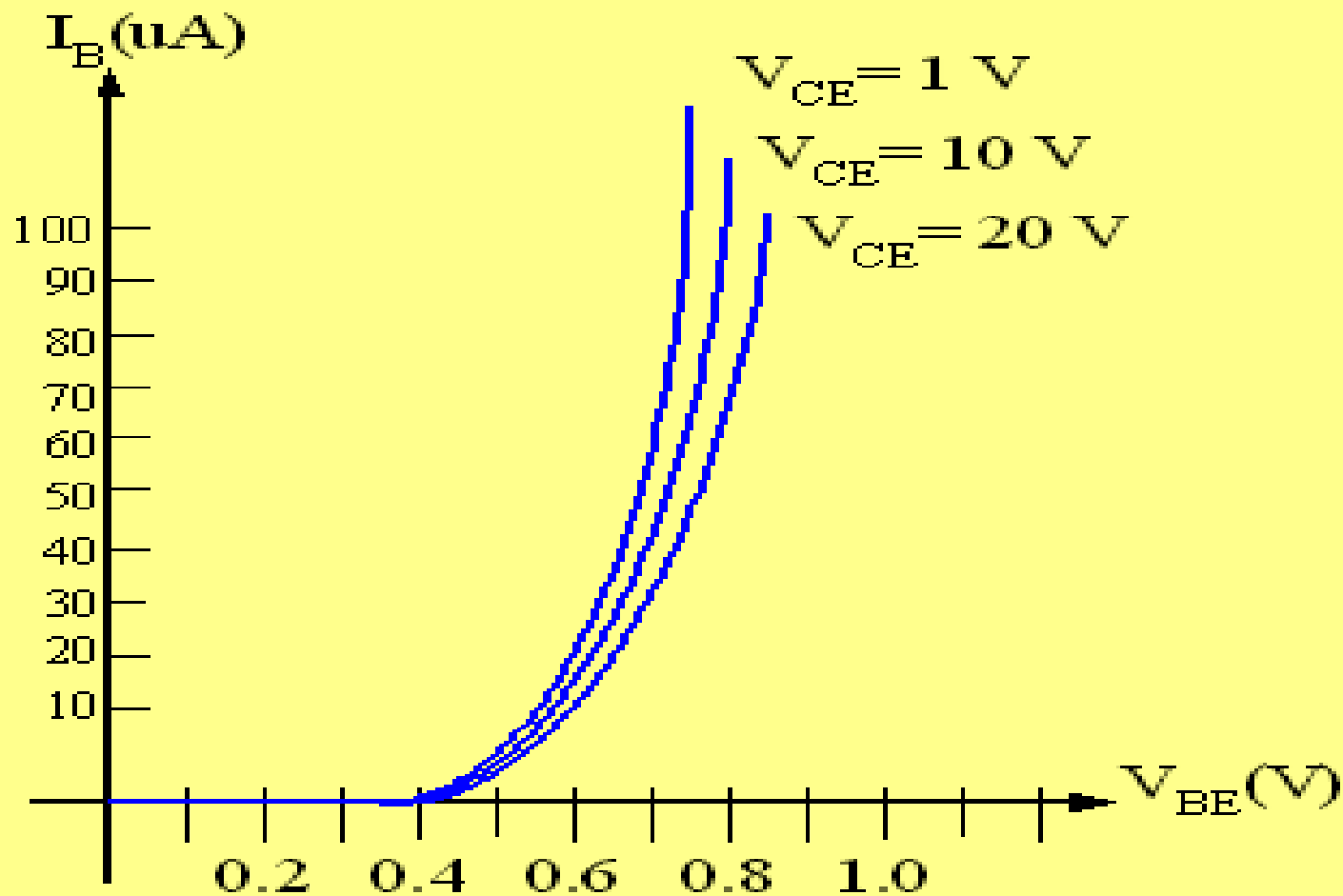

Input characteristics for a common-emitter NPN transistor

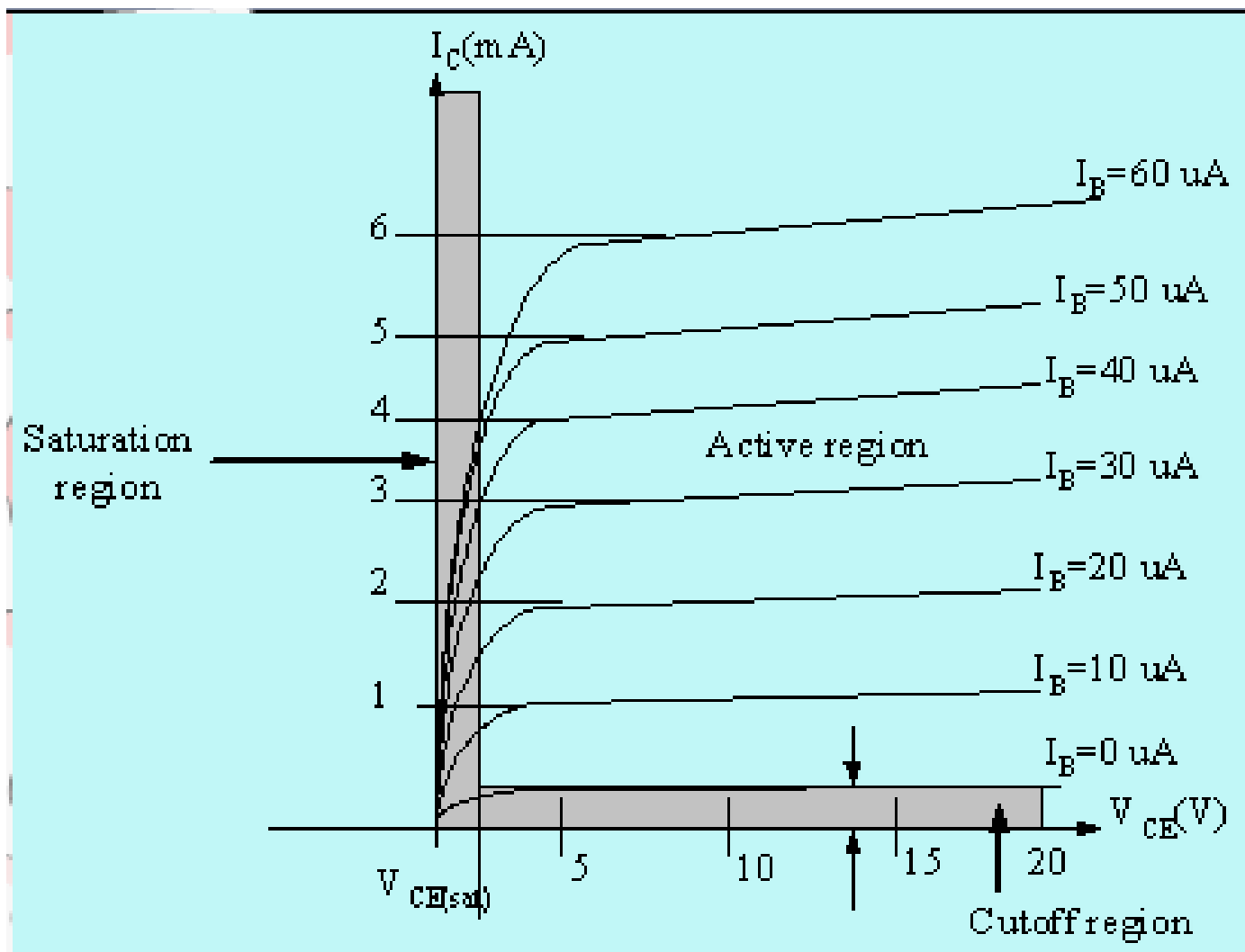Output characteristics for a common-emitter npn transistor



RELATIONSHIP ANALYSIS BETWEEN A AND B

CASE 1

$$I_E = I_C + I_B \quad (1)$$

substitute equ. $I_C = \beta I_B$ into (1) we get

$$\underline{\underline{I_E = (\beta + 1)I_B}}$$

CASE 2

$$\text{known : } \alpha = \frac{I_C}{I_E} \Rightarrow I_E = \frac{I_C}{\alpha} \quad (2)$$

$$\text{known : } \beta = \frac{I_C}{I_B} \Rightarrow I_B = \frac{I_C}{\beta} \quad (3)$$

substitute (2) and (3) into (1) we get,





$$\underline{\underline{\alpha = \frac{\beta}{\beta + 1}}}$$

and

$$\underline{\underline{\beta = \frac{\alpha}{1 - \alpha}}}$$

COMMON – COLLECTOR CONFIGURATION

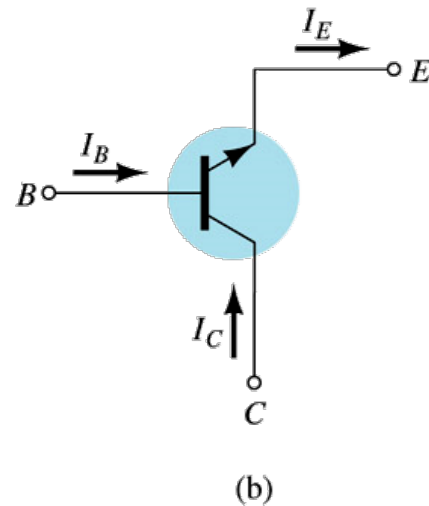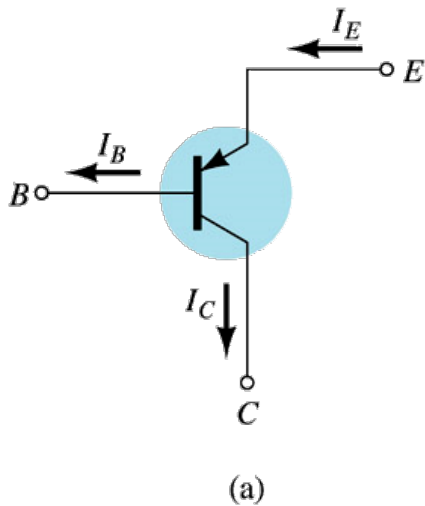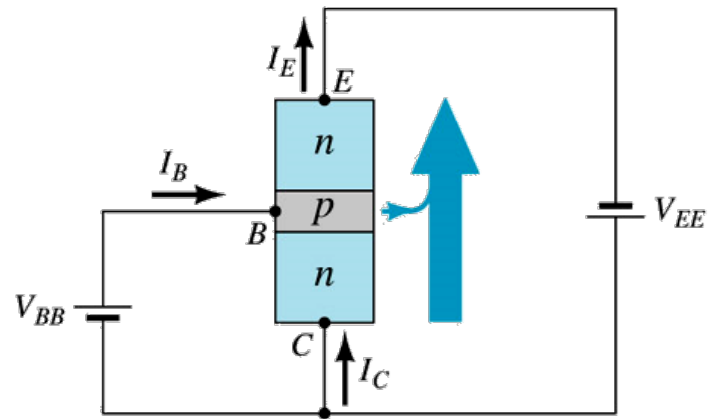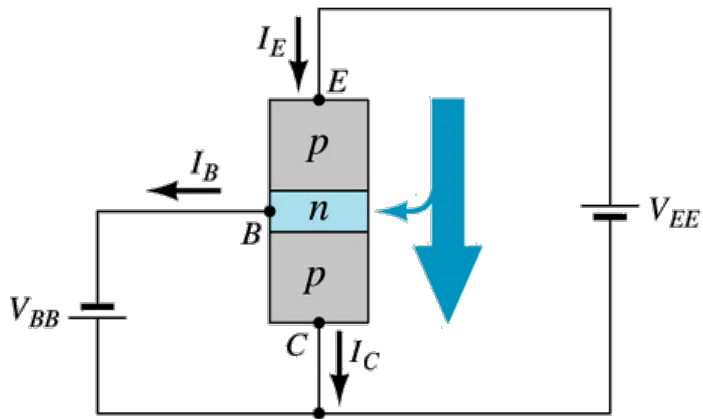- ◉ The input characteristic of common-collector configuration is similar with common-emitter. configuration.
- ◉ Common-collector circuit configuration is provided with the load resistor connected from emitter to ground.



Notation and symbols used with the common-collector configuration:

(a) pnp transistor ; (b) npn transistor.



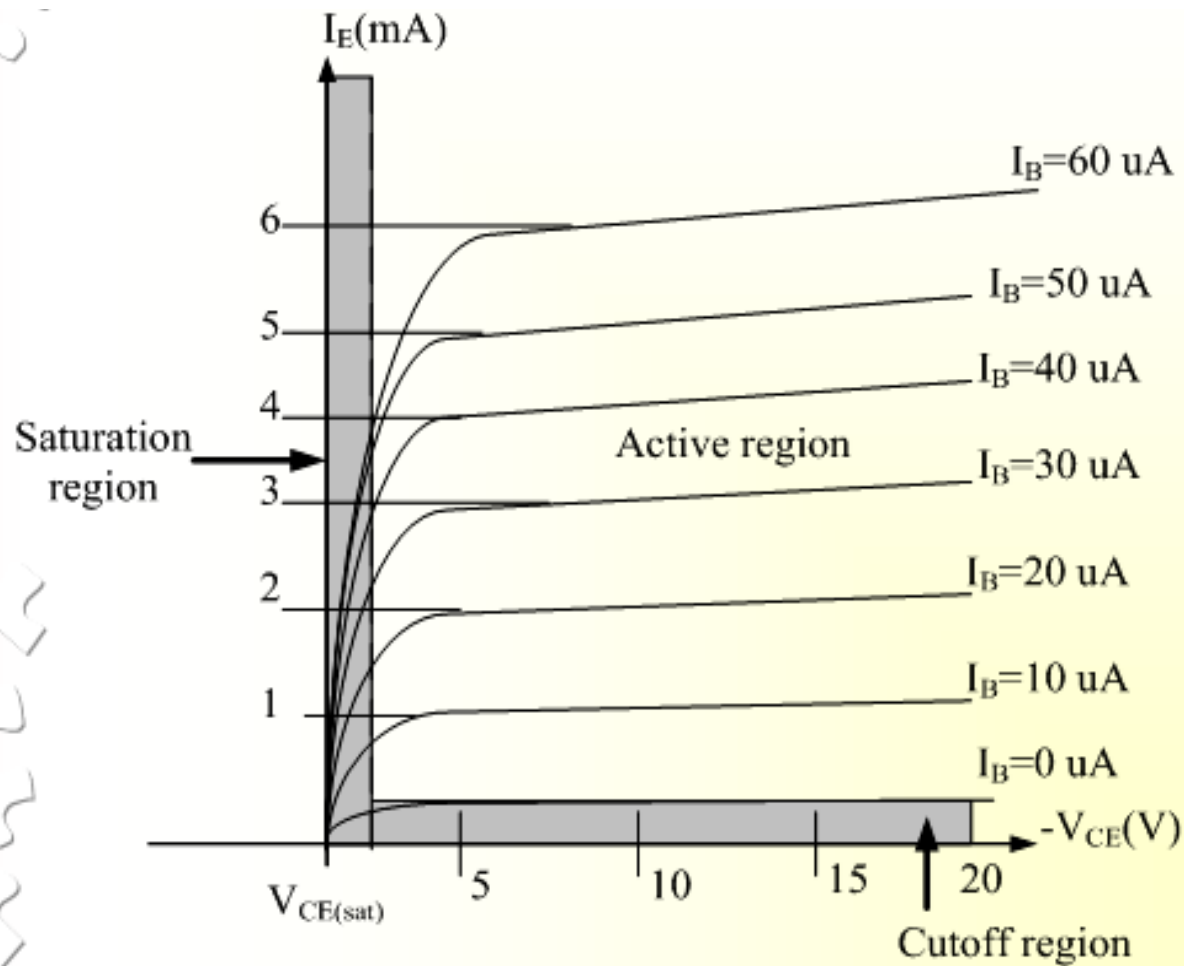
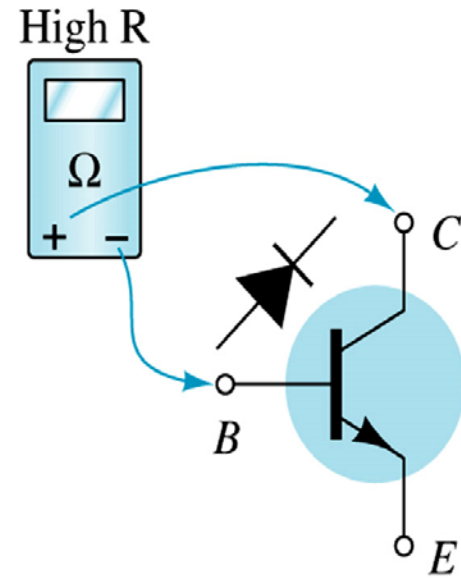


Fig 4.9 : Output characteristic in CC configuration for npn transistor

TRANSISTOR TESTING

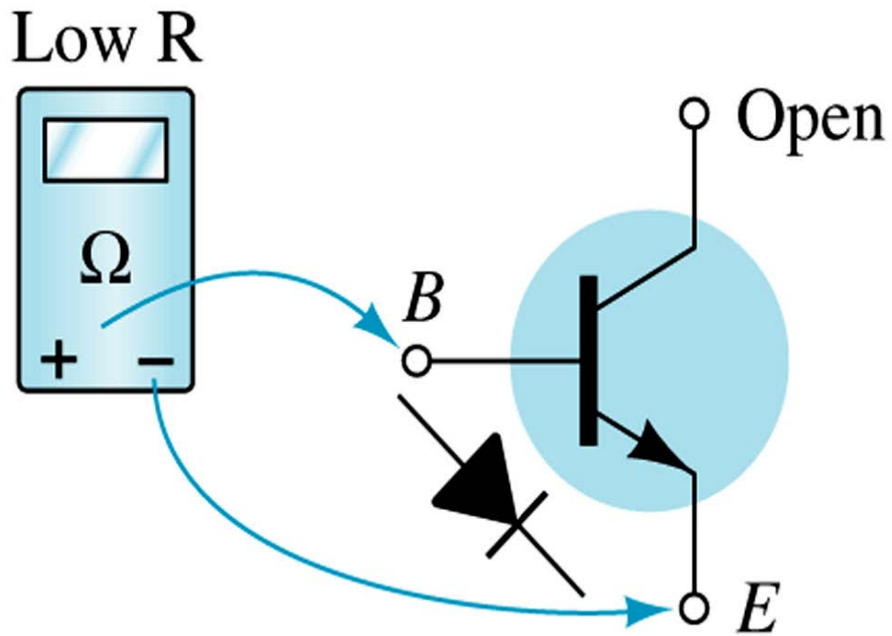

R-C COUPLED AMPLIFIERS

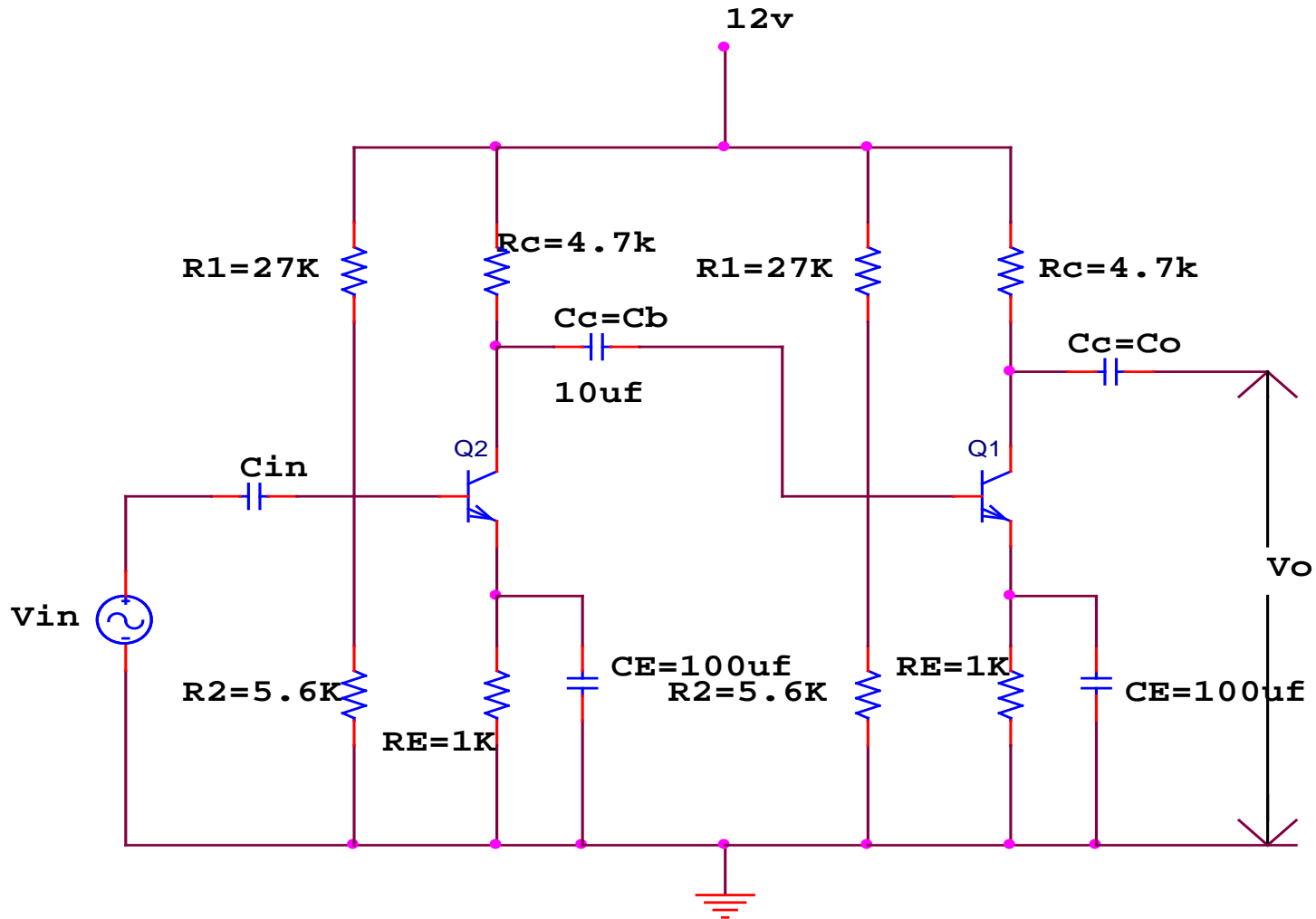

RC COUPLED AMPLIFIER

FREQUENCY RESPONSE of R-C COUPLED AMPLIFIERS

