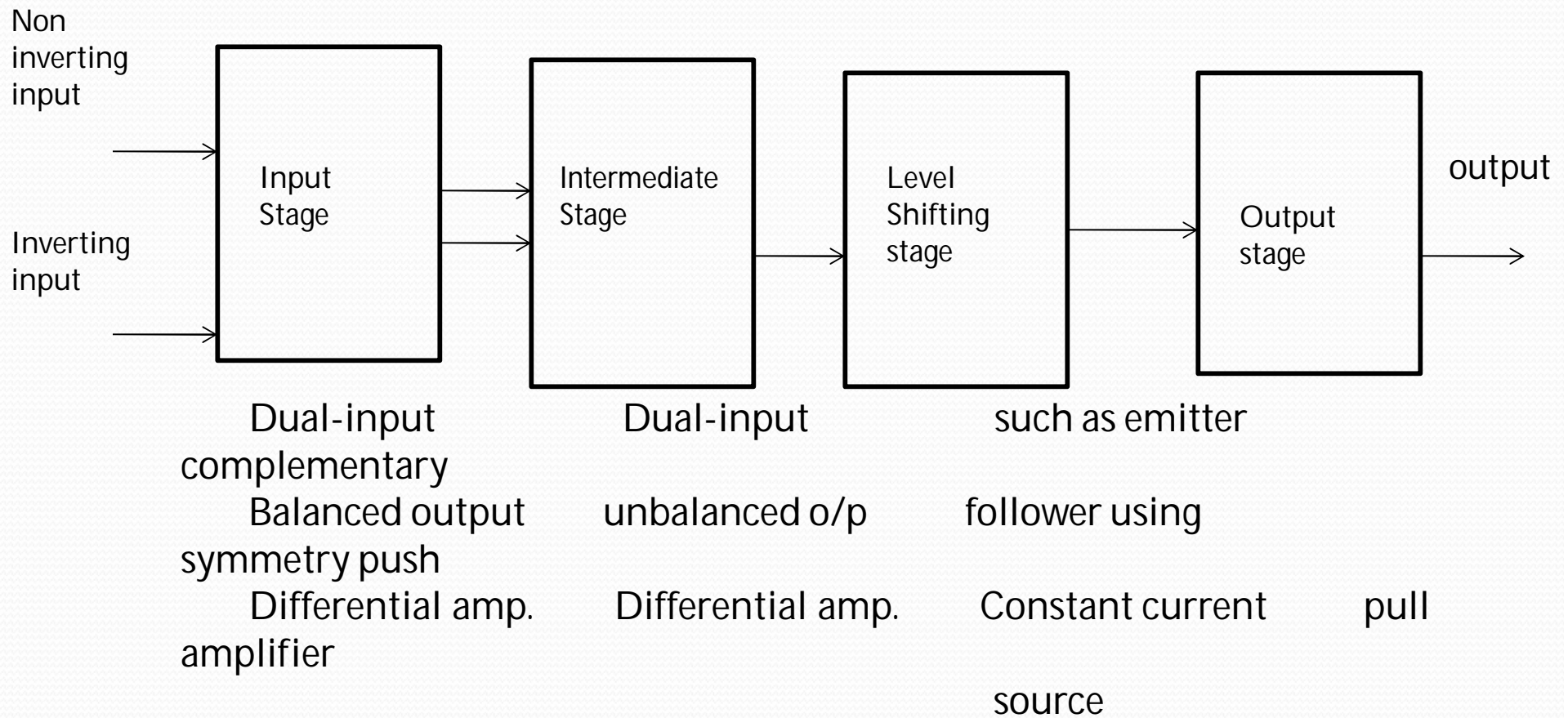




Operational Amplifier


Block Diagram of typical Op-amp



INTRODUCTION

- ❑ An amplifier is a device that accepts a varying input signal and produces a similar output signal with a larger amplitude.
- ❑ Usually connected so part of the output is fed back to the input. (Feedback Loop)
- ❑ They are the basic components used to build analog circuits.
- ❑ The name “operational amplifier” comes from the fact that they were originally used to perform mathematical operations such as integration and differentiation.

Schematic Symbol

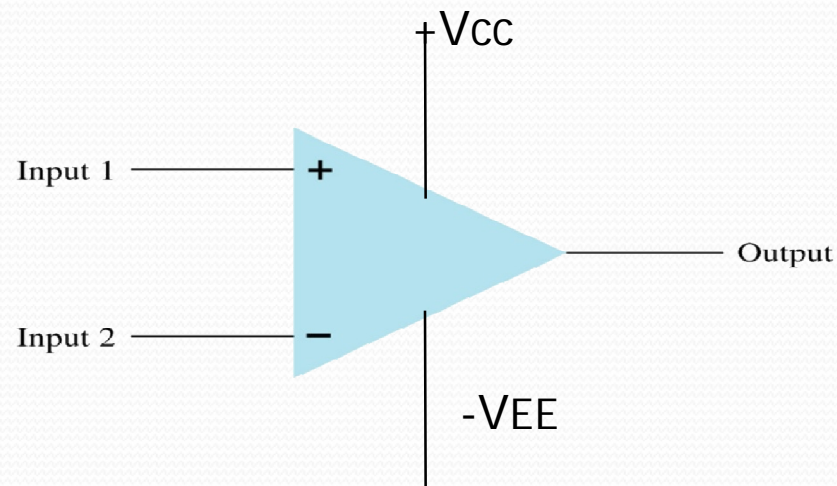


Input1- non inverting input (volts)

Input2- inverting input (volts)

Output- output voltage (volts)


A-Large signal voltage gain
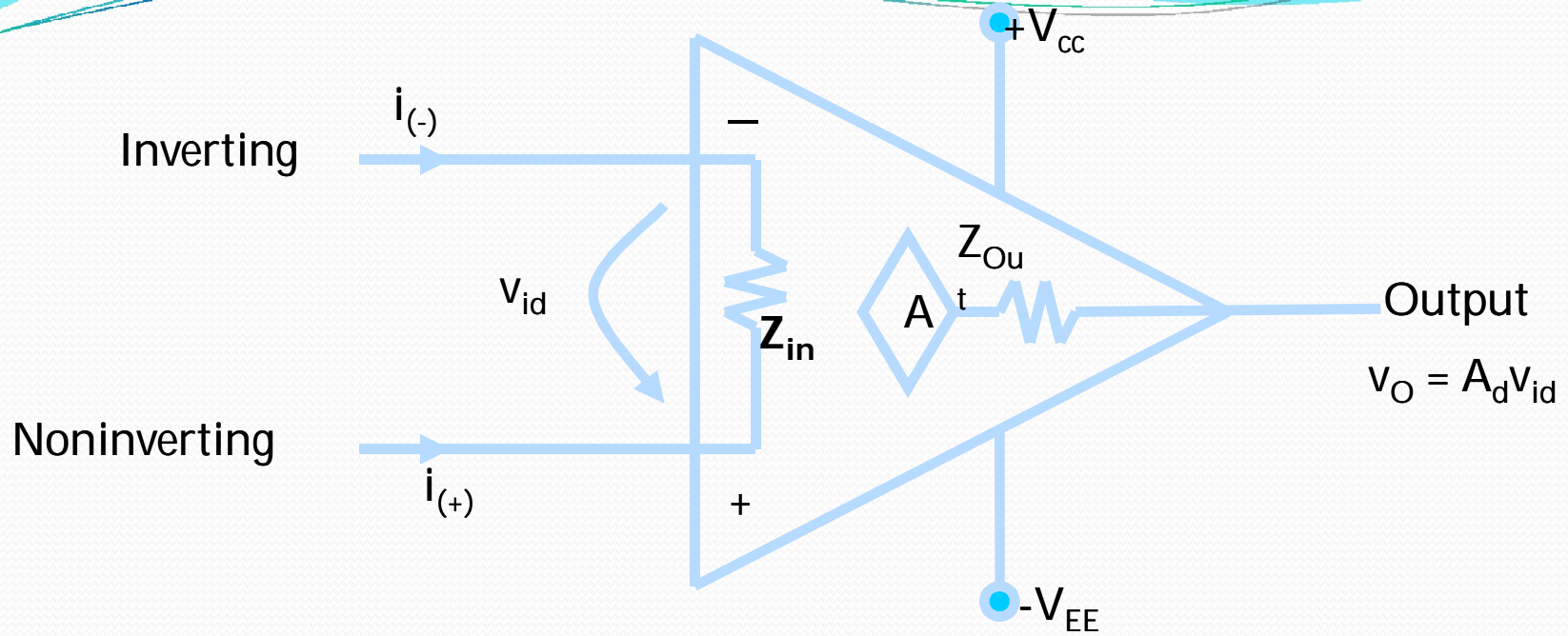
$$\text{Output} = A (\text{input1} - \text{input2})$$




Equivalent circuit of an op-amp


- $i_{(+)}$, $i_{(-)}$: Currents into the amplifier on the inverting and noninverting lines respectively
- v_{id} : The input voltage from inverting to non-inverting inputs
- $+V_{CC}$, $-V_{EE}$: DC source voltages, usually +15V and -15V
- Z_{in} : The input resistance, ideally infinity
- A : The gain of the amplifier. Ideally very high, in the 1×10^{10} range.
- Z_{Out} : The output resistance, ideally zero
- v_o : The output voltage; $v_o = A_{OL}v_{id}$ where A_{OL} is the open-loop voltage gain
- V_{id} : Difference input voltage

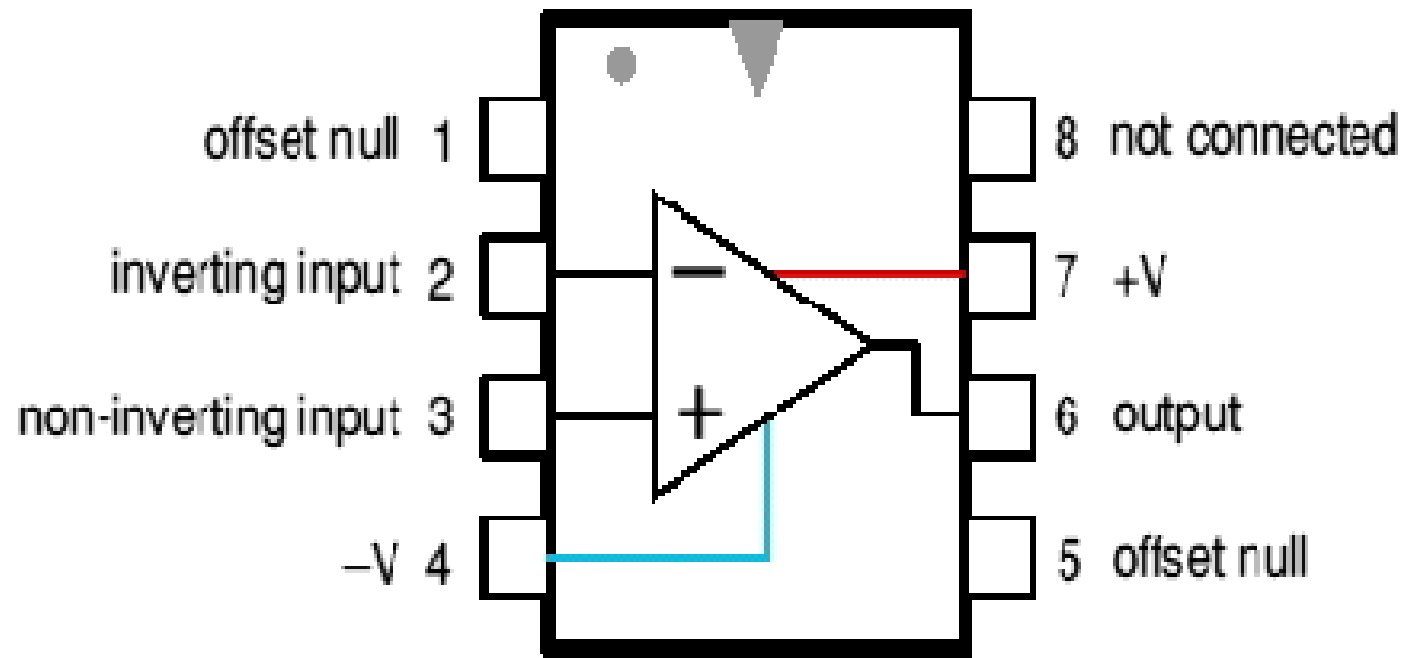

(viewed from above)

Ideal Voltage transfer curve

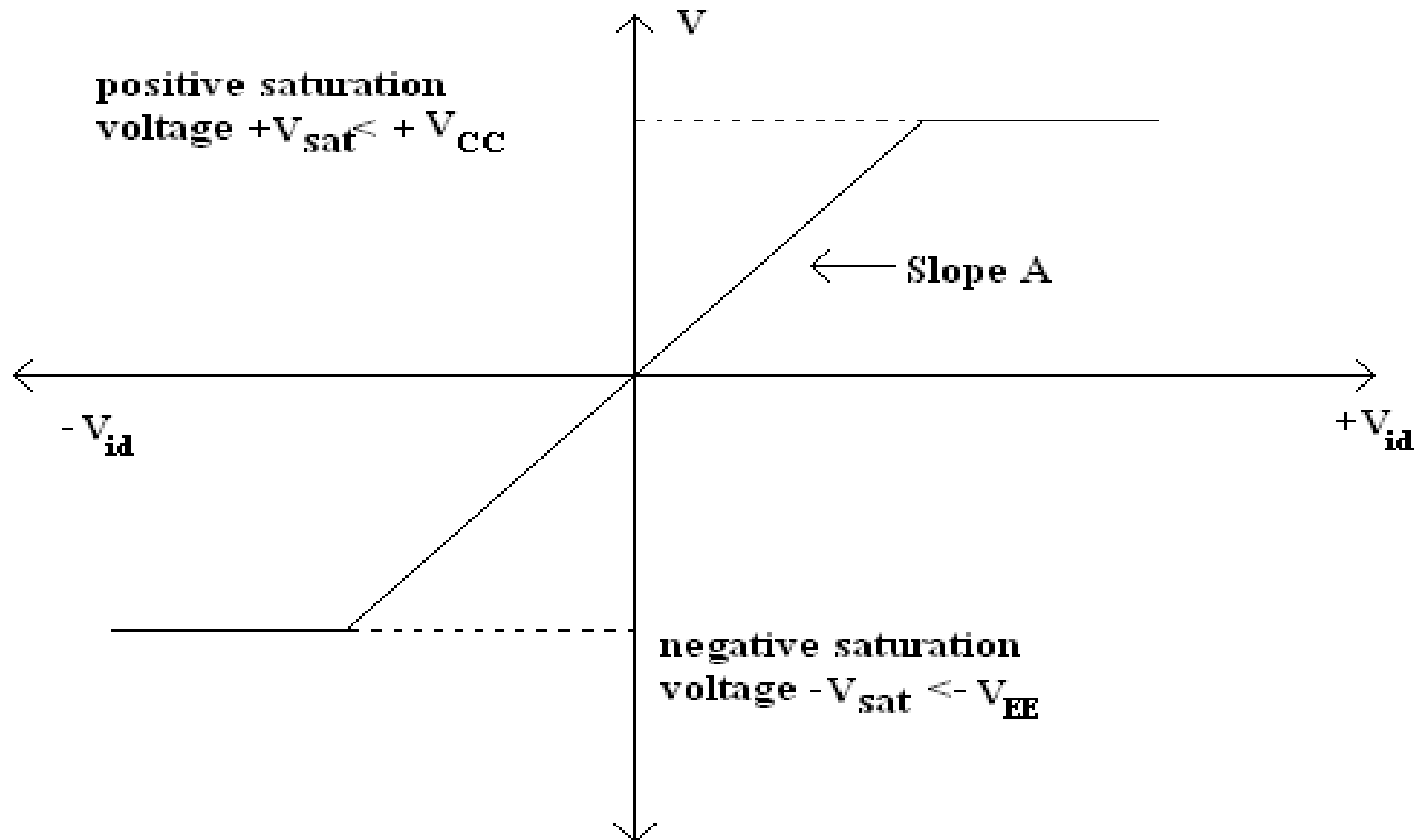

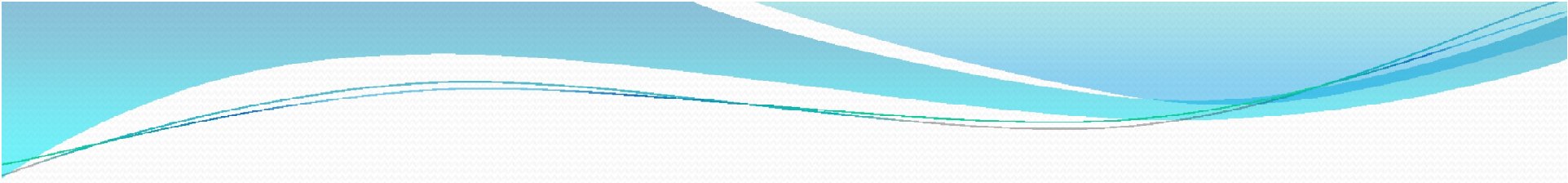

- $V_O = A_{OL}V_{id}$ This is the basic op-amp equation in which the output offset voltage is assumed to be zero.


- The graphic representation of this equation is shown; where the output voltage, V_o is plotted against input difference voltage V_{id} , keeping gain A constant.

- The output voltage cannot exceed the positive and negative saturation voltage.


- The output voltage is directly proportional to the input difference voltage until it reaches the saturation voltages and thereafter the output voltage remains constant.

- This curve is called ideal voltage transfer curve.

Ideal op-amp

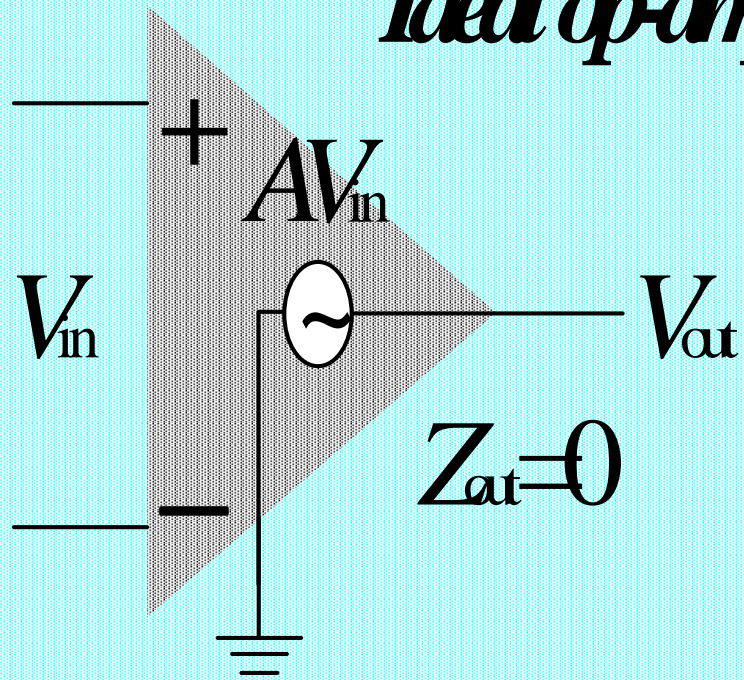

Practical op-amp

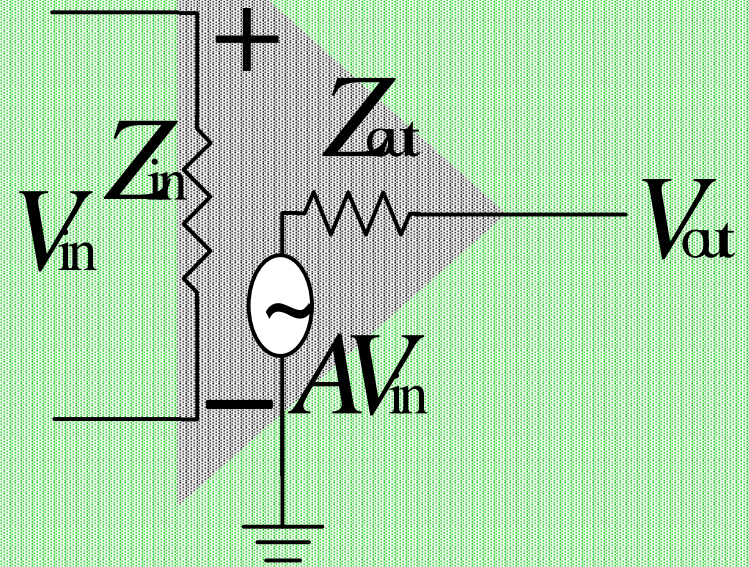

Ideal Vs Practical Op-Amp

	Ideal	Practical
Open Loop gain A	∞	10^5
Bandwidth BW	∞	10-100Hz
Input Impedance Z_{in}	∞	$>1M\Omega$
Output Impedance Z_{out}	0Ω	10-100 Ω
Output Voltage V_{out}	Depends only on $V_d = (V_+ - V_-)$ Differential mode signal	Depends slightly on average input $V_c = (V_+ + V_-)/2$ Common-Mode signal
CMRR	∞	10-100dB


Open loop op-amp configuration

When connected in open loop configuration, there are 3 open loop op amp configuration:

- 1) Differential amplifier**
- 2) Inverting amplifier**
- 3) Non inverting amplifier**

These configuration are classed according to number of inputs used and the terminal to which input is applied when a single input is used.


Inverting Amplifier

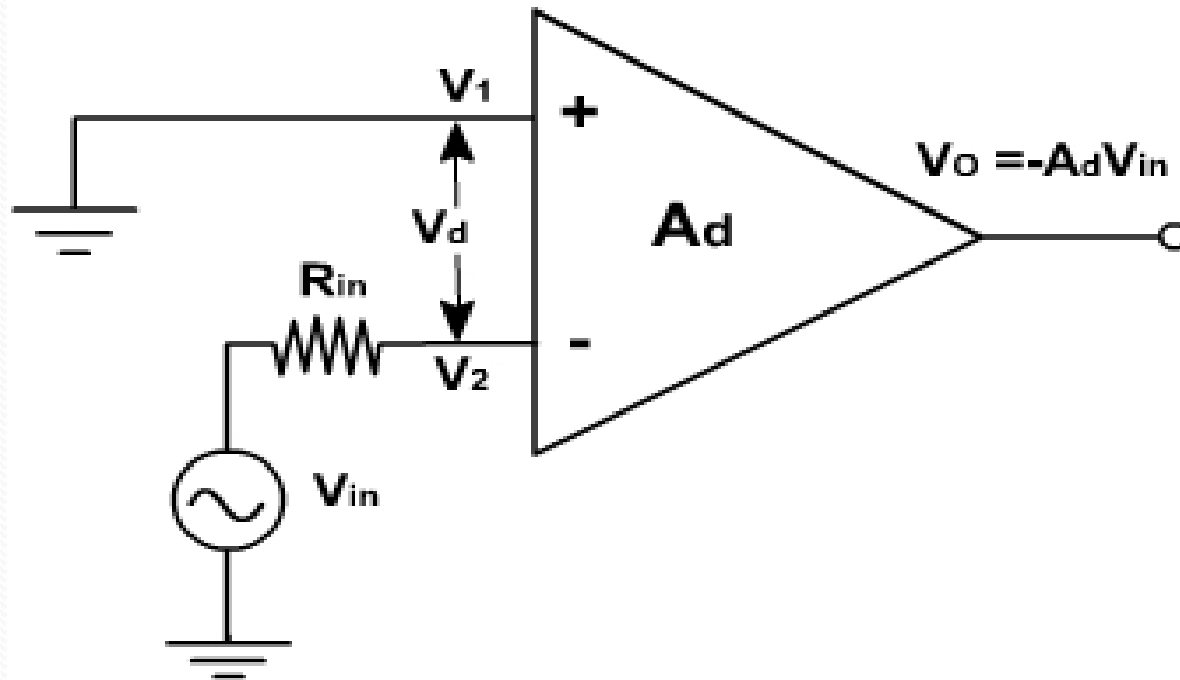

$$V_1 = 0, V_2 = V_{in}.$$

$$V_o = -A_d V_{in}$$

Non-inverting Amplifier

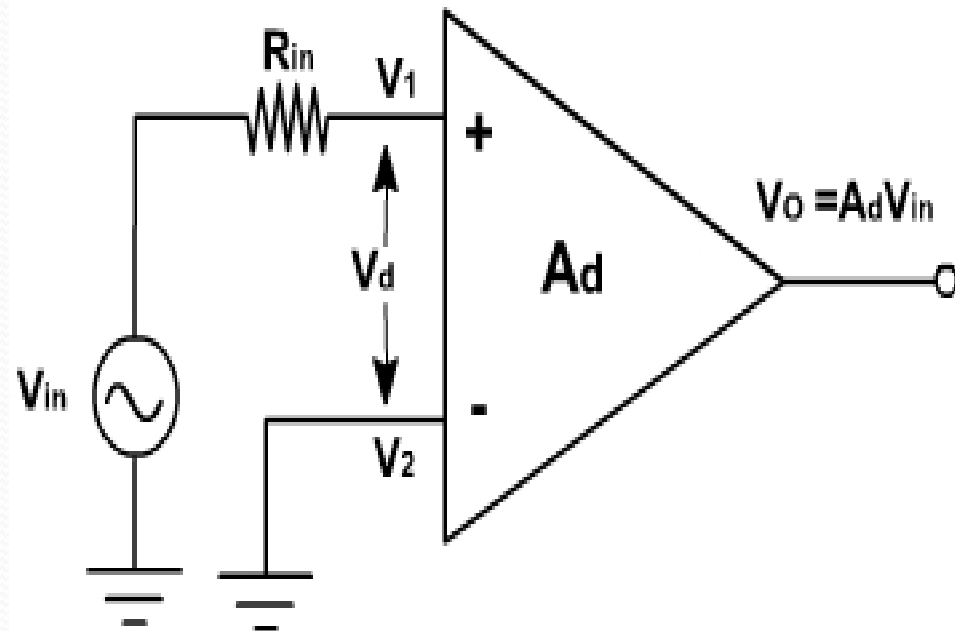


$$V_1 = +V_{in}$$

$$V_2 = 0$$

$$V_o = +A_d V_{in}$$

OP-AMP AS A Summing Amplifier or Adder

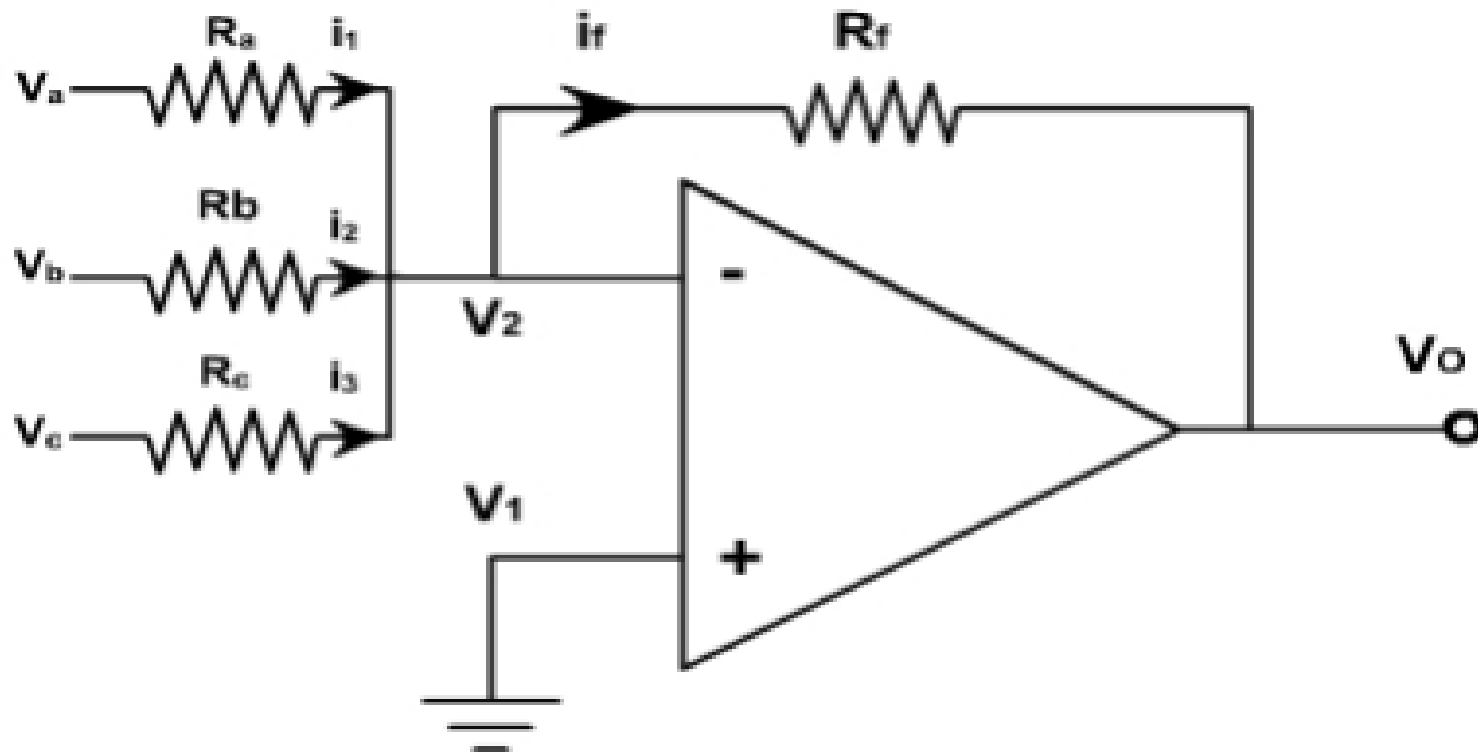

If each input voltage is amplified by a different factor in other words weighted differently at the output, the circuit is called then scaling amplifier.

$$\frac{R_f}{R_a} \neq \frac{R_f}{R_b} \neq \frac{R_f}{R_c}$$
$$V_o = - \left(\frac{R_f}{R_a} V_a + \frac{R_f}{R_b} V_b + \frac{R_f}{R_c} V_c \right)$$

The circuit can be used as an averaging circuit, in which the output voltage is equal to the average of all the input voltages.

In this case, $R_a = R_b = R_c = R$ and $R_f / R = 1 / n$ where n is the number of inputs. Here $R_f / R = 1 / 3$.

$$V_o = -(V_a + V_b + V_c) / 3$$

In all these applications input could be either ac or dc.

OP- AMP AS Integrator

A circuit in which the output voltage waveform is the integral of the input voltage waveform is called integrator. **figure** shows an integrator circuit using OPAMP.


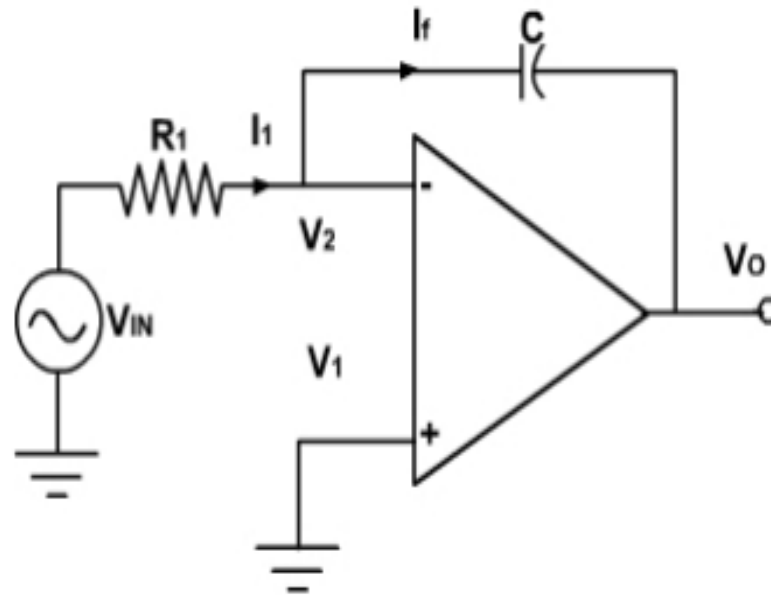


Fig.

Here, the feedback element is a capacitor. The current drawn by OPAMP is zero and also the V_2 is virtually grounded.


Therefore, $i_1 = i_f$ and $v_2 = v_1 = 0$
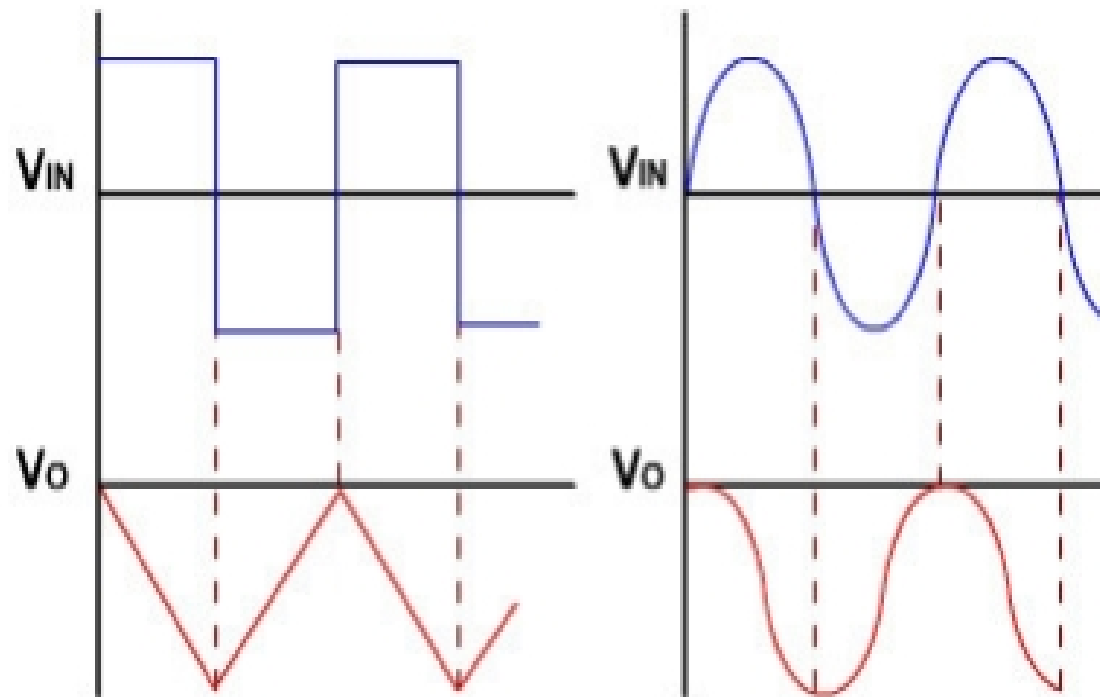
$$v_o(t) = -\frac{1}{RC} \int v_i(t) dt$$



OP-AMP AS Differentiator

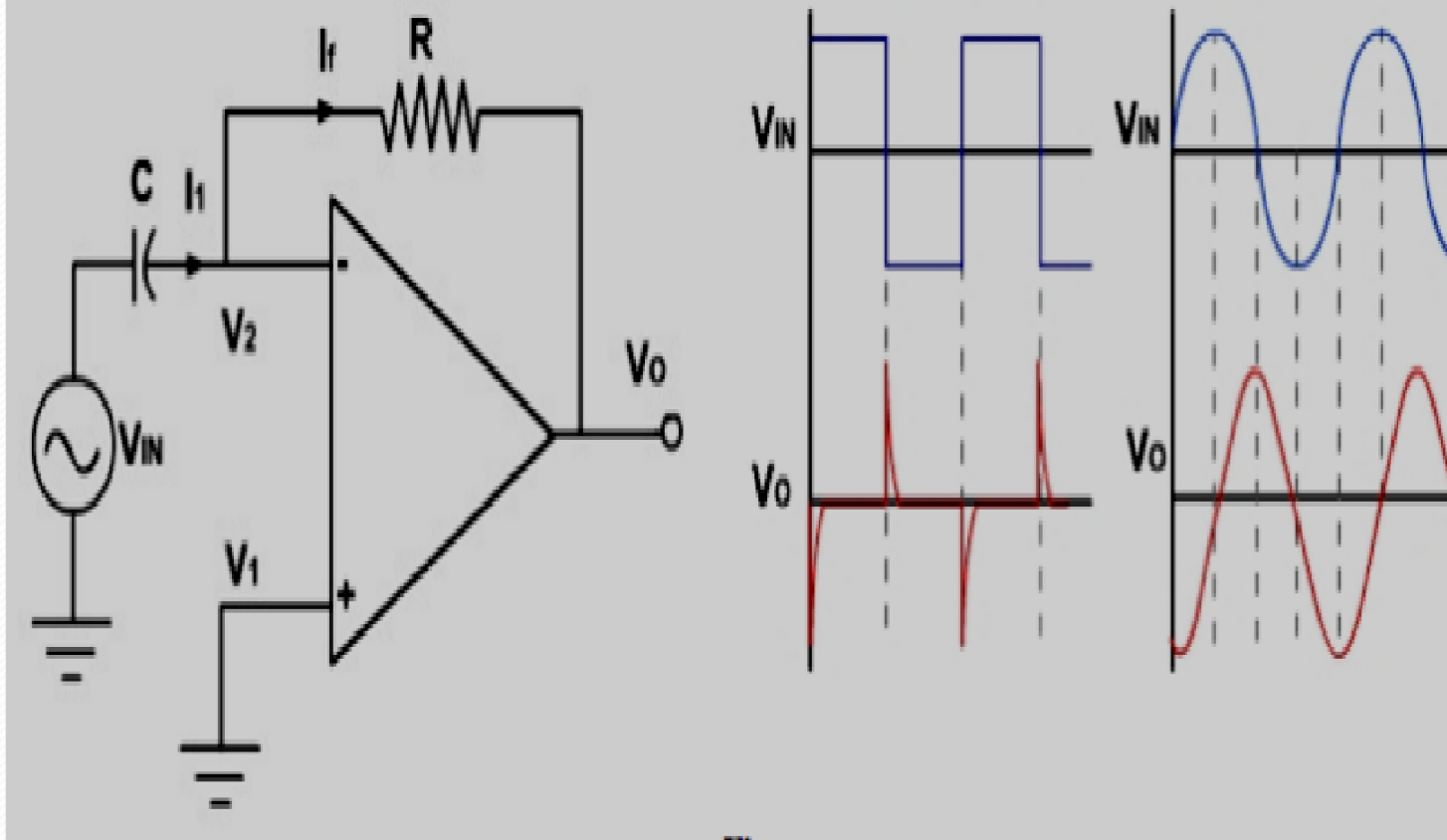A circuit in which the output voltage waveform is the differentiation of input voltage is called differentiator, as shown in Fig. .



Since, $i_{in} = i_f$

$$\text{Therefore, } C \frac{d}{dt}(V_{in} - 0) = \frac{0 - V_o}{R}$$

$$V_o = -RC \frac{dV_{in}}{dt}$$

Thus the output v_o is equal to the RC times the negative instantaneous rate of change of the input voltage v_{in} with time. A cosine wave input produces sine output.

Op amp gain bandwidth product

When designing an op amp circuit, a figure known as the op amp gain bandwidth product is important.

- The op amp gain bandwidth product is generally specified for a particular op amp type in an open loop configuration and the output loaded:

Where:

$$\text{Gain bandwidth product} = A_v \times f$$

GB = op amp gain bandwidth product

A_v = Voltage gain

f = cut off frequency (Hz)

- The op amp gain bandwidth product is constant for voltage-feedback amplifiers. However it is not applicable for current feedback amplifiers because relationship between gain and bandwidth is not linear.

Slew RATE

- The slew rate of an op amp or any amplifier circuit is the rate of change in the output voltage caused by a step change on the input.
- It is measured as a voltage change in a given time - typically $V / \mu s$ or V / ms .
- Low power op-amps may only have figures of a volt per microsecond, whereas there are fast operational amplifiers capable to providing rates of $1000 V / \mu s$.
- $SR = \frac{dv_{out}}{dv_{ios}}$