

# OSCILLATORS


# OSCILLATORS

Oscillation: an effect that repeatedly and regularly fluctuates about the mean value

Oscillator: circuit that produces oscillation

Characteristics: wave-shape, frequency, amplitude, distortion, stability

# BASIC LINEAR OSCILLATOR

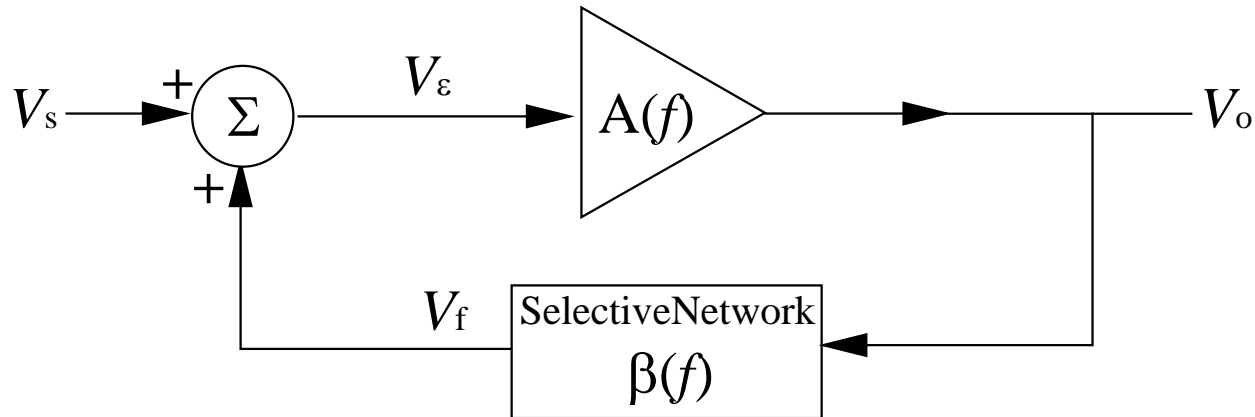

$$V_o = AV_\varepsilon = A(V_s + V_f) \quad \text{and} \quad V_f = \beta V_o$$


$$\Rightarrow \frac{V_o}{V_s} = \frac{A}{1 - A\beta}$$

If  $V_s = 0$ , the only way that  $V_o$  can be nonzero is that **loop gain  $A\beta=1$**  which implies that


$$|A\beta| = 1 \quad (\mathbf{Barkhausen\ Criterion})$$

$$\angle A\beta = 0$$

# TYPES OF OSCILLATIONS

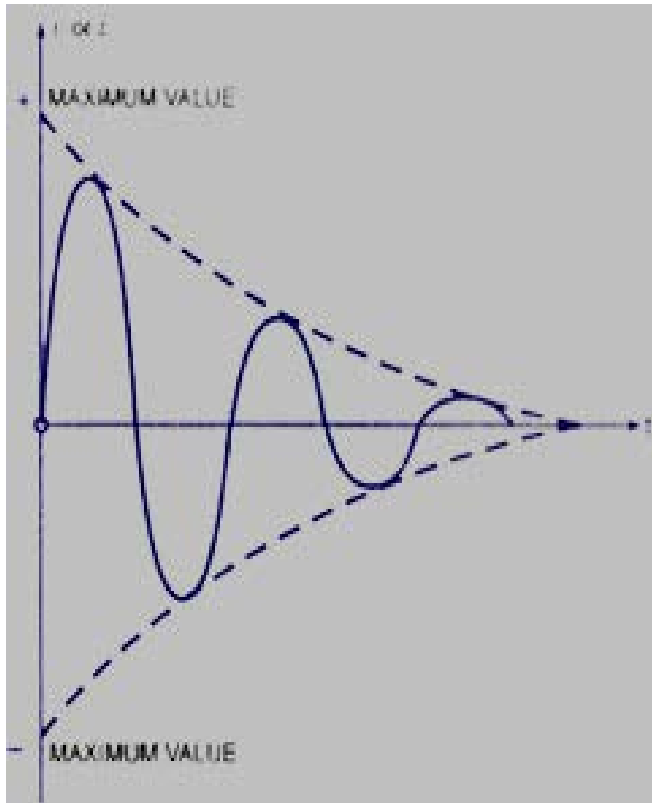


*(a) Damped Oscillations*

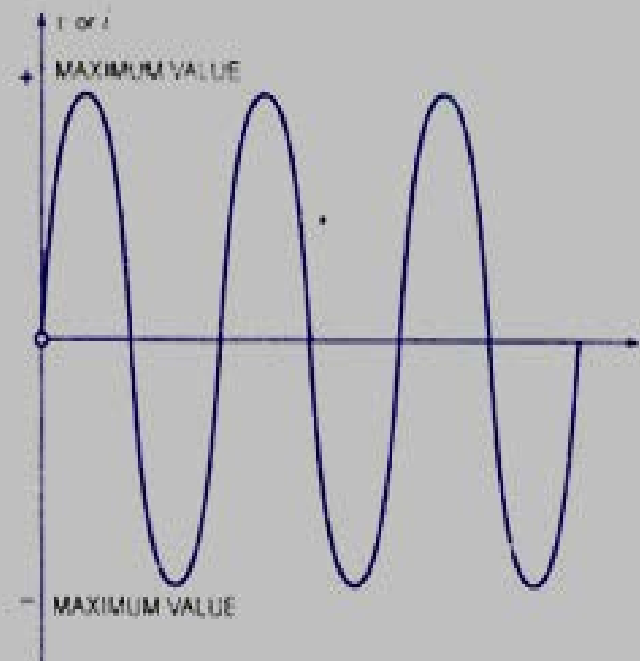

*(b) Undamped or Sustained Oscillations*

# Oscillator Operation

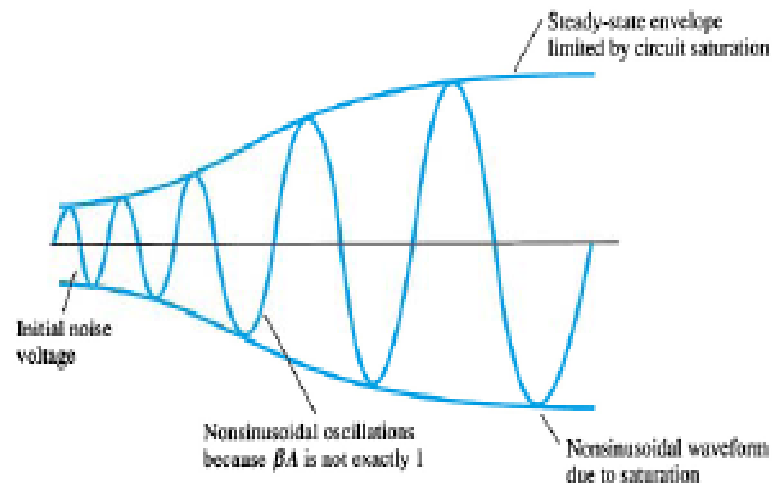


**The feedback signal must be positive.**

**If the feedback signal is not positive or the gain is less than one, the oscillations dampens out.**

**The overall gain must equal one (unity gain).**


**If the overall gain is greater than one, the oscillator eventually saturates.**

# SIGNAL GENERATORS / OSCILLATORS

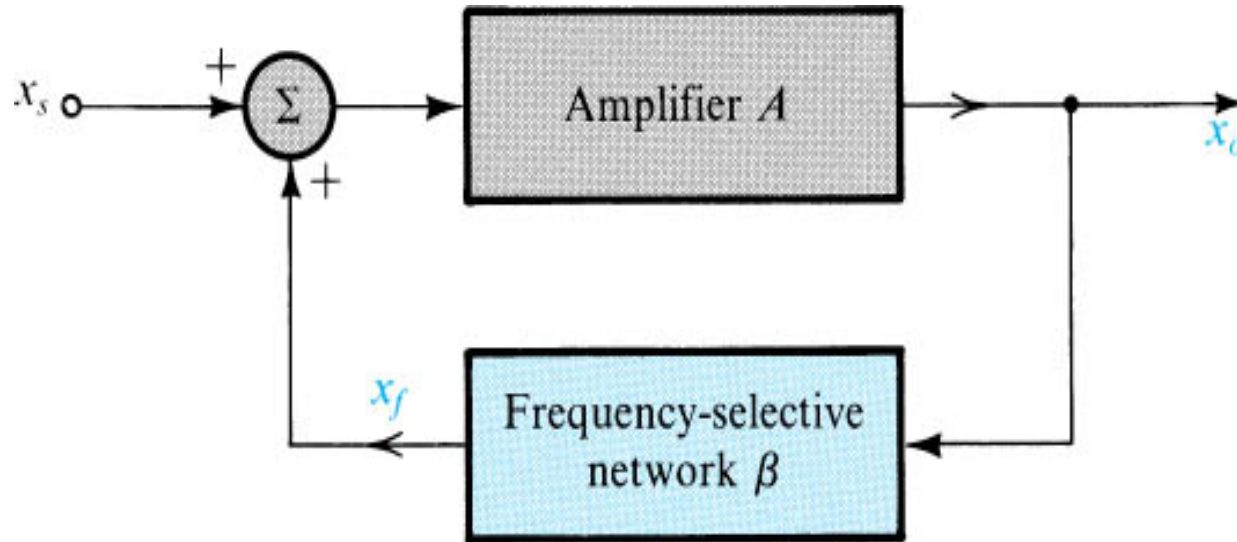

- A positive-feedback loop is formed by an amplifier and a frequency-selective network
- In an actual oscillator circuit, no input signal will be present

# INTEGRANT OF LINEAR OSCILLATORS

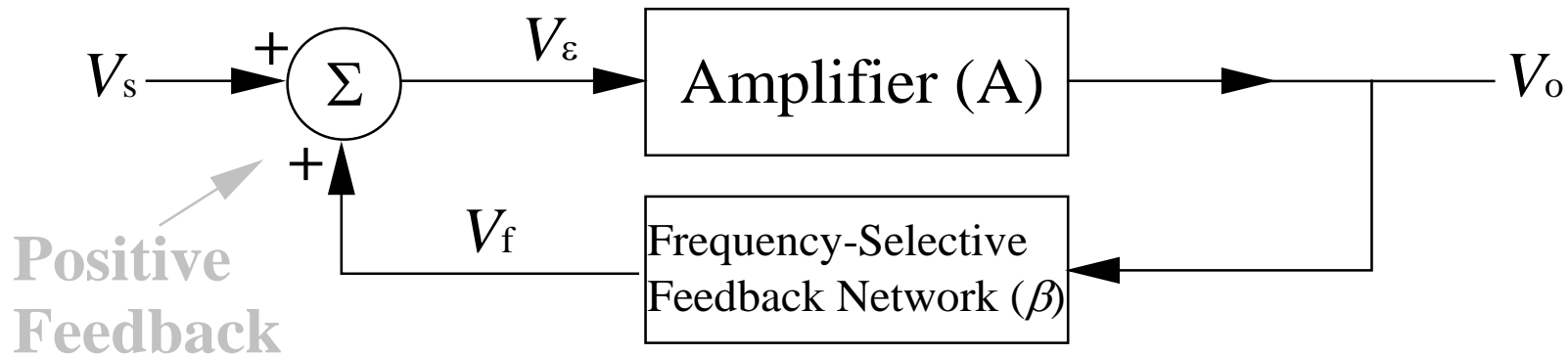

For sinusoidal input is connected

“**Linear**” because the output is approximately sinusoidal

A linear oscillator contains:

- a frequency selection feedback network
- an amplifier to maintain the loop gain at **unity**

# TYPES OF OSCILLATORS

1. Hartley Oscillator
2. Colpitt's oscillator
3. Wien Bridge Oscillators
4. RC Phase-Shift Oscillators
5. Crystal Oscillator




# Hartley Oscillator Circuit

The frequency of oscillation is determined by:


$$f_o = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

where:

$$L_{eq} = L_1 + L_2 + 2M$$

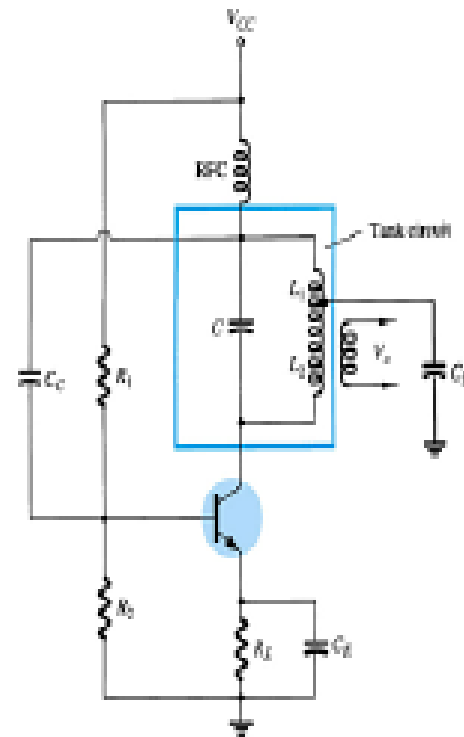

# COLPITTS OSCILLATOR

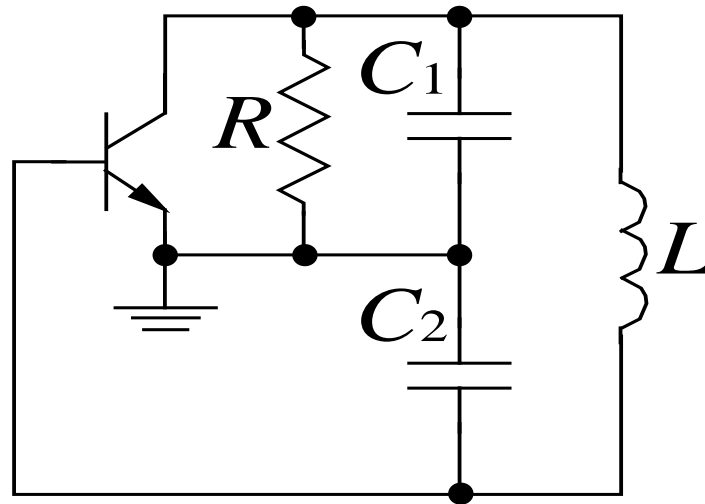

In the equivalent circuit, it is assumed that:

- Linear small signal model of transistor is used
- The transistor capacitances are neglected
- Input resistance of the transistor is large enough


# Phase-Shift Oscillator

The amplifier must supply enough gain to compensate for losses. The overall gain must be unity.

The RC networks provide the necessary phase shift for a positive feedback.

The values of the RC components also determine the frequency of oscillation:

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

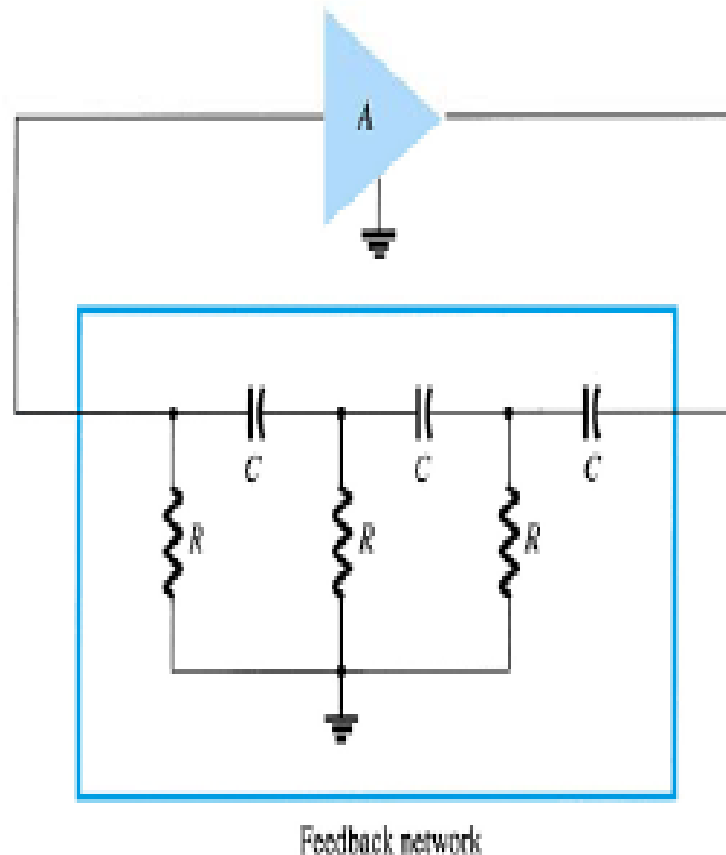

# Crystal Oscillators

The crystal appears as a resonant circuit.

The crystal has two resonant frequencies:


## Series resonant condition

- RLC determine the resonant frequency
- The crystal has a low impedance
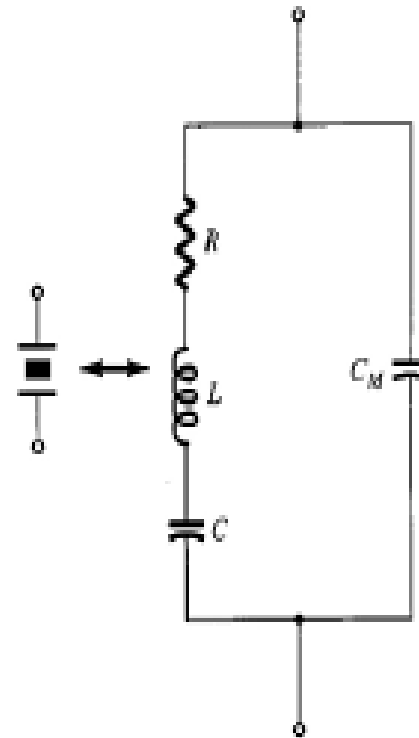
## Parallel resonant condition



- $RL$  and  $C_M$  determine the resonant frequency
- The crystal has a high impedance

The series and parallel resonant frequencies are very close, within 1% of each other.



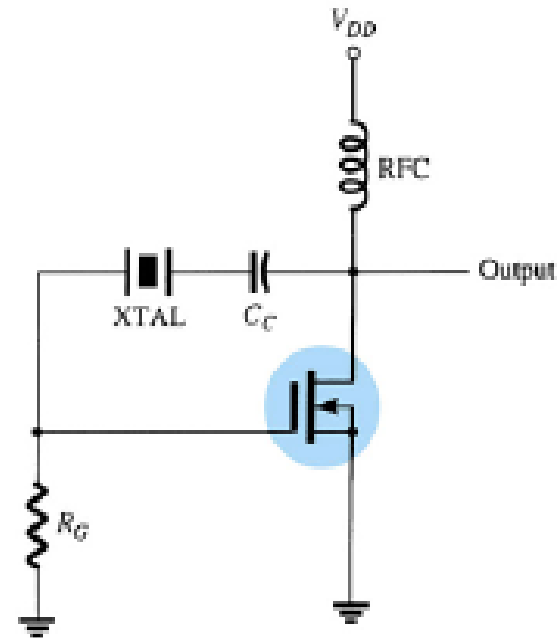
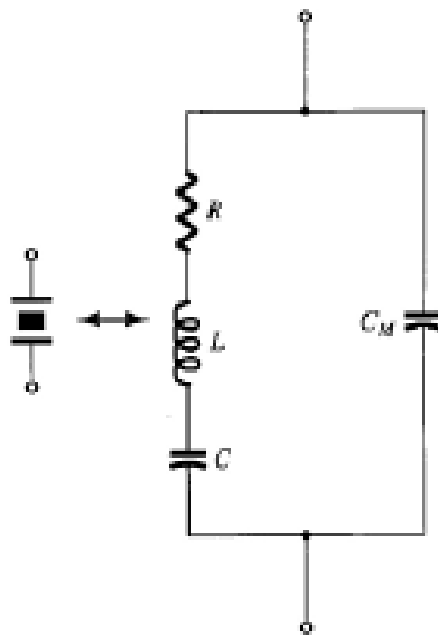
# Series Resonant Crystal Oscillator

- RLC determine the resonant frequency
- The crystal has a low impedance


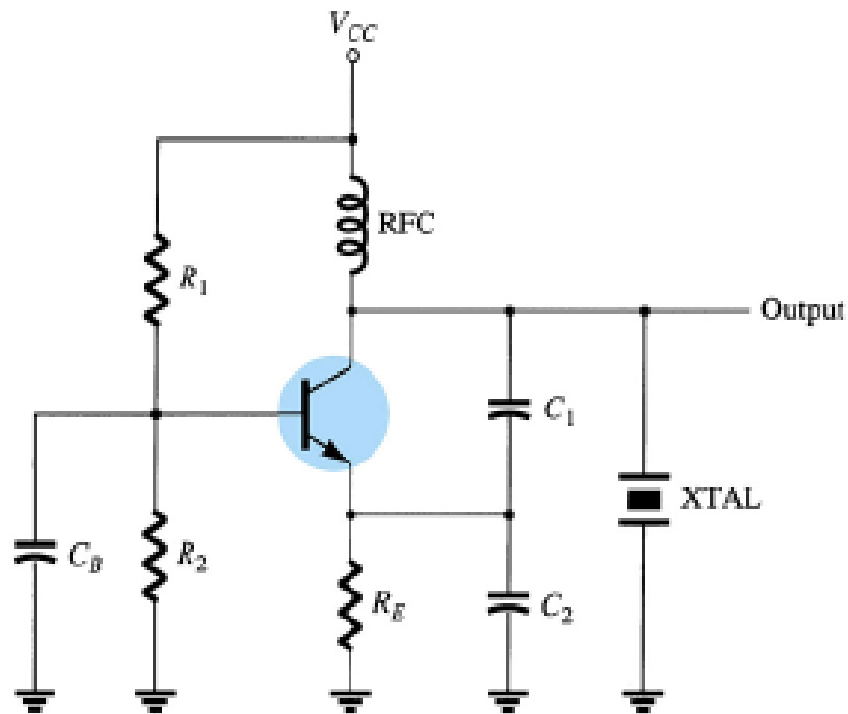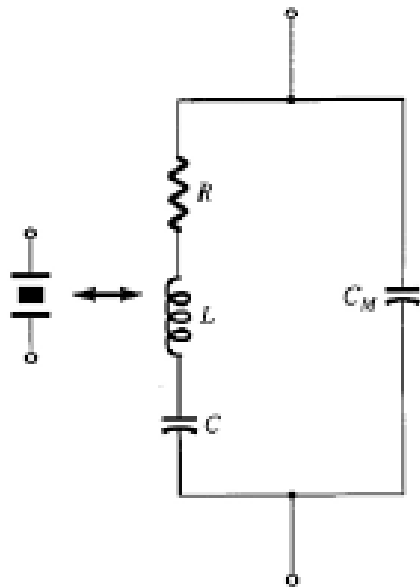
# Parallel Resonant Crystal Oscillator


- $R_L$  and  $C_M$  determine the resonant frequency
- The crystal has a high impedance


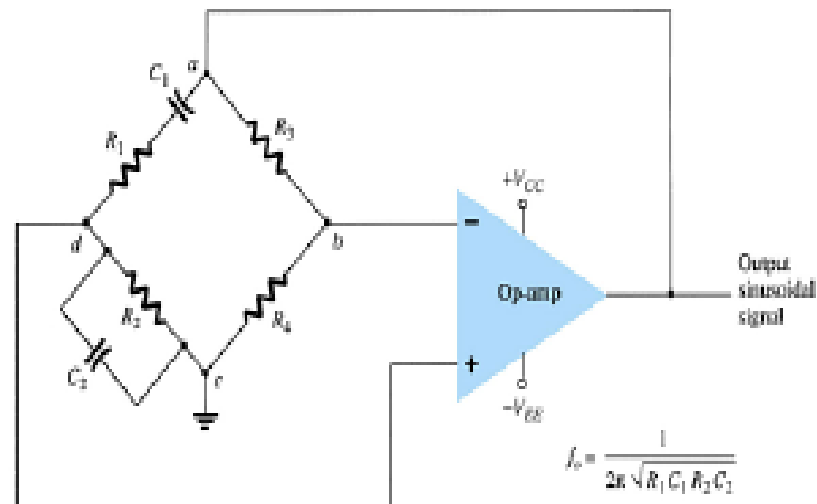
# Wien Bridge Oscillator

The amplifier must supply enough gain to compensate for losses. The overall gain must be unity.

- The feedback resistors are  $R_3$  and  $R_4$ .
- The phase-shift components are  $R_1$ ,  $C_1$  and  $R_2$ ,  $C_2$ .



# APPLICATION OF OSCILLATORS

- Oscillators are used to generate signals, e.g.
  - Used as a local oscillator to transform the RF signals to IF signals in a receiver;
  - Used to generate RF carrier in a transmitter
  - Used to generate clocks in digital systems;
  - Used as sweep circuits in TV sets and CRO.