

# Electrical Technology

# Contents

- Half Power point frequencies in series resonance
- Parallel resonance
- Impedance curve in parallel resonance
- Test yourself
- NPTEL Link

# Series Resonance

The peak power delivered to the circuit is;

$$P = \frac{V_m^2}{R}$$

The so-called half-power is given when  $I = \frac{V_m}{\sqrt{2}R}$ .

We find the frequencies,  $\omega_1$  and  $\omega_2$ , at which this half-power occurs by using;

$$\sqrt{2}R = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

# Series Resonance

After some insightful algebra one will find two frequencies at which the previous equation is satisfied, they are:

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

and

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

The two half-power frequencies are related to the resonant frequency by

$$\omega_o = \sqrt{\omega_1 \omega_2}$$

# Series Resonance

The bandwidth of the series resonant circuit is given by;

$$BW = w_b = w_2 - w_1 = \frac{R}{L}$$

We define the Q (quality factor) of the circuit as;

$$Q = \frac{w_o L}{R} = \frac{1}{w_o RC} = \frac{1}{R} \sqrt{\left(\frac{L}{C}\right)}$$

Using Q, we can write the bandwidth as;


$$BW = \frac{w_o}{Q}$$

These are all important relationships.


# Parallel Resonance

## Background

Consider the circuits shown below:

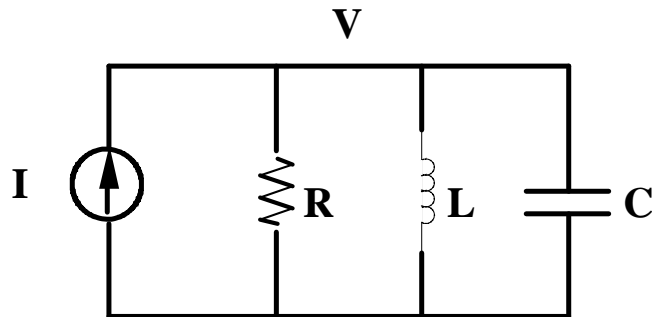
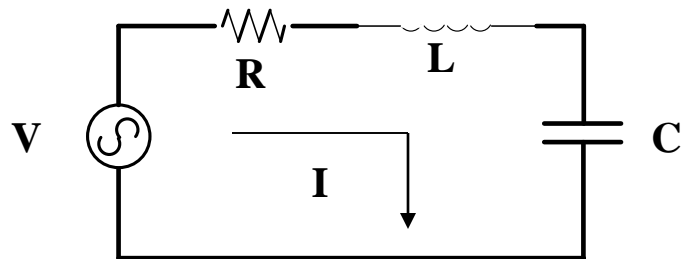
$$I = V \left[ \frac{1}{R} + j\omega L + \frac{1}{j\omega C} \right]$$



$$V = I \left[ R + j\omega L + \frac{1}{j\omega C} \right]$$

# Series Resonance-Parallel Resonance

## Duality

$$I = V \left[ \frac{1}{R} + j\omega C + \frac{1}{j\omega L} \right] \quad V = I \left[ R + j\omega L + \frac{1}{j\omega C} \right]$$

We notice the above equations are the same provided:

$$I \longleftrightarrow V$$

$$R \longleftrightarrow \frac{1}{R}$$

$$L \longleftrightarrow C$$

If we make the inner-change, then one equation becomes the same as the other.

For such case, we say the one circuit is the dual of the other.

# Parallel Resonance

## Background

What this means is that for all the equations we have derived for the parallel resonant circuit, we can use for the series resonant circuit provided we make the substitutions:

$R$  replaced by  $\frac{1}{R}$

$L$  replaced by  $C$

$C$  replaced by  $L$



# Series Resonance

## Duality

$$I = V \left[ \frac{1}{R} + j\omega C + \frac{1}{j\omega L} \right] \quad V = I \left[ R + j\omega L + \frac{1}{j\omega C} \right]$$

We notice the above equations are the same provided:

$$I \longleftrightarrow V$$


$$R \longleftrightarrow \frac{1}{R}$$

$$L \longleftrightarrow C$$


If we make the inner-change, then one equation becomes the same as the other.

For such case, we say the one circuit is the dual of the other.

# PARALLEL RESONANCE

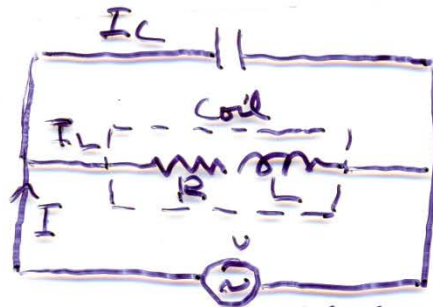

Typical parallel Resonant Circuit

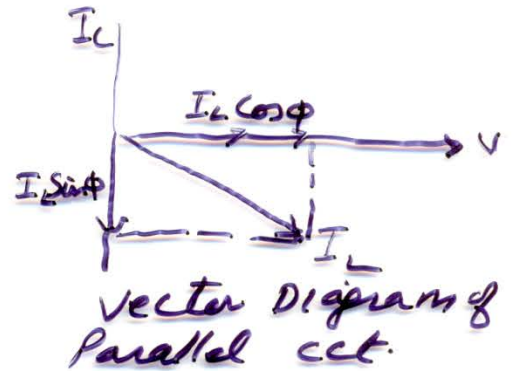

$$I_C = \frac{V}{X_C}$$

$$I_L = \frac{V}{Z_L} = \frac{V}{\sqrt{R^2 + X_L^2}}$$

$$\cos \phi = \frac{R}{Z_L}$$

At resonance

$$I_C = I_L \sin \phi$$

(capacitive current = inductive part of coil current)  
ie imaginary components of  $I_L$  &  $I_C$  cancel each other

$$\frac{V}{X_C} = \frac{V}{Z_L} \times \frac{X_L}{Z_L}$$

$$Z_L^2 = X_C X_L$$

$$= \frac{1}{\omega C} \times \omega L = \frac{L}{C}$$

$$Z_L = \sqrt{\frac{L}{C}} \quad \text{--- (1)}$$

$$\sqrt{R^2 + \omega_0^2 L^2} = \sqrt{\frac{L}{C}}$$

$$R^2 + \omega_0^2 L^2 = \frac{L}{C}$$

$$\omega_0^2 L^2 = \frac{L}{C} - R^2$$

## Q-factor

$$Q = \frac{I_C}{I} = \frac{V/X_C}{V/Z_L}$$

$$= \frac{Z_L}{X_C} = \frac{L}{CR} \times \frac{1}{\omega RC}$$

$$= \frac{L}{CR} \times \omega RC$$

$$= \omega \frac{L}{R}$$

$Q = \omega \frac{L}{R} = Q \text{ factor of series circuit}$

$$\omega_0^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$


∴ resistance of coil is neglected (low  
 $f_0 = \frac{1}{2\pi\sqrt{LC}}$  is frequency of the resonance of the series ckt.

At resonance, only  $I_L$  (or)  $I_C$  remains

$$\frac{V}{Z_0} = \frac{V}{Z_L} \cdot \frac{R}{Z_L} \text{ or } Z_0 = \frac{Z_L^2}{R} = \frac{L}{CR} \quad \text{fm(1)}$$

The equivalent impedance of the parallel resonating circuit is  $\frac{L}{CR}$ . This impedance is called DYNAMIC RESISTANCE of the parallel circuit.  $R$  is less, Impedance is very high at resonance. Current is much lower as parallel circuit. This circuit is also called REFLECTOR CIRCUIT.  $P_f$  is unity
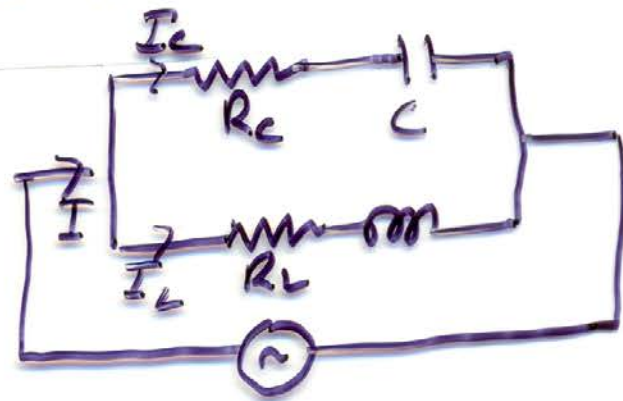
# RESONANCE BETWEEN PARALLEL R-C & R-L CIRCUIT



$$Y = \frac{1}{R_C - jX_C} + \frac{1}{R_L + jX_L}$$

$$= \frac{R_C}{R_C^2 + X_C^2} + \frac{R_L}{R_L^2 + X_L^2}$$

$$+ j \left[ \frac{X_C}{R_C^2 + X_C^2} - \frac{X_L}{R_L^2 + X_L^2} \right] = G + jB$$

At resonance susceptance is zero i.e.  $\frac{X_C}{R_C^2 + X_C^2} = \frac{X_L}{R_L^2 + X_L^2}$

So  $R_C^2 = R_L^2 = \frac{L}{C}$  then

B is always zero.

This shows that the circuit will be at resonance for any frequency provided  $R_C = R_L = \sqrt{\frac{L}{C}}$ .

Again in this ckt  $I_c \sin \phi_1 = I_L \sin \phi_2$

$$\frac{V}{R_c^2 + \frac{1}{\omega_0^2 C^2}} \cdot \frac{1}{\omega_0 C} = \frac{V}{\sqrt{R_L^2 + \omega_0^2 L^2}} \cdot \frac{\omega_0 L}{\sqrt{R_L^2 + \omega_0^2 L^2}}$$

gives  $\omega_0^2 [L^2 - R_c^2 LC] = \frac{L}{C} - R_L^2$

$$\omega_0^2 = \frac{\frac{L}{C} - R_L^2}{L^2 - R_c^2 LC}$$

$$\omega_0^2 = \frac{1}{LC} \left[ \frac{\frac{L}{C} - R_L^2}{\frac{L}{C} - R_c^2} \right]$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{\frac{L}{C} - R_L^2}{\frac{L}{C} - R_c^2}}$$

$$\begin{cases} \sin \phi_1 = \frac{x_c}{Z_{RC \text{ ckt}}} \\ \sin \phi_2 = \frac{x_L}{Z_{RL \text{ ckt}}} \end{cases}$$

# PARALLEL RESONANCE

$$Y(j\omega) = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C$$

$$= G + j\left(\omega C - \frac{1}{\omega L}\right)$$

$$= G + jB \quad (B = B_C - B_L)$$

$$|Y(j\omega)| = \sqrt{G^2 + B^2} = \sqrt{G^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}$$

$$I = VY = V \sqrt{G^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}$$

The ckt is at resonance when Susceptance is Zero  
The admittance then becomes Minimum.  $\phi = G$ .


The current the ckt is minimum.  $I = VG$

frequency is fr.

$$\omega_r C = \frac{1}{\omega_r L}$$


$$\omega_r^2 = \frac{1}{LC}$$
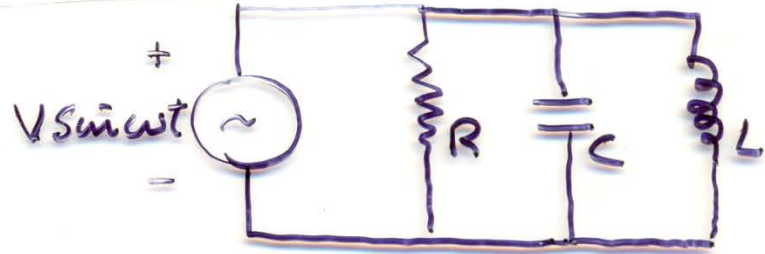
$$\text{or } \omega_r = \frac{1}{\sqrt{LC}}$$




Parallel Resonance ckt


$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

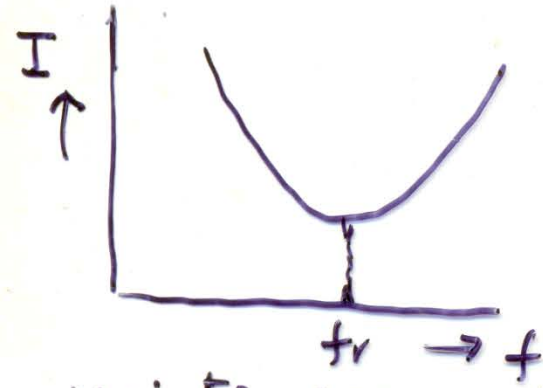

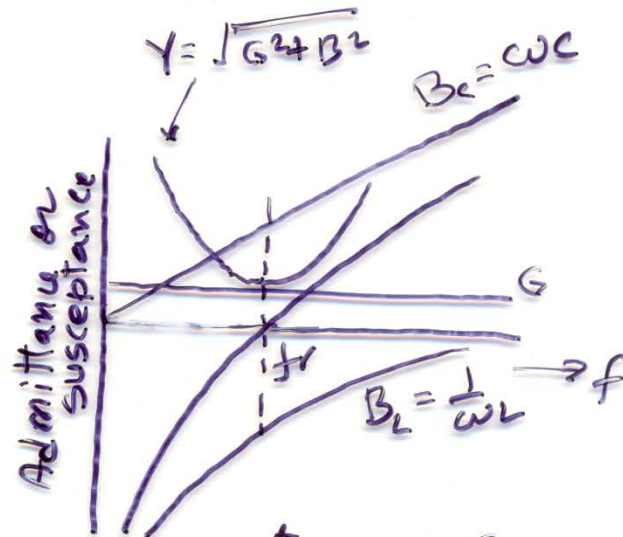variation of Current near Parallel Resonance



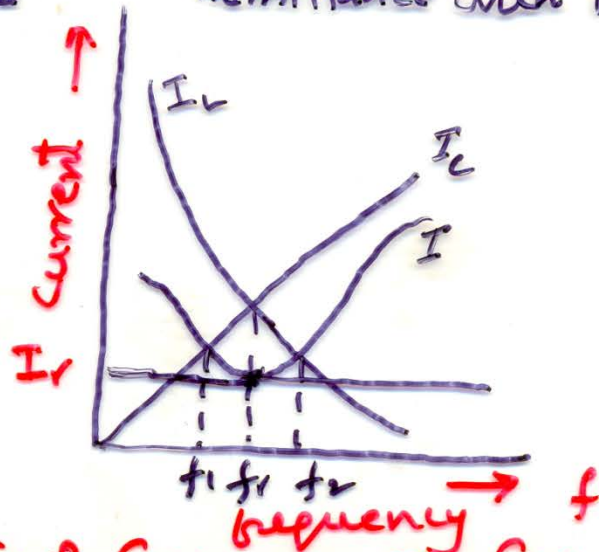variation of Susceptance, Admittance with Frequency in Parallel LC



variation of Current with Frequency in Parallel Resonant circuit

# Q-FACTOR OF PARALLEL RESONANCE

The condition of resonance occurs when susceptance is zero

$$Y = G + jB$$

$$= \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$= \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

$$\omega_r C = \frac{1}{\omega_r L}$$



$$\omega_r = \frac{1}{\sqrt{LC}}$$

$$\text{Bandwidth} = f_2 - f_1$$

For parallel circuit

$$\omega_1 C - \frac{1}{\omega_1 L} = -\frac{1}{R} \quad \text{--- (i)}$$
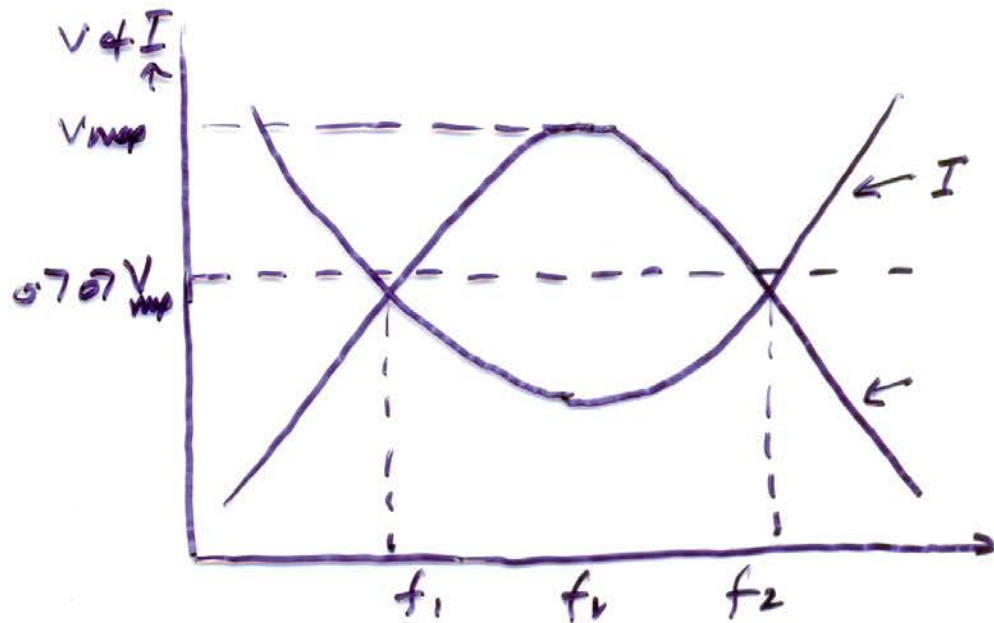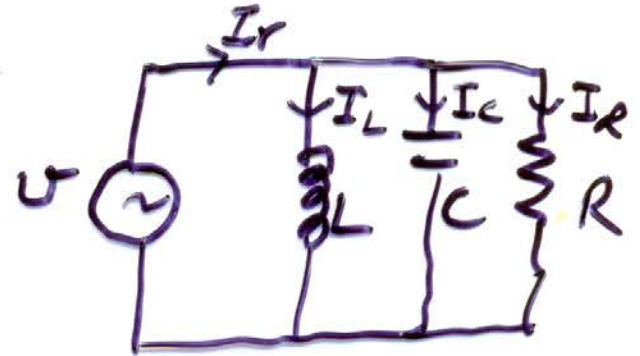
$$\omega_2 C - \frac{1}{\omega_2 L} = \frac{1}{R} \quad \text{--- (ii)}$$





$$\omega_1^2 + \frac{\omega_1}{RC} - \frac{1}{LC} = 0$$

$$\omega_1 = \frac{-1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 - \omega_1 = \frac{1}{RC} = \frac{\omega_r}{R\omega_r C}$$

$$\boxed{BW = \frac{1}{RC}}$$

$$Q_r = \frac{\omega_r}{\omega_2 - \omega_1} = \frac{\omega_r}{1/RC} = \omega_r RC$$

$$Q_r = \frac{2\pi \times \frac{1}{2} LI^2}{\frac{I^2}{2} R \times \frac{1}{f}} \cdot \frac{2\pi f \cdot \frac{1}{2} L \left(\frac{V}{\omega L}\right)^2 \cdot R}{\frac{V^2}{2}}$$





$$= \frac{2\pi f L R}{\omega^2 L^2} = \frac{R}{\omega L}$$

$$Q_r = 2\pi \frac{\frac{1}{2} CV^2}{\left(\frac{V^2}{2R}\right) \times \frac{1}{f}} = 2\pi f CR = \omega CR$$

current magnification occurs in parallel Resonant ckt.  $V=IR$

$$I_L = \frac{V}{\omega L} = \frac{IR}{\omega L} = I Q_r; \quad I_C = \frac{V}{1/\omega RC} = \frac{IR}{\omega R} = I Q_r$$

# COMPARISON B/W SERIES & PARALLEL RESONANCE

S.No	Point of Comparison	SERIES	PARALLEL
1	Impedance	Minimum $Z$ 	maximum $Z$ 
2	Current	maximum $I$ 	minimum $I$ 
3.	$f < f_r$	$X_L > X_C$	$B_C > B_L$
4.	$f > f_r$	$X_C > X_L$	$B_L > B_C$
5	p.f	Unity	Unity
6	Q-factor	$Q = \frac{\omega L}{R}$	$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$
7	$f_r$	$\frac{1}{2\pi\sqrt{LC}}$	$\frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$
8	magnification	voltage	current
9	$Z$	$Z = R$	$Z = \frac{L}{CR}$
10	Admittance	maximum	minimum
11	Type of behaviour	Selective (Acceptance ckt)	Rejective

# Parallel Resonance

## Parallel Resonance

$$\omega_o = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{\omega_o L}{R}$$

$$BW = (\omega_2 - \omega_1) = \omega_{BW} = \frac{R}{L}$$

$$\omega_1, \omega_2 = \left[ \frac{\mp R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$$

$$\omega_1, \omega_2 = \omega_o \left[ \frac{\mp 1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$$

## Series Resonance

$$\omega_o = \frac{1}{\sqrt{LC}}$$

$$Q = \omega_o RC$$

$$BW = \omega_{BW} = \frac{1}{RC}$$

$$\omega_1, \omega_2 = \left[ \frac{\mp 1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \right]$$

$$\omega_1, \omega_2 = \omega_o \left[ \frac{\mp 1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$$