

Electrical Technology

Contents

- Transformer Test
- Open Circuit Test
- Short Circuit Test
- Regulation of Transformer
- Efficiency of Transformer & condition for maximum efficiency
- Test Yourself
- NPTEL Link

Transformer tests

- The performance of a transformer can be calculated on the basis of its equivalent circuit which contains the 4 main parameters:
 1. Equivalent resistance R_{01} (or R_{02})
 2. Equivalent leakage reactance X_{01} (or X_{02})
 3. Core loss resistance R_0
 4. Magnetizing reactance X_0
- These parameters are determined from the following tests:
 - a) Open circuit test
 - b) Short circuit test

Open circuit test



Short Circuit test


- This test is conducted to determine:
 1. Full-load copper loss
 2. Equivalent resistance & reactance referred to metering side.




Regulation of a transformer

- Voltage regulation is defined as: *“the change in secondary voltage when rated load at a specified power is removed”*.
- Let, E_2 = sec. terminal voltage at no load
 V_2 = sec. terminal voltage at full load

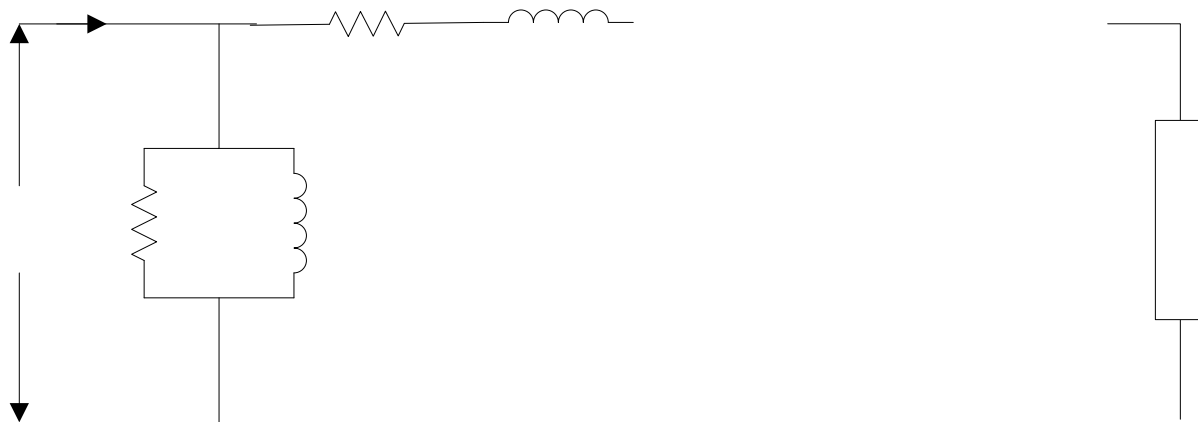Then, % regulation =
$$\frac{E_2 - V_2}{V_2} \times 100$$



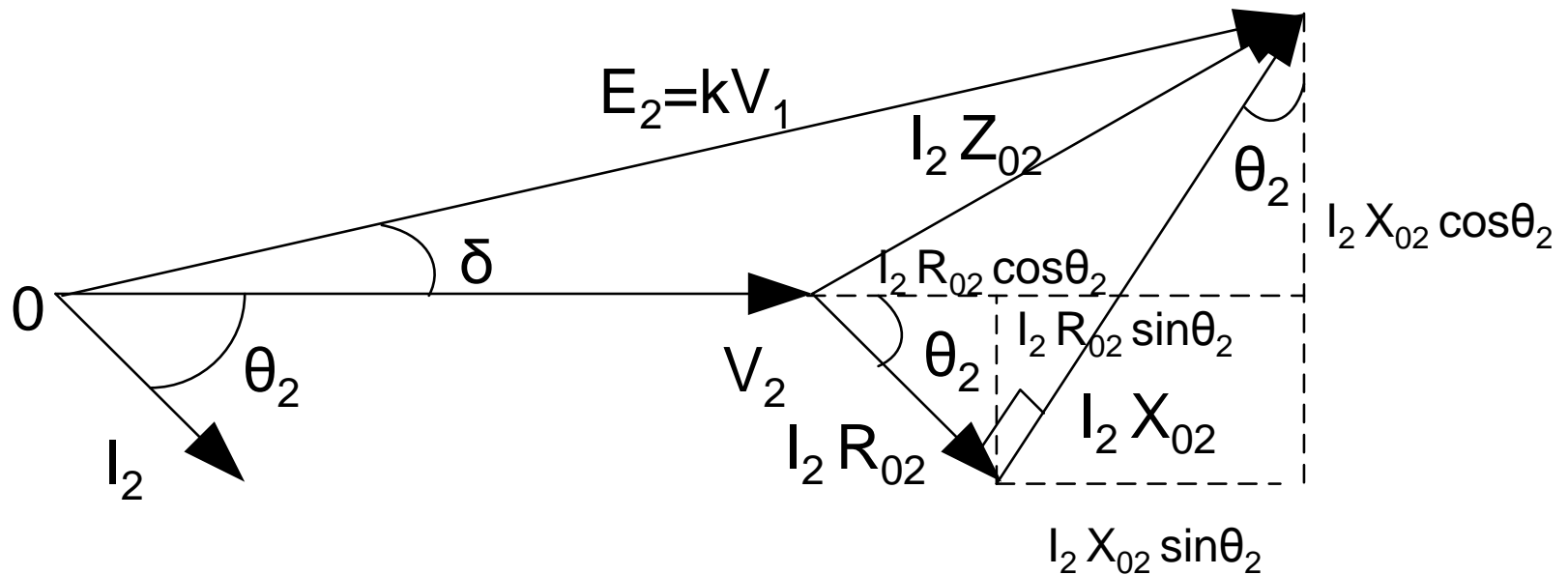Regulation expressed in terms of secondary values



$$\begin{aligned}
E_2^2 &= (V_2 + I_2 R_{02} \cos \theta_2 + I_2 X_{02} \sin \theta_2)^2 + (I_2 X_{02} \cos \theta_2 - I_2 R_{02} \sin \theta_2)^2 \\
&= V_2^2 + I_2^2 R_{02}^2 \cos^2 \theta_2 + I_2^2 X_{02}^2 \sin^2 \theta_2 + 2V_2 I_2 R_{02} \cos \theta_2 \\
&\quad + 2I_2^2 R_{02} X_{02} \sin \theta_2 \cos \theta_2 + 2V_2 I_2 X_{02} \sin \theta_2 + I_2^2 X_{02}^2 \cos^2 \theta_2 + I_2^2 R_{02}^2 \sin^2 \theta_2 \\
&\quad - 2I_2^2 R_{02} X_{02} \sin \theta_2 \cos \theta_2 \\
&= V_2^2 + I_2^2 R_{02}^2 + I_2^2 X_{02}^2 + 2V_2 I_2 R_{02} \cos \theta_2 + 2V_2 I_2 X_{02} \sin \theta_2 \\
E_2 &= \sqrt{V_2^2 + I_2^2 R_{02}^2 + I_2^2 X_{02}^2 + 2V_2 I_2 R_{02} \cos \theta_2 + 2V_2 I_2 X_{02} \sin \theta_2}
\end{aligned}$$

Efficiency of a transformer

- Losses in a transformer –
 1. Core or Iron loss = Hysteresis loss + Eddy Current loss (from OC test)
 2. Copper loss = $I_1^2 R_1 + I_2^2 R_2 = I_1^2 R_{01} = I_2^2 R_{02}$
(from SC test)

$$\begin{aligned} \text{Efficiency} &= \frac{\text{Output}}{\text{Input}} = \frac{\text{Output}}{\text{Output} + \text{Losses}} \\ &= \frac{\text{Output}}{\text{Output} + \text{Iron loss} + \text{Cu loss}} \end{aligned}$$

Condition for maximum efficiency

- Cu loss = $I_1^2 R_{01}$ Iron loss = $W_h + W_e = W_i$
considering primary side

Primary input = $V_1 I_1 \cos \phi_1$

$$\begin{aligned}\eta &= \frac{V_1 I_1 \cos \phi_1 - \text{losses}}{V_1 I_1 \cos \phi_1} \\ &= \frac{V_1 I_1 \cos \phi_1 - I_1^2 R_{01} - W_i}{V_1 I_1 \cos \phi_1} \\ &= 1 - \frac{I_1 R_{01}}{V_1 \cos \phi_1} - \frac{W_i}{V_1 I_1 \cos \phi_1}\end{aligned}$$

Differentiating both sides w.r.t I_1 , we get

$$\frac{d\eta}{dI_1} = 0 - \frac{R_{01}}{V_1 \cos\phi_1} + \frac{W_i}{V_1 I_1^2 \cos\phi_1}$$

For η to be maximum, $\frac{d\eta}{dI_1} = 0$

$$0 = 0 - \frac{R_{01}}{V_1 \cos\phi_1} + \frac{W_i}{V_1 I_1^2 \cos\phi_1}$$

$$\Rightarrow \frac{R_{01}}{V_1 \cos\phi_1} = \frac{W_i}{V_1 I_1^2 \cos\phi_1}$$

$$\Rightarrow I_1^2 R_{01} = W_i$$

Cu loss = Iron loss

The current corresponding to maximum efficiency is:

$$I_1 = \sqrt{\frac{W_i}{R_{01}}}$$

$$I_2 = \frac{I_1}{k} = \sqrt{\frac{W_i}{R_{02}}}$$

Efficiency of Transformer at any load

$$\eta = \frac{x \times \text{Full Load kVA} \times \text{p.f}}{x \times \text{Full Load kVA} \times \text{p.f} + \text{Iron Loss} + x^2 \times \text{Full Load Copper Loss}} \times 100\%$$

x = Ratio of Actual to Full Load kVA

Ex: A 2300/208 V, 500kVA, 60Hz transformer has the following data:

Test	V	A	W	Side used
O.C	208	85	1800	L.V
S.C	95	217.4	8200	H.V

Calculate efficiency of the transformer at 0.8 pf lagging & 1/4th rated load.

Solution

$$\eta = \frac{x \times \text{Full Load kVA} \times \text{p.f}}{x \times \text{Full Load kVA} \times \text{p.f} + \text{Iron Loss} + x^2 \times \text{Full Load Copper Loss}} \times 100\%$$

$$\eta = \frac{\frac{1}{4} \times 500 \times 0.8}{\left(\frac{1}{4} \times 500 \times 0.8\right) + \left(\frac{1}{4}\right)^2 \times 8.2 + 1.8}$$
$$= 97.74\%$$