




Design of Basic Computer

◆ The basic computer consists of the following hardware components

- 1. A memory unit with 4096 words of 16bits
- 2. Nine registers : AR, PC, DR, AC, IR, TR, OUTF, INPR, and SC
- 3. Seven F/Fs : I, S, E, R, IEN, FGI, and FGO
- 4. Two decoder in control unit : 3 x 8 operation decoder, 4 x 16 timing decoder
- 5. A 16-bit common bus
- **6. Control Logic Gates :**
- **7. Adder and Logic circuit connected to the AC input**

◆ Control Logic Gates

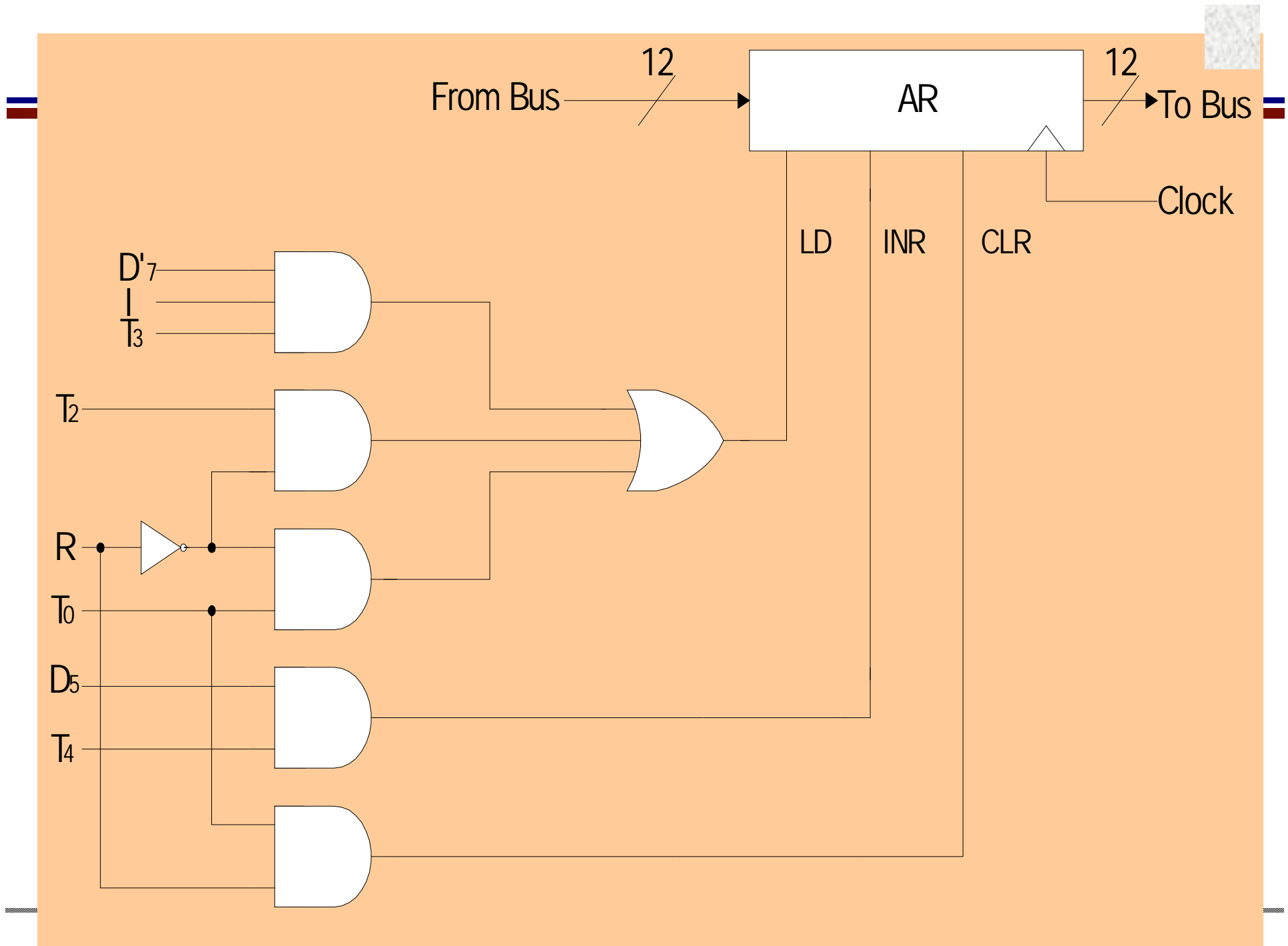- 1. Signals to control the inputs of the nine registers
 - 2. Signals to control the read and write inputs of memory
 - 3. Signals to set, clear, or complement the F/Fs
 - 4. Signals for $S_2 S_1 S_0$ to select a register for the bus
 - 5. Signals to control the AC adder and logic circuit
-





◆ Register Control : AR

- Control inputs of AR : **LD, INR, CLR**
- Find all the statements that change the AR

AR ← ?

in Tab. 5-6



$R'T_0 : AR \leftarrow PC$
$R'T_1 : AR \leftarrow IR(0-11)$
$D_7'IT_3 : AR \leftarrow M[AR]$
$RT_0 : AR \leftarrow 0$
$D_5T_4 : AR \leftarrow AR + 1$

- Control functions

$$\begin{cases} LD(AR) = R'T_0 + R'T_1 + D_7'IT_3 \\ CLR(AR) = RT_0 \\ INR(AR) = D_5T_4 \end{cases}$$



◆ Memory Control : READ

- Control inputs of Memory : **READ, WRITE**
- Find all the statements that specify a **read operation** in Tab. 5-6
- Control function

M[AR] ← ?


? ← M[AR]

$$READ = R'T_1 + D_7'IT_3 + (D_0 + D_1 + D_2 + D_3)T_4$$

◆ F/F Control : IEN IEN ← ?

- Control functions
 
$$\begin{cases} pB_7 : IEN \leftarrow 1 \\ pB_6 : IEN \leftarrow 0 \\ RT_2 : IEN \leftarrow 0 \end{cases}$$



J	K	Q(t+1)
0	1	0
1	0	1



◆ Bus Control

- Encoder for Bus Selection : *Tab. 5-7*

- » $S_0 = x_1 + x_3 + x_5 + x_7$

- » $S_1 = x_2 + x_3 + x_6 + x_7$

- » $S_2 = x_4 + x_5 + x_6 + x_7$

- $x_1 = 1$: *Bus ← AR = Find ? ← AR*

- » $D_4T_4 : PC ← AR$

- » $D_5T_5 : PC ← AR$

- » Control Function : $x_1 = D_4T_4 + D_5T_5$

- $x_2 = 1$: *Bus ← PC = Find ? ← PC*


"

"

- $x_7 = 1$: *Bus ← Memory = Find ? ← M[AR]*


- » Same as Memory Read

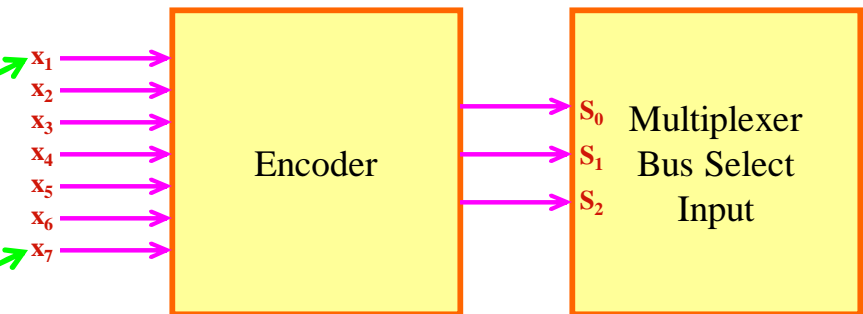- » Control Function : $x_7 = R'T_1 + D_7'IT_3 + (D_0 + D_1 + D_2 + D_3)T_4$






■ Design of Accumulator Logic

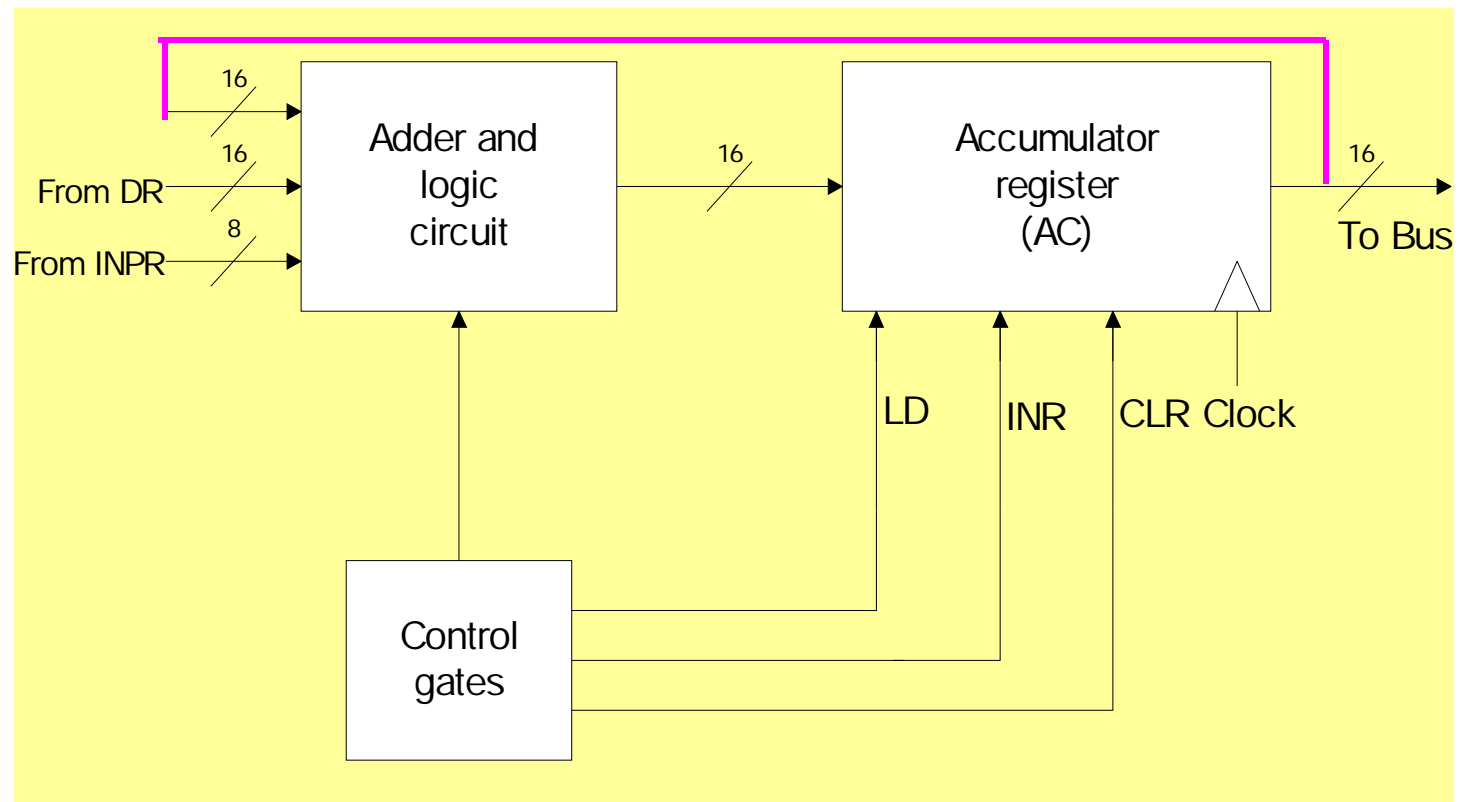


Circuits associated with Accumulator

◆ Control of AC Register :

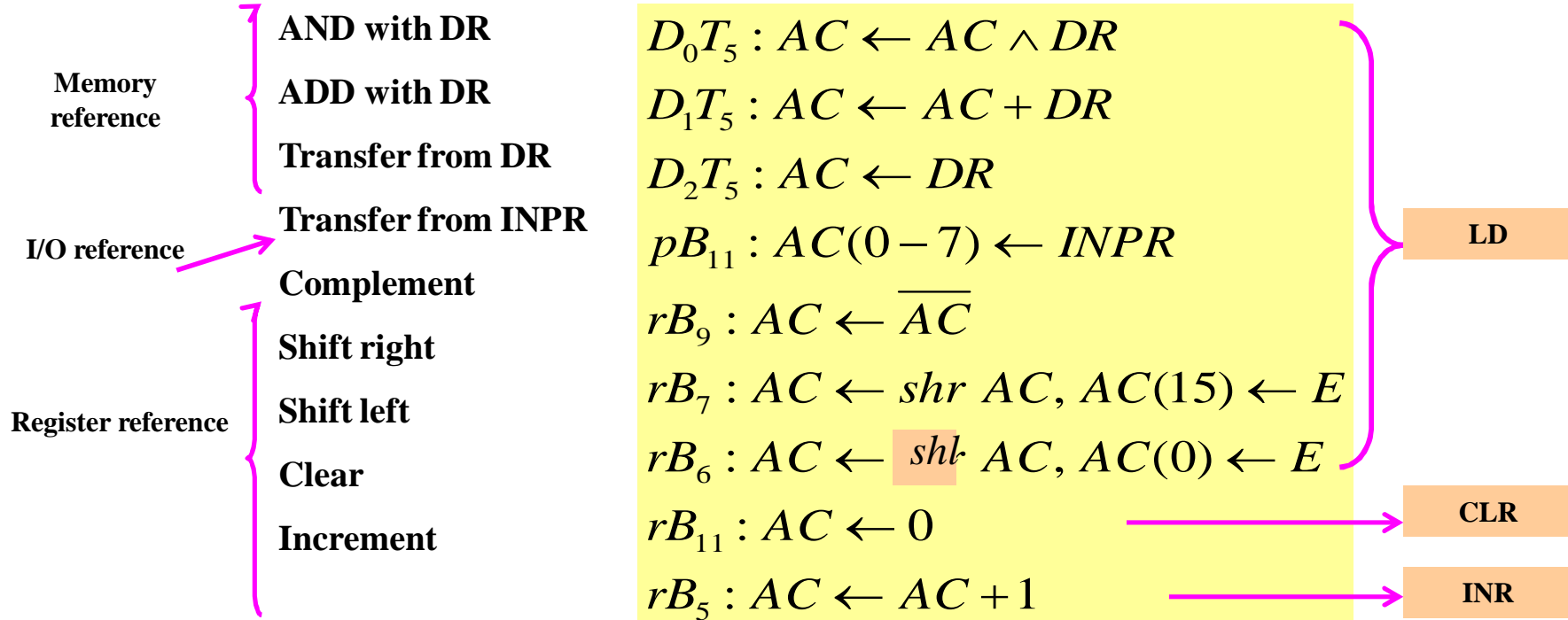

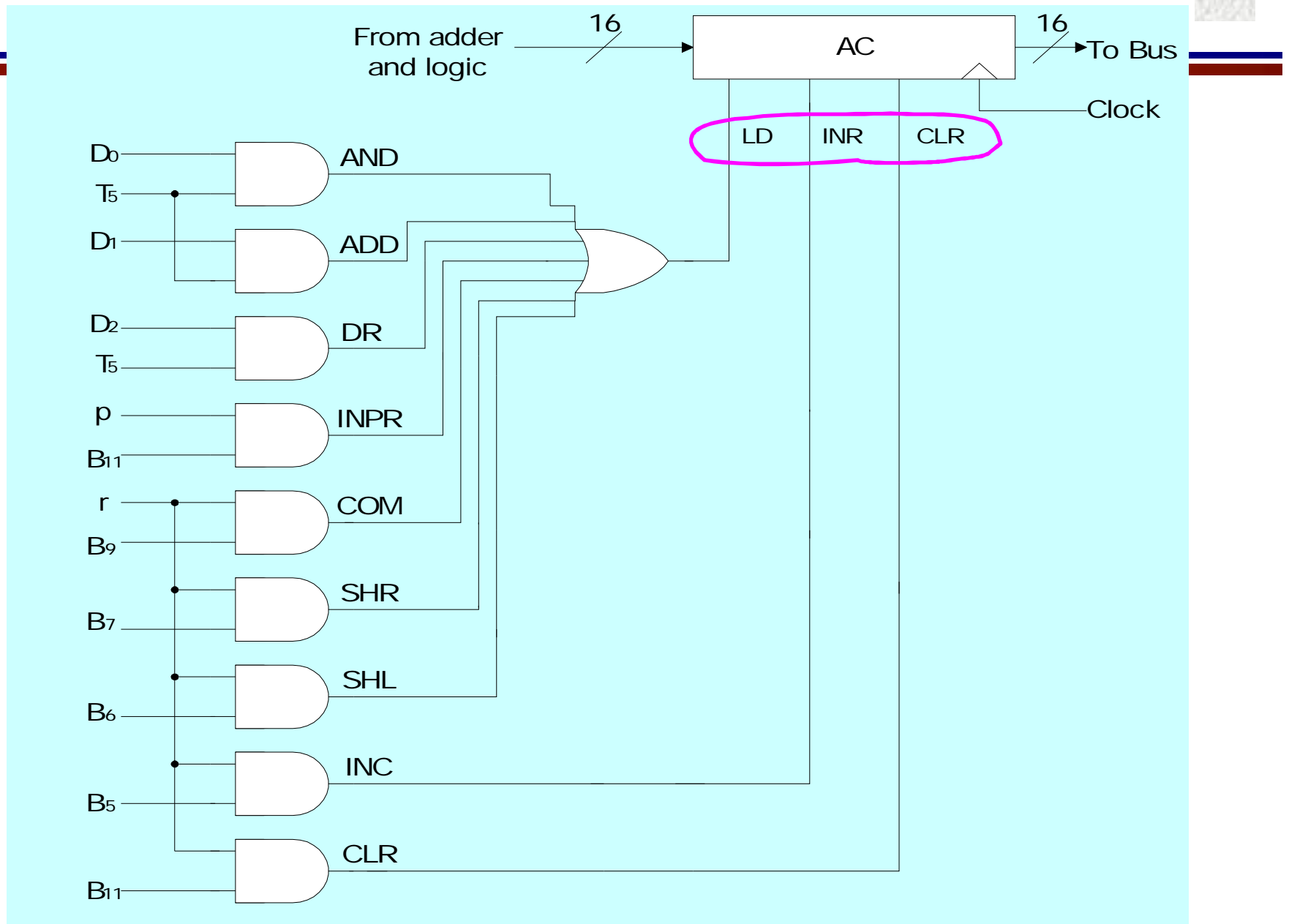Gate Structure for Controlling LD, INR, CLR & AC



The control function for the clear operation is rB_{11} where $r = D_7I'T_3$ AND $B_{11} = IR(11)$.



-
- ◆ **Adder and Logic Circuit : *The adder and logic circuit is divided into 16 stages with each stage corresponding to one bit of AC.***
 - ◆ ***Each stage has a JK flip flop, 2 OR gate , and two AND gate.***
 - ◆ ***The LD input is connected to the input of AND Gate.***

 - ◆ ***Note: one stage of Adder and logic ckt consist of seven AND Gate, One OR Gate and a FULL ADDER(FA).***
 - ◆ ***The AND operation is achieved with ANDing $AC(i)$ with the corresponding bit in the $DR(i)$.***
-

