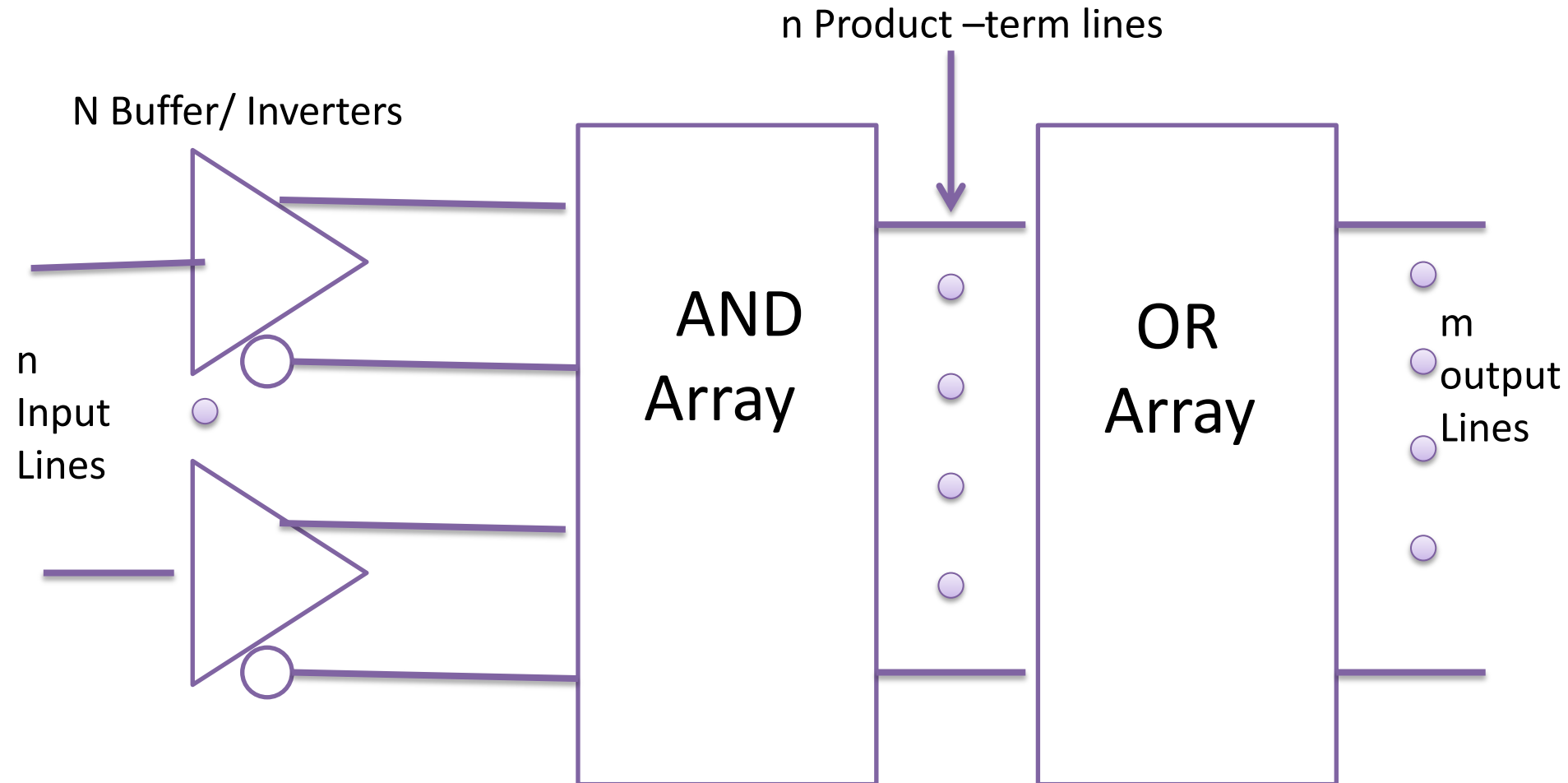


PLD (Programmable Logic Device)

- Can be programmed by the users as per their requirement
- Large circuit is designed on a single chip
- Possible to implement a combinational or sequential circuit using the PLD
- Consist of array of NOT, AND and OR gates
- Any Boolean function can be represented by sum of the product form.

PLDs



Types of PLD

- PROM (Programmable read only memory)
- PLA (programmable logic array)
- PAL (Programmable array logic)
- GAL (Generic array logic)
- PEEL (Programmable Electrically Erasable Logic)
- CPLDs (Complex programmable logic device)
- FPGA (Field programmable gate array)

Programmable Array

Device	AND Array	OR Array
ROM	Fixed	Programmable
PLA	Programmable	Programmable
PAL	Programmable	Fixed
GAL	Programmable	Fixed


ROM as PLD

- Consider a ROM with m outputs (the address lines) and n inputs (the data lines).
- When used as a memory, the ROM contains words of n bits each

TYPES

- PROMs (programmable ROMs),
- EPROMs (ultraviolet-erasable PROMs)
- EEPROMs (electrically erasable PROMs)

Programmable ROM (PROM)

 


- Address: m bits; data: n bits
- ROM contains 2^N word of M bit each
- The input bits decide the particular word that becomes available on output lines

- A ROM (Read Only Memory) has a fixed AND plane and a programmable OR plane
- Size of AND plane is 2^n where n = number of input pins
 - Has an AND gate for every possible minterm so that all input combinations access a different AND gate
- OR plane dictates function mapped by the ROM

4x4 ROM

 - ▶ $2^2 \times 4$ bit ROM has 4 addresses that are decoded




ROM Types

- ▶ Programmable PROM
 - Break links through current pulses
 - Write once, Read multiple times
- ▶ Erasable PROM (EPROM)
 - Program with ultraviolet light
 - Write multiple times, Read multiple times
- ▶ Electrically Erasable PROM (EEPROM)/ Flash Memory
 - Program with electrical signal
 - Write multiple times, Read multiple times

Combinational Circuit Implementation using PROM


I0 I1 I2 F0 F1 F2

0	0	0	1	0	0
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	1	0	0
1	1	1	0	1	0

 


Programmable Logic Array (PLA)

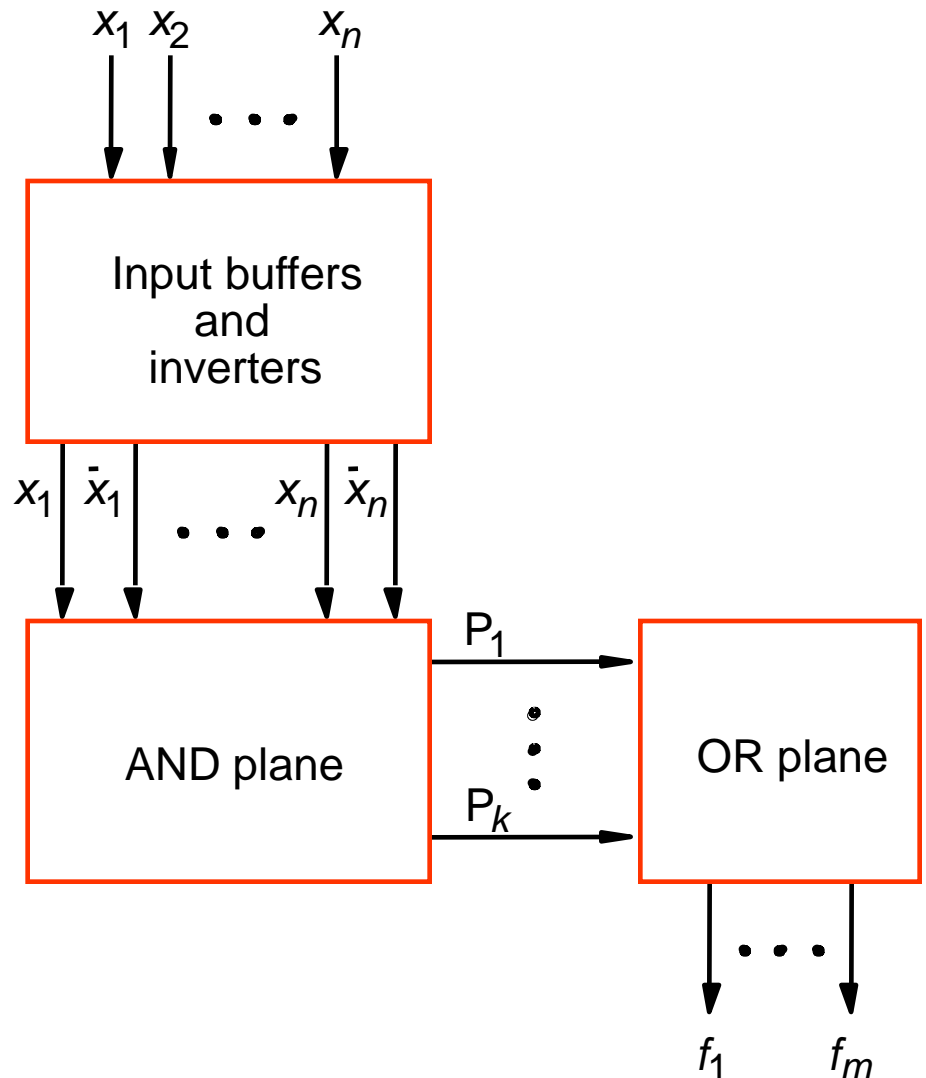- Use to implement circuits in SOP form
- The connections in the AND plane are programmable
- The connections in the OR plane are programmable




Gate Level Version of PLA

 

Customary Schematic of a PLA

$$f_1 = x_1x_2 + x_1x_3' + x_1'x_2'x_3$$


$$f_2 = x_1x_2 + x_1'x_2'x_3 + x_1x_3$$

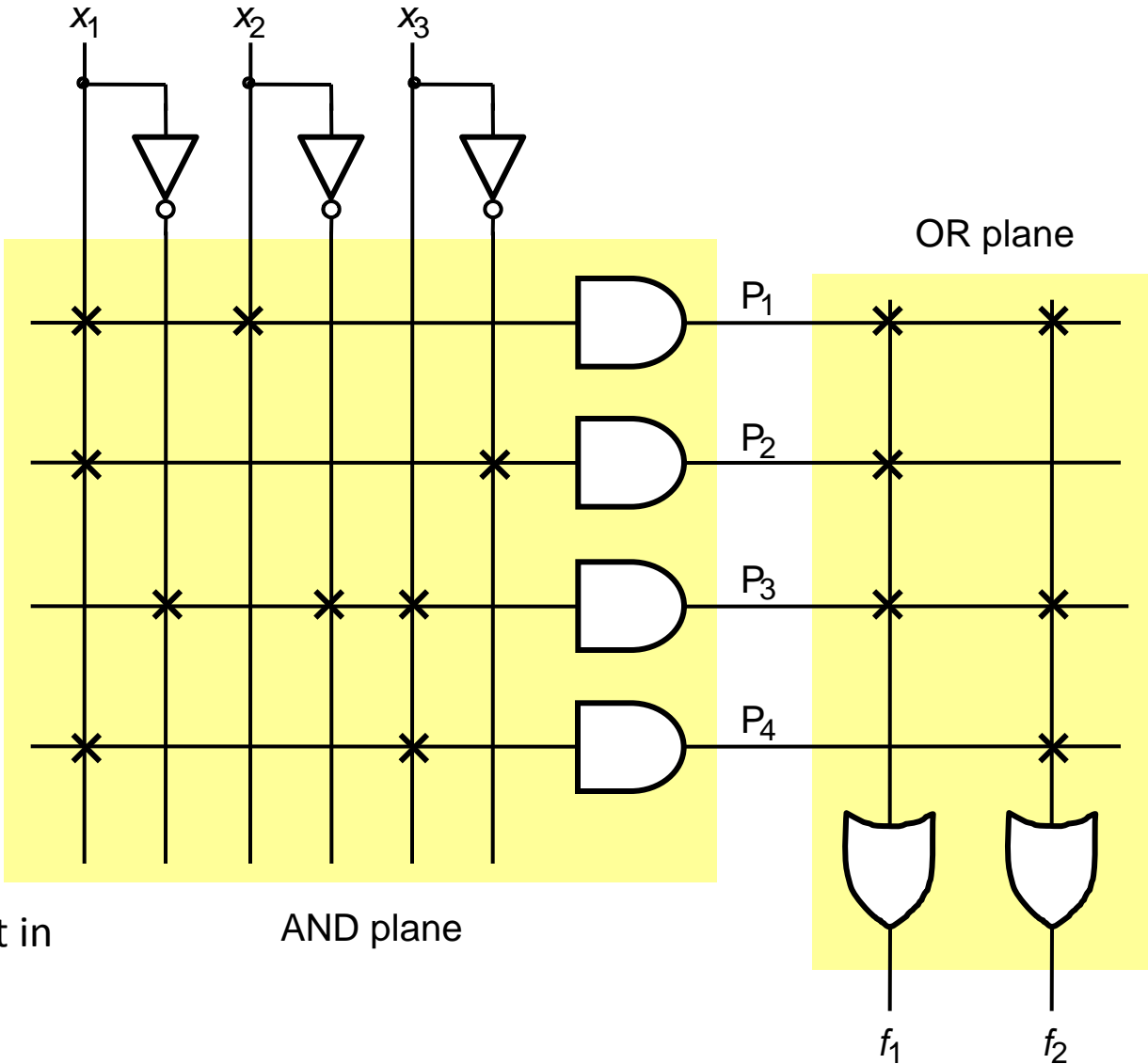

x marks the connections left in place after programming

Programmable Array Logic (PAL)

 - Also used to implement circuits in SOP form
- The connections in the AND plane are programmable
- The connections in the OR plane are NOT programmable



Example Schematic of a PAL

$$f_1 = x_1x_2x_3' + x_1'x_2x_3$$

$$f_2 = x_1'x_2' + x_1x_2x_3$$

