


# NETWORK THEORY

# LECTURE 1


SECTION A

TOPIC COVERED : INTRODUCTION OF TRANSIENT  
RESPONSE

# WHAT IS TRANSIENT RESPONSE

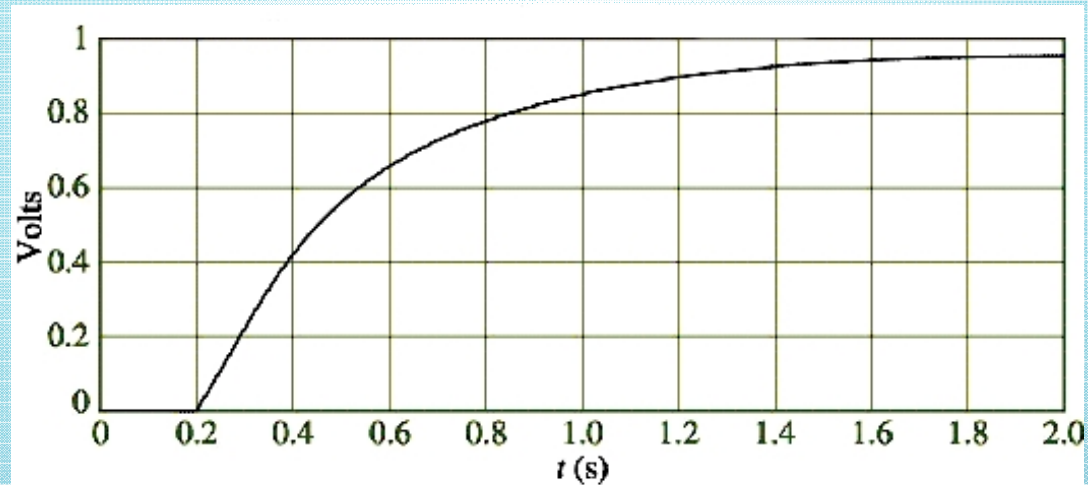

(a) Transient DC voltage

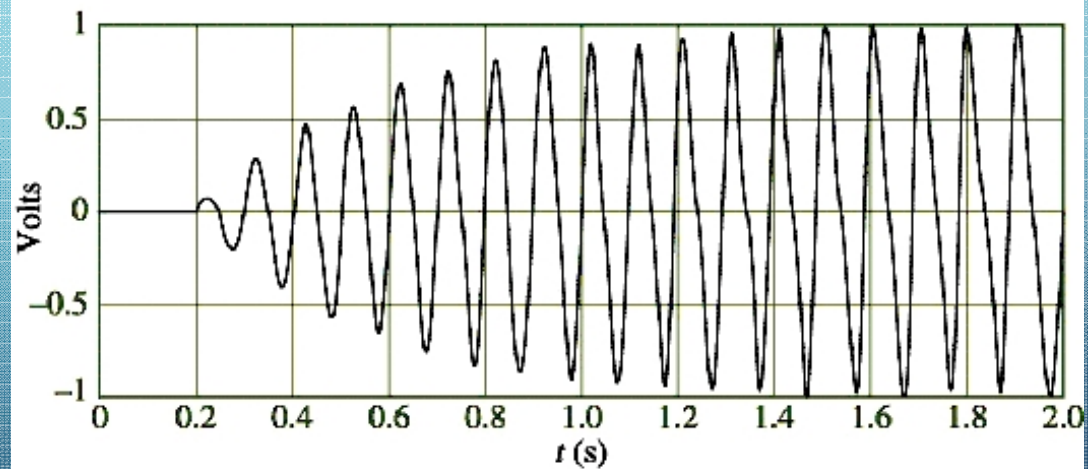

(b) Transient sinusoidal voltage

# SOLUTION TO FIRST ORDER DIFFERENTIAL EQUATION

Consider the general Equation

$$\tau \frac{dx(t)}{dt} + x(t) = K_s f(t)$$

Let the initial condition be  $x(t=0) = x(0)$ , then we solve the differential equation:

$$\tau \frac{dx(t)}{dt} + x(t) = K_s f(t)$$

The complete solution consists of two parts:

- the homogeneous solution (natural solution)
- the particular solution (forced solution)

# THE NATURAL RESPONSE

Consider the general Equation

$$\tau \frac{dx(t)}{dt} + x(t) = K_s f(t)$$

Setting the excitation  $f(t)$  equal to zero,

$$\tau \frac{dx_N(t)}{dt} + x_N(t) = 0 \text{ or } \frac{dx_N(t)}{dt} = -\frac{x_N(t)}{\tau}, \frac{dx_N(t)}{x_N(t)} = -\frac{dt}{\tau}$$

$$\int \frac{dx_N(t)}{x_N(t)} = \int -\frac{dt}{\tau}, \quad x_N(t) = \alpha e^{-t/\tau}$$

**It is called the natural response.**

# THE FORCED RESPONSE

Consider the general Equation

$$\tau \frac{dx(t)}{dt} + x(t) = K_S f(t)$$

Setting the excitation  $f(t)$  equal to  $F$ , a constant for  $t \geq 0$

$$\tau \frac{dx_F(t)}{dt} + x_F(t) = K_S F$$

$$x_F(t) = K_S F \text{ for } t \geq 0$$

**It is called the forced response.**

# THE COMPLETE RESPONSE

Consider the general Equation

$$\tau \frac{dx(t)}{dt} + x(t) = K_s f(t)$$

The complete response is:

- **the natural response** +
- **the forced response**

$$\begin{aligned}x &= x_N(t) + x_F(t) \\ &= \alpha e^{-t/\tau} + K_S F \\ &= \alpha e^{-t/\tau} + x(\infty)\end{aligned}$$

Solve for  $\alpha$ ,

for  $t = 0$

$$x(t = 0) = x(0) = \alpha + x(\infty)$$

$$\alpha = x(0) - x(\infty)$$


The Complete solution:

$$x(t) = [x(0) - x(\infty)]e^{-t/\tau} + x(\infty)$$


$[x(0) - x(\infty)]e^{-t/\tau}$  **called transient response**

$x(\infty)$  **called steady state response**

## Circuit with switched DC excitation

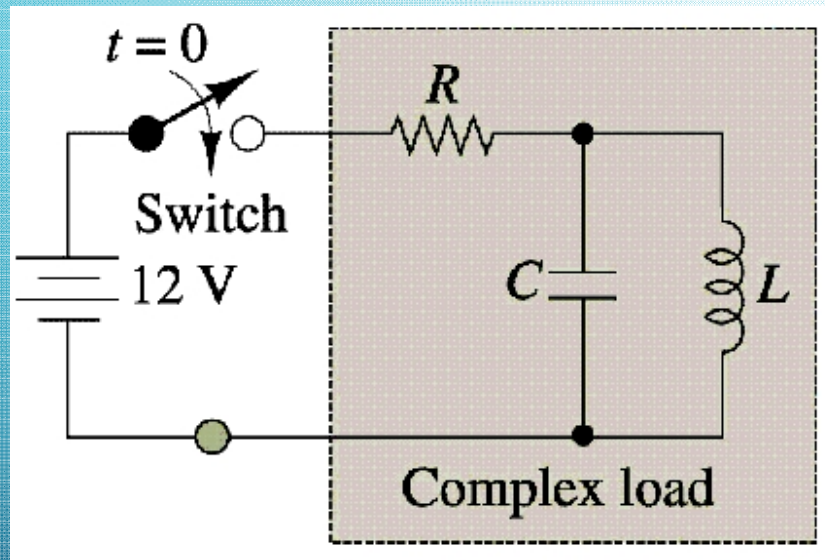
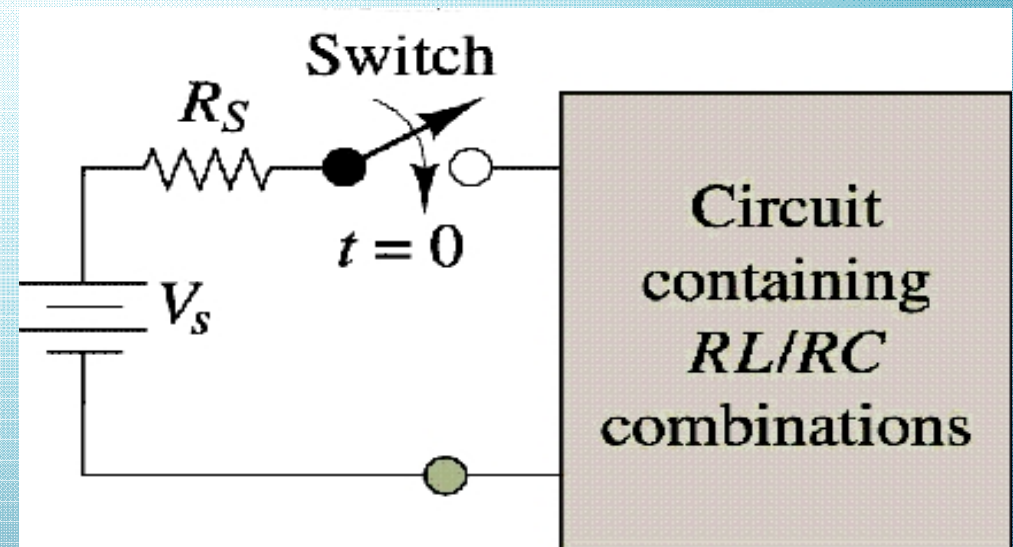
## A general model of the transient analysis problem





## In general, any circuit containing energy storage element

A circuit containing energy-storage elements is described by a differential equation. The differential equation describing the series  $RC$  circuit shown is

$$\frac{di_C}{dt} + \frac{1}{RC} i_C = \frac{dv_S}{dt}$$

