

# NETWORK THEORY

# LECTURE 2


## SECTION A

TOPIC COVERED : TRANSIENT RESPONSE OF RC, RL

**(a) Circuit at  $t = 0$**

**(b) Same circuit a long time after the switch is closed**


Figure 5.9,

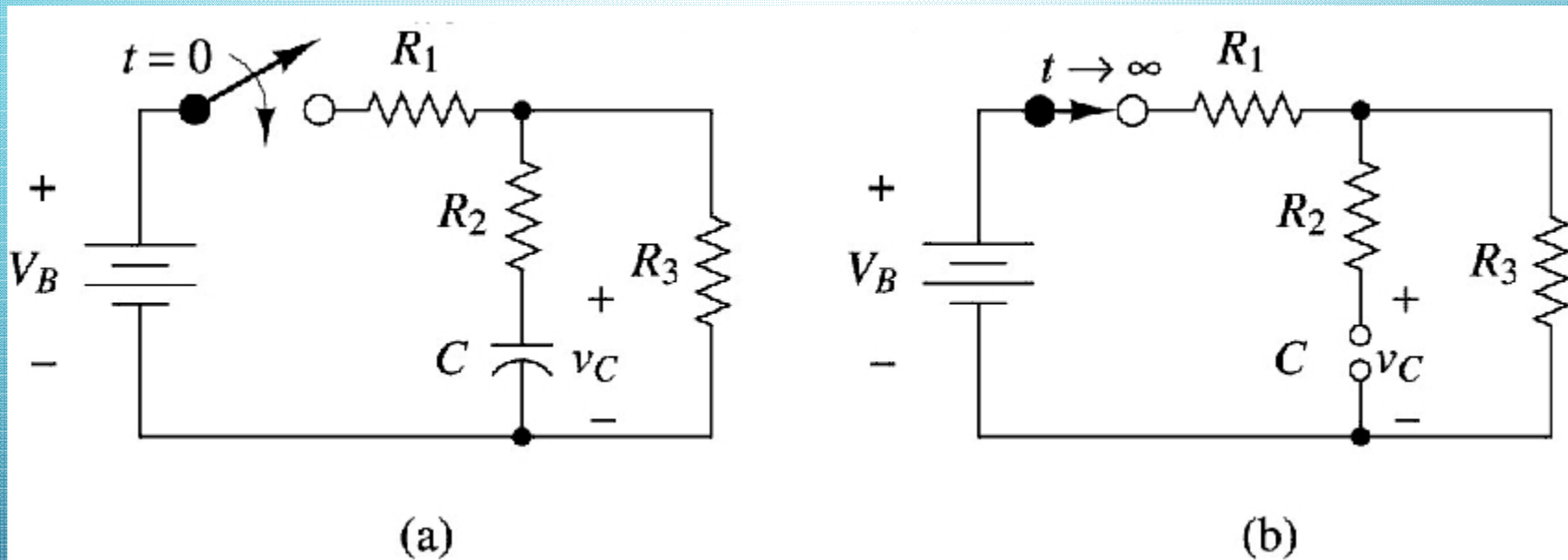

The capacitor acts as open circuit for the steady state condition (a long time after the switch is closed).

(a) Circuit for  $t = 0$

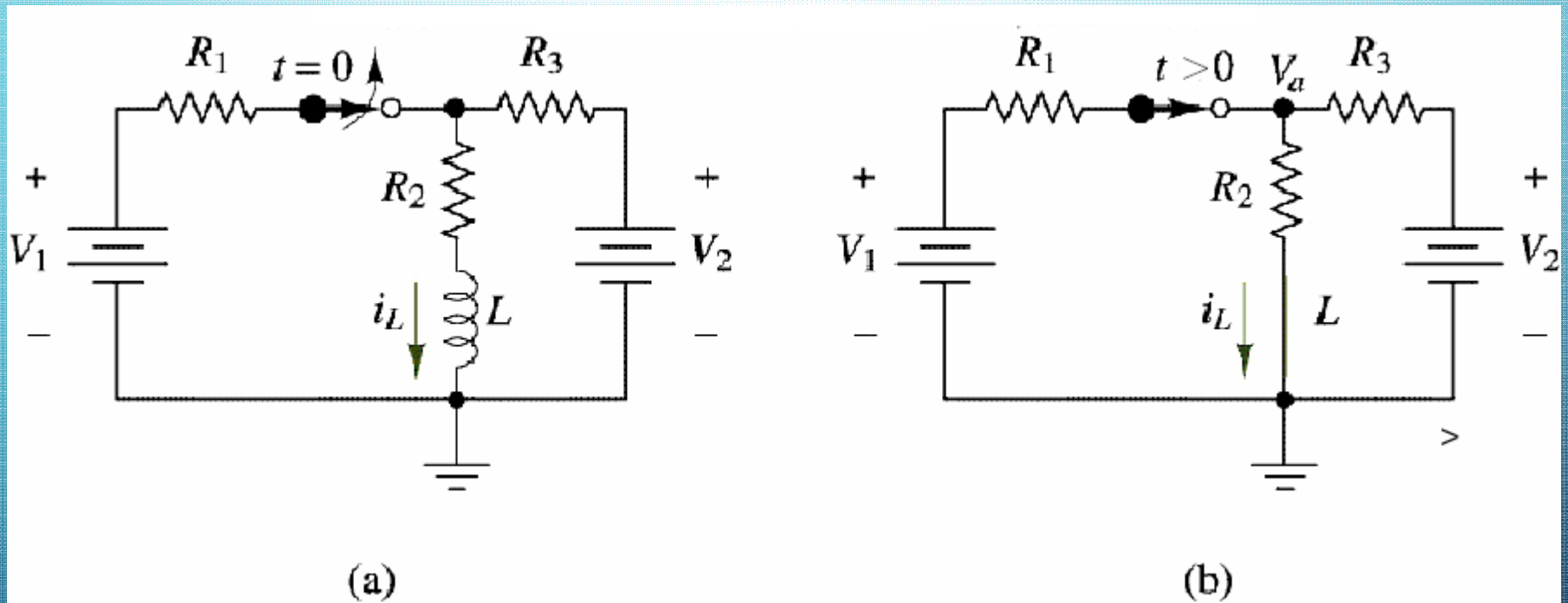(b) Same circuit a long time before the switch is opened



The inductor acts as short circuit for the steady state condition (a long time after the switch is closed).

# WHY THERE IS A TRANSIENT RESPONSE?




- The voltage across a capacitor cannot be changed instantaneously.

$$V_C(0^-) = V_C(0^+)$$

- The current across an inductor cannot be changed instantaneously.

$$I_L(0^-) = I_L(0^+)$$

# Example

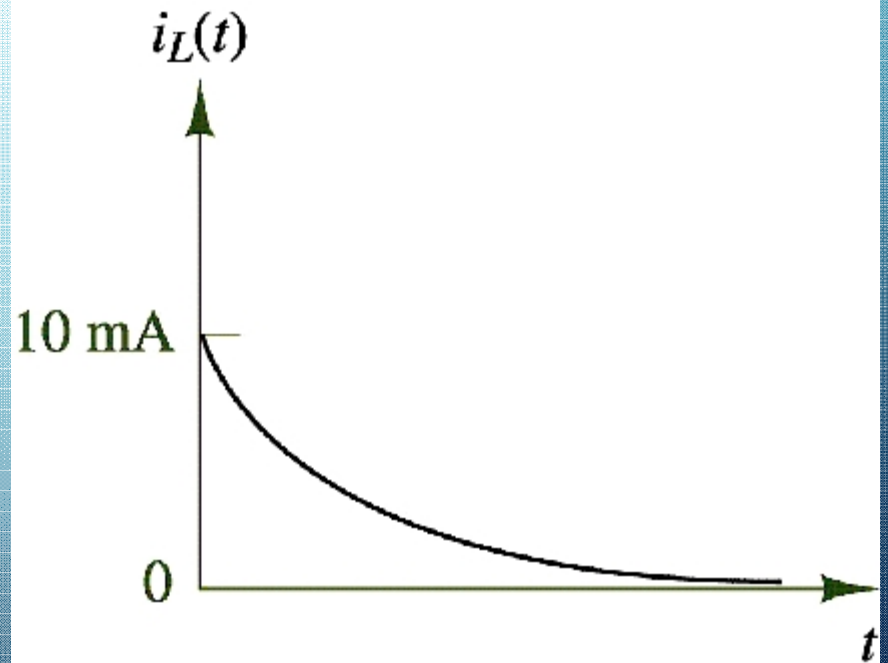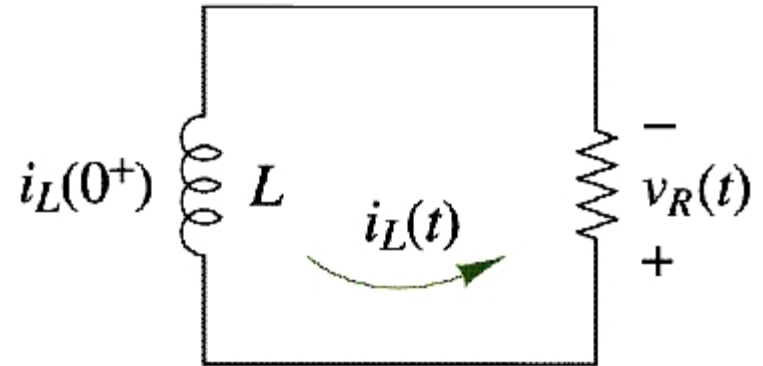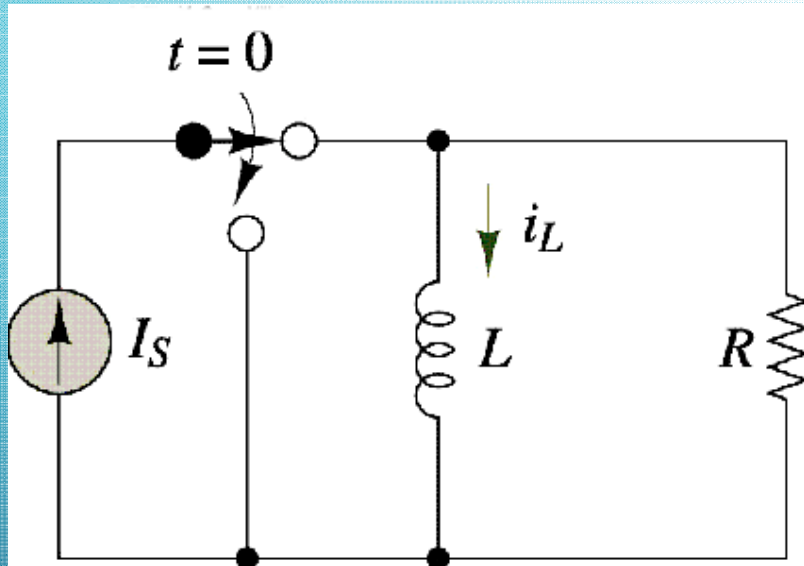

# TRANSIENTS ANALYSIS

1. Solve first-order  $RC$  or  $RL$  circuits.
2. Understand the concepts of transient response and steady-state response.
3. Relate the transient response of first-order circuits to the time constant.


# TRANSIENTS

The solution of the differential equation represents are response of the circuit. It is called *natural response*.

The response must eventually die out, and therefore referred to as *transient response*.  
(source free response)


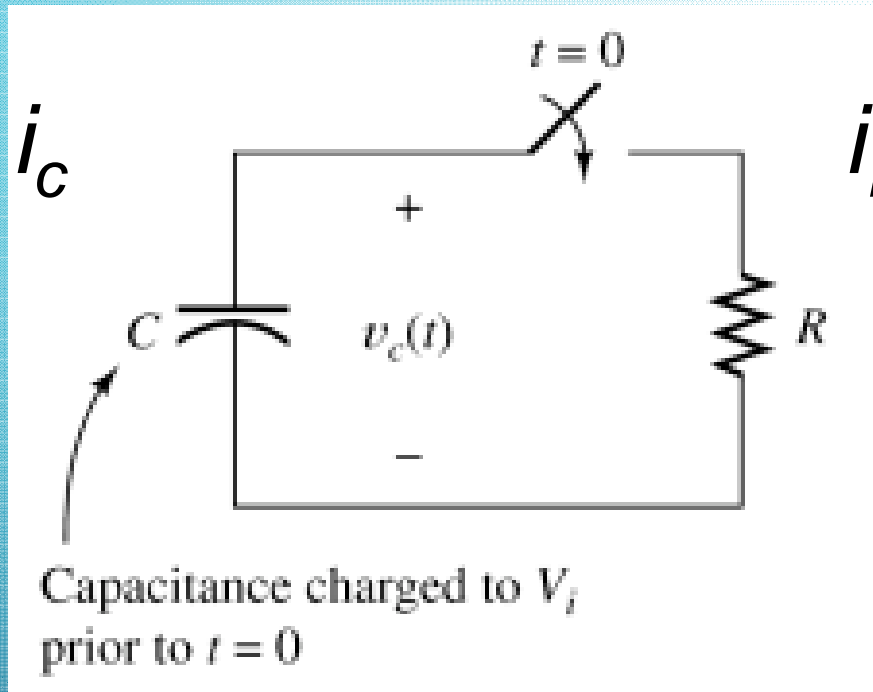
# DISCHARGE OF A CAPACITANCE THROUGH A RESISTANCE



$$i_R \quad \sum i = 0, \quad i_C + i_R = 0$$

$$C \frac{dv_c(t)}{dt} + \frac{v_c(t)}{R} = 0$$

Solving the above equation  
with the initial condition  
 $V_c(0) = V_i$