

NETWORK THEORY

NETWORK THEORY

SECTION A

TOPIC COVERED: TRANSIENT RESPONSE OF RL TO VARIOUS
EXCITATION SIGNALS


SECTION A : TRANSIENT RESPONSE

- Transient Response of RC, RL, and RLC Circuits to various excitation signals such as step, ramp, impulse and sinusoidal excitations using Laplace transform

RC CIRCUIT

Power dissipation in the resistor is:

$$p_R = V^2/R = (V_o^2/R) e^{-2t/RC}$$

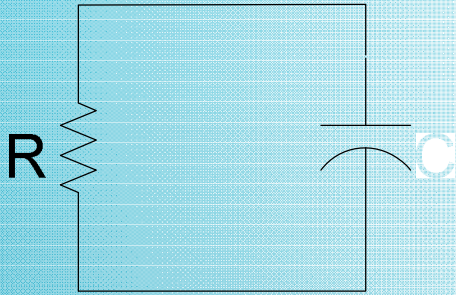

Total energy turned into heat in the resistor

$$W_R = \int_0^{\infty} p_R dt = \frac{V_o^2 \int_0^{\infty} e^{-2t/RC} dt}{R}$$


$$= V_o^2 R \left(-\frac{1}{2RC} \right) e^{-2t/RC} \Big|_0^{\infty}$$

$$= \frac{1}{2} C V_o^2$$

RL CIRCUITS

Initial condition

$$i(t=0) = I_0$$

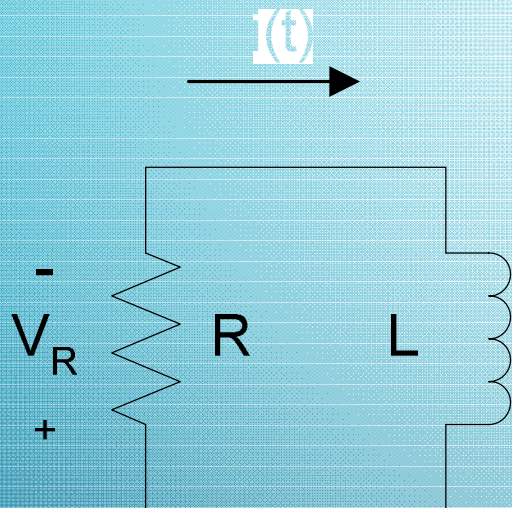


$$v_R + v_L = 0 = Ri + L \frac{di}{dt}$$

$$\frac{L}{R} \frac{di}{dt} + i = 0$$

Solving the differential equation

RL CIRCUITS

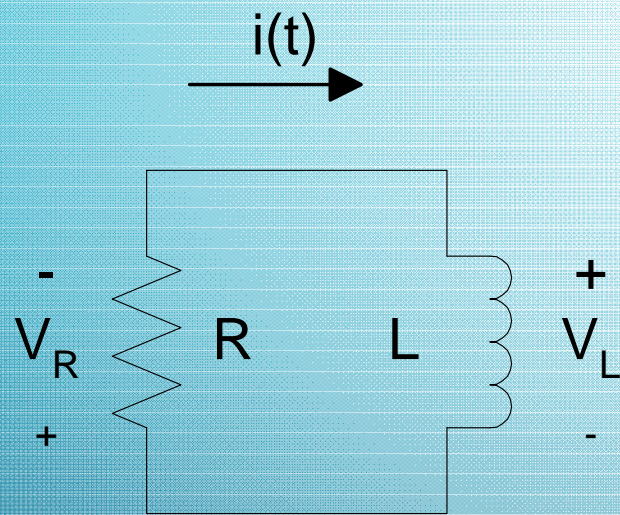

Initial condition
 $i(t=0) = I_o$

$$\frac{di}{dt} + \frac{R}{L}i = 0$$

$$\frac{di}{i} = -\frac{R}{L}dt, \quad \int_{I_o}^{i(t)} \frac{di}{i} = \int_0^t -\frac{R}{L}dt$$

$$\ln i \Big|_{I_o}^i = -\frac{R}{L}t \Big|_0^t$$

$$\ln i - \ln I_o = -\frac{R}{L}t$$


$$i(t) = I_o e^{-Rt/L}$$

RL CIRCUIT

Power dissipation in the resistor is:

$$p_R = i^2 R = I_0^2 e^{-2Rt/L} R$$

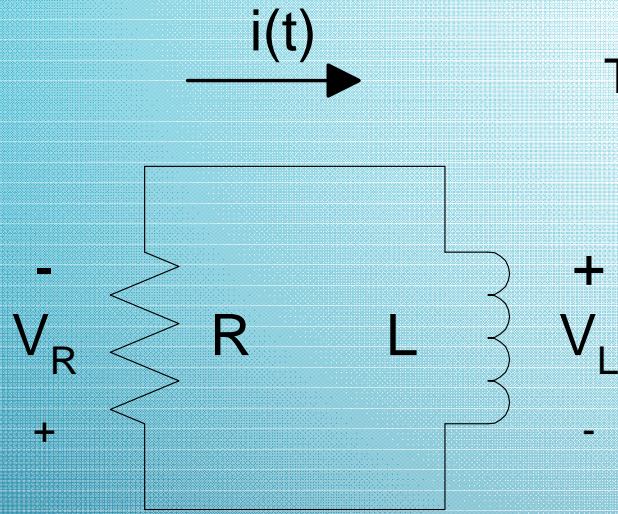Total energy turned into heat in the resistor




$$\begin{aligned} W_R &= \int_0^{\infty} p_R dt = I_0^2 R \int_0^{\infty} e^{-2Rt/L} dt \\ &= I_0^2 R \left(-\frac{L}{2R} \right) e^{-2Rt/L} \Big|_0^{\infty} \\ &= \frac{1}{2} L I_0^2 \end{aligned}$$

It is expected as the energy stored in the inductor is

$$\frac{1}{2} L I_0^2$$

RL CIRCUIT

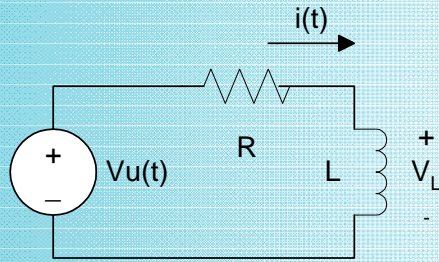


$$Ri + L \frac{di}{dt} = V$$

$$\frac{Ldi}{V - Ri} = dt$$

Integrating both sides,

$$-\frac{L}{R} \ln(V - Ri) = t + k$$

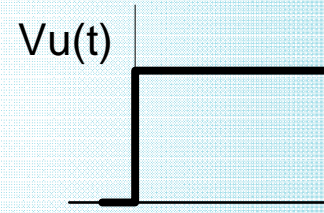

$$i(0^+) = 0, \text{ thus } k = -\frac{L}{R} \ln V$$

$$-\frac{L}{R} [\ln(V - Ri) - \ln V] = t$$

$$\frac{V - Ri}{V} = e^{-Rt/L} \quad \text{or}$$

$$i = \frac{V}{R} - \frac{V}{R} e^{-Rt/L}, \text{ for } t > 0$$

where L/R is the time constant

DC STEADY STATE

The steps in determining the forced response for *RL* or *RC* circuits with dc sources are:

1. Replace capacitances with open circuits.
2. Replace inductances with short circuits.
3. Solve the remaining circuit.