

A decorative graphic on the left side of the slide consists of light blue lines and circles, resembling a circuit board or network diagram. The lines are vertical and horizontal, with some diagonal connections, and the circles are small and white with blue outlines.

NETWORK THEORY



LECTURE 4

SECTION B

TOPIC COVERED :TWO PORT NETWORK

Scattering Parameters

$$b_1(0) = S_{11}a_1(0) + S_{12}a_2(0)$$

$$b_2(0) = S_{21}a_1(0) + S_{22}a_2(0)$$


$S_{11} = \left. \frac{b_1(0)}{a_1(0)} \right _{a_2=0}$	← Output is matched	← input reflection coef. w/ output matched
$S_{12} = \left. \frac{b_1(0)}{a_2(0)} \right _{a_1=0}$	← Input is matched	← reverse transmission coef. w/ input matched
$S_{21} = \left. \frac{b_2(0)}{a_1(0)} \right _{a_2=0}$	← Output is matched	← forward transmission coef. w/ output matched
$S_{22} = \left. \frac{b_2(0)}{a_2(0)} \right _{a_1=0}$	← Input is matched	← output reflection coef. w/ input matched

Scattering Parameters (cont.)

For a general multiport network:


$$S_{ij} = \left. \frac{b_i(0)}{a_j(0)} \right|_{a_k=0, k \neq j}$$

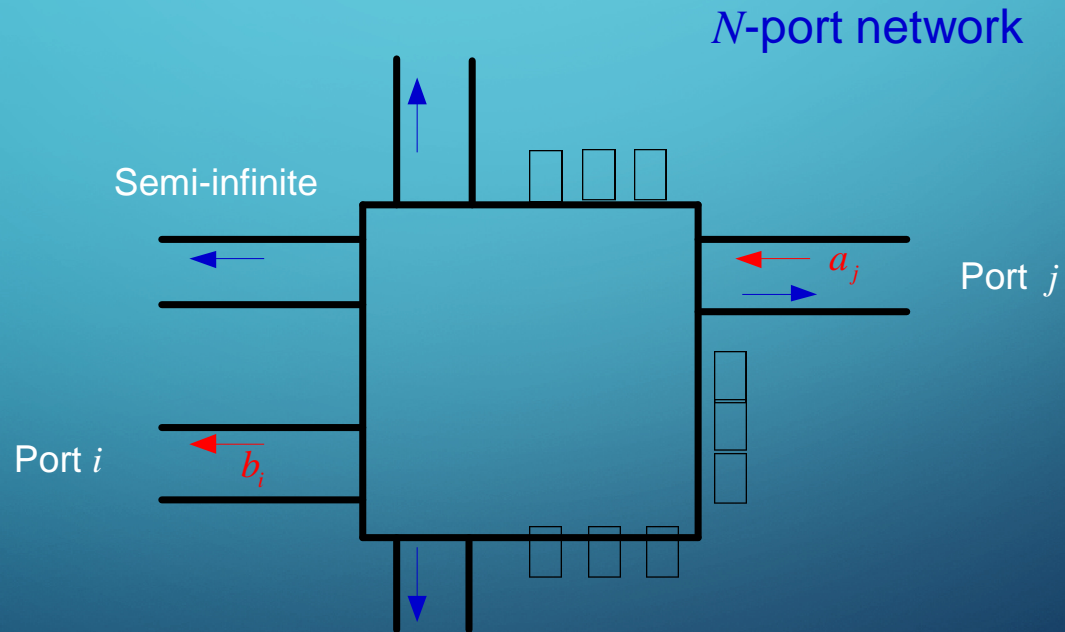All ports except j are semi-infinite (or matched)



Scattering Parameters (cont.)

Illustration of a three-port network

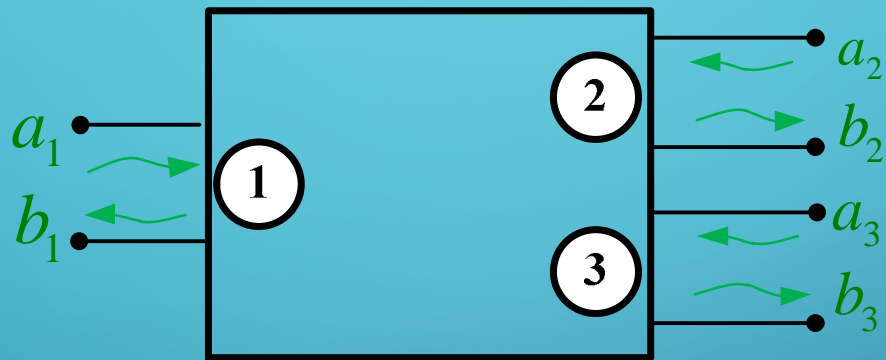

Scattering Parameters (cont.)

For **reciprocal** networks, the S -matrix is symmetric.


$$\Rightarrow S_{ij} = S_{ji} \quad i \neq j$$

Note: If all lines entering the network have the same characteristic impedance, then

$$S_{ij} = \frac{V_i^-(0)}{V_j^+(0)} \Big|_{V_k^+=0 \quad k \neq j}$$

Scattering Parameters (cont.)

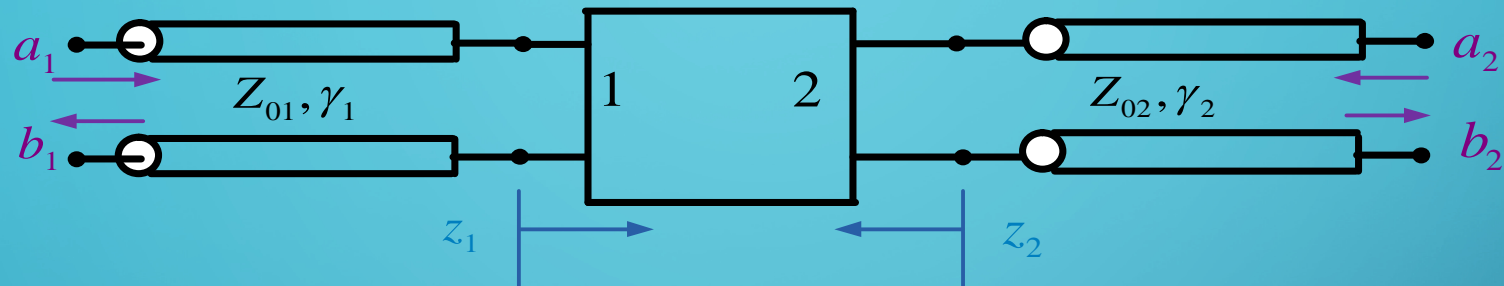Why are the wave functions (a and b) defined as they are?



$$P_i^+(0) = \frac{1}{2} \operatorname{Re} [V_i^+(0) I_i^{+*}(0)] = \frac{1}{2} \frac{|V_i^+(0)|^2}{Z_{0i}} \quad (\text{assuming lossless lines})$$

Note:

$$a_i(0) = V_i^+(0) / \sqrt{Z_{0i}}$$
$$\Rightarrow P_i^+(0) = \frac{1}{2} |a_i(0)|^2$$

Scattering Parameters (cont.)

Similarly,

$$P_i^-(0) = \frac{1}{2} \frac{|V_i^-(0)|^2}{Z_{0i}} = \frac{1}{2} |b_i(0)|^2$$

Also,

$$V_i^+(-l_i) = V_i^+(0) e^{+\gamma_i l_i}$$


$$V_i^-(-l_i) = V_i^-(0) e^{-\gamma_i l_i}$$

$$\Rightarrow P_i^+(-l_i) = \frac{1}{2} |a_i(-l_i)|^2 = \frac{1}{2} |a_i(0)|^2 e^{+2\alpha_i l_i}$$

$$P_i^-(-l_i) = \frac{1}{2} |b_i(-l_i)|^2 = \frac{1}{2} |b_i(0)|^2 e^{-2\alpha_i l_i}$$

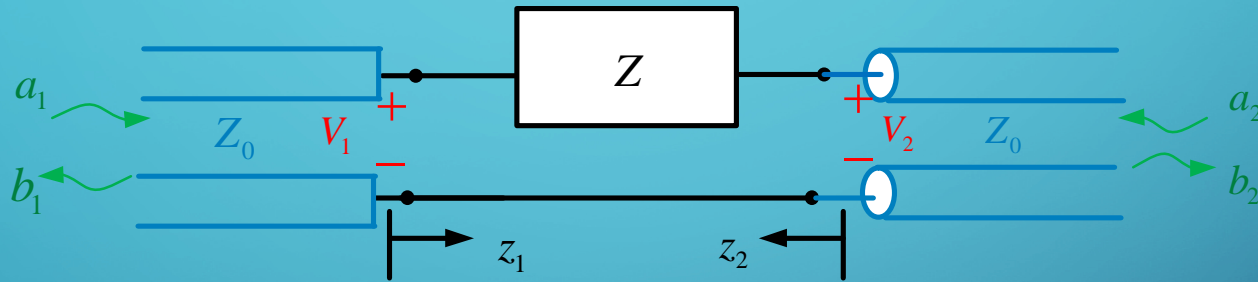
Example

Find the S parameters for a series impedance Z .



Note that **two** different coordinate systems are being used here!

Example (cont.)

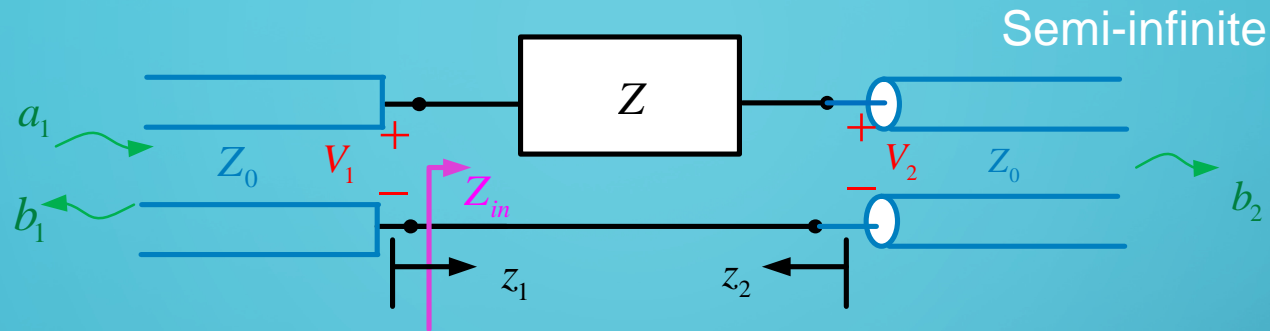

S_{11} Calculation:

$$S_{11} = \left. \frac{b_1(0)}{a_1(0)} \right|_{a_2=0} = \frac{V_1^-(0)}{V_1^+(0)} = \left. \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \right|_{a_2=0} = \frac{(Z + Z_0) - Z_0}{(Z + Z_0) + Z_0}$$


$$\Rightarrow S_{11} = \frac{Z}{Z + 2Z_0}$$

By symmetry:

$$S_{22} = S_{11}$$

Example (cont.)

S_{21} Calculation:

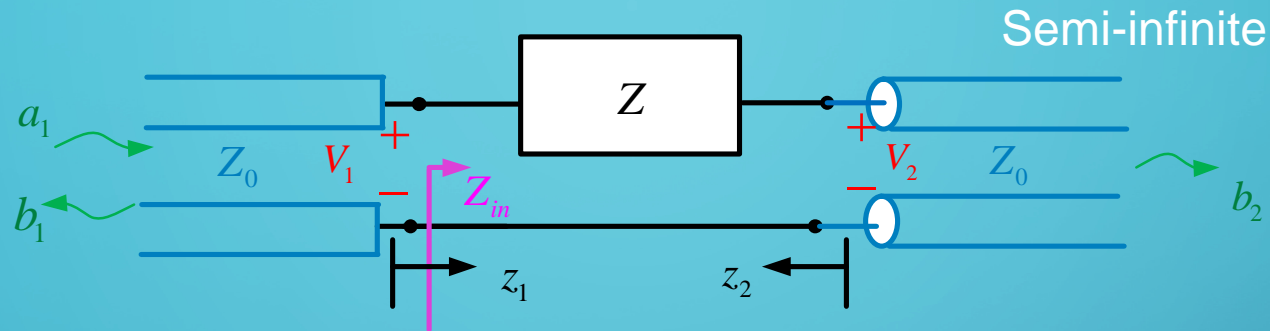

$$S_{21} = \left. \frac{b_2(0)}{a_1(0)} \right|_{a_2=0}$$

$$= \left. \frac{V_2^-(0)}{V_1^+(0)} \right|_{a_2=0}$$

$$V_1^+(0) = a_1(0) \sqrt{Z_0}$$


$$a_2 = 0 \Rightarrow V_2^-(0) = V_2(0)$$

$$V_2(0) = V_1(0) \left(\frac{Z_0}{Z + Z_0} \right)$$

$$V_1(0) = a_1 \sqrt{Z_0} (1 + S_{11})$$

$$\Rightarrow V_2^-(0) = V_2(0) = a_1 \sqrt{Z_0} (1 + S_{11}) \left(\frac{Z_0}{Z + Z_0} \right)$$

Example (cont.)

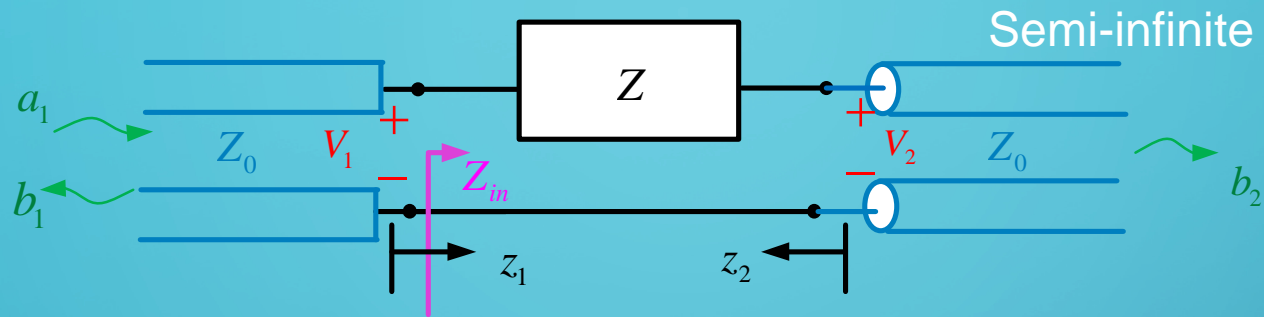

$$S_{21} = \frac{a_1(0)\sqrt{Z_0}(1+S_{11})\left(\frac{Z_0}{Z+Z_0}\right)}{a_1(0)\sqrt{Z_0}}$$

$$= (1+S_{11})\left(\frac{Z_0}{Z+Z_0}\right) = \left(1+\frac{Z}{Z+2Z_0}\right)\left(\frac{Z_0}{Z+Z_0}\right) = \left(\frac{2Z+2Z_0}{Z+2Z_0}\right)\left(\frac{Z_0}{Z+Z_0}\right)$$


Hence

$$S_{21} = \frac{2Z_0}{Z+2Z_0}$$

$$S_{12} = S_{21}$$

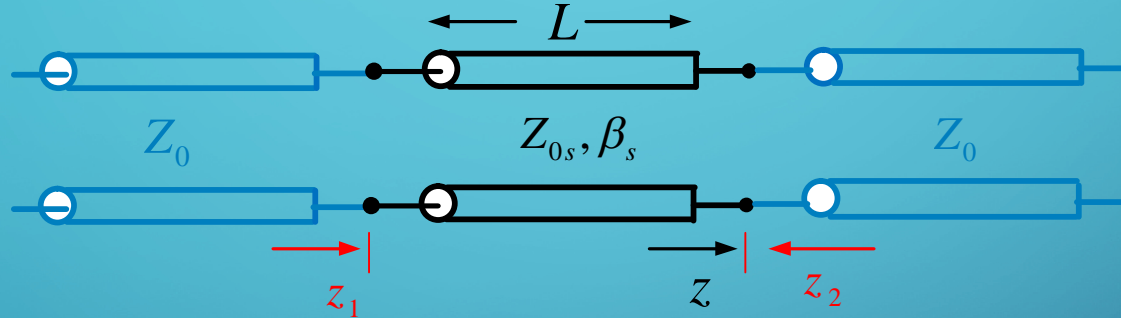Example


Find the S parameters for a length L of transmission line.



Note that **three** different coordinate systems are being used here!

Example (cont.)


S_{11} Calculation:

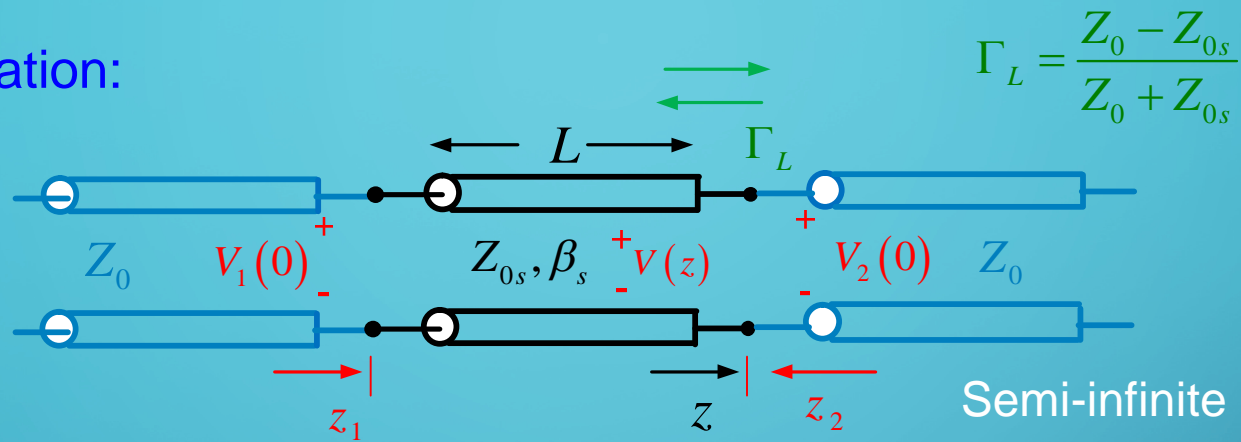

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \frac{Z_{in}|_{a_2=0} - Z_0}{Z_{in}|_{a_2=0} + Z_0} = S_{22} \text{ (by symmetry)}$$

$$Z_{in}|_{a_2=0} = Z_{0s} \frac{(Z_0 + jZ_{0s} \tan \beta_s L)}{(Z_{0s} + jZ_0 \tan \beta_s L)} = Z_{0s} \frac{(1 + \Gamma_L e^{-j2\beta_s L})}{(1 - \Gamma_L e^{-j2\beta_s L})}$$

Example (cont.)

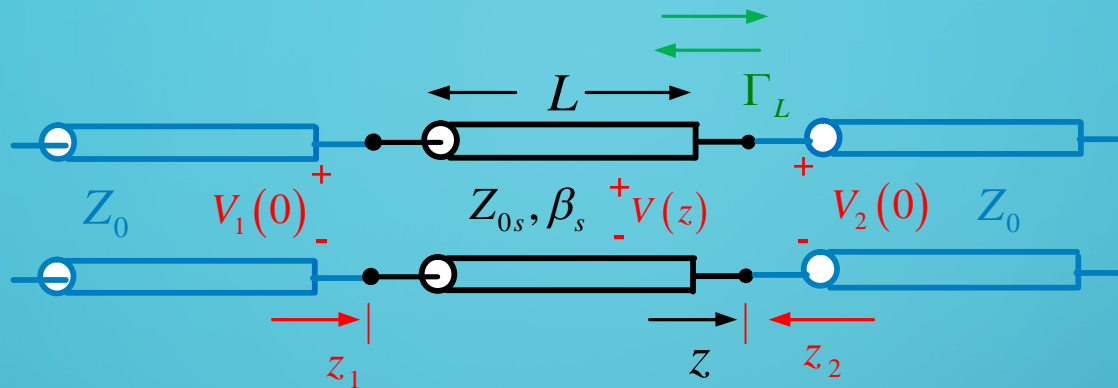


Hence

$$S_{11} = S_{22} = \frac{Z_{0s} \frac{(Z_0 + jZ_{0s} \tan \beta_s L)}{(Z_{0s} + jZ_0 \tan \beta_s L)} - Z_0}{Z_{0s} \frac{(Z_0 + jZ_{0s} \tan \beta_s L)}{(Z_{0s} + jZ_0 \tan \beta_s L)} + Z_0}$$

Note: If $Z_{0s} = Z_0 \Rightarrow Z_{in}|_{z=0} = Z_0 \Rightarrow S_{11} = S_{22} = 0$

Example (cont.)

S_{21} Calculation:

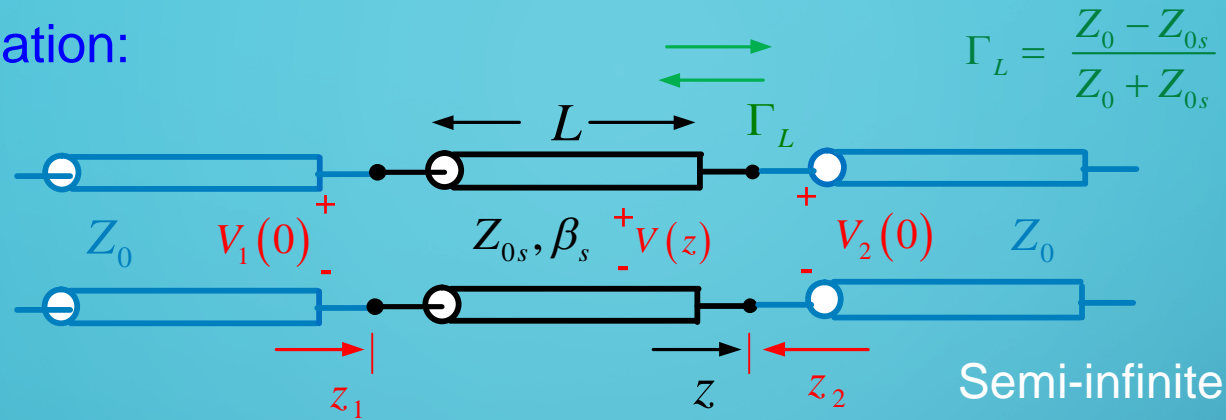

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} = \frac{V_2^-(0)/\sqrt{Z_0}}{V_1^+(0)/\sqrt{Z_0}} \Big|_{a_2=0}$$


$$V_1(0) = V_1^+(0)(1 + S_{11})$$

Hence, for the denominator of the S_{21} equation we have

$$V_1^+(0) = \frac{V_1(0)}{1 + S_{11}}$$

We now try to put the numerator of the S_{21} equation in terms of $V_1(0)$.

Example (cont.)

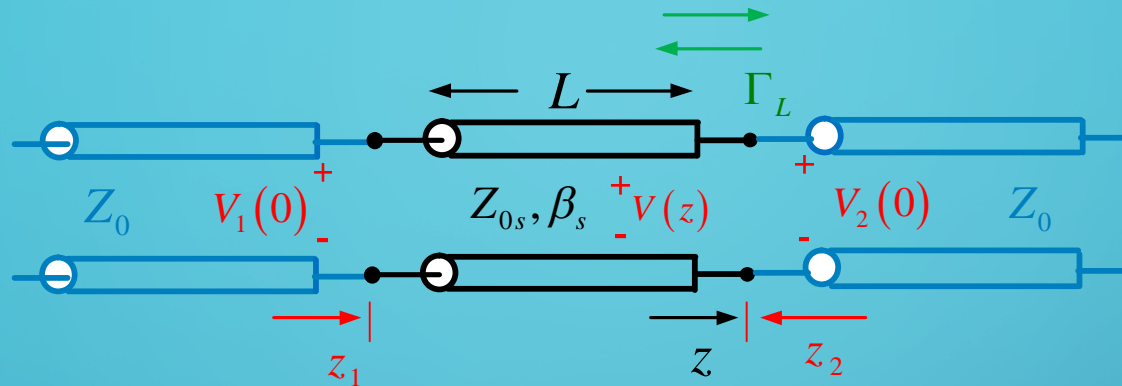

$$V_2^-(0) = V_2(0) = V(0) = V^+(0)(1 + \Gamma_L)$$

Next, use

$$V(z) = V^+(0)e^{-j\beta_s z} (1 + \Gamma_L e^{+j2\beta_s z})$$


$$\Rightarrow V_1(0) = V(-L) = V^+(0)e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})$$

Hence, we have

$$\Rightarrow V^+(0) = \frac{V_1(0)}{e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})}$$

$$V_2^-(0) = \frac{V_1(0)}{e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})} (1 + \Gamma_L)$$

Example (cont.)

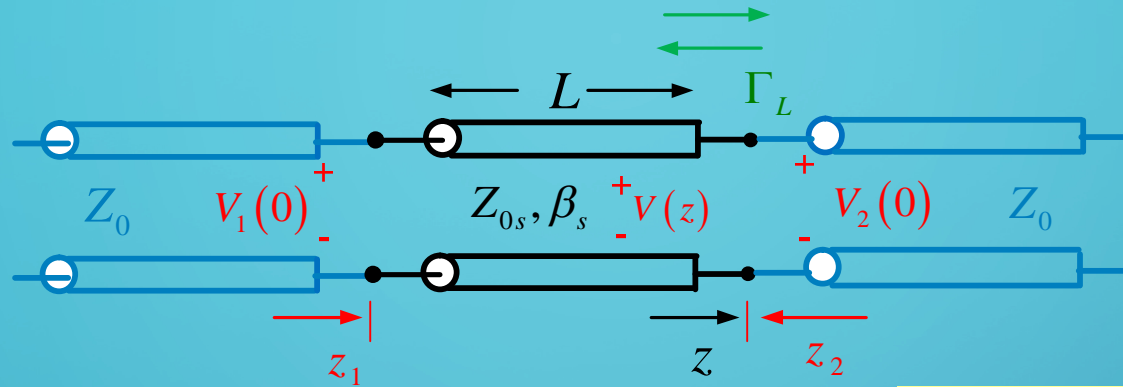

$$V_2^-(0) = \frac{V_1(0)}{e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})} (1 + \Gamma_L)$$

Therefore, we have

$$V_1^+(0) = \frac{V_1(0)}{1 + S_{11}}$$


$$S_{21} = \left. \frac{V_2^-(0)}{V_1^+(0)} \right|_{a_2=0} = \frac{(1 + S_{11})(1 + \Gamma_L) e^{-j\beta_s L}}{1 + \Gamma_L e^{-j2\beta_s L}}$$

so

$$S_{21} = \frac{(1 + S_{11})(1 + \Gamma_L) e^{-j\beta_s L}}{1 + \Gamma_L e^{-j2\beta_s L}} = S_{12} \text{ by symmetry}$$

Example (cont.)

Special cases:

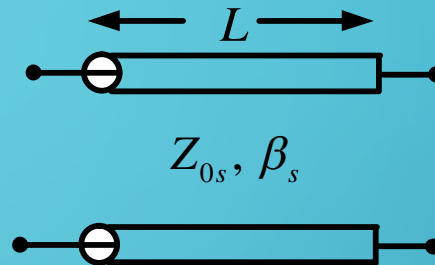

$$a) \quad Z_{0s} = Z_0 \Rightarrow S_{11} = S_{22} = 0, \quad \Gamma_L = 0$$

$$S_{21} = S_{12} = e^{-j\beta_s L}$$

$$[S] = \begin{bmatrix} 0 & e^{-j\beta_s L} \\ e^{-j\beta_s L} & 0 \end{bmatrix}$$

$$b) \quad L = \frac{\lambda_g}{2} \Rightarrow \beta_s L = \frac{2\pi}{\lambda_g} \frac{\lambda_g}{2} = \pi$$

$$\Rightarrow Z_{in}|_{a_2=0} = Z_0 \Rightarrow S_{11} = S_{22} = 0$$


$$e^{-j\beta_s L} = -1 \Rightarrow S_{21} = -1$$

$$[S] = \begin{bmatrix} 0 & -1 \\ -1 & 0 \end{bmatrix}$$

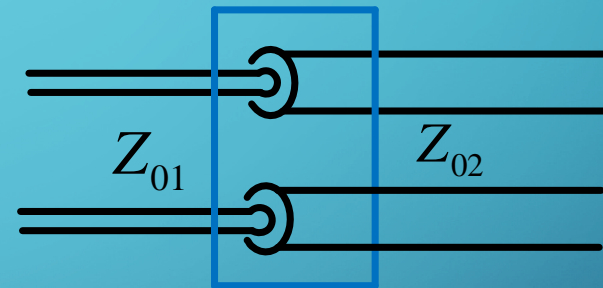Example

Find the S parameters for a step-impedance discontinuity.

$$S_{11} = \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}}$$
$$S_{22} = \frac{Z_{01} - Z_{02}}{Z_{02} + Z_{01}} = -S_{11}$$




$$S_{21} = \frac{b_2(0)}{a_1(0)} \Big|_{a_2=0} = \frac{\frac{V_2^-(0)}{\sqrt{Z_{02}}}}{\frac{V_1^+(0)}{\sqrt{Z_{01}}}} \Big|_{a_2=0}$$

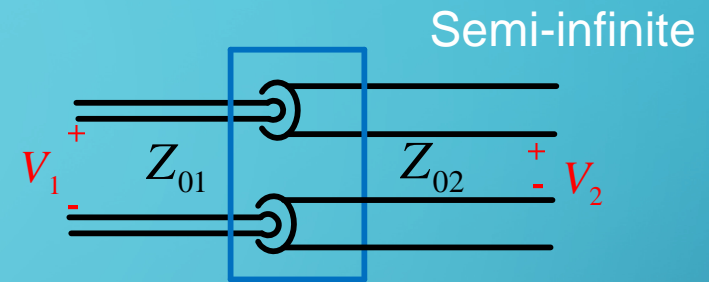Example (cont.)

S_{21} Calculation:

Because of continuity of the voltage across the junction, we have:



$$V_2^-(0)\Big|_{a_2=0} = V_2(0)\Big|_{a_2=0} = V_1(0)\Big|_{a_2=0} = V_1^+(0)(1 + S_{11})$$

$$S_{21} = \frac{\frac{V_2^-(0)}{\sqrt{Z_{02}}}\Big|_{a_2=0}}{\frac{V_1^+(0)}{\sqrt{Z_{01}}}\Big|_{a_2=0}} = \frac{\frac{V_1^+(0)(1 + S_{11})}{\sqrt{Z_{02}}}\Big|_{a_2=0}}{\frac{V_1^+(0)}{\sqrt{Z_{01}}}\Big|_{a_2=0}}$$

$$\begin{aligned} 1 + S_{11} &= 1 + \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}} \\ &= \frac{2Z_{02}}{Z_{02} + Z_{01}} \end{aligned}$$

so

$$S_{21} = (1 + S_{11}) \sqrt{\frac{Z_{01}}{Z_{02}}}$$

Hence

$$S_{21} = S_{12} = 2 \frac{\sqrt{Z_{01}Z_{02}}}{Z_{01} + Z_{02}}$$

Properties of the S Matrix (cont.)

Example:

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

$$\text{Unitary} \Rightarrow S_{11}S_{11}^* + S_{21}S_{21}^* + S_{31}S_{31}^* = 1$$

$$S_{12}S_{12}^* + S_{22}S_{22}^* + S_{32}S_{32}^* = 1$$

$$S_{13}S_{13}^* + S_{23}S_{23}^* + S_{33}S_{33}^* = 1$$

$$S_{11}S_{12}^* + S_{21}S_{22}^* + S_{31}S_{32}^* = 0$$

$$S_{11}S_{13}^* + S_{21}S_{23}^* + S_{31}S_{33}^* = 0$$

$$S_{12}S_{13}^* + S_{22}S_{23}^* + S_{32}S_{33}^* = 0$$

The column vectors form an orthogonal set.

The rows also form orthogonal sets (see the note on the previous slide).