

A decorative graphic on the left side of the slide, consisting of white lines and circles that resemble a circuit board or network diagram. The lines are of varying lengths and angles, connecting to small white circles. The background is a gradient of blue, transitioning from a lighter shade at the top to a darker shade at the bottom.

NETWORK THEORY



LECTURE 1

SECTION C

TOPIC COVERED :RELATIONSHIP OF TWO-PORT VARIABLES, SHORT-CIRCUIT ADMITTANCE PARAMETERS, OPEN CIRCUIT IMPEDANCE,PARAMETERS

RELATIONSHIP OF TWO-PORT VARIABLES

S.No	Two port parameters	function	Matrix equation
1.	Open circuit Impedance [Z]	$(V_1, V_2) = f(I_1, I_2)$	$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$
2.	Short circuit admittance [Y]	$(I_1, I_2) = f(V_1, V_2)$	$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$
3.	Transmission or chain [T]	$(V_1, I_1) = f(V_2, -I_2)$	$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$
4.	Inverse Transmission [T']	$(V_2, I_2) = f(V_1, -I_1)$	$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$
5.	Hybrid parameter [h]	$(V_1, I_2) = f(I_1, V_2)$	$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$
6.	Inverse hybrid [g]	$(I_1, V_2) = f(V_1, I_2)$	$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$

OPEN CIRCUIT IMPEDANCE [Z] PARAMETER

The terminal characteristics of a two-port network, having linear elements and dependent sources may be written in the s -domain as

$$\left. \begin{aligned} V_1 &= Z_{11}I_1 + Z_{12}I_2 \\ V_2 &= Z_{21}I_1 + Z_{22}I_2 \end{aligned} \right\} \text{ or } \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad \dots(5.1)$$

The coefficients Z_{ij} have the dimension of impedance and are called the Z -parameters of the network. The equivalent circuit of a two port network in terms of Z -parameters is shown in Fig. 5.2.

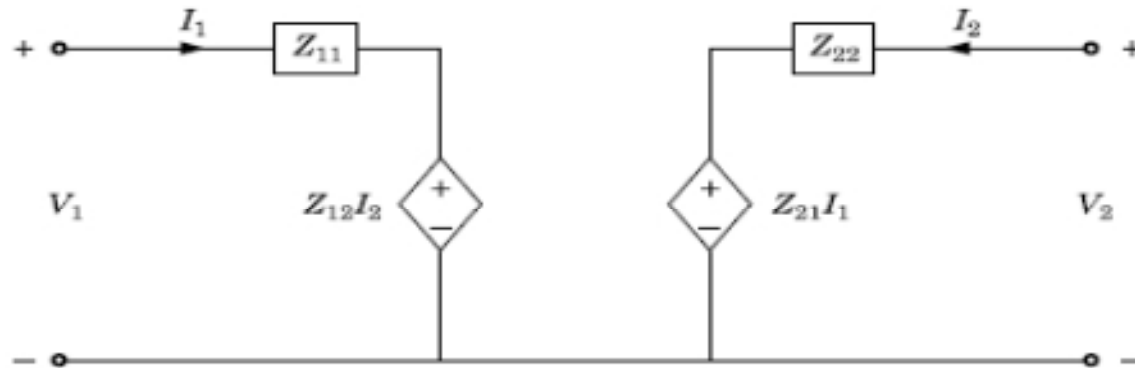


Fig. 5.2 Equivalent circuit of a two port networks in terms of Z -parameters

Calculation of Z-parameters: The Z-parameters are also called open-circuit impedance parameters since they may be measured at one terminal while the other terminal is open. They are

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

and

SHORT CIRCUIT ADMITTANCE [Y] PARAMETER

The terminal characteristics may also be written as in eq. 5.2, where I_1 and I_2 are expressed in terms of V_1 and V_2 .

$$\left. \begin{aligned} I_1 &= Y_{11}V_1 + Y_{12}V_2 \\ I_2 &= Y_{21}V_1 + Y_{22}V_2 \end{aligned} \right\} \text{ or } \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \dots(5.2)$$

The coefficients Y_{ij} have the dimension of admittance which are called the Y-parameters. The Y-parameters or short-circuit admittance parameters because they may be measured at one port while the other port is short circuited. The equivalent circuit of a two port network in terms of Y-parameters is shown in Fig. 5.16.

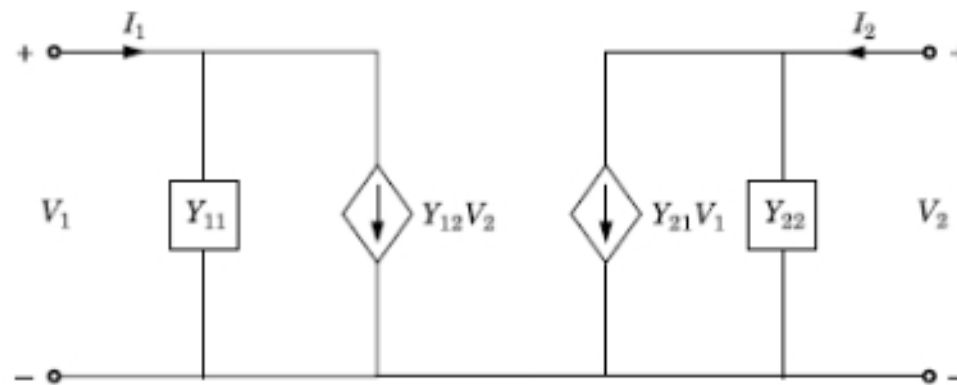


Fig. 5.16 Equivalent circuit of a two-port network in terms of Y parameters.

Calculation of Y parameters. The Y parameters are

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

HYBRID PARAMETERS

Hybrid parameters are defined by voltage of input port (V_1) and current of output port (I_2) in terms of input port (I_1) and voltage of output port (V_2) i.e.,

$$\left. \begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned} \right\} \text{ or } \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} \quad \dots (5.3)$$

The equivalent circuit of a two port network in terms of h -parameters is shown in Fig. 5.26.

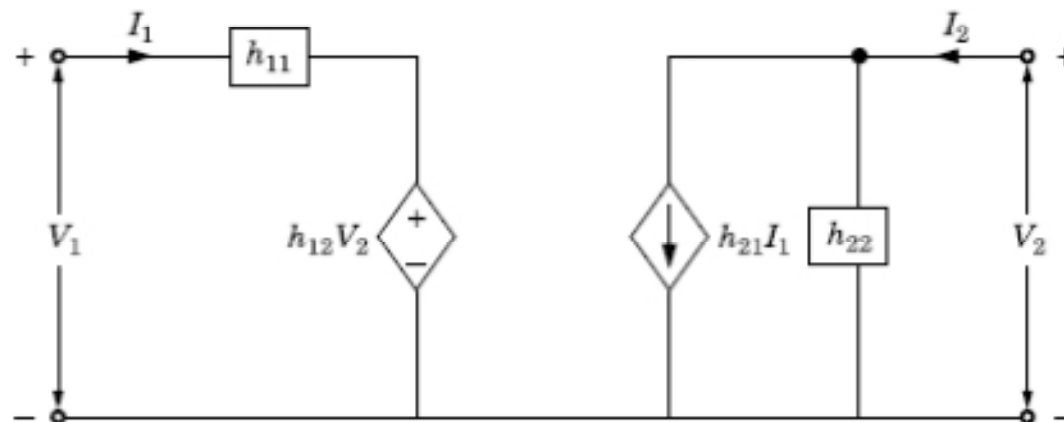


Fig. 5.26