

A decorative graphic on the left side of the slide, consisting of light blue lines and circles that resemble a circuit board or network diagram. The lines are vertical and horizontal, with some diagonal connections, and the circles are small and white with light blue outlines.


# NETWORK THEORY



# LECTURE 1

SECTION-D: TYPES OF FILTERS AND THEIR CHARACTERISTICS

# Active Filters

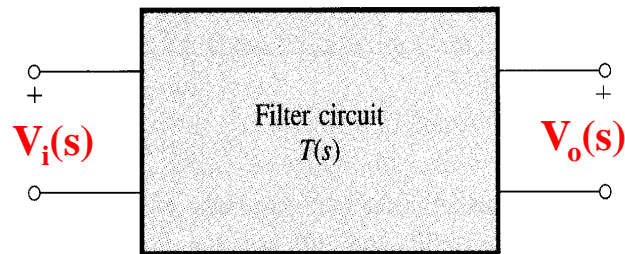

**Fig. 11.1** The filters studied in this chapter are linear circuits represented by the general two-port network shown. The filter transfer function  $T(s) \equiv V_o(s)/V_i(s)$ .

## Transfer Function

$$T(s) = \frac{V_o(s)}{V_i(s)}$$

Magnitude can be expressed as:

Gain function  $G(\omega)$  for  $|A(\omega)| > 1$

$$G(\omega) = 20 \log |T(\omega)| \text{ in dB}$$

or


Attenuation function  $A(\omega)$  for  $|A(\omega)| < 1$

$$A(\omega) = -20 \log |T(\omega)| \text{ in dB}$$


- \* **Based on use of amplifiers to achieve filter function**
- \* **Frequently use op amps so filter may have some gain as well.**
- \* **Alternative to LRC-based filters**
- \* **Benefits**
  - **Provide improved characteristics**
  - **Smaller size and weight**
  - **Monolithic integration in IC**
  - **Implement without inductors**
  - **Lower cost**
  - **More reliable**
  - **Less power dissipation**
- \* **Price**
  - **Added complexity**
  - **More design effort**
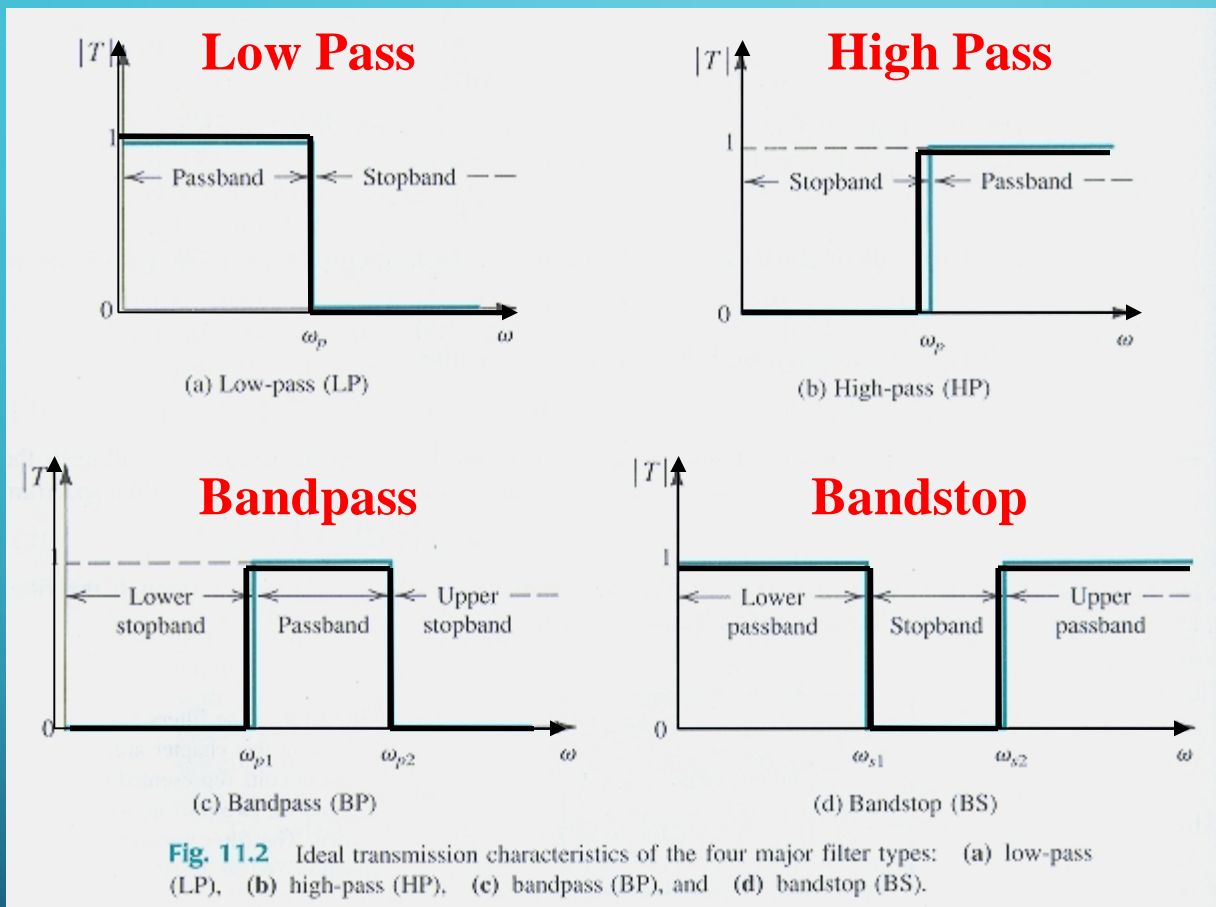
# Filter Types


- \* Four major filter types:
- **Low pass**  
(blocks high frequencies)
  - **High pass**  
(blocks low frequencies)
  - **Bandpass**  
(blocks high and low frequencies except in narrow band)
  - **Bandstop**  
(blocks frequencies in a narrow band)



# Filter Specifications

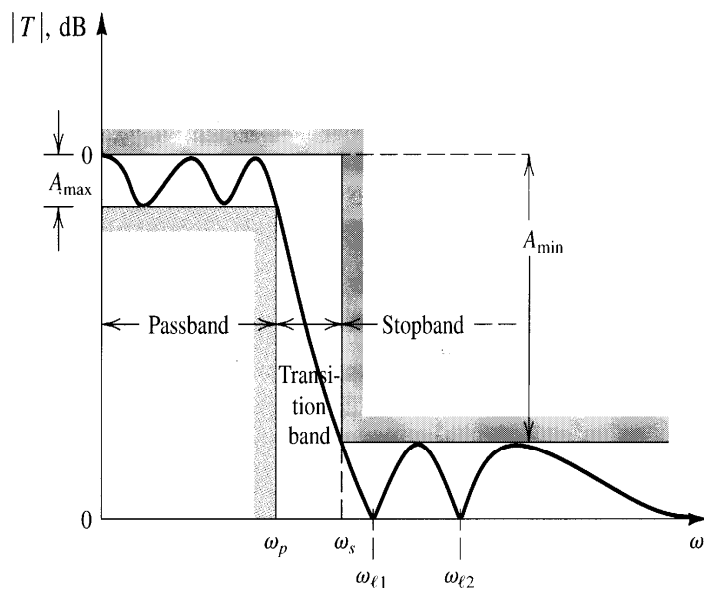

**Fig. 11.3** Specification of the transmission characteristics of a low-pass filter. The magnitude response of a filter that just meets specifications is also shown.

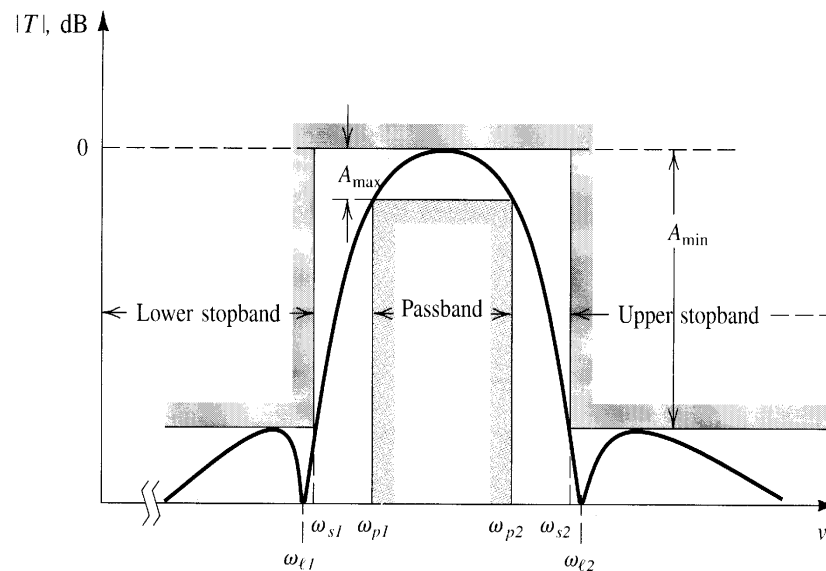

**Fig. 11.4** Transmission specifications for a bandpass filter. The magnitude response of a filter that just meets specifications is also shown. Note that this particular filter has a monotonically decreasing transmission in the passband on both sides of the peak frequency.

## \* Specifications - four parameters needed

- **Example – low pass filter:  $A_{\min}$ ,  $A_{\max}$ , Passband, Stopband**
- **Parameters specify the basic characteristics of filter, e.g. low pass filtering**
- **Specify limitations to its ability to filter, e.g. nonuniform transmission in passband, incomplete blocking of frequencies in stopband**

# Filter Transfer Function

- \* *Any filter transfer function  $T(s)$  can be written as a ratio of two polynomials in “s”*

$$T(s) = \frac{a_M s^M + a_{M-1} s^{M-1} + \dots + a_0}{s^N + b_{N-1} s^{N-1} + \dots + b_0}$$

- \* Where  $M < N$  and  $N$  is called the “order” of the filter function
  - Higher  $N$  means better filter performance
  - Higher  $N$  also means more complex circuit implementation
- \* Filter transfer function  $T(s)$  can be rewritten as

$$T(s) = \frac{a_M (s - z_1)(s - z_2) \dots (s - z_M)}{(s - p_1)(s - p_2) \dots (s - p_N)}$$

- where  $z$ 's are “zeros” and  $p$ 's are “poles” of  $T(s)$
- where poles and zeroes can be real or complex
- \* *Form of transfer function is similar to low frequency function  $F_L(s)$  seen previously for amplifiers where  $A(s) = A_M F_L(s) F_H(s)$*

# First Order Filter Functions

\* First order filter functions are of the **general form**

$$T(s) = \frac{a_1 s + a_0}{s + \omega_0} = \frac{a_1 \left( s + \frac{a_0}{a_1} \right)}{s + \omega_0}$$

Low Pass

High Pass

906


Filter Type and $T(s)$	$s$ -Plane Singularities	Bode Plot for $ T $	Passive Realization	Op Amp-RC Realization
(a) Low-Pass (LP) $T(s) = \frac{a_0}{s + \omega_0}$ <b><math>a_1 = 0</math></b>			<p><math>CR = \frac{1}{\omega_0}</math> dc gain = 1</p>	<p><math>CR_2 = \frac{1}{\omega_0}</math> dc gain = <math>-\frac{R_2}{R_1}</math></p>
(b) High-Pass (HP) $T(s) = \frac{a_1 s}{s + \omega_0}$ <b><math>a_0 = 0</math></b>			<p><math>CR = \frac{1}{\omega_0}</math> High-frequency gain = 1</p>	<p><math>CR_1 = \frac{1}{\omega_0}</math> High-frequency gain = <math>-\frac{R_2}{R_1}</math></p>

# First Order Filter Functions

\* First order filter functions are of the form

$$T(s) = \frac{a_1 s + a_o}{s + \omega_0} = \frac{a_1 \left( s + \frac{a_o}{a_1} \right)}{s + \omega_0}$$

General

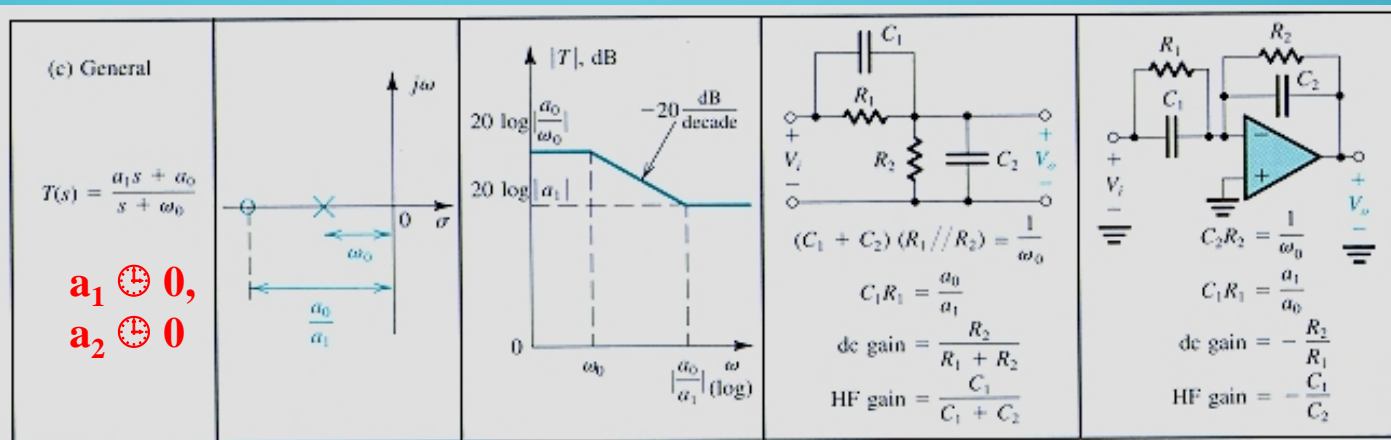

All Pass

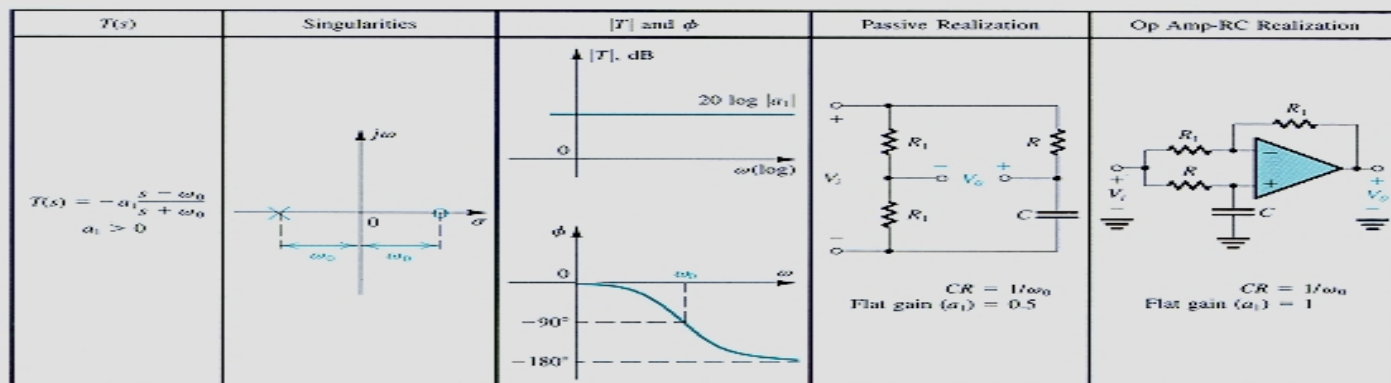


Fig. 11.14 First-order all-pass filter.