

A decorative graphic on the left side of the slide, consisting of white lines and circles that resemble a circuit board or network diagram. The lines are vertical and horizontal, with some diagonal connections, and the circles are small and white, placed at various points along the lines.


NETWORK THEORY



LECTURE 2

SECTION-D: TYPES OF FILTERS AND THEIR CHARACTERISTICS

Example of First Order Filter - Passive

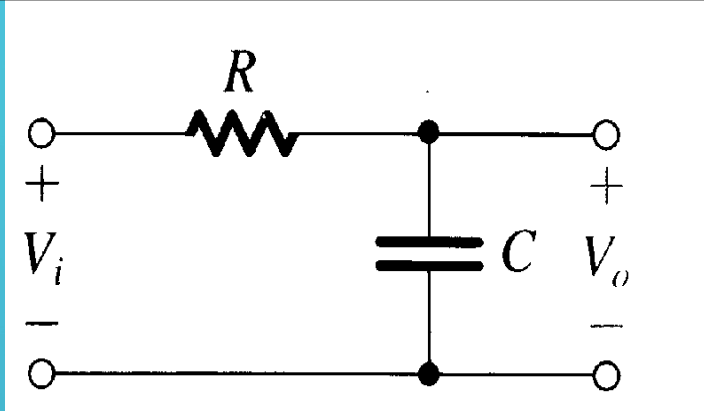


* Low Pass Filter

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{Z_C}{Z_C + R} = \frac{\left(\frac{1}{sC}\right)}{R + \frac{1}{sC}} = \frac{1}{1 + sRC}$$

$$= \frac{1}{1 + s \frac{1}{(1/RC)}} = \frac{1}{1 + \frac{s}{\omega_0}} = \frac{\omega_0}{s + \omega_0}$$

where $\omega_0 = \frac{1}{RC}$

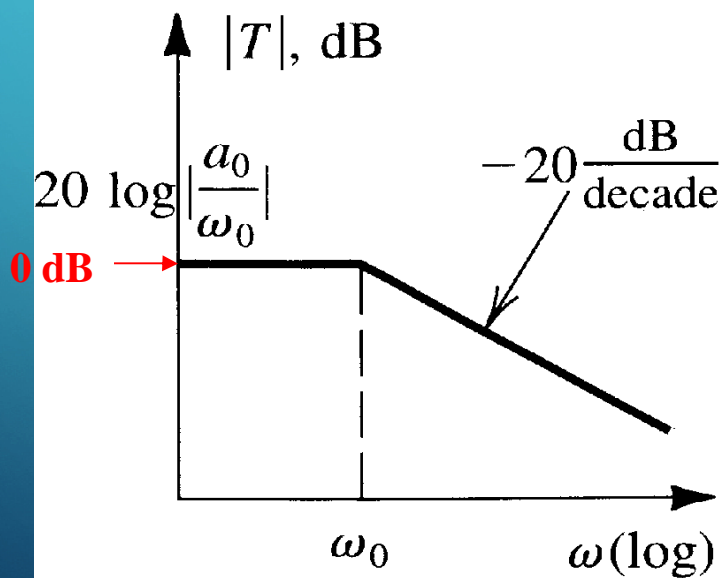This has the form of a first order (low pass) filter with $a_1 = 0$ $a_0 = \omega_0$





$$T(\omega)(in\ dB) = 20 \log \left[\frac{1}{1 + \left(\frac{\omega}{\omega_0}\right)^2} \right]^{1/2} = -10 \log \left[1 + \left(\frac{\omega}{\omega_0}\right)^2 \right]$$

For $\omega \ll \omega_0$, $T(\omega) \approx 1 \rightarrow 0\ dB$

For $\omega \gg \omega_0$, $T(\omega) \approx -20 \log \left(\frac{\omega}{\omega_0} \right)$

Example of First Order Filter - Active

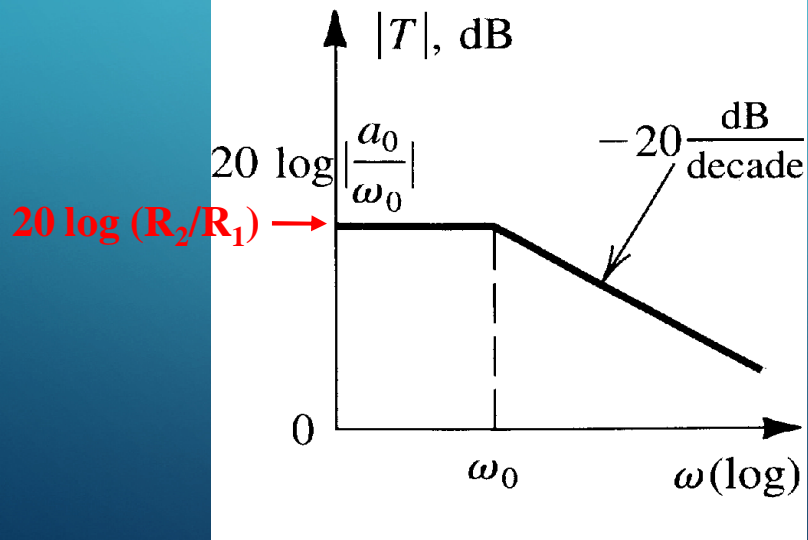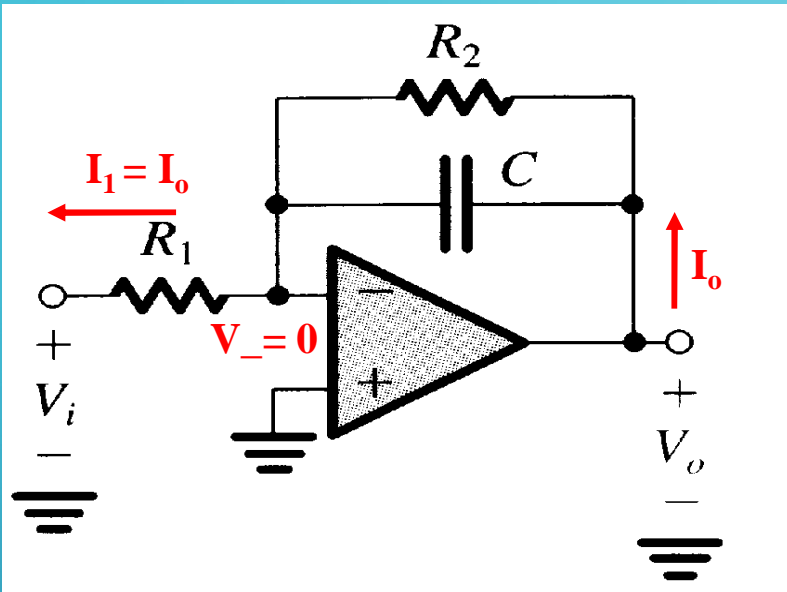

* Low Pass Filter

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{I_o(R_2 \parallel Z_C)}{-I_1 R_1} = \frac{-(R_2 \parallel Z_C)}{R_1} = \frac{\left(\frac{1}{(1/R_2) + sC} \right)}{R_1} = \frac{-R_2}{R_1(1 + sR_2C)}$$

$$= \frac{-R_2}{R_1} \frac{1}{1 + s \frac{1}{(1/R_2C)}} = \frac{-R_2}{R_1} \frac{1}{1 + \frac{s}{\omega_0}} = \frac{-R_2}{R_1} \frac{\omega_0}{s + \omega_0}$$

where $\omega_0 = \frac{1}{R_2C}$

This has the form of a first order (low pass) filter with

$$a_1 = 0 \quad a_0 = \frac{-R_2}{R_1} \omega_0$$

Gain Filter function

$$T(\omega)(in \text{ dB}) = 20 \log \left(\frac{R_2}{R_1} \right) + 20 \log \left[\frac{1}{1 + \left(\frac{\omega}{\omega_0} \right)^2} \right]^{1/2}$$

$$= 20 \log \left(\frac{R_2}{R_1} \right) - 10 \log \left[1 + \left(\frac{\omega}{\omega_0} \right)^2 \right]$$

For $\omega \ll \omega_0$, $T(\omega) \approx 20 \log \left(\frac{R_2}{R_1} \right) > 0 \text{ dB}$ for $R_2 > R_1$

For $\omega \gg \omega_0$, $T(\omega) \approx 20 \log \left(\frac{R_2}{R_1} \right) - 20 \log \left(\frac{\omega}{\omega_0} \right)$

Second-Order Filter Functions

* Second order filter functions are of the form


$$T(s) = \frac{a_2 s^2 + a_1 s + a_o}{s^2 + b_1 s + b_o}$$

which we can rewrite as

$$T(s) = \frac{a_2 s^2 + a_1 s + a_o}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

where ω_0 and Q determine the poles
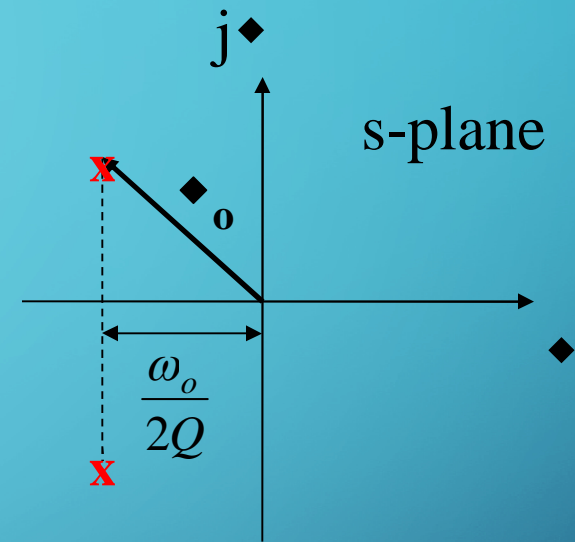
$$p_1, p_2 = \omega_{P1}, \omega_{P2} = -\frac{\omega_0}{2Q} \pm j \frac{\omega_0}{2Q} \sqrt{1-4Q^2}$$



This looks like the expression for the new poles that we had for a feedback amplifier with two poles.

* There are seven second order filter types:
 Low pass, high pass, bandpass, notch,
 Low-pass notch, High-pass notch and
 All-pass

Second-Order Filter Functions

$$T(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

Low Pass

$$a_1 = 0, a_2 = 0$$

High Pass

$$a_0 = 0, a_1 = 0$$

Bandpass

$$a_0 = 0, a_2 = 0$$

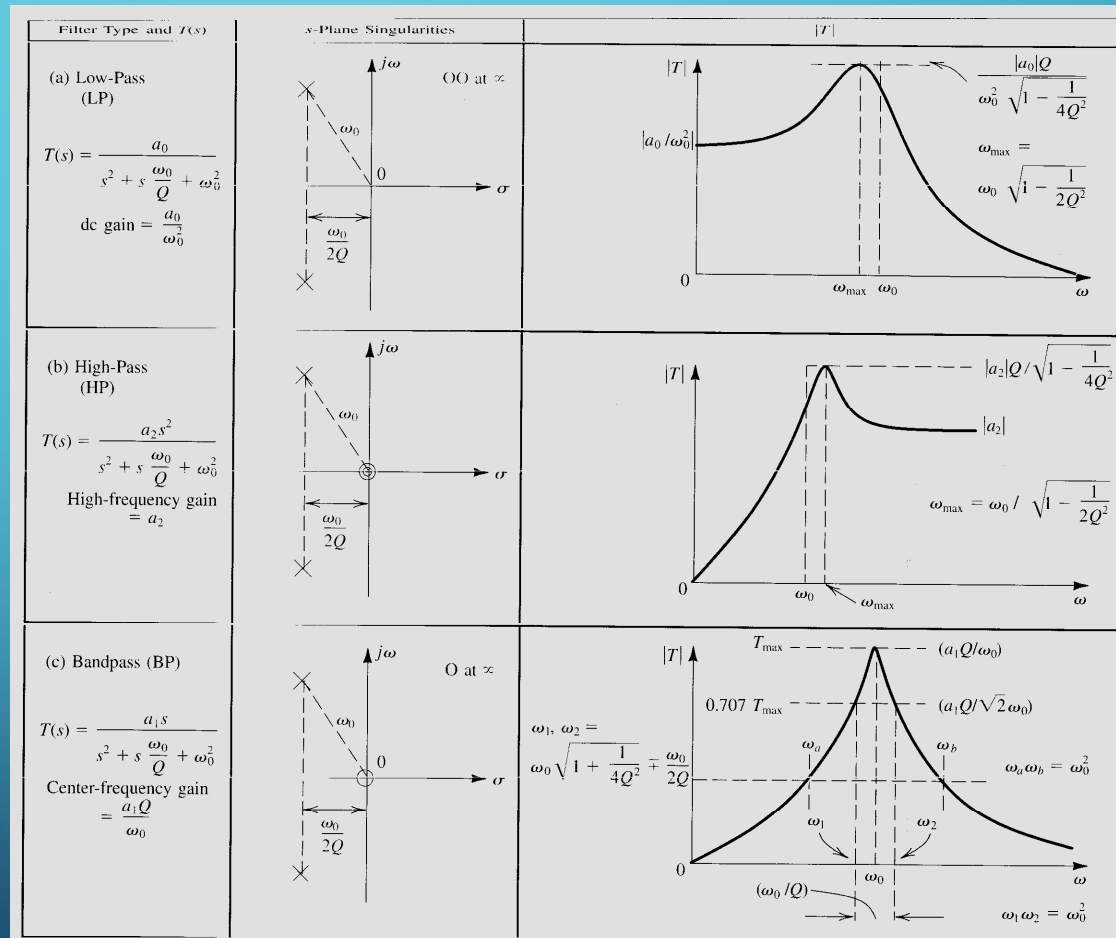


Fig. 11.16 Second-order filtering functions.

Second-Order Filter Functions

$$T(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

Notch

$$a_1 = 0, a_0 = \omega_0^2$$


Low Pass Notch (LPN)

$$a_1 = 0, a_0 > \omega_0^2$$

High Pass Notch (HPN)

$$a_1 = 0, a_0 < \omega_0^2$$

All-Pass

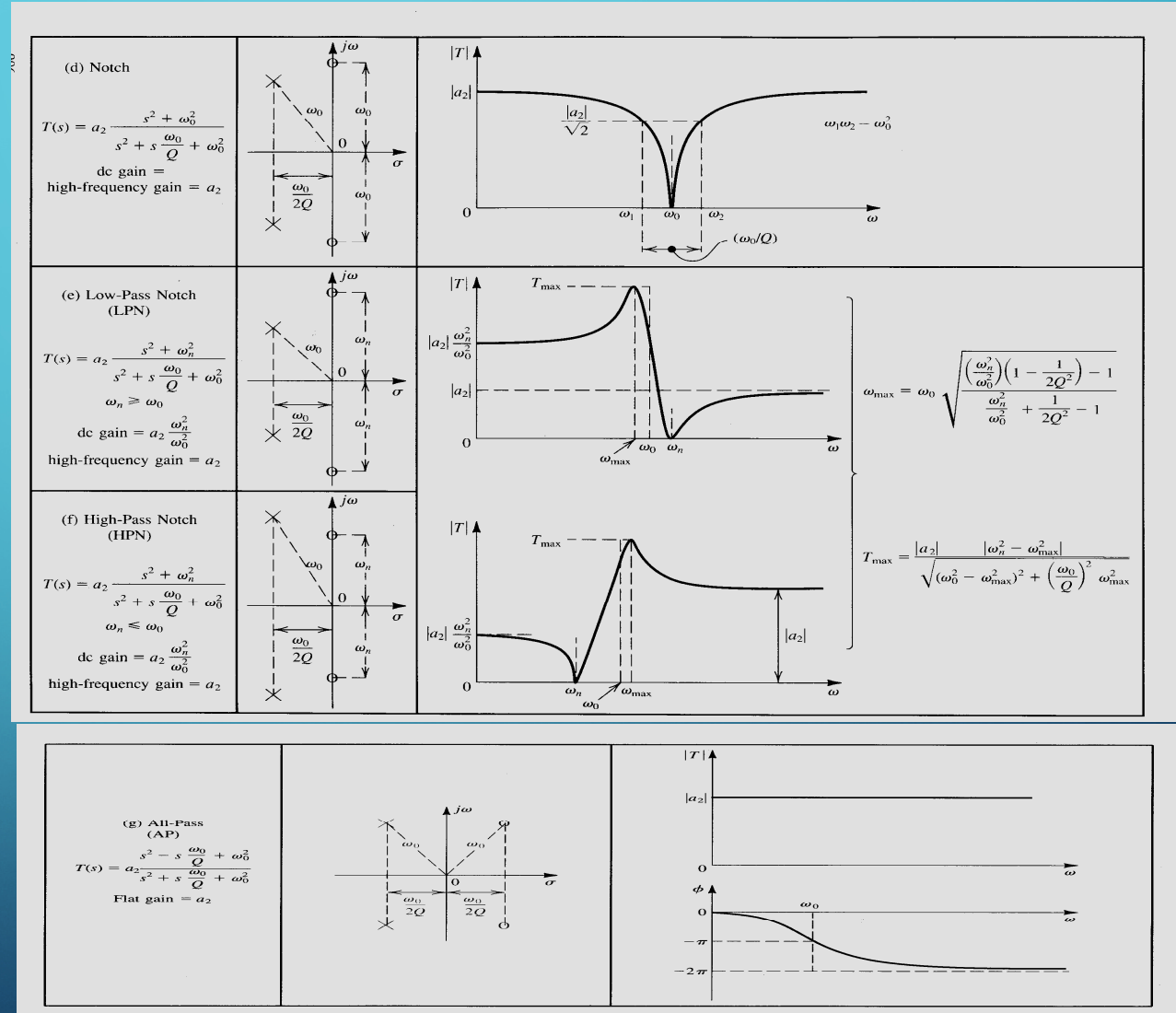

Passive Second Order Filter Functions

* Second order filter functions can be implemented with simple RLC circuits

* General form is that of a voltage divider with a transfer function given by

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{a_2s^2 + a_1s + a_0}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

* Seven types of second order filters

- High pass
- Low pass
- Bandpass
- Notch at ω_0
- General notch
- Low pass notch
- High pass notch

