

A decorative graphic on the left side of the slide, consisting of white lines and circles that resemble a circuit board or network diagram. The lines are vertical and horizontal, with some diagonal connections, and the circles are small and white, placed at various points along the lines.


# NETWORK THEORY



# LECTURE 3

SECTION-D: TYPES OF FILTERS AND THEIR CHARACTERISTICS
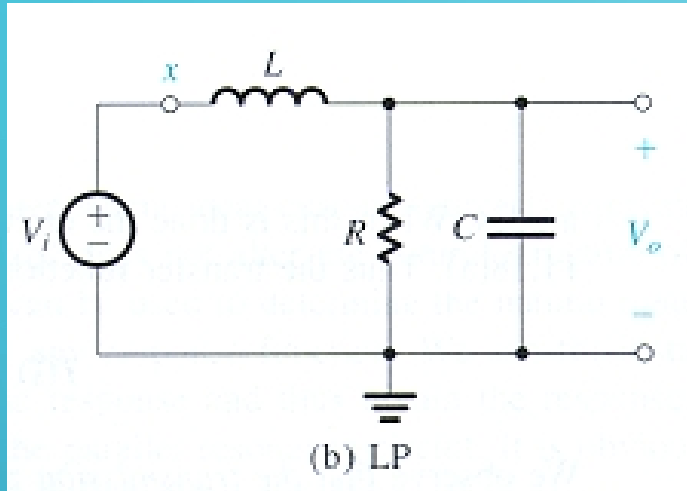
# Example - Passive Second Order Filter Function



\* Low pass filter

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{Z_C \parallel R}{Z_C \parallel R + Z_L}$$

$$\text{where } Z_C \parallel R = \frac{1}{\frac{1}{Z_C} + \frac{1}{R}} = \frac{1}{sC + \frac{1}{R}} = \frac{R}{1 + sRC} \quad \text{so}$$

$$T(s) = \frac{Z_C \parallel R}{Z_C \parallel R + Z_L} = \frac{\left(\frac{R}{1 + sRC}\right)}{sL + \frac{R}{1 + sRC}} = \frac{1}{\left(\frac{1 + sRC}{R}\right)\left(sL + \frac{R}{1 + sRC}\right)}$$

$$= \frac{1}{1 + s\frac{L}{R} + s^2LC} = \frac{\left(\frac{1}{LC}\right)}{s^2 + s\left(\frac{1}{RC}\right) + \frac{1}{LC}} = \frac{\omega_o^2}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2}$$

$$\text{where } \omega_o = \frac{1}{\sqrt{LC}} \quad \text{and} \quad Q = RC\omega_o = R\sqrt{\frac{C}{L}}$$


This has the form of a second order filter with

$$a_2 = 0, \quad a_1 = 0 \quad a_0 = \omega_o^2$$

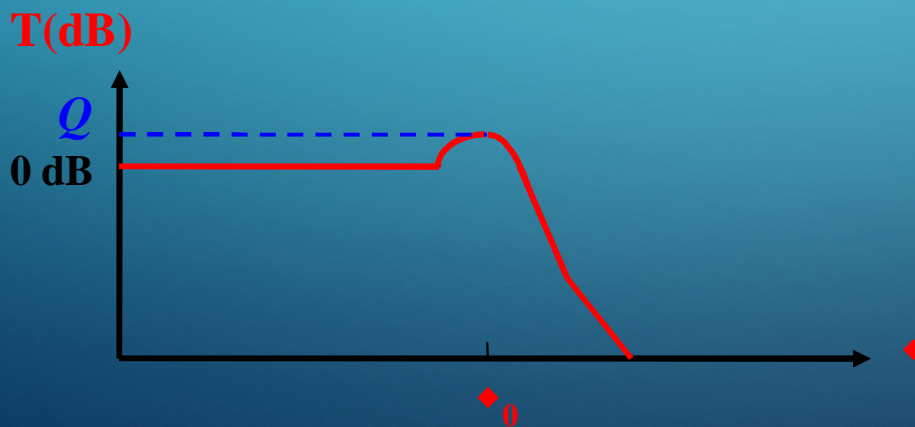
**General form of transfer function**

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$


$$T(s) = \frac{\omega_o^2}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2} = \begin{cases} \rightarrow 0 \text{ as } s \rightarrow \infty \\ \rightarrow Q \text{ as } s = j\omega_o \\ \rightarrow 1 \text{ as } s \rightarrow 0 \end{cases}$$


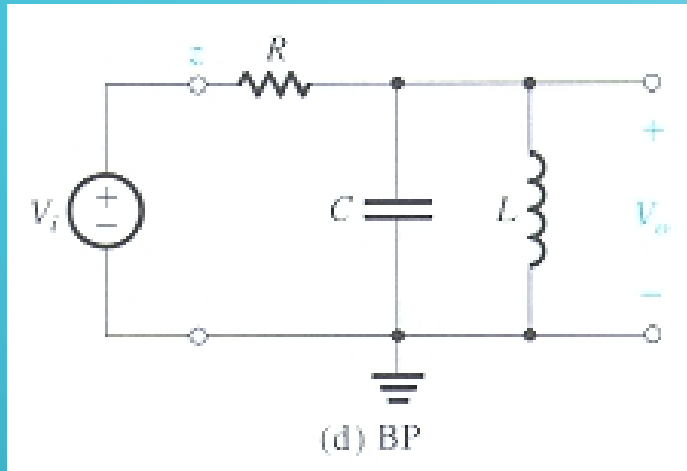
# Example - Passive Second Order Filter Function


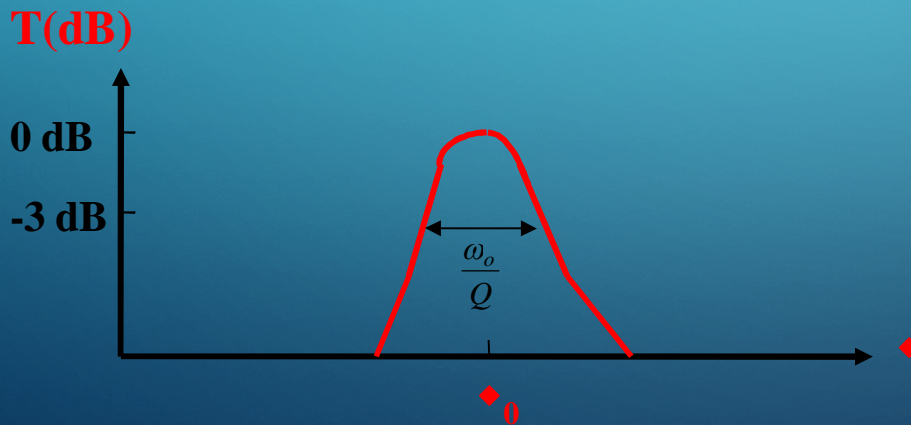
$$T(s) = \frac{s \frac{\omega_0}{Q}}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} = \begin{cases} \rightarrow \frac{s}{s^2} \rightarrow 0 \text{ as } s \rightarrow \infty \\ \rightarrow 1 \text{ at } s = j\omega_0 \\ \rightarrow \frac{s}{\omega_0^2} \rightarrow 0 \text{ as } s \rightarrow 0 \end{cases}$$



## \* Bandpass filter

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{Z_C \parallel Z_L}{Z_C \parallel Z_L + R}$$

$$\text{where } Z_C \parallel Z_L = \frac{1}{\frac{1}{Z_C} + \frac{1}{Z_L}} = \frac{1}{sC + \frac{1}{sL}} = \frac{sL}{1 + s^2LC} \quad \text{so}$$

$$T(s) = \frac{Z_C \parallel Z_L}{Z_C \parallel Z_L + R} = \frac{\left( \frac{sL}{1 + s^2LC} \right)}{R + \frac{sL}{1 + s^2LC}} = \frac{sL}{sL + R(1 + s^2LC)}$$

$$= \frac{s \frac{1}{RC}}{s^2 + s \frac{1}{RC} + \frac{1}{LC}} = \frac{\frac{1}{RC} s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

$$\text{where } \omega_0 = \frac{1}{\sqrt{LC}} \quad \text{and} \quad Q = RC\omega_0 = R\sqrt{\frac{C}{L}}$$



This has the form of a second order filter with

$$a_2 = 0, \quad a_1 = \frac{1}{RC} = \frac{\omega_0}{Q}, \quad a_0 = 0$$

## General form of transfer function

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

# Low Pass Butterworth Filter Design

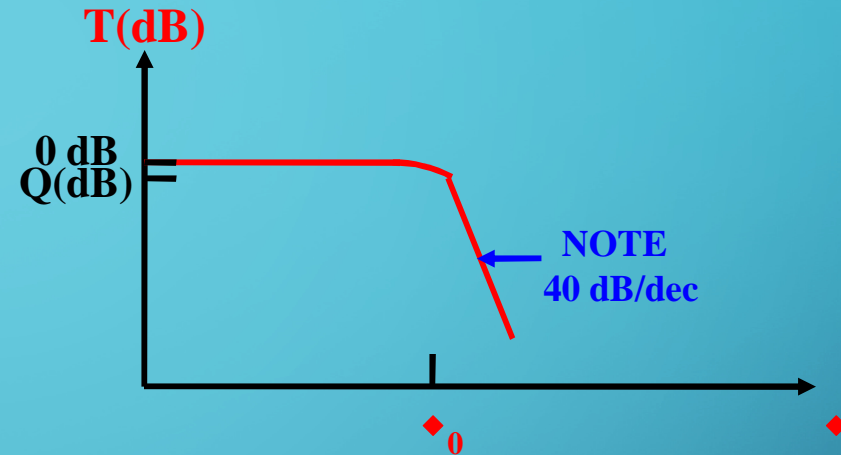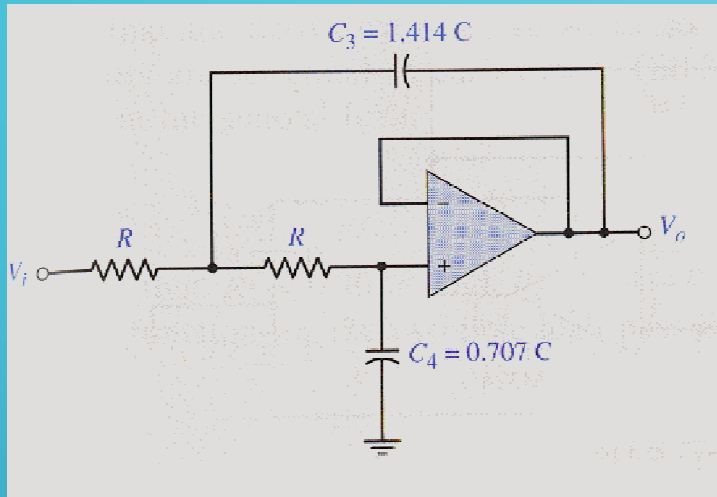

Hurwitz Polynomials

$$T(s) = \frac{V_o}{V_i} = \frac{1/R^2C^2}{s^2 + s \frac{2}{RC} + \frac{1}{R^2C^2}} = \begin{cases} \rightarrow 1 \text{ as } s \rightarrow 0 \\ \rightarrow -j/2 \text{ as } s \rightarrow j\omega_o \\ \rightarrow 0 \text{ as } s \rightarrow \infty \end{cases}$$

- \* Given the filter specification ( $\omega_o$ ), we can determine the R and C.
- \* One specification, two parameters – R and C
- \* Pick a convenient value, say  $C = 5 \text{ nF}$ .
- \* Calculate R from C and  $\omega_o$ .

$$\omega_o = \frac{1}{RC} \quad \text{so} \quad R = \frac{1}{C\omega_o}$$

Example: Given  $\omega_o = 2\pi(2\text{MHz}) = 1.26 \times 10^7 \text{ rad/sec}$

Choose  $C = 5 \text{ nF}$ , then

$$R = \frac{1}{C\omega_o} = \frac{1}{(5 \times 10^{-9} \text{ F})(1.26 \times 10^7 \text{ rad/sec})} = 16 \Omega$$

# PROPERTY 1. L-C IMMITTANCE FUNCTION

- 1.  $Z_{LC}(s)$  or  $Y_{LC}(s)$  is the ratio of odd to even or even to odd polynomials.

- Consider the impedance  $Z(s)$  of passive one-port network.  
$$Z(s) = \frac{M_1(s) + N_1(s)}{M_2(s) + N_2(s)}$$

(M is even N is odd)

As we know, when the input current is  $I$ , the average power dissipated by one-port network is zero:

$$\frac{1}{2} \operatorname{Re}[Z(j\omega)] |I|^2$$

$$\text{Average Power} = \quad = 0$$

$$\text{EvZ}(s) = \frac{M_1(s)M_2(s) - N_1(s)N_2(s)}{M_2(s)^2 + N_2(s)^2} = 0$$

$$M_1(j\omega)M_2(j\omega) - N_1(j\omega)N_2(j\omega) = 0$$

$$M_1 = 0 = N_2 \quad \text{OR} \quad M_2 = 0 = N_1$$

$$Z(s) = \frac{M_1}{N_2}, Z(s) = \frac{N_1}{M_2}$$

**Z(s) or Y(s) is the ratio of even to odd or odd to even!!**

# PROPERTY 2. L-C IMMITTANCE FUNCTION

- 2. The poles and zeros are simple and lie on the  $j\omega$  axis.

$$Z(s) = \frac{M_1}{N_2}, Z(s) = \frac{N_1}{M_2}$$

- Since both M and N are Hurwitz, they have only imaginary roots, and it follows that the poles and zeros of Z(s) or Y(s) are on the imaginary axis.

- Consider the example

$$Z(s) = \frac{a_4s^4 + a_2s^2 + a_0}{b_5s^5 + b_3s^3 + b_1s}$$



$$Z(s) = \frac{a_4s^4 + a_2s^2 + a_0}{b_5s^5 + b_3s^3 + b_1s}$$

In order for the impedance to be positive real  $\rightarrow$  the coefficients must be real and positive.

Impedance function **cannot have multiple poles or zeros** on the  $j\omega$  axis.

The highest powers of the numerator and the denominator polynomials can differ by, at most, unity.

Ex) highest order of the numerator :  $2n \rightarrow$  highest order of the denominator can either be  $2n-1$  (simple pole at  $s = \infty$ ) or the order can be  $2n+1$  (simple zero at  $s = \infty$ ).