

A decorative graphic on the left side of the slide, consisting of white lines and circles that resemble a circuit board or network diagram. The lines are vertical and horizontal, with some diagonal connections, and the circles are small and white, placed at various points along the lines.

NETWORK THEORY



LECTURE 5

SECTION-D :NETWORK SYNTHESIS

SYNTHESIS OF L-C DRIVING POINT IMMITTANCES

- L-C immittance is a positive real function with poles and zeros on the $j\omega$ axis only.

$$Z(s) = \frac{K_0}{s} + \frac{2K_2s}{s^2 + \omega_2^2} + \frac{2K_4s}{s^2 + \omega_4^2} + \dots + K_\infty s$$


- The synthesis is accomplished directly from the partial fraction .
- $F(s)$ is impedance \rightarrow then the term K_0/s :
capacitor of $1/K$ farads
the $K(\text{infinite})s$ is an inductance of $K(\text{infinite})$ henrys.

OR Z(S) PARTIAL FRACTION

$2K_i s / (s^2 + \omega_i^2)$ Is a parallel tank capacitance and inductance.

$$1/2K_i, \quad 2K_i / \omega_i^2$$

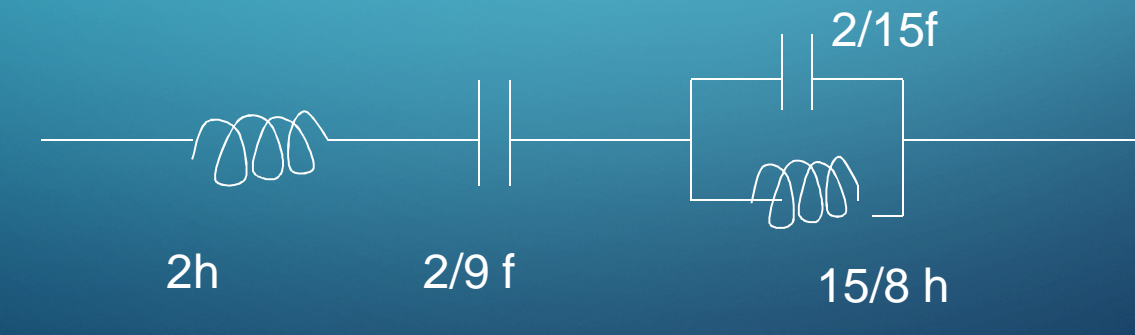
$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)} = 2s + \frac{9}{s} + \frac{15}{s^2 + 4} s$$



FOR $Y(S)$ PARTIAL FRACTION

n admittance
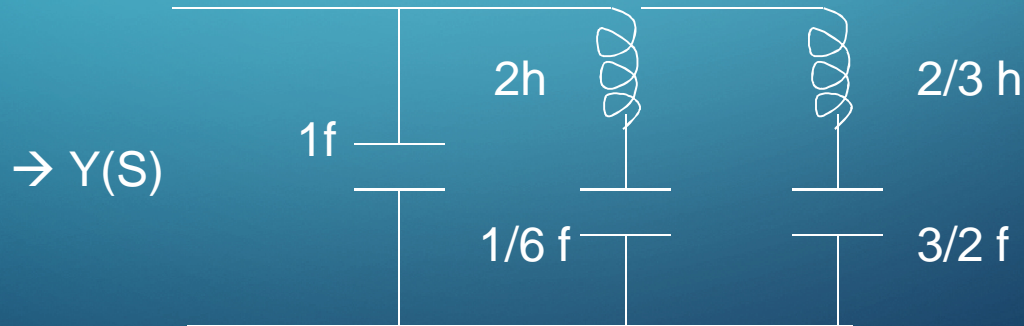
$$Y(s) = \frac{s(s^2 + 2)(s^2 + 4)}{(s^2 + 1)(s^2 + 3)} = s + \frac{\frac{1}{2}s}{s^2 + 3} + \frac{\frac{3}{2}s}{s^2 + 1}$$



ANOTHER METHODOLOGY

- Using property 4 “The highest powers of numerator and denominator must differ by unity; the lowest powers also differ by unity.”
 - Therefore, there is always a zero or a pole at $s=\infty$.
 - suppose $Z(s)$ numerator: $2n$, denominator: $2n-1$
 - this network has pole at ∞ . \rightarrow we can remove this pole by removing an impedance $L_1 s$

$$Z_2(s) = Z(s) - L_1 s$$

- Degree of denominator : $2n-1$ numerator: $2n-2$
 - $Z_2(s)$ has zero at $s=\infty$.
 - $Y_2(s) = 1/Z_2(s)$, $\rightarrow Y_3(s) = Y_2(s) - C_2 s$



- This infinite term removing process continues until the remainder is zero.
- Each time we remove the pole, we remove an inductor or capacitor depending upon whether the function is an impedance or an admittance.
- → Final synthesized is a ladder whose series arms are inductors and shunt arms are capacitors.



$$Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$$

$$Z_2(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3} - 2s = \frac{4s^3 + 10s}{s^4 + 4s^2 + 3}$$

$$Y_3(s) = \frac{s^4 + 4s^2 + 3}{4s^3 + 10s} - \frac{1}{4}s = \frac{\frac{3}{2}s^2 + 3}{4s^3 + 10s}$$

$$Z_4(s) = Z_3 - \frac{8}{3}s = \frac{2s}{\frac{3}{2}s^2 + 3} \quad 2h$$

