

The slide features a teal-to-blue gradient background. On the left side, there are decorative white lines resembling a circuit board or network diagram, with several small circles at the end of the lines. The text "NETWORK THEORY" is centered in the upper half of the slide in a white, sans-serif font.

NETWORK THEORY




LECTURE 6

SECTION-D :NETWORK SYNTHESIS

- This circuit (Ladder) called as Cauer because Cauer discovered the continues fraction method.
- Without going into the proof of the statement m in can be said that both the Foster and Cauer form gice the minimum number of elements for a specified L-C network.

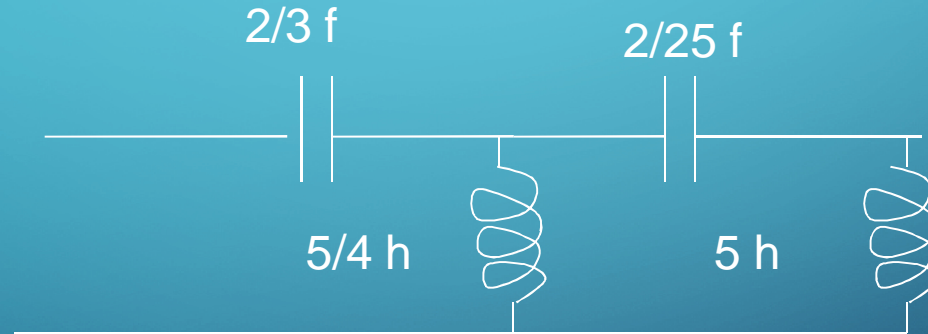EXAMPLE OF CAUER METHOD

$$Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$$




ACTIVE NETWORK SYNTHESIS

- An operational amplifier, commonly called Op-Amp, is a three stage circuit namely, the input stage, gain stage and output stage and which is fabricated as an integrated circuit. The IC 741 is a widely used all-bipolar general purpose Op-Amp.

OPERATIONAL AMPLIFIER (OP-AMP)

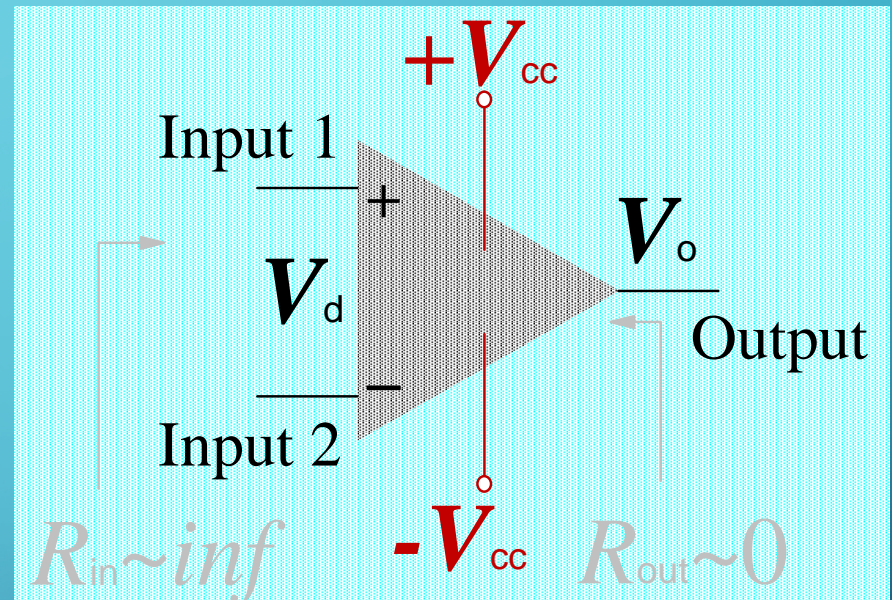
- Very high differential gain
- High input impedance
- Low output impedance
- Provide voltage changes (amplitude and polarity)
- Used in oscillator, filter and instrumentation
- Accumulate a very high gain by multiple stages




$$V_o = G_d V_d$$

G_d : differential gain normally very large, say 10^5

IC PRODUCT

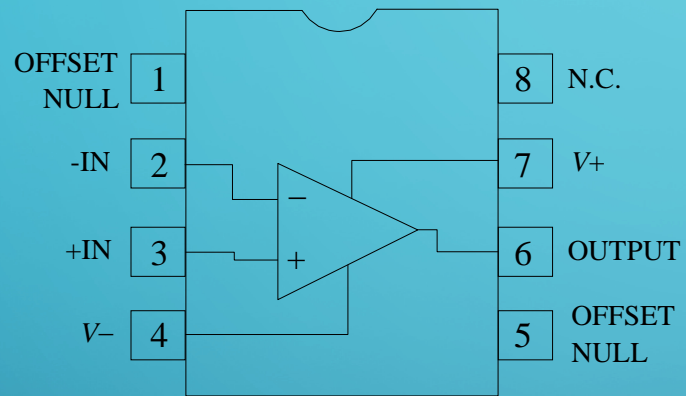


DIP-741

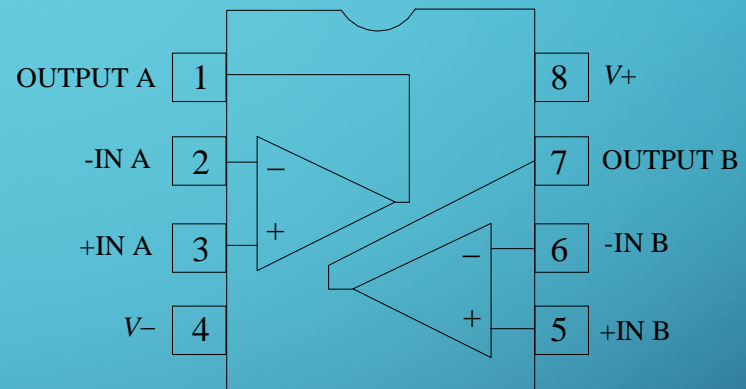


Dual op-amp 1458 device

SINGLE-ENDED INPUT

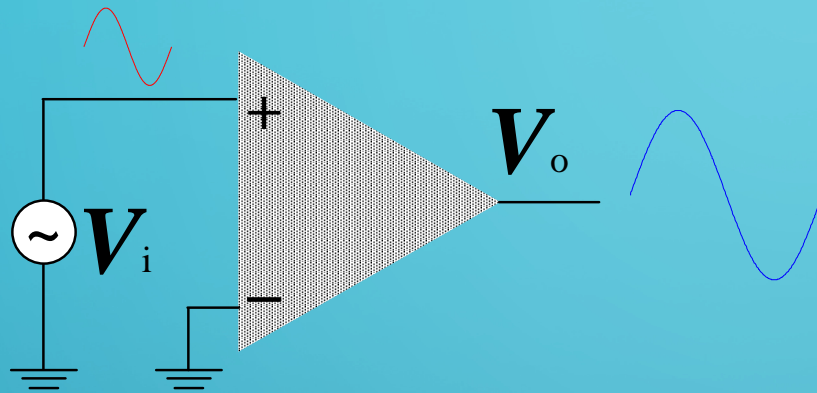

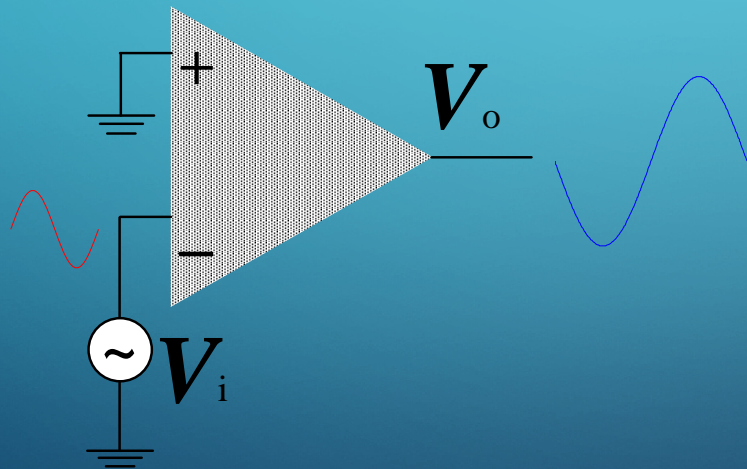- + terminal : Source
- - terminal : Ground
- 0° phase change



- + terminal : Ground
- - terminal : Source
- 180° phase change