

A decorative graphic on the left side of the slide, consisting of white lines and circles that resemble a circuit board or network diagram. The lines are vertical and horizontal, with some diagonal connections, and the circles are small and white, placed at various points along the lines.


NETWORK THEORY




LECTURE 7

SECTION-D :NETWORK SYNTHESIS


DOUBLE-ENDED INPUT

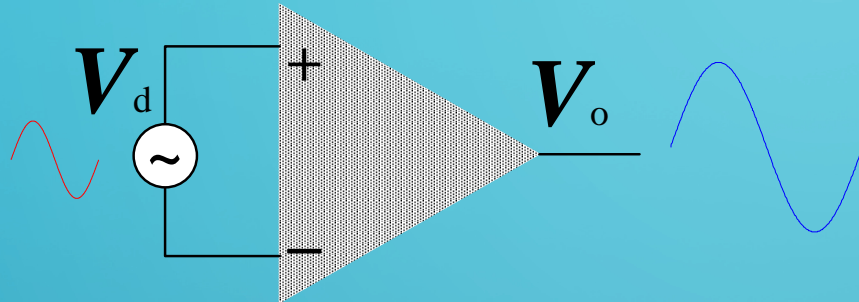

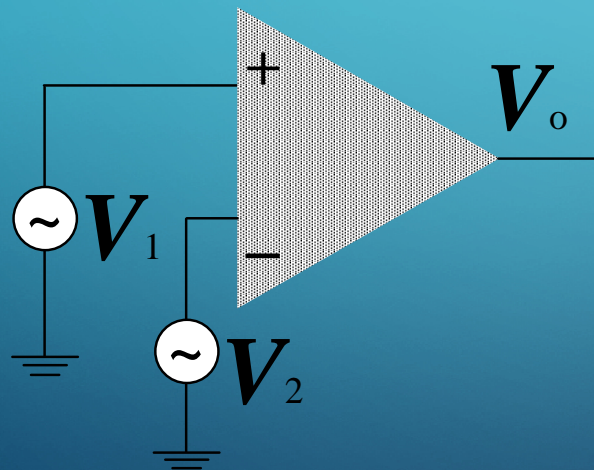
- Differential input
- $V_d = V_+ - V_-$
- 0° phase shift change between V_o and V_d




Qu: What V_o should be if,

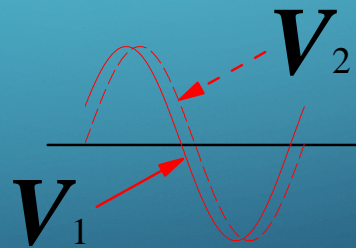

Ans: (A or B) ?

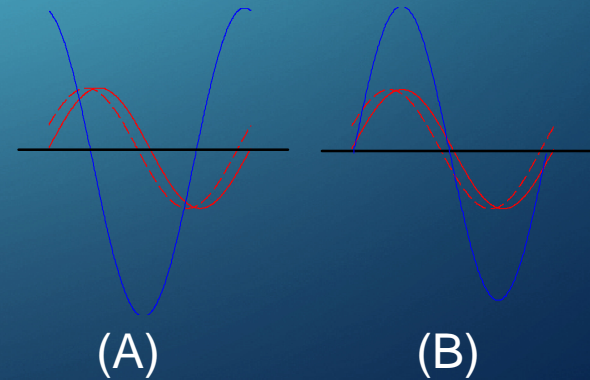


DISTORTION

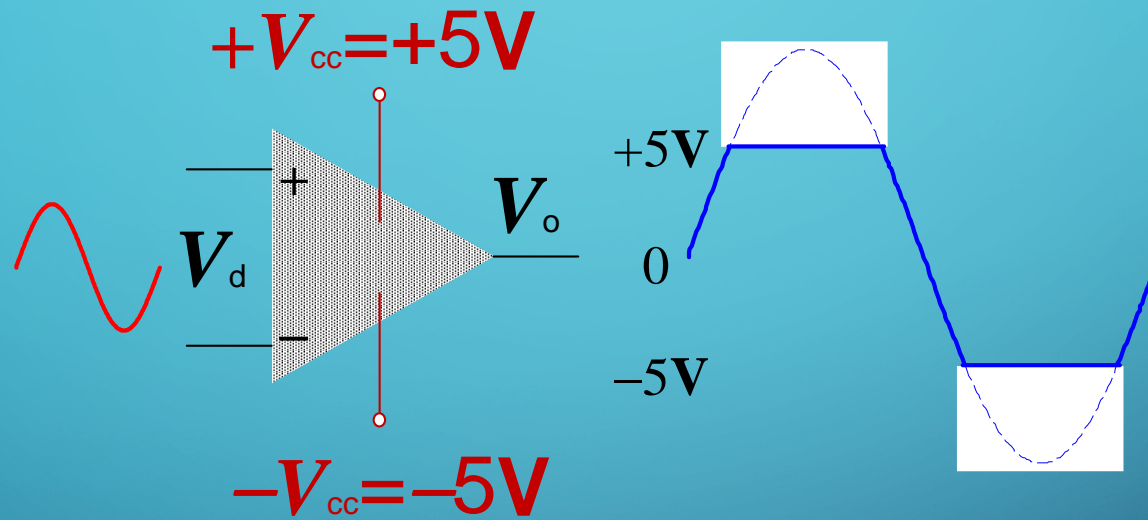

The output voltage never exceeds the DC voltage supply of the Op-Amp

COMMON-MODE OPERATION

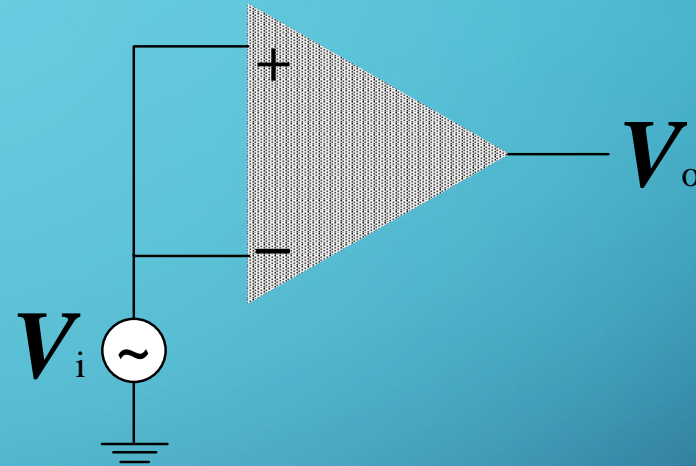- Same voltage source is applied at both terminals
- Ideally, two input are equally amplified
- Output voltage is ideally zero due to differential voltage is zero
- Practically, a small output signal can still be measured



Note for differential circuits:
Opposite inputs : highly amplified
Common inputs : slightly amplified

⇒ Common-Mode Rejection

COMMON-MODE REJECTION RATIO (CMRR)

Differential voltage input :

$$V_d = V_+ - V_-$$

Common voltage input :


$$V_c = \frac{1}{2}(V_+ + V_-)$$

Output voltage :

$$V_o = G_d V_d + G_c V_c$$

G_d : Differential gain

G_c : Common mode gain

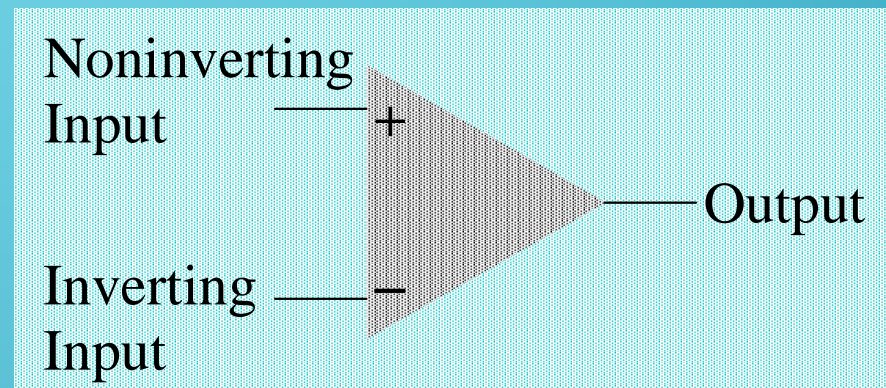

Common-mode rejection ratio:

$$\text{CMRR} = \frac{G_d}{G_c} = 20 \log_{10} \frac{G_d}{G_c} \text{ (dB)}$$



Note:

When $G_d \gg G_c$ or $\text{CMRR} \rightarrow \infty$

$\Rightarrow V_o = G_d V_d$

CMRR EXAMPLE

What is the CMRR?

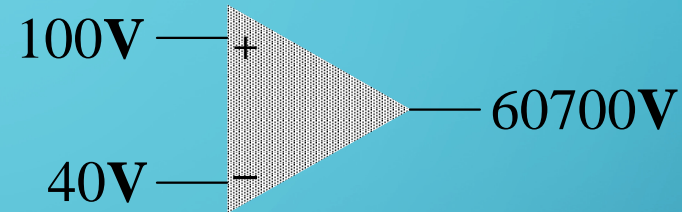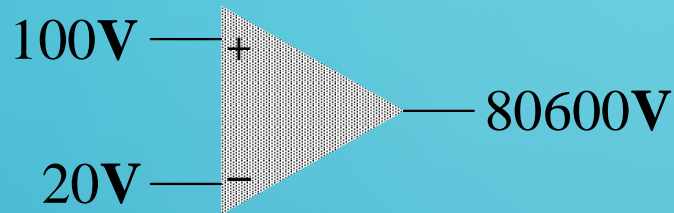

Solution :

$$\left. \begin{aligned} V_{d1} &= 100 - 20 = 80\text{V} \\ V_{c1} &= \frac{100 + 20}{2} = 60\text{V} \end{aligned} \right\} (1)$$

$$\left. \begin{aligned} V_{d2} &= 100 - 40 = 60\text{V} \\ V_{c2} &= \frac{100 + 40}{2} = 70\text{V} \end{aligned} \right\} (2)$$

From (1) $V_o = 80G_d + 60G_c = 80600\text{V}$

From (2) $V_o = 60G_d + 70G_c = 60700\text{V}$

$G_d = 1000$ and $G_c = 10 \Rightarrow \text{CMRR} = 20\log(1000/10) = 40\text{dB}$

NB: This method is Not work! Why?

OP-AMP PROPERTIES

(1) Infinite Open Loop gain

- The gain without feedback
- Equal to differential gain
- Zero common-mode gain
- Practically, $G_d = 20,000$ to $200,000$

(2) Infinite Input impedance

- Input current $i_i \sim 0A$
- T- Ω in high-grade op-amp
- m-A input current in low-grade op-amp

(3) Zero Output Impedance

- act as perfect internal voltage source
- No internal resistance
- Output impedance in series with load
- Reducing output voltage to the load
- Practically, $R_{out} \sim 20-100 \Omega$

