

A decorative graphic on the left side of the slide, consisting of white lines and circles on a blue gradient background, resembling a circuit board or network diagram.

NETWORK THEORY




LECTURE 8

SECTION-D :NETWORK SYNTHESIS

FREQUENCY-GAIN RELATION

- Ideally, signals are amplified from DC to the highest AC frequency
- Practically, bandwidth is limited
- 741 family op-amp have a limit bandwidth of few KHz.
- Unity Gain frequency f_1 : the gain at unity
- Cutoff frequency f_c : the gain drop by 3dB from dc gain G_d

$$\text{GB Product : } f_1 = G_d f_c$$

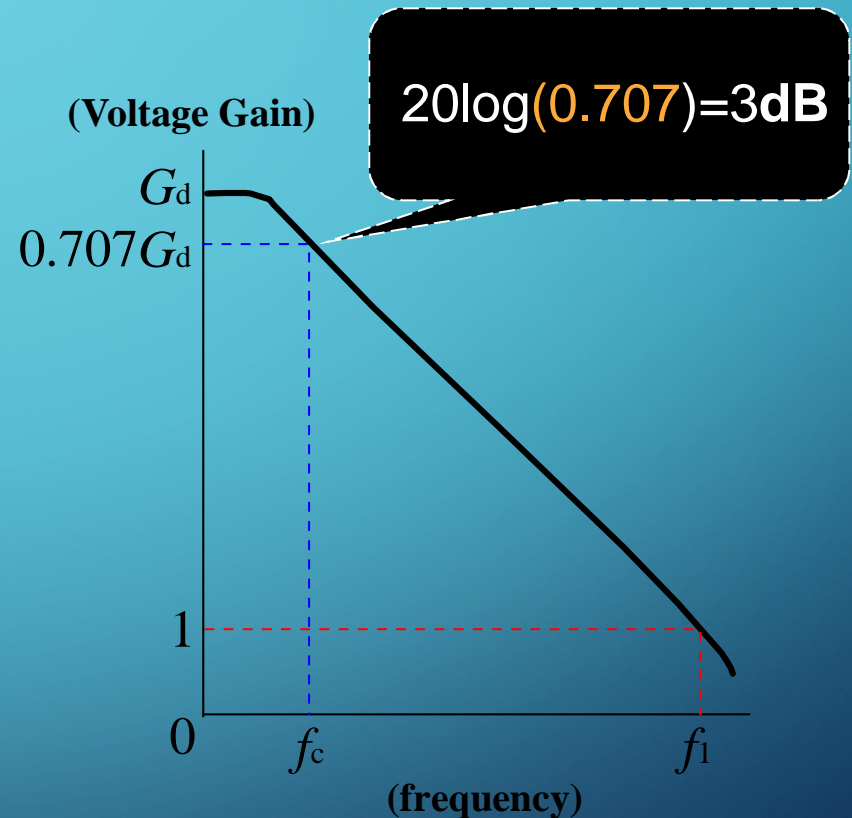

GB PRODUCT

Example: Determine the cutoff frequency of an op-amp having a unit gain frequency $f_1 = 10 \text{ MHz}$ and voltage differential gain $G_d = 20 \text{ V/mV}$

Sol:

Since $f_1 = 10 \text{ MHz}$


By using GB production equation

$$f_1 = G_d f_c$$

$$f_c = f_1 / G_d = 10 \text{ MHz} / 20 \text{ V/mV}$$



$$= 10 \times 10^6 / 20 \times 10^3$$

$$= 500 \text{ Hz}$$

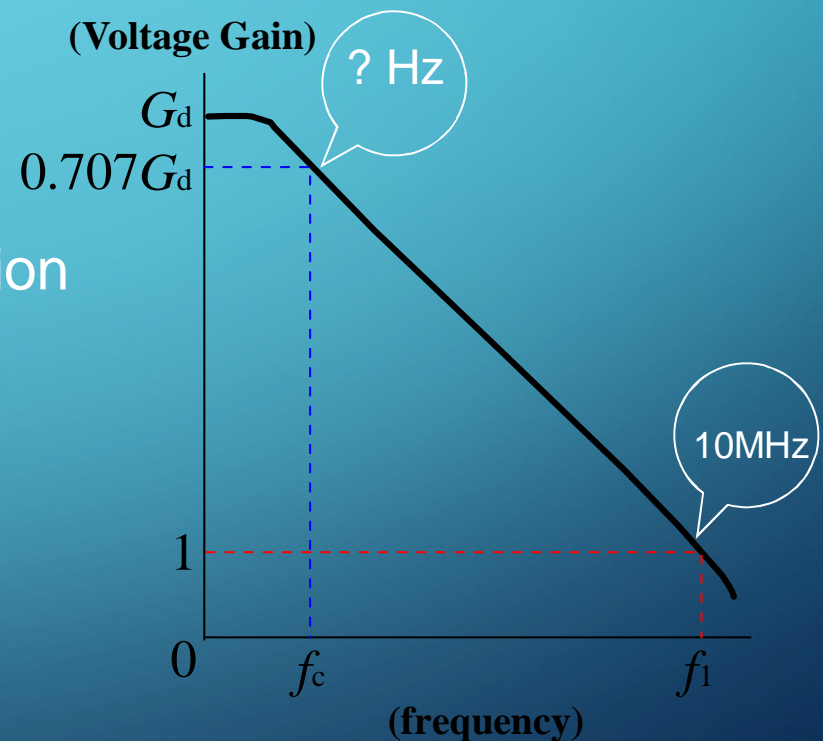

IDEAL VS PRACTICAL OP-AMP

	Ideal	Practical
Open Loop gain A	∞	10^5
Bandwidth BW	∞	10-100Hz
Input Impedance Z_{in}	∞	$>1\text{M}\Omega$
Output Impedance Z_{out}	$0\ \Omega$	10-100 Ω
Output Voltage V_{out}	Depends only on $V_d = (V_+ - V_-)$ Differential mode signal	Depends slightly on average input $V_c = (V_+ + V_-)/2$ Common-Mode signal
CMRR	∞	10-100dB

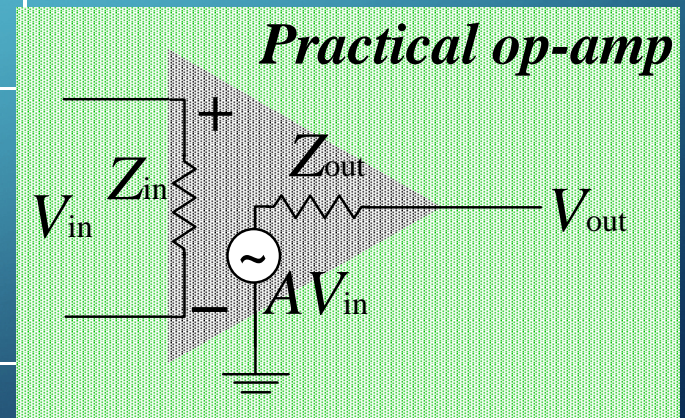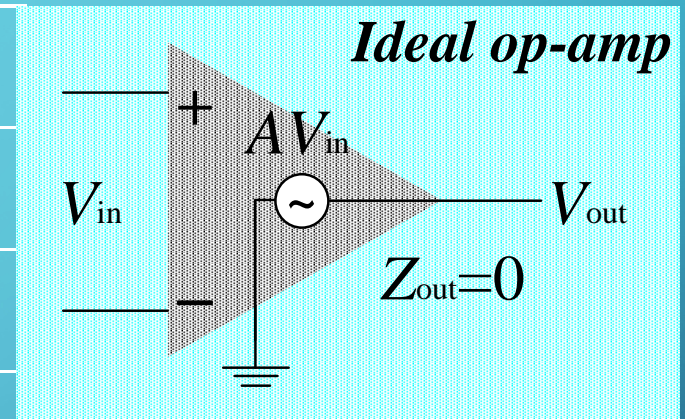

IDEAL OP-AMP APPLICATIONS

Analysis Method :

Two ideal Op-Amp Properties:

- (1) The voltage between V_+ and V_- is zero $V_+ = V_-$
- (2) The current into both V_+ and V_- terminals is zero

For ideal Op-Amp circuit:

- (1) Write the kirchhoff node equation at the noninverting terminal V_+
- (2) Write the kirchhoff node equation at the inverting terminal V_-
- (3) Set $V_+ = V_-$ and solve for the desired closed-loop gain


Noninverting Amplifier


(1) Kirchhoff node equation at V_+ yields, $V_+ = V_i$

(2) Kirchhoff node equation at V_- yields, $\frac{V_- - 0}{R_a} + \frac{V_- - V_o}{R_f} = 0$

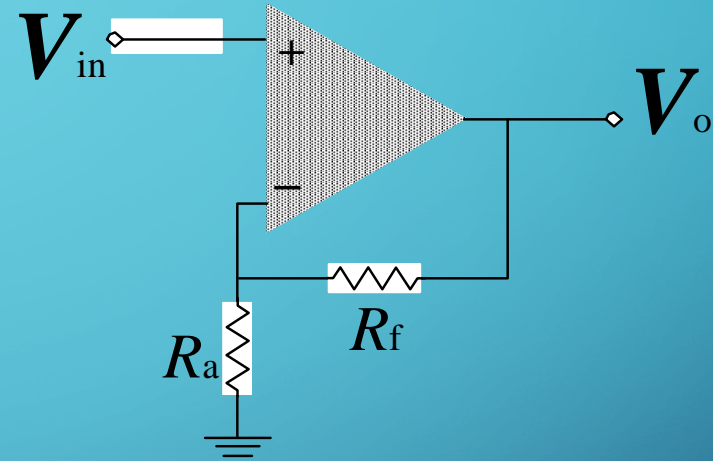(3) Setting $V_+ = V_-$ yields


$$\frac{V_i}{R_a} + \frac{V_i - V_o}{R_f} = 0 \quad \text{or} \quad \frac{V_o}{V_i} = 1 + \frac{R_f}{R_a}$$



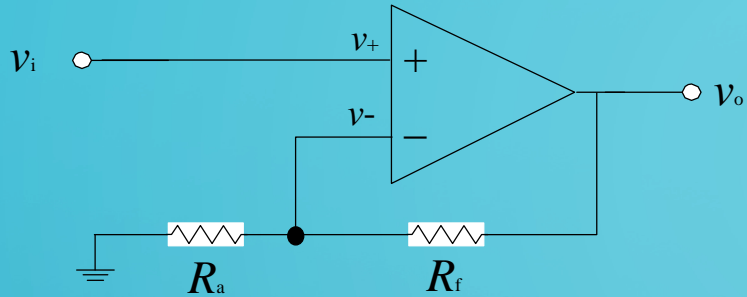


Noninverting amplifier
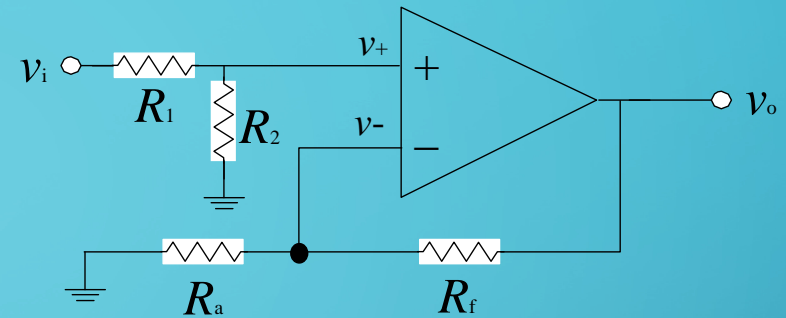
$$v_o = \left(1 + \frac{R_f}{R_a}\right)v_i$$




Noninverting input with voltage divider
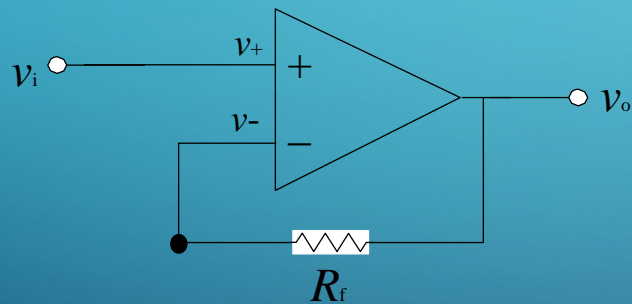
$$v_o = \left(1 + \frac{R_f}{R_a}\right)\left(\frac{R_2}{R_1 + R_2}\right)v_i$$



Voltage follower

$$v_o = v_i$$

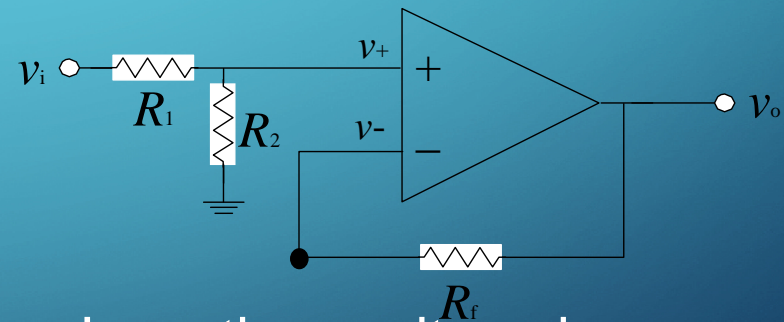

Less than unity gain

$$v_o = \frac{R_2}{R_1 + R_2}v_i$$