

CAO: Lecture 5
Combinational Logic Blocks:
Examples

Topics Covered

- Examples of Combinational circuits
- Decoder
- 2:4 Decoder
- 3:8 Decoder
- Combinational Circuit Design with Decoders
- Multiplexers

Examples of Combinational Circuits

- a) Decoders
- b) Encoders
- c) Multiplexers
- d) Demultiplexers


Decoder

- **Accepts a value and decodes it**
 - Output corresponds to value of n inputs
- **Consists of:**
 - Inputs (n)
 - Outputs (2^n , numbered from $0 \rightarrow 2^n - 1$)
 - Selectors / Enable (active high or active low)

The truth table of 2-to-4 Decoder

S_1	S_0	E	O_0	O_1	O_2	O_3
X	X	0	0	0	0	0
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1


2-to-4 Decoder

 


S_1	S_0	E	O_0	O_1	O_2	O_3
X	X	0	0	0	0	0
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1

(b)


2-to-4 Decoder

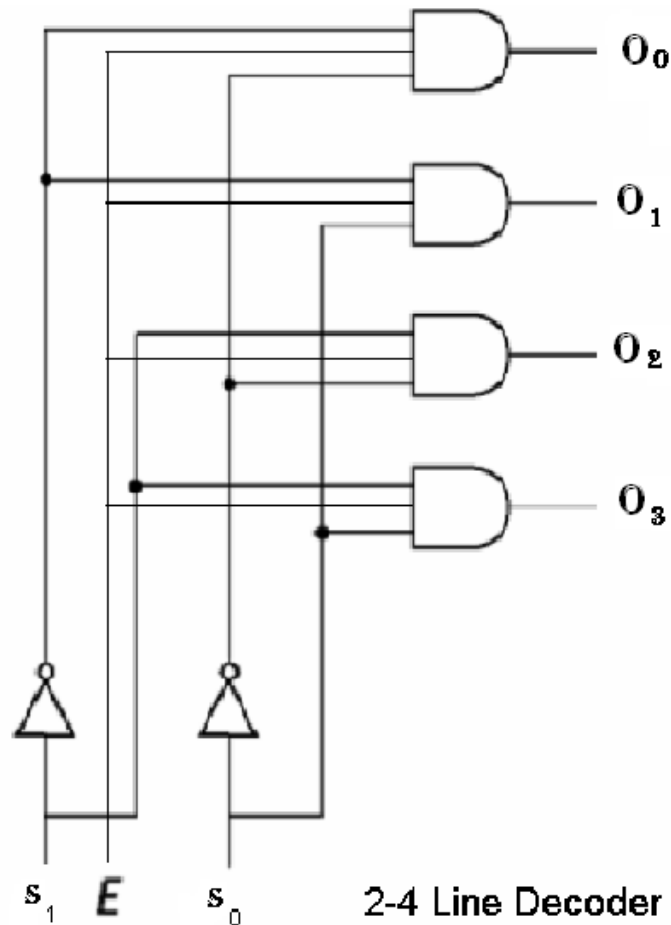

3-to-8 Decoder

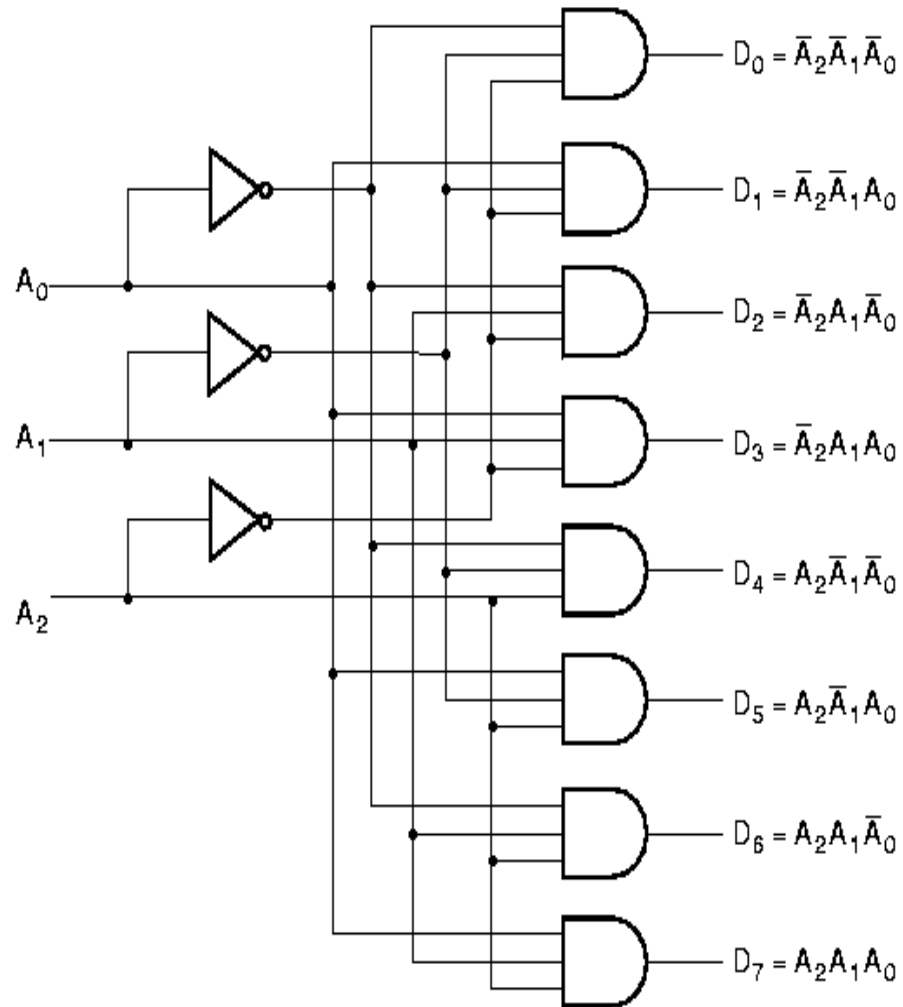


3-to-8 Decoder with Enable

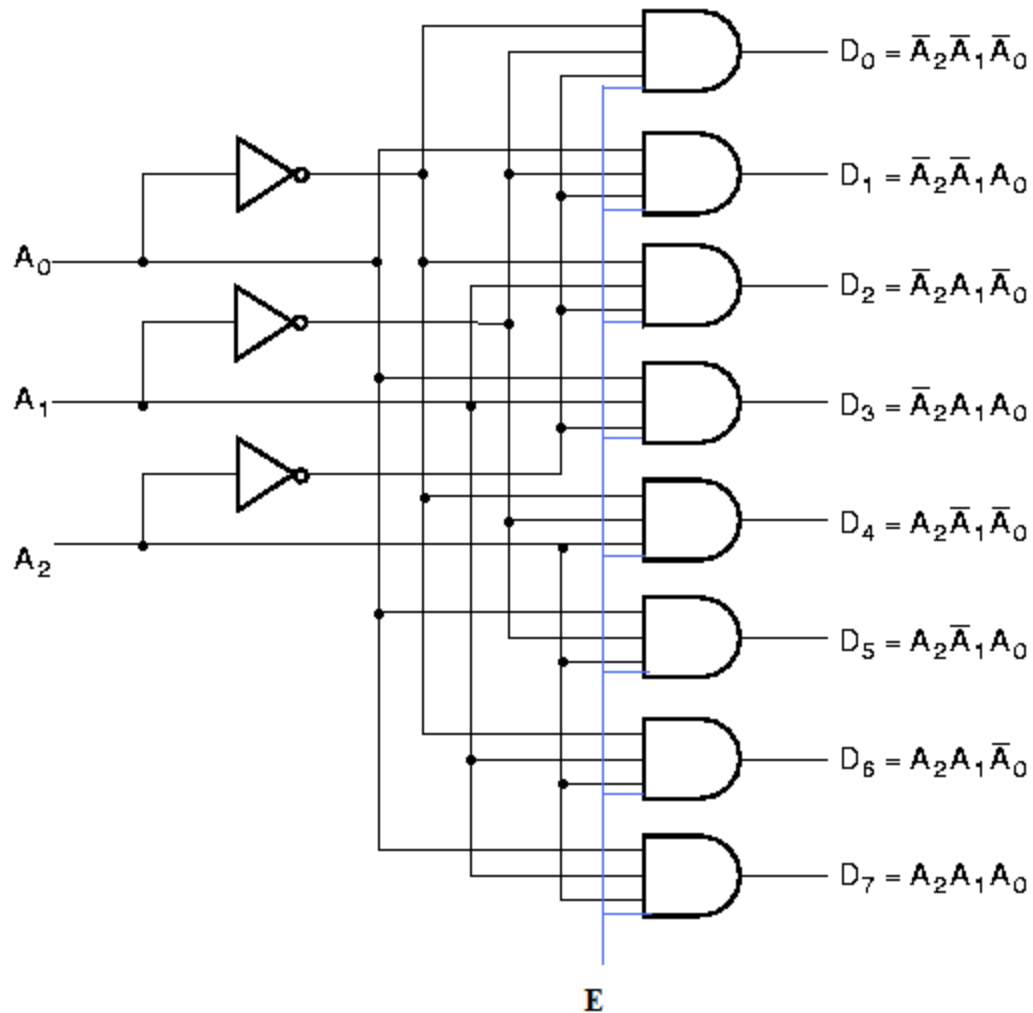

2-to-4 Decoder: NAND implementation

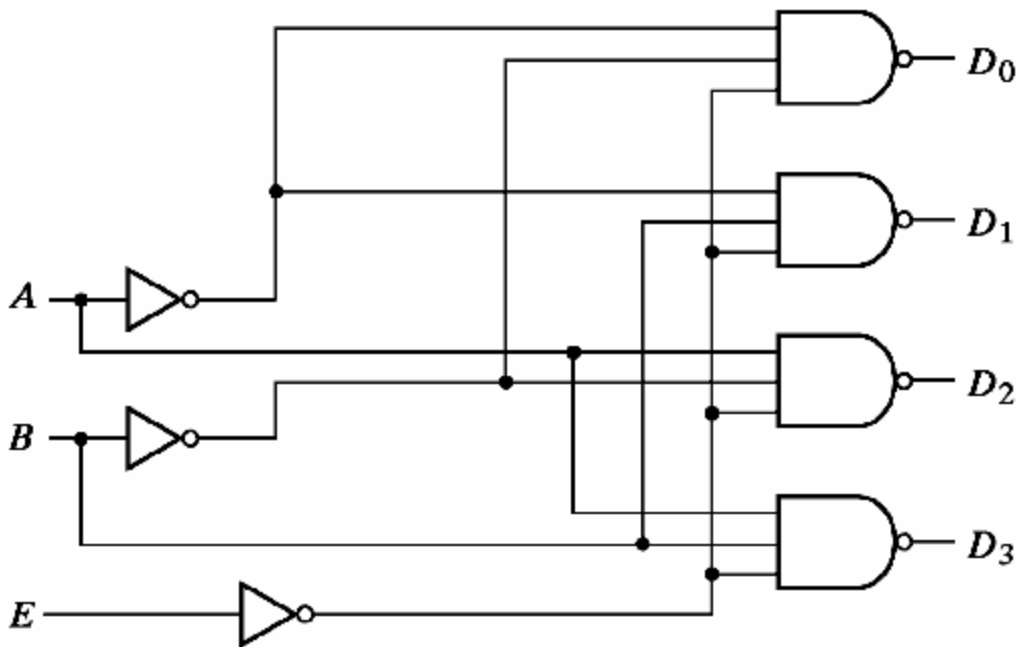Decoder is enabled when $E=0$ and an output is active if it is 0




(a) Logic diagram

E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

2-to-4-Line Decoder with Enable Input


2-4 Decoder with 2-input and Enable

 

Decoder Expansion


- Decoder expansion
 - Combine two or more small decoders with enable inputs to form a larger decoder
 - 3-to-8-line decoder constructed from two 2-to-4-line decoders
 - **The MSB is connected to the enable inputs**
 - **if $A_2=0$, upper is enabled; if $A_2=1$, lower is enabled.**

Decoder Expansion

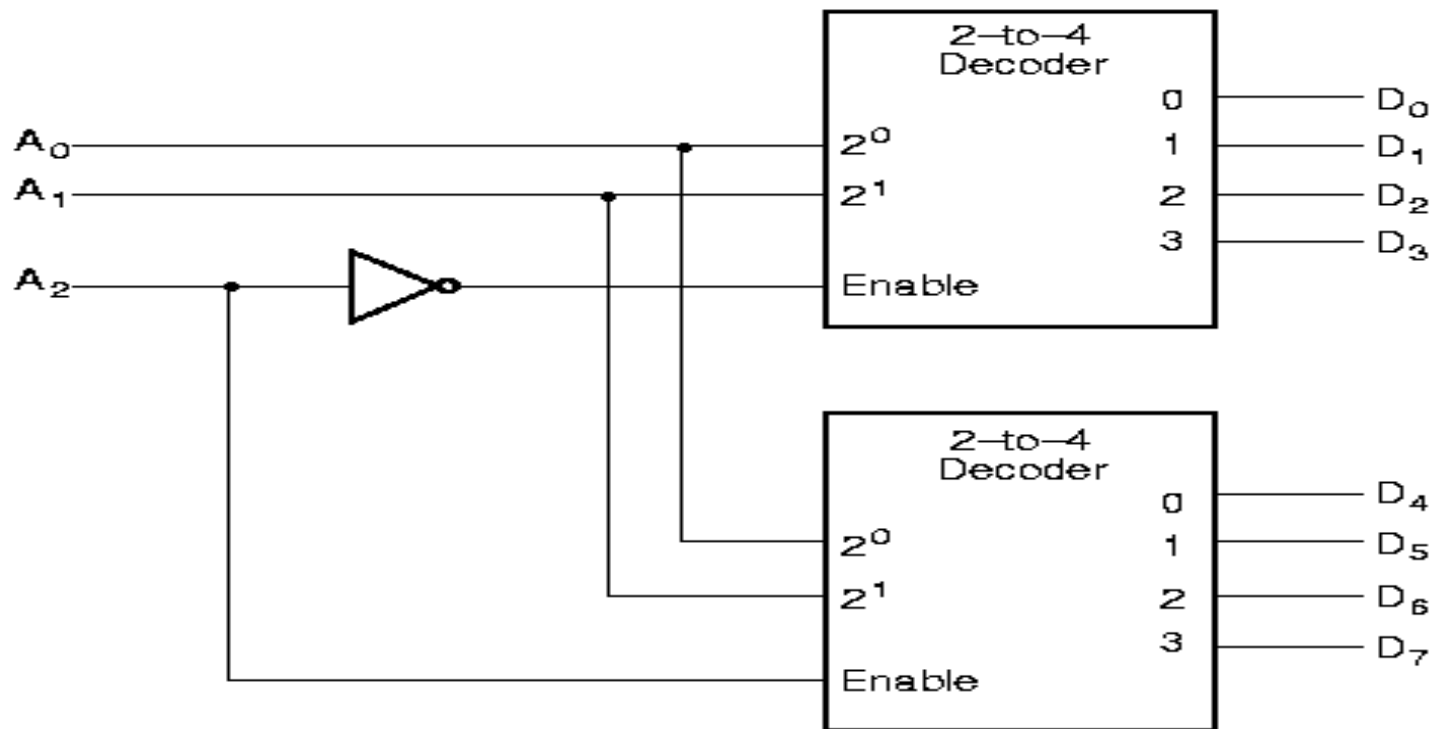

Combining two 2-4 decoders to form one 3-8 decoder using enable switch

A_2	A_1	A_0	D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

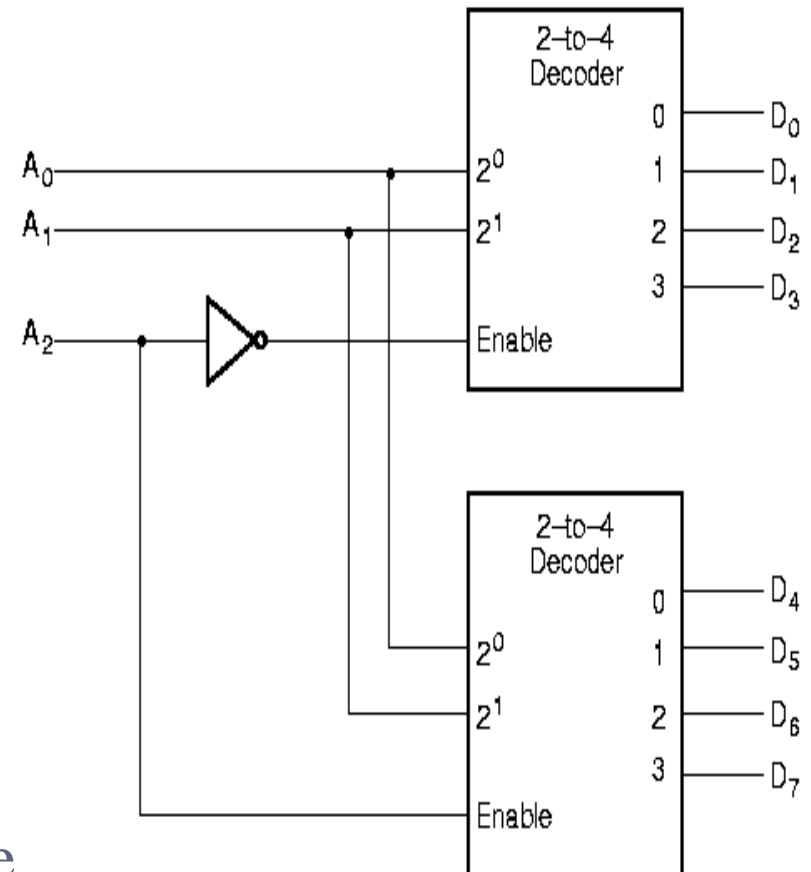


The highest bit is used for the enable

Combinational Circuit Design with Decoders

- Combinational circuit implementation with decoders
 - A decoder provide 2^n minterms of n input variables
 - Since any Boolean function can be expressed as a sum of minterms, one can use a decoder and external OR gates to implement any combinational function.


Combinational Circuit Design with Decoders

 Example Realize $F(X, Y, Z) = \Sigma(1, 4, 7)$ with a decoder:




Multiplexers

 - Select an input value with one or more select bits
- Use for transmitting data
- Allows for conditional transfer of data
- Sometimes called a mux
- EXAMPLE- 2:1 LINE MUX




(a) Logic diagram

 


(b) Block diagram

4-to-1-Line Multiplexer

 

Quadruple 2-to-1-Line Multiplexer

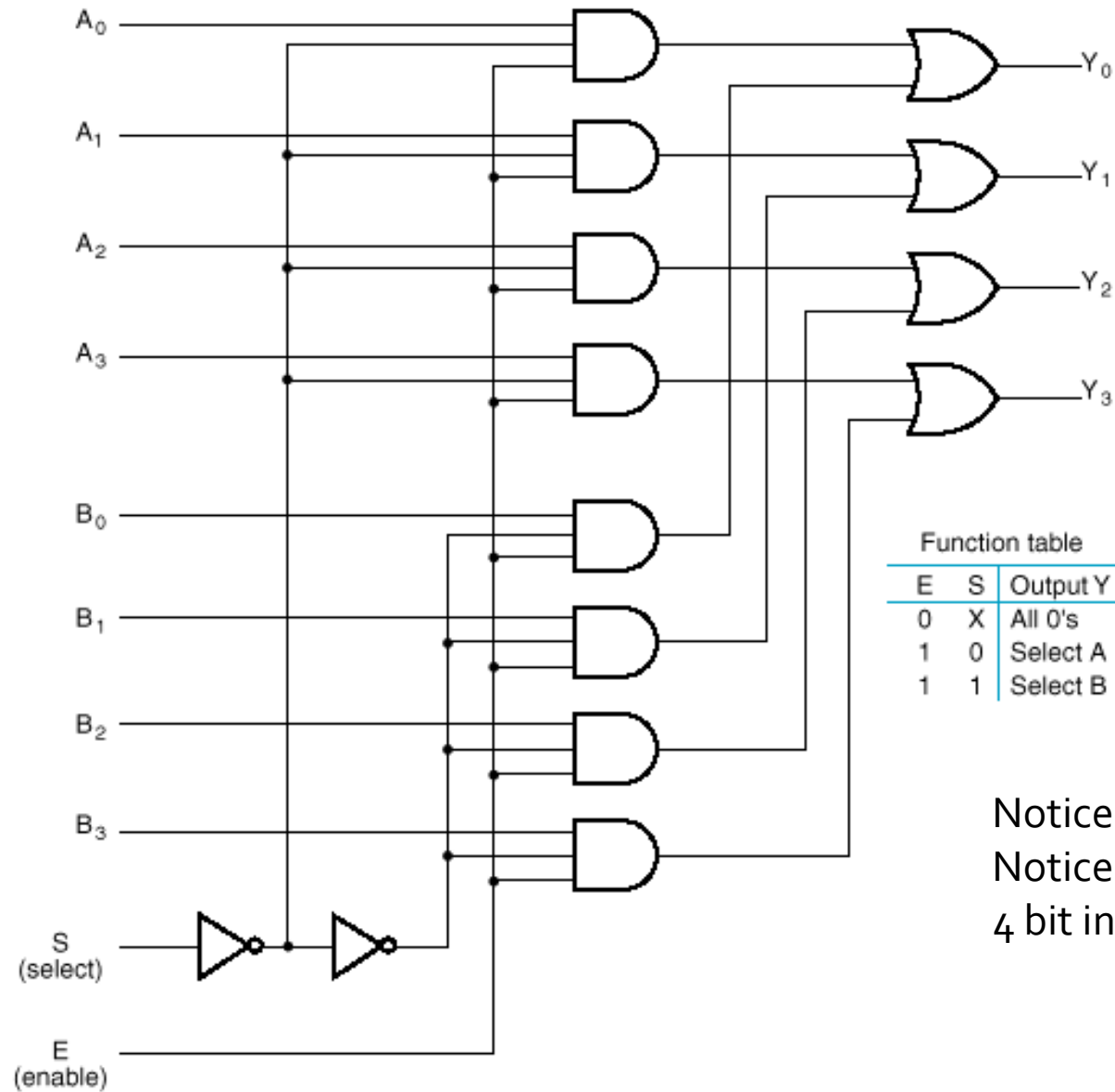


Multiplexer as combinational modules

- Connect input variables to select inputs of multiplexer ($n-1$ for n variables)
- Set data inputs to multiplexer equal to values of function for corresponding assignment of select variables
- Using a variable at data inputs reduces size of the multiplexer

x	y	z	F	
0	0	0	0	
0	0	1	1	$F = z$
0	1	0	1	
0	1	1	0	$F = z'$
1	0	0	0	
1	0	1	0	$F = 0$
1	1	0	1	
1	1	1	1	$F = 1$

(a) Truth table

 

(b) Multiplexer implementation

Fig. 4-27 Implementing a Boolean Function with a Multiplexer

Implementing a Four- Input Function with a Multiplexer

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = \bar{D}$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

