

CAO: Lecture 6
Sequential logic blocks
(Latches, Flip-Flops,
Registers, Counters)

Topics Covered

- Overview
- Sequential Circuits
- Cross-coupled Inverters
- S-R Latch with NORs
- S-R Latch with NANDs
- D Latch
- Symbols for Latches


Overview

- Circuits require memory to store intermediate data
- Sequential circuits use a periodic signal to determine when to store values.
 - A clock signal can determine storage times
 - Clock signals are periodic
- Single bit storage element is a flip flop
- A basic type of flip flop is a latch
- Latches are made from logic gates
 - NAND, NOR, AND, OR, Inverter

The story so far ...


- Logical operations which respond to combinations of inputs to produce an output.
 - Call these combinational logic circuits.
- For example, can add two numbers. But:
 - No way of adding two numbers, then adding a third (a sequential operation);
 - No way of remembering or storing information after inputs have been removed.
- To handle this, we need sequential logic capable of storing intermediate (and final) results.

Sequential Circuits

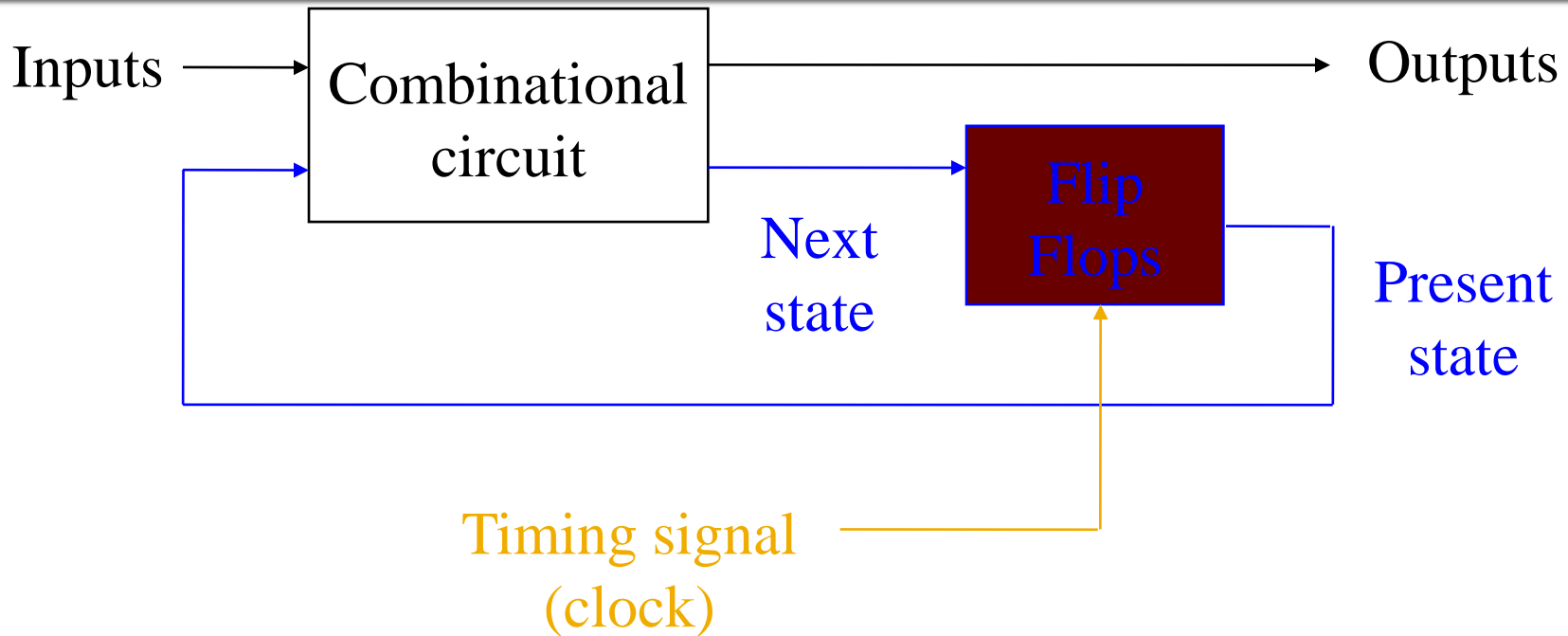

Clock

a periodic external event (input)

 


Clock


synchronizes when current state changes happen
keeps system well-behaved
makes it easier to design and build large systems

Cross-coupled Inverters

- A stable value can be stored at inverter outputs

 


State 1

 

State 2

S-R Latch with NORs

R (reset)

 


S (set)

S	R	Q	Q'	
1	1	0	0	Undefined
1	0	1	0	Set
0	1	0	1	Reset
0	0	0	1	Stable
		1	0	

- S-R latch made from **cross-coupled** NORs
- If $Q = 1$, set state
- If $Q = 0$, reset state
- Usually $S=0$ and $R=0$
- $S=1$ and $R=1$ generates unpredictable results


S-R Latch with NANDs

 

S	R	Q	Q'	
0	0	1	1	Disallowed
0	1	1	0	Set
1	0	0	1	Reset
1	1	0	1	Store
		1	0	

- Latch made from **cross-coupled NANDs**
- Sometimes called **S'-R'** latch
- Usually **S=1** and **R=1**
- **S=0** and **R=0** generates unpredictable results


S-R Latches

 

(a) Logic diagram

S	R	Q	\bar{Q}	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

(b) Function table

 


(a) Logic diagram

S	R	Q	\bar{Q}	
0	1	1	0	Set state
1	1	1	0	
1	0	0	1	Reset state
1	1	0	1	
0	0	1	1	Undefined

(b) Function table

S-R Latch with control input

 

(a) Logic diagram

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; set state
1	1	1	Indeterminate

(b) Function table


Fig. 5-5 SR Latch with Control Input

- Occasionally, desirable to avoid latch changes
- **C = 0** disables all latch state changes
- Control signal **enables** data change when **C = 1**
- Right side of circuit same as ordinary S-R latch.

NOR S-R Latch with Control Input


Latch is **level-sensitive**, in regards to C

Only stores data if $C' = 0$

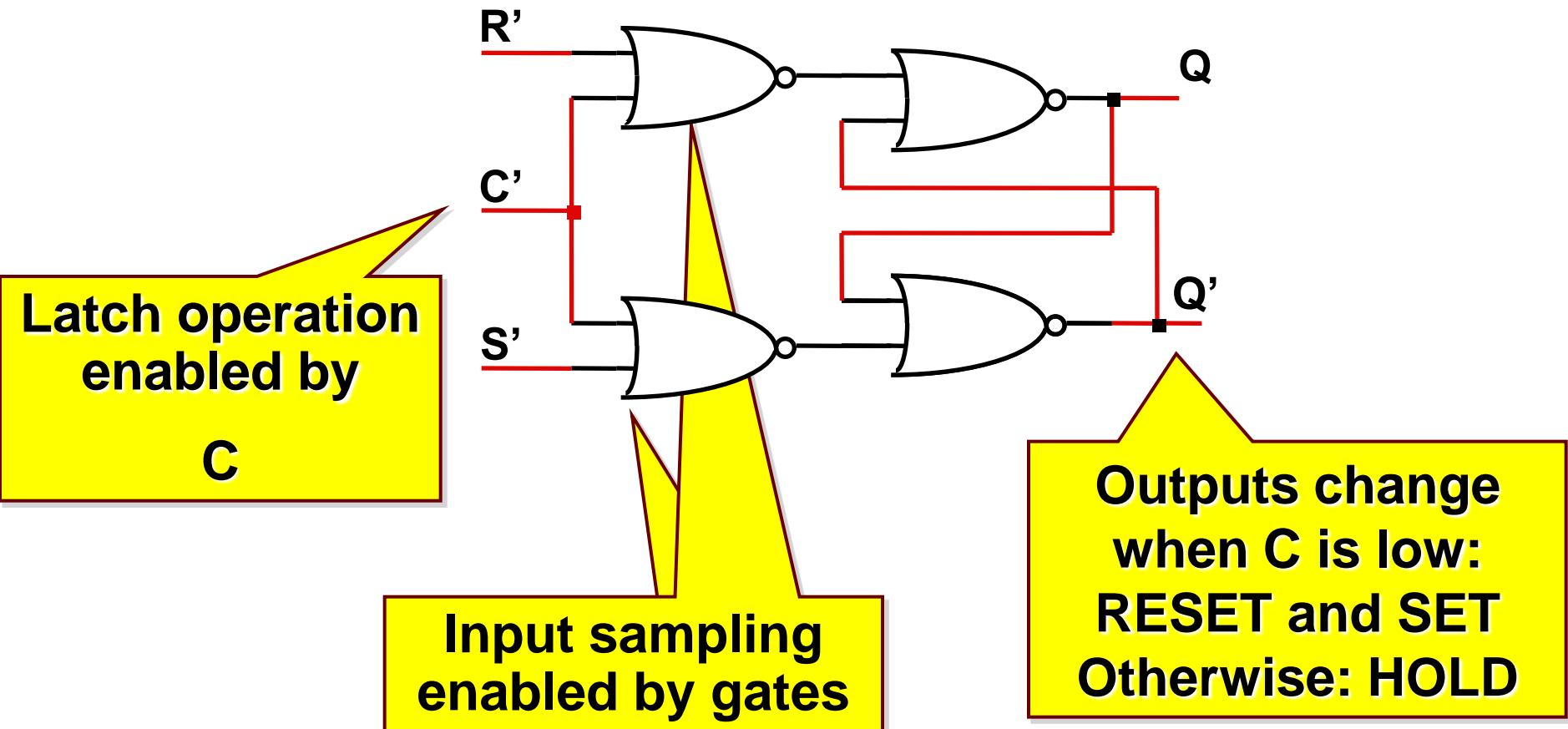

D Latch

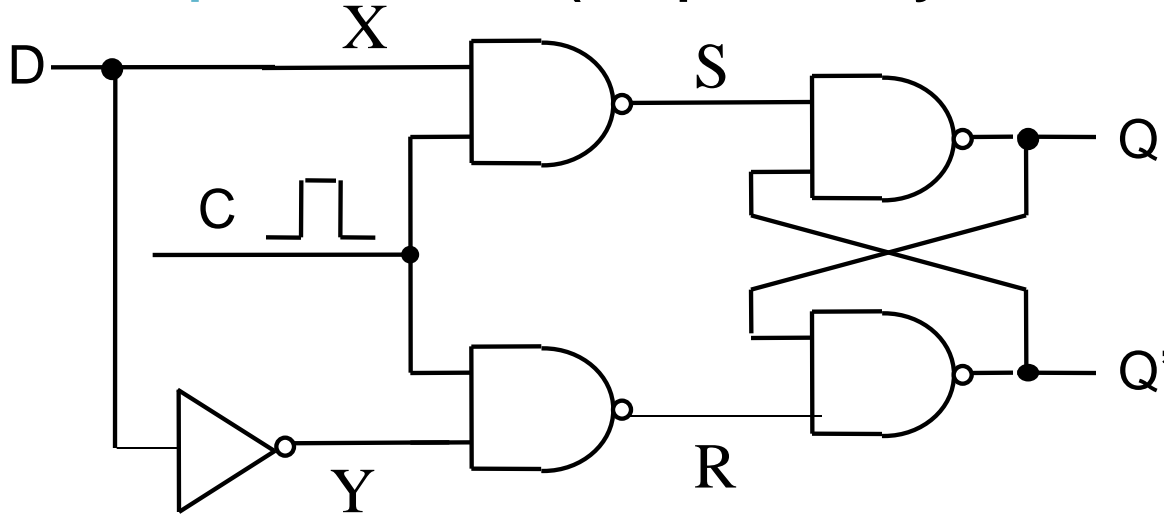
Q_0 indicates the **previous state** (the previously stored value)



D	C	Q	Q'
0	1	0	1
1	1	1	0
X	0	Q_0	Q_0'

X	Y	C	Q	Q'	
0	0	1	Q_0	Q_0'	Store
0	1	1	0	1	Reset
1	0	1	1	0	Set
1	1	1	1	1	Disallowed
X	X	0	Q_0	Q_0'	Store

D Latch

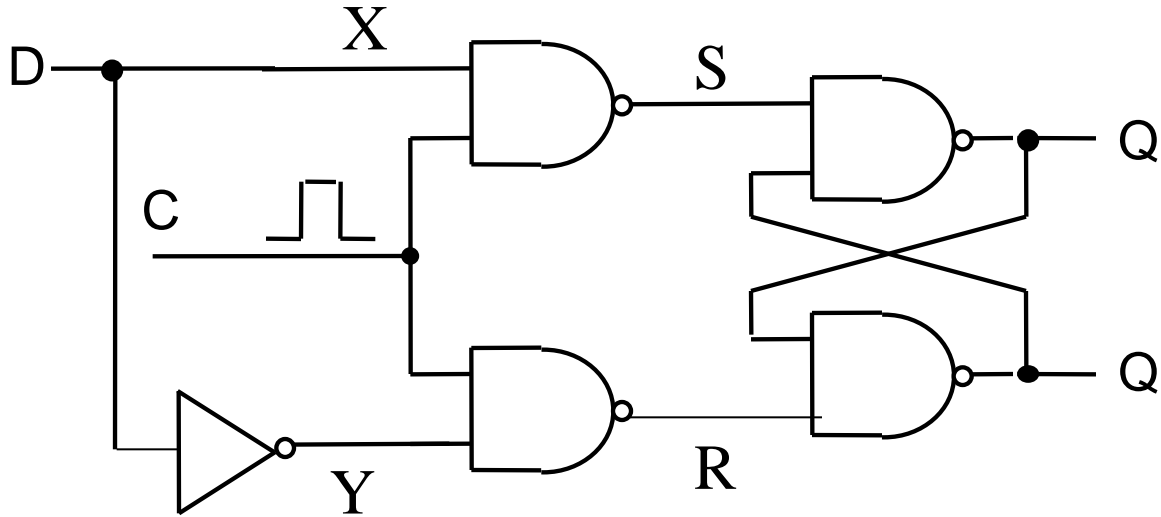

D	C	Q	Q'
0	1	0	1
1	1	1	0
X	0	Q_0	Q_0'

- Input value **D** is passed to output **Q** when **C** is high
- Input value **D** is ignored when **C** is low

Symbols for Latches

 


Fig. 5-7 Graphic Symbols for Latches

- **SR latch is based on NOR gates**
- **S'R' latch based on NAND gates**
- **D latch can be based on either.**
- **D latch sometimes called transparent latch**

Summary

- Latches are based on combinational gates (e.g. NAND, NOR)
- Latches store data even after data input has been removed
- S-R latches operate like cross-coupled inverters with control inputs (S = set, R = reset)
- With additional gates, an S-R latch can be converted to a D latch (D stands for data)
- D latch is simple to understand conceptually
 - When $C = 1$, data input D stored in latch and output as Q
 - When $C = 0$, data input D ignored and previous latch value output at Q
- Next time: more storage elements!