

Analog Communication Systems EC-413-F



Lecture no 2

Topics to be covered

- **FM modulation**
- **VCO**

Comparison Between FM & AM

Ans.

Table 1

| 5. No. | AM Broadcasting | FM Broadcasting |
|--------|--|--|
| 1. | It requires smaller transmission bandwidth | It requires larger bandwidth. |
| 2. | It can be operated in low, medium and high frequency bands. | It needs to be operated in very high and high frequency bands. |
| 3. | It has wider coverage. | Its range is restricted to 50 km. |
| 4. | The demodulation is simple. | The process of demodulation is complex. |
| 5. | The stereophonic transmission is not possible. | In this, stereophonic transmission is possible. |
| 6. | The system has poor noise performance. | It has an improved noise performance. |
| 7. | The AM signal reception does not have any threshold in the useful range of signal noise ratio (SNR). | The FM signal reception exhibits a three the useful range of signal noise ratio (SM, SNR value should be higher than the ????) |

FM generation using VCO

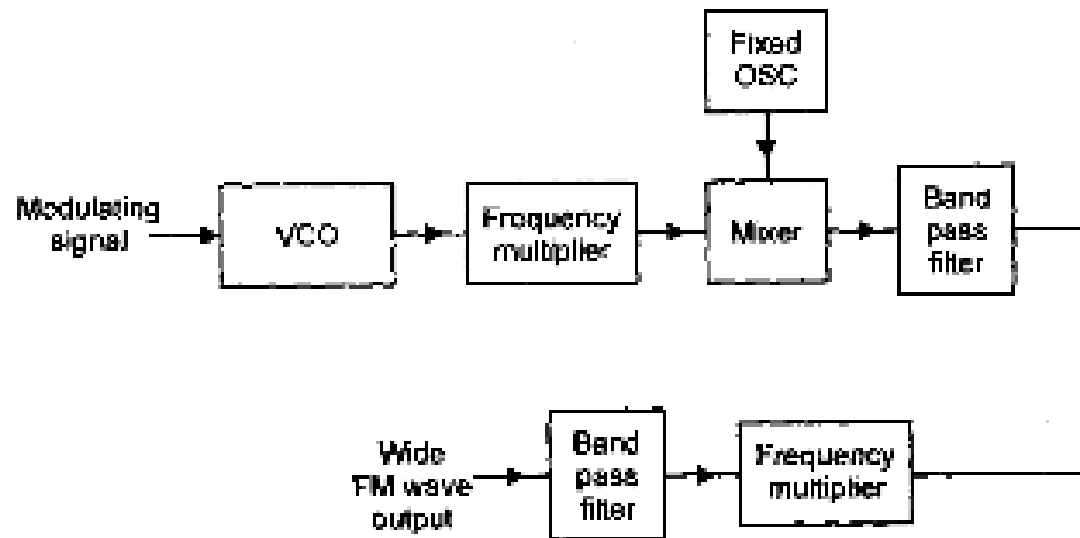


Fig. 2

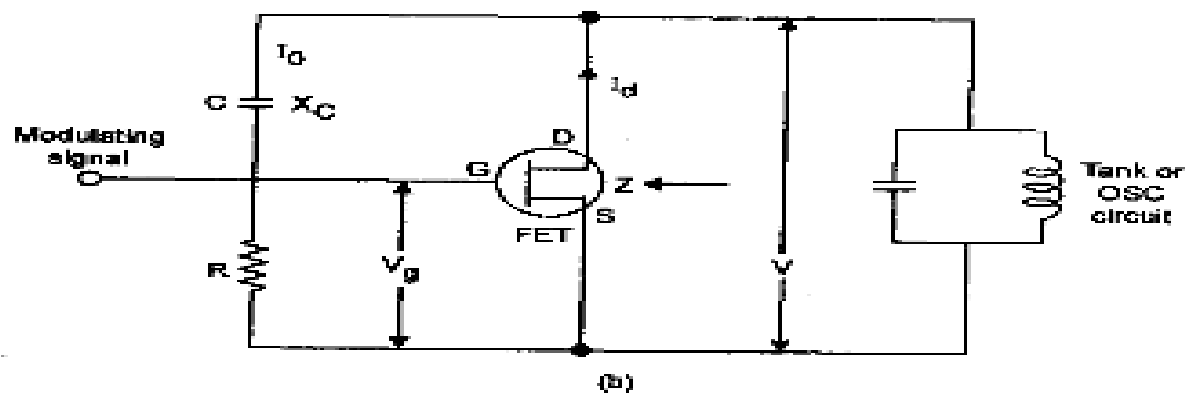
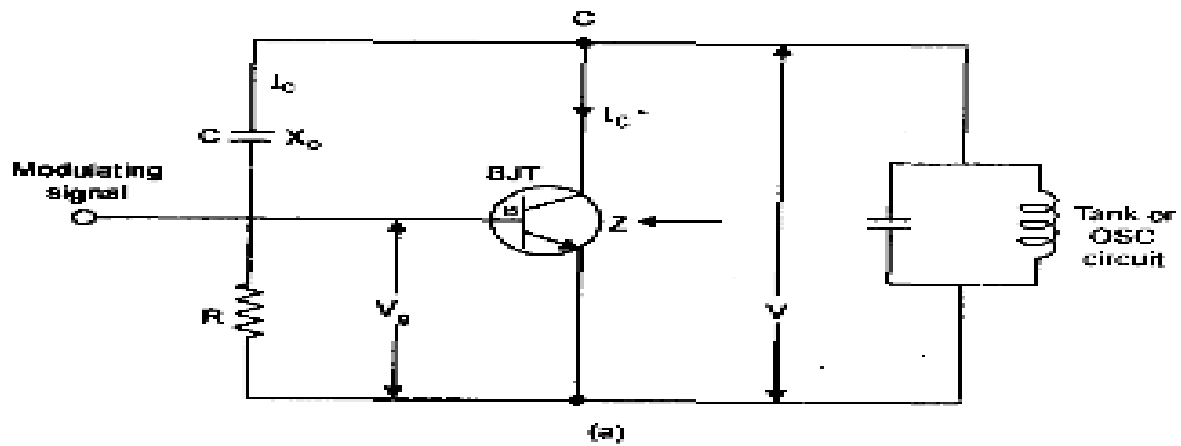


Fig. 4

Varactor Modulator

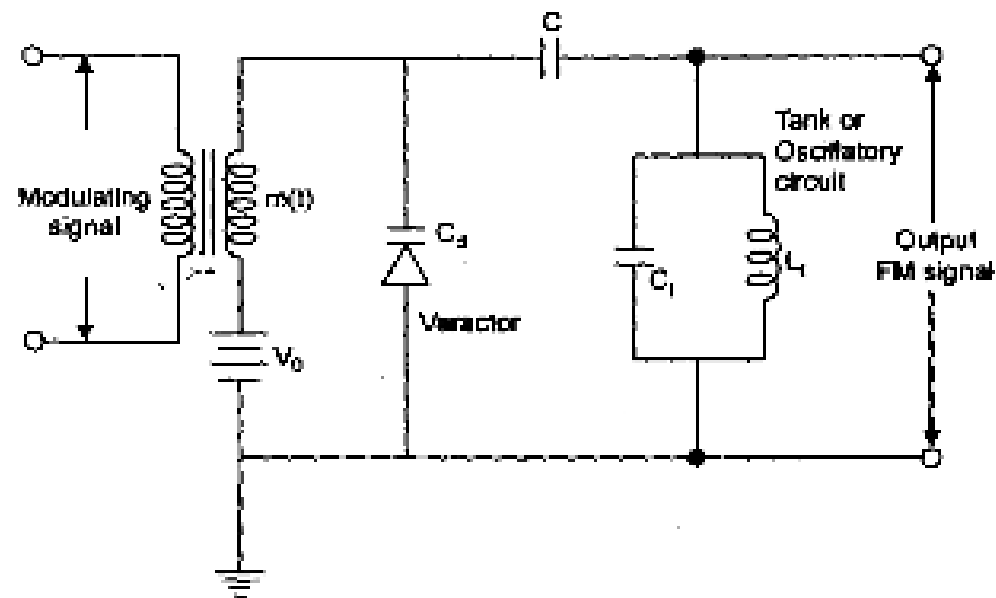


Fig. 5

(b) Hence the frequency of oscillation is given by

$$f = \frac{1}{2\pi\sqrt{L_1(C_1 + C_d)}}$$

Indirect-Armstrong Method

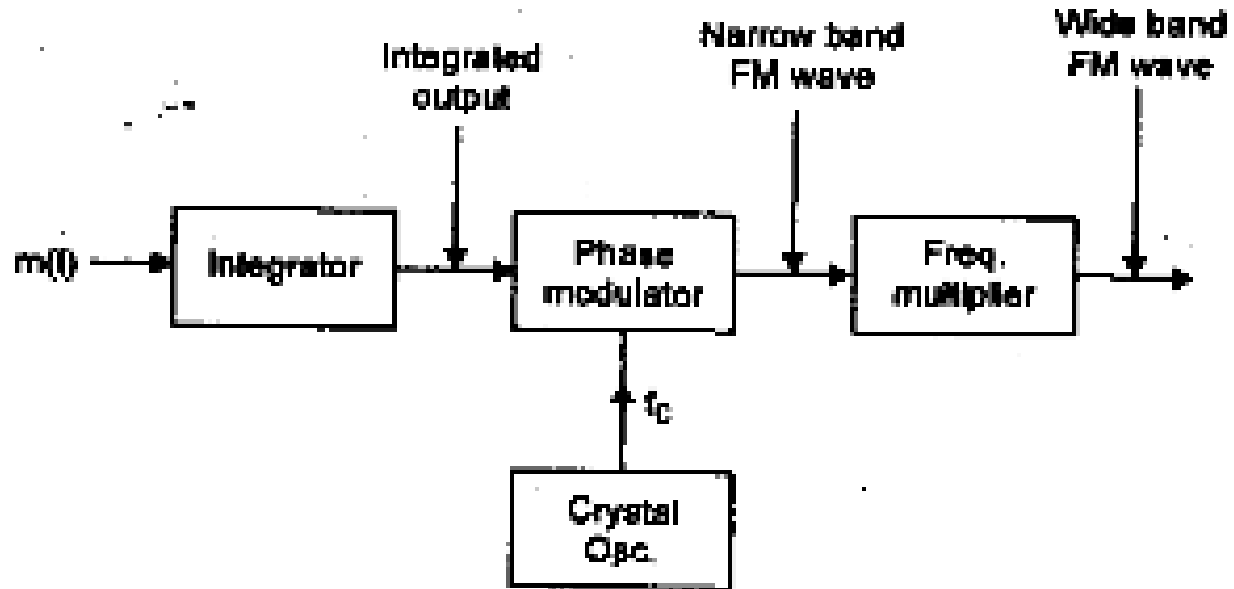


Fig. 9


$$e_o(t) = E_c \cos [2\pi f_c t + \beta_1 \sin (2\pi f_m t)]$$

where

$$e(t) = E_c \cos [2\pi n f_c t + \beta_2 \sin 2\pi f_m t]$$


$$\beta_2 = n \cdot \beta_1$$

FM receiver

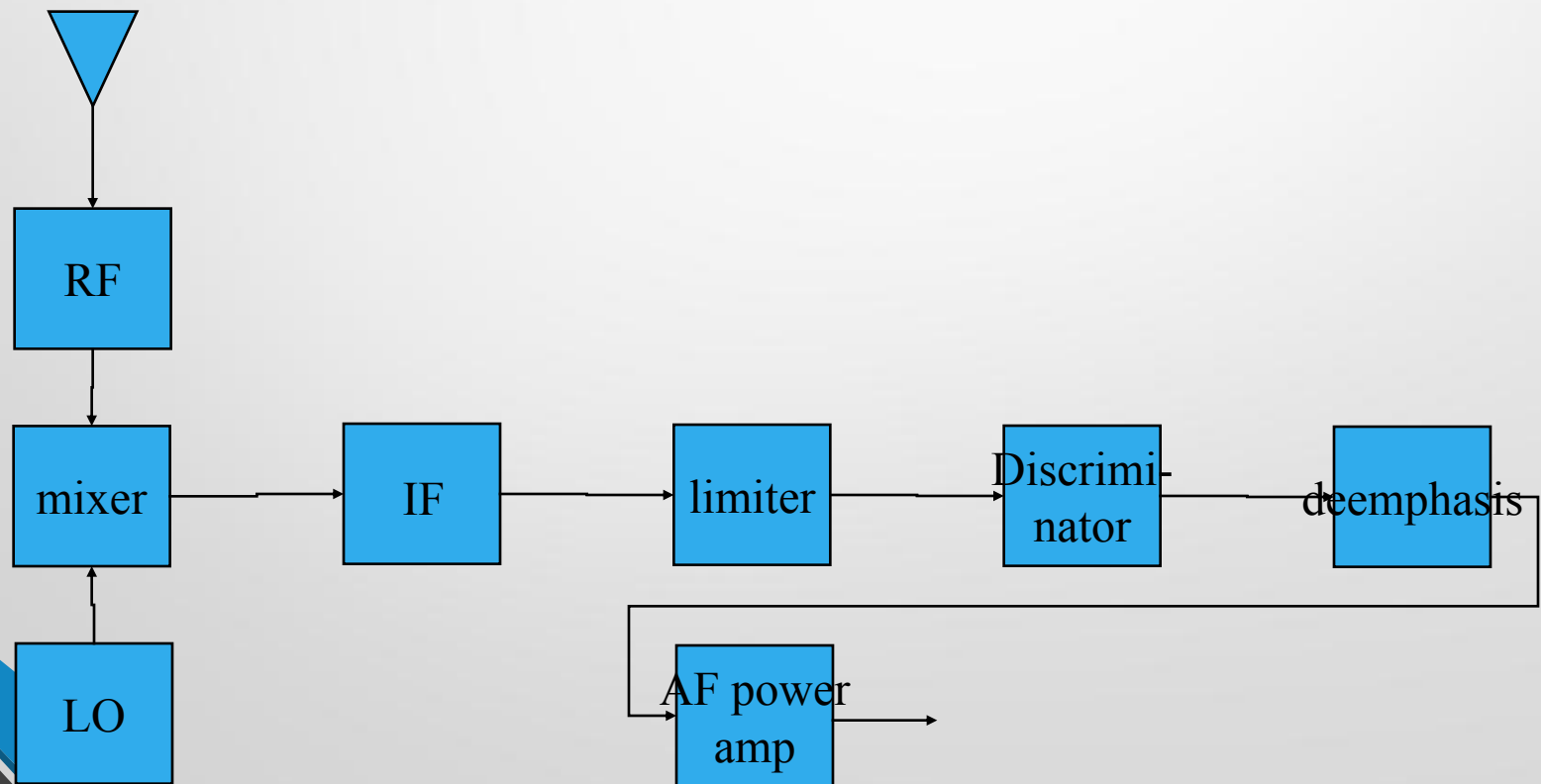

Frequency demodulation

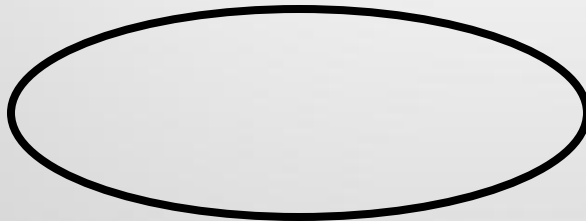- Remember that message in an FM signal is in the instantaneous frequency or equivalently derivative of carrier angle




Do envelope detection on $s'(t)$

Receiver components:RF amplifier

- AM may skip RF amp but FM requires it
- FM receivers are called upon to work with weak signals ($\sim 1\mu\text{V}$ or less as compared to $30\mu\text{V}$ for AM)
- An RF section is needed to bring up the signal to at least 10 to $20\mu\text{V}$ before mixing

Limiter

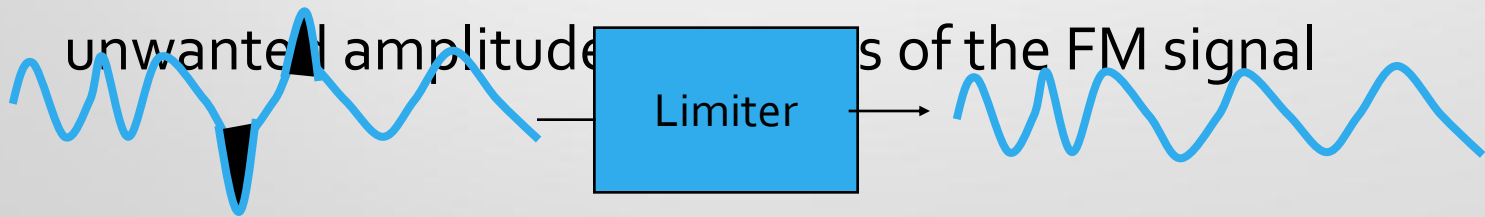- A limiter is a circuit whose output is constant for all input amplitudes above a threshold
- Limiter's function in an FM receiver is to remove unwanted amplitude variations of the FM signal



Limiting and sensitivity

- A limiter needs about 1V of signal, called *quieting* or *threshold* voltage, to begin limiting
- When enough signal arrives at the receiver to start limiting action, the set quiets, i.e. background noise disappears
- Sensitivity is the min. RF signal to produce a specified level of quieting, normally

Sensitivity example

- An FM receiver provides a voltage gain of 200,000 (106dB) prior to its limiter. The limiter's quieting voltage is 200 mV. What is the receiver's sensitivity?
- What we are really asking is the required signal at RF's input to produce 200 mV at the output



$$200 \text{ mV} / 200,000 = 1 \mu\text{V} \rightarrow \text{sensitivity}$$


Discriminator

$$f_i(t) = f_c + k_f m(t)$$


- The heart of FM is this relationship

f_{carrier} is at the IF frequency
Of 10.7 MHz

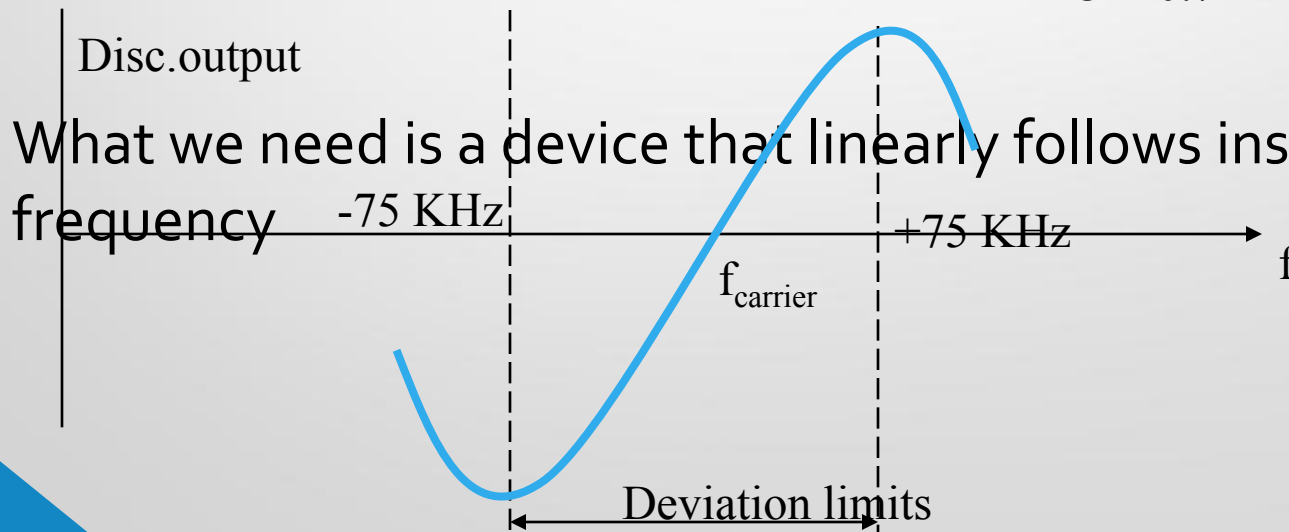- What we need is a device that linearly follows inst.




Examples of discriminators

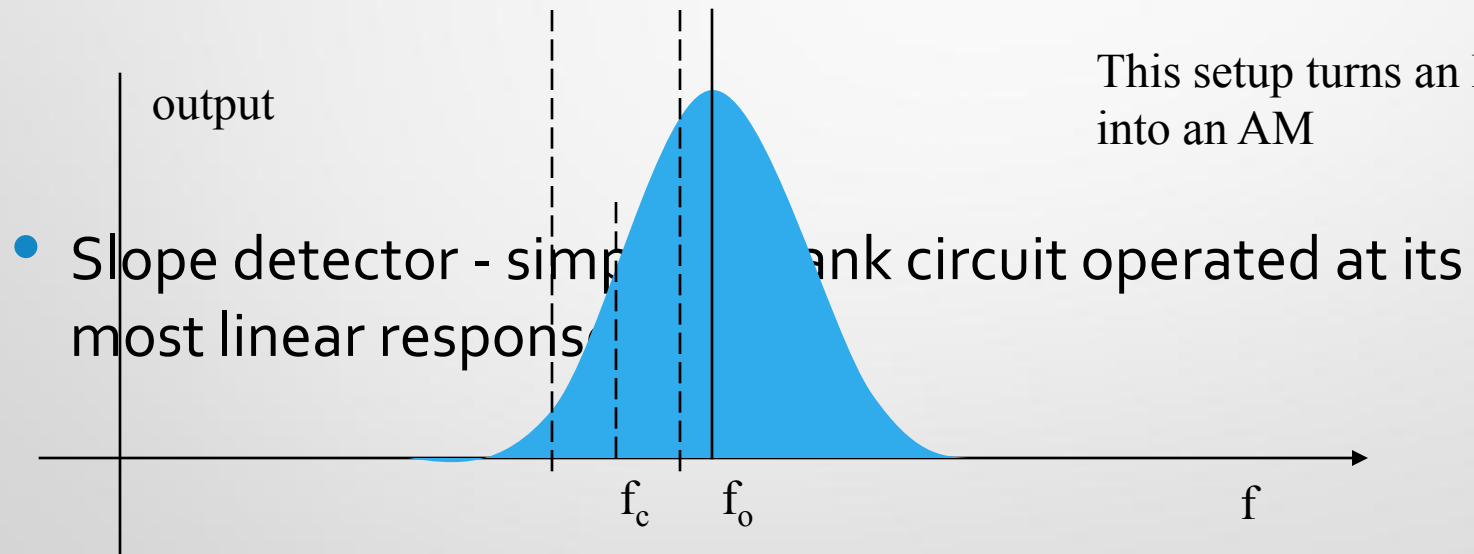


This setup turns an FM signal into an AM

Foster-Seeley Discriminator

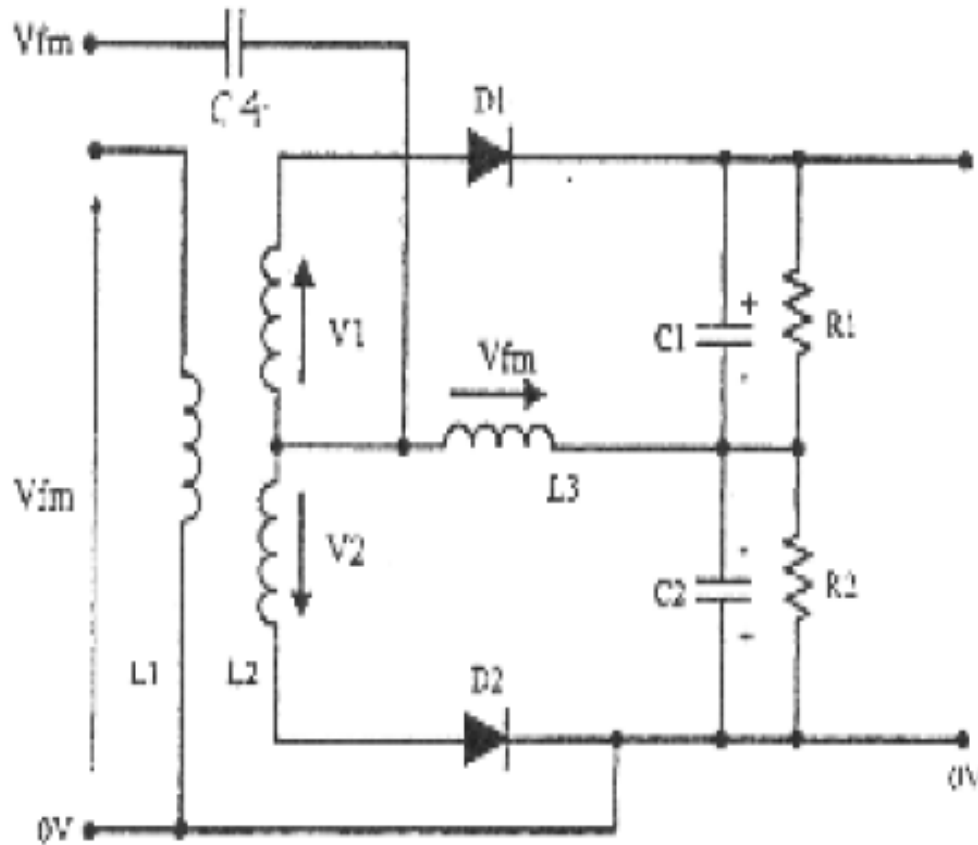


Circuit diagram

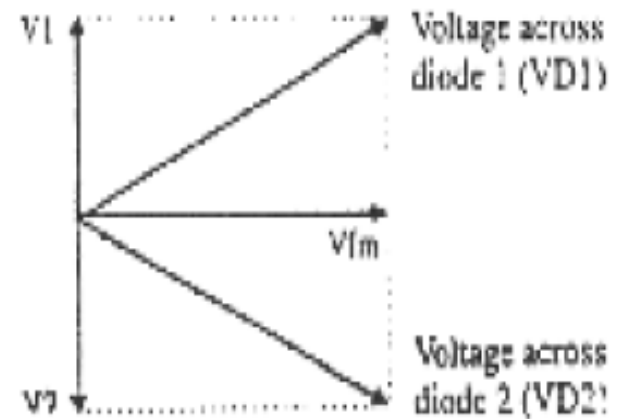

Phasor diagram

Phase-Locked Loop

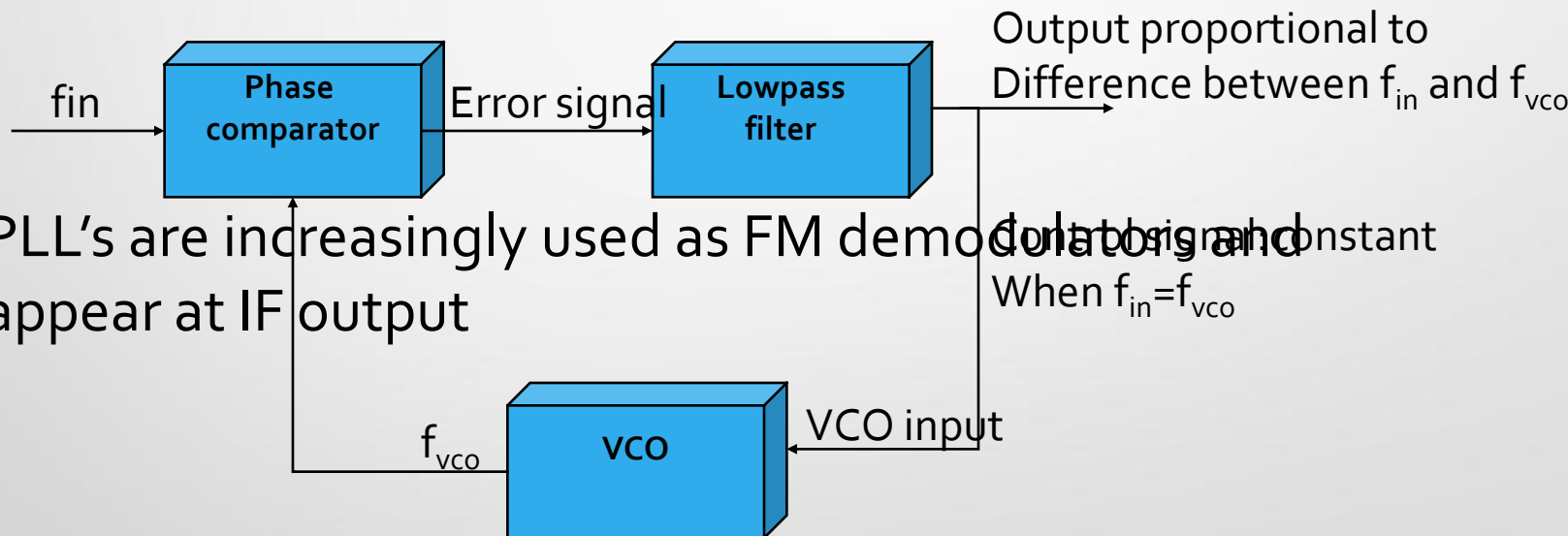

- PLL's are increasingly used as FM demodulators and appear at IF output

PLL states


- Free-running
 - If the input and VCO frequency are too far apart, PLL free-runs
- Capture
 - Once VCO closes in on the input frequency, PLL is said to be in the tracking or capture mode
- Locked or tracking
 - Can stay locked over a wider range than was necessary for capture

PLL example


- VCO free-runs at 10 MHz. VCO does not change frequency until the input is within 50 KHz.
- In the tracking mode, VCO follows the input to ± 200 KHz of 10 MHz before losing lock. What is the lock and capture range?
 - Capture range = $2 \times 50 \text{ KHz} = 100 \text{ KHz}$
 - Lock range = $2 \times 200 \text{ KHz} = 400 \text{ KHz}$

Advantages of PLL

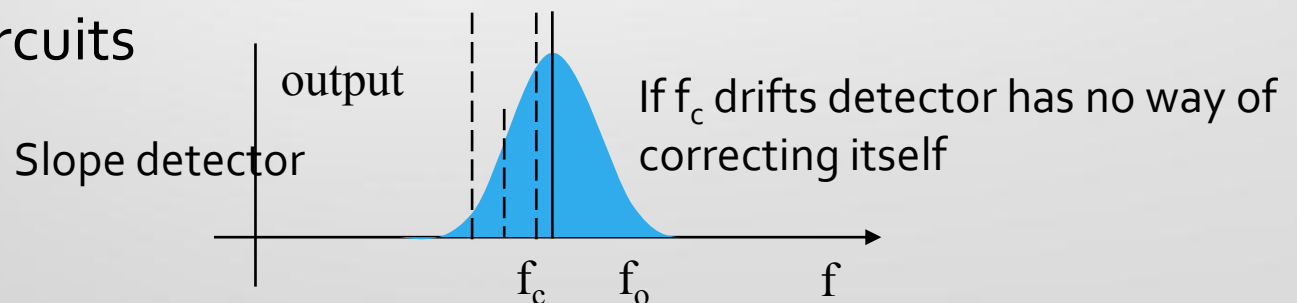- If there is a carrier center frequency or LO frequency drift, conventional detectors will be untuned
- PLL, on the other hand, can correct itself. PLL's need no tuned circuits



Zero crossing detector

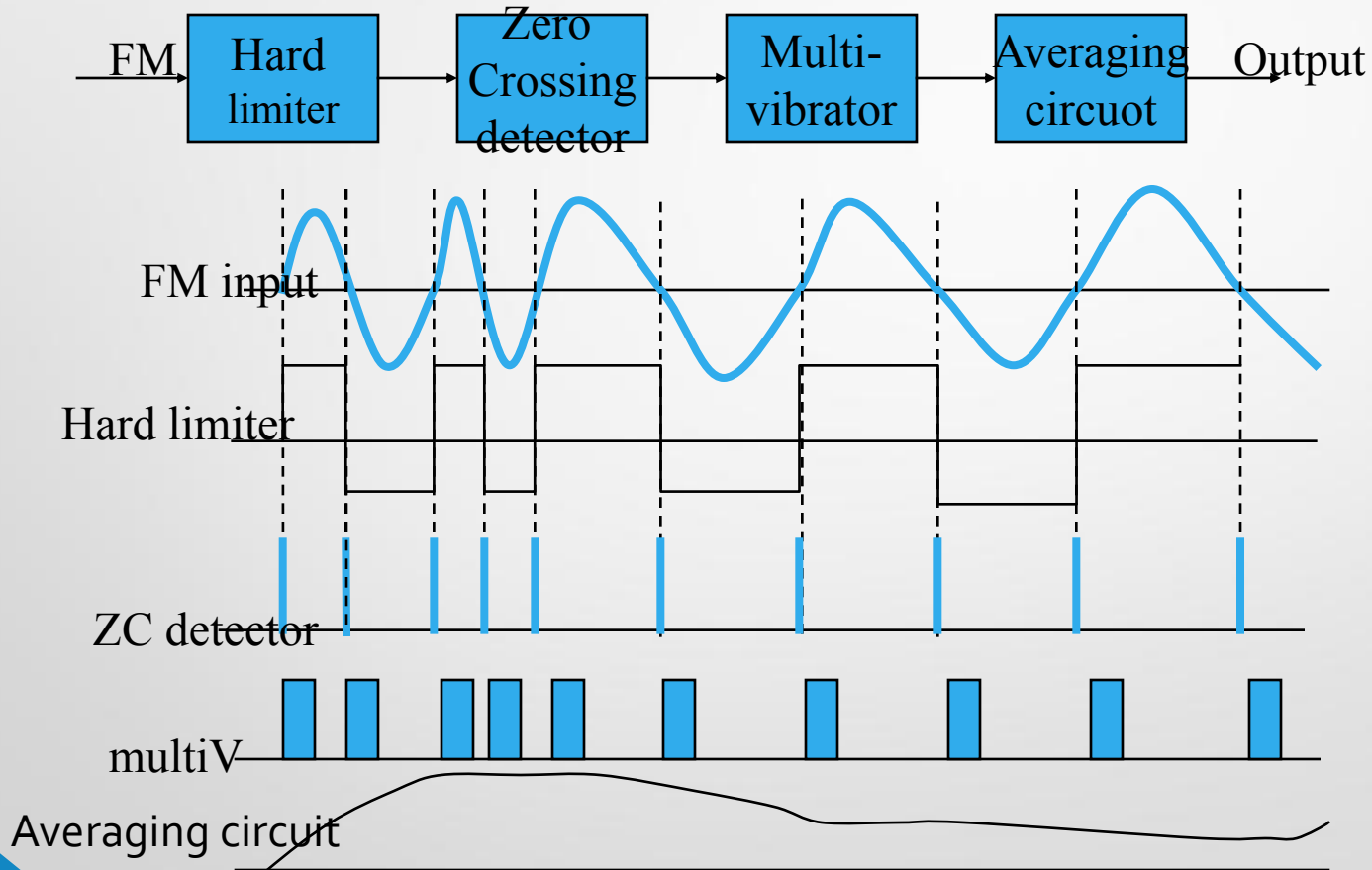

more frequent
ZC's means
higher inst freq
in turn means
Larger message
amplitudes