

**Dronacharya College of Engineering, Gurgaon**

**Department of Electronics and Computers Engineering**

**Subject:**Digital Electronics( EC-412-F)

**Semester/Branch:** IV ECS

---

**Important Questions**

**Section A**

- Q1. What is flip flop? Different types of flip flops with truth table and diagram.
- Q2. Conversion of flip flops
- Q3. Explain edge triggered and level triggered flip flop. (Hint: Clock, levels, edges, flip flop working, difference between clocked and unclocked flip flop, timing diagram using some input and then corresponding output using diff levels and edges).
- Q4. Race around condition

**Section B**

- Q1. Modulo – N Ripple Counter (N is no of bits)
- Q2. Modulo – M or Divide by M Ripple Counter (where  $M < 2^N$  and N is no of bits)
- Q3. Asynchronous Down Counter, Up/Down Counter
- Q4. Design of Synchronous Counter (N is no of bits)
- Q5. Ring Counter and Johnson Counter

**Section C**

- Q1 Register, Different types of registers (SISO, SIPO, PIPO, PISO, bidirectional, universal).
- Q2. Counters, Synchronous Counter, Asynchronous (Ripple) Counter
- Q3. What is the range of unsigned decimal values that can be represented in 10 bits?  
What is the range of signed decimal values using the same number of bits?
- Q4. The reason why the sign –magnitude method for representing signed numbers is

not used in most computers can readily be illustrated by performing the following.

- (a) Represent +12 in 5 bits using the sign –magnitude form.
- (b) Represent -12 in 5 bits using the sign –magnitude form.
- (c) Add the two binary numbers and note that the sum does not look anything like zero.

### **Section D**

Q1 Perform the following operations in the 2's complement system. Use 8 bits (including sign bit) for each number. Check your results by converting the binary result back to decimal

- a. Add +9 to +6.
- b. Add +14 to -17.
- c. Add +19 to -24.
- d. Add -48 to -80.
- e. Subtract +16 from +17.
- f. Subtract +21 from -13.
- g. Subtract -36 from -15.
- h. Add +17 to -17.
- i. Subtract -17 from -17.

Q 2. Perform the following operations in the 2's complement system. Use 8 bits (including sign bit) for each number. Show that overflow occurs in each case

- a. Add +9 to +6.
- b. Add +14 to -17.

Q 3. Multiply the following pairs of binary numbers and check by doing multiplication in decimal.

- (a)  $111 \times 101$
- (b)  $1011 \times 1011$
- (c)  $101.101 \times 110.010$
- (d)  $.1101 \times .1011$

Q 4. Perform the divisions. Check the results by doing division in decimal.

- (a)  $1100 \div 100$
- (b)  $111111 \div 1001$
- (c)  $10111 \div 100$
- (d)  $10110.1101 \div 1.1$

