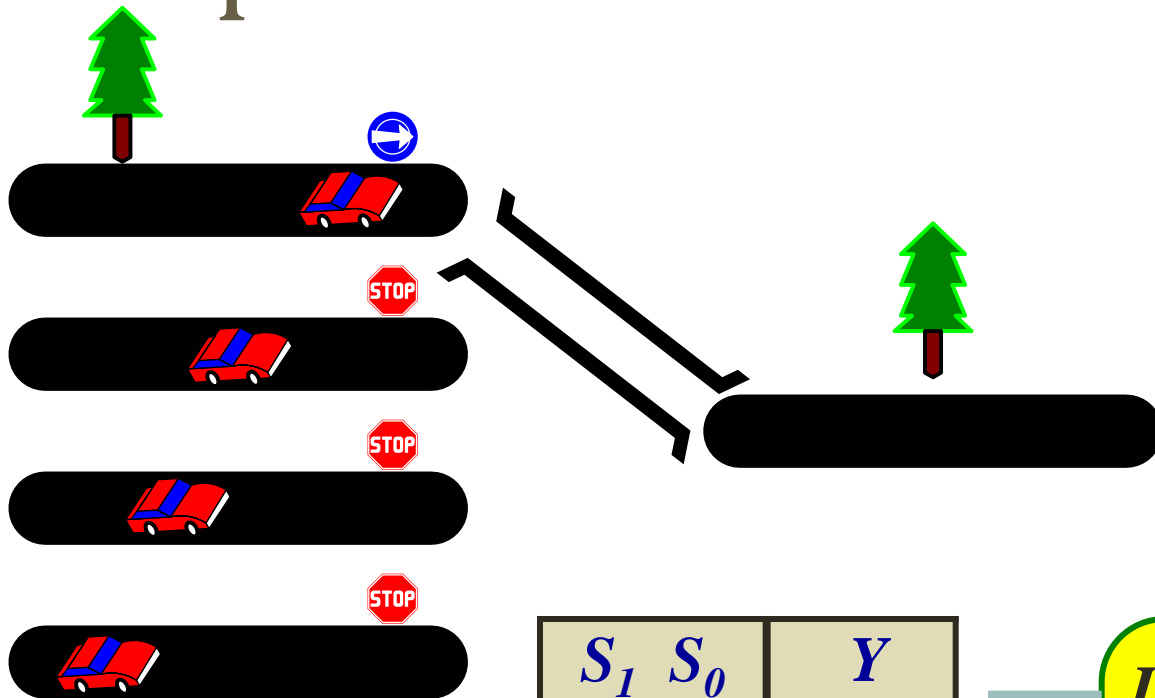



LECTURE 6

COMBINATIONAL DESIGN USING MSI DEVICES

Multiplexers





S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


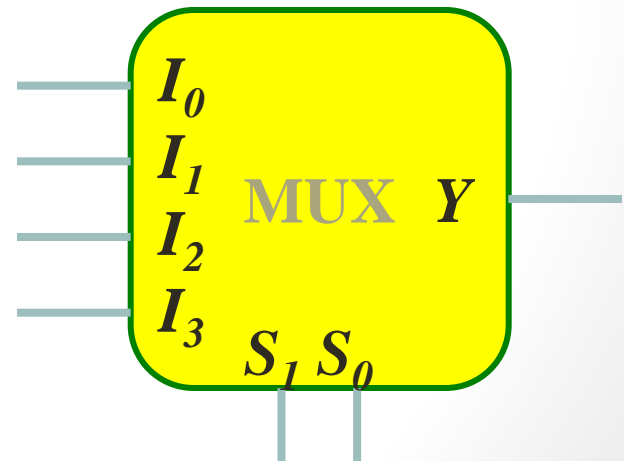


Multiplexers

- 2-to-1 MUX

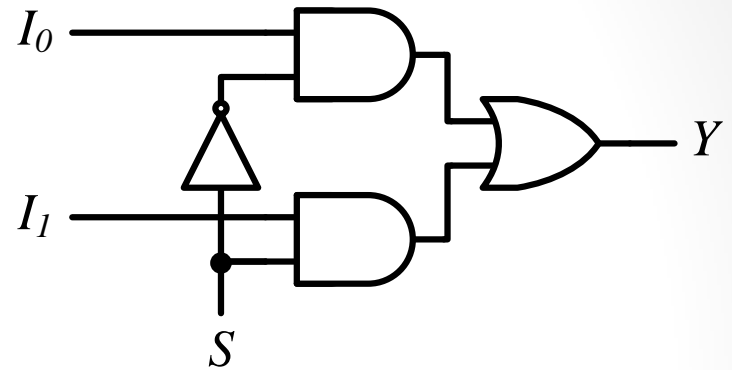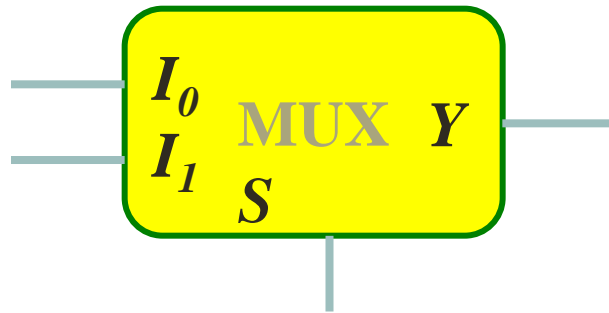


- 4-to-1 MUX

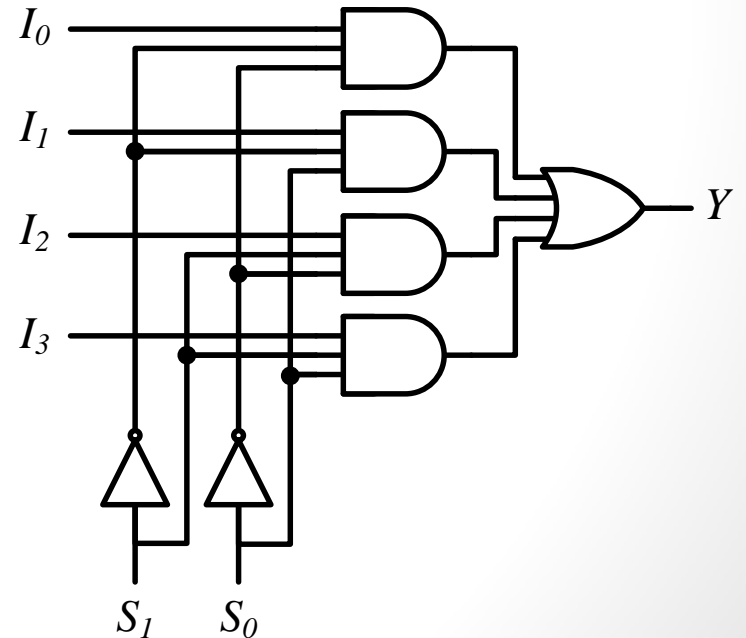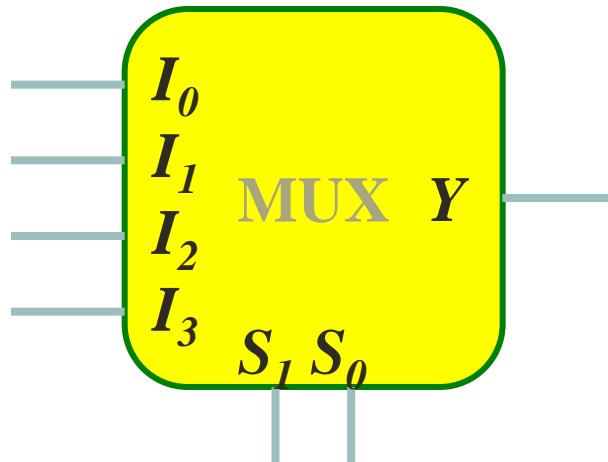



Multiplexers

- Quad 2-to-1 MUX

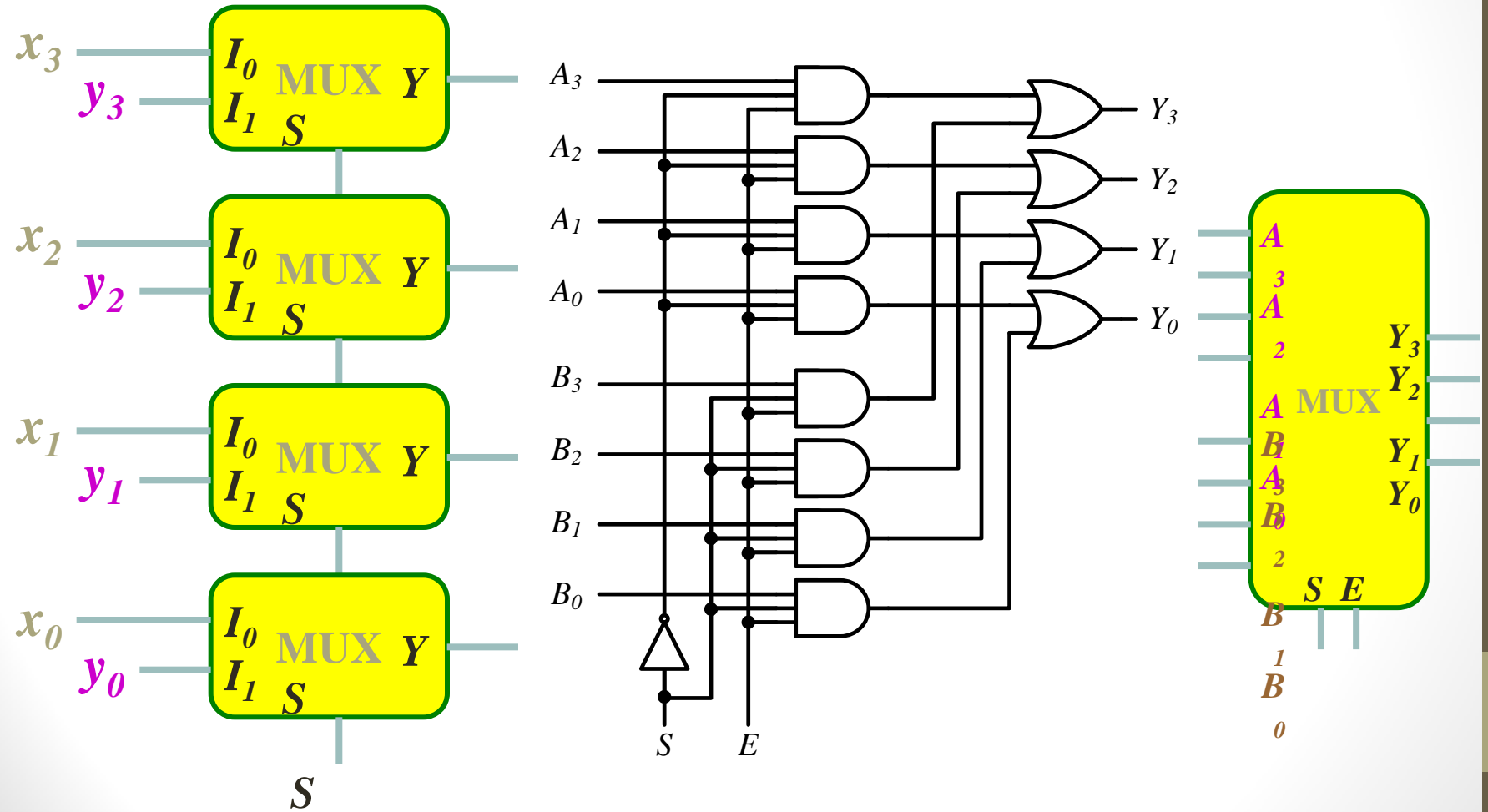

Multiplexers


- Quad 2-to-1 MUX

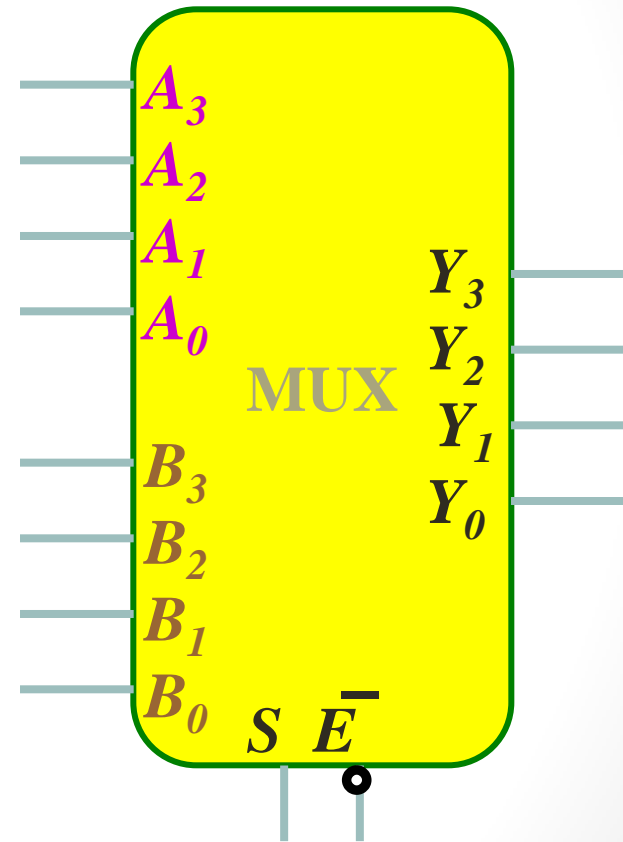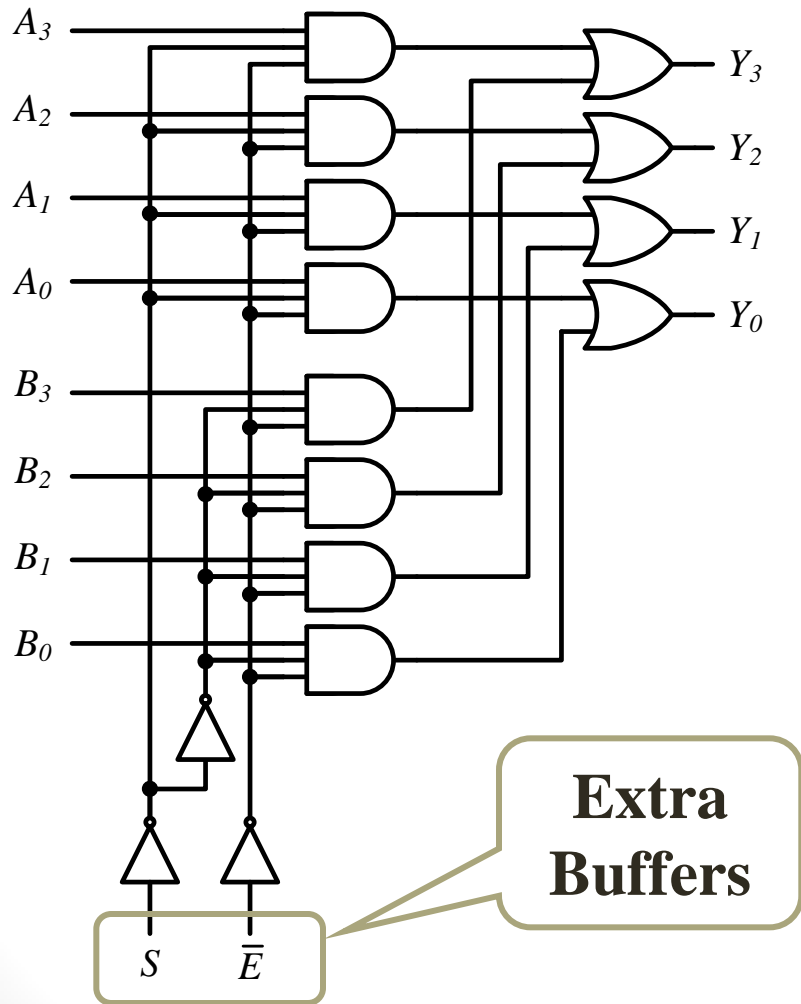

Implementation Using Multiplexers

- Example

$$F(x, y) = \sum(0, 1, 3)$$

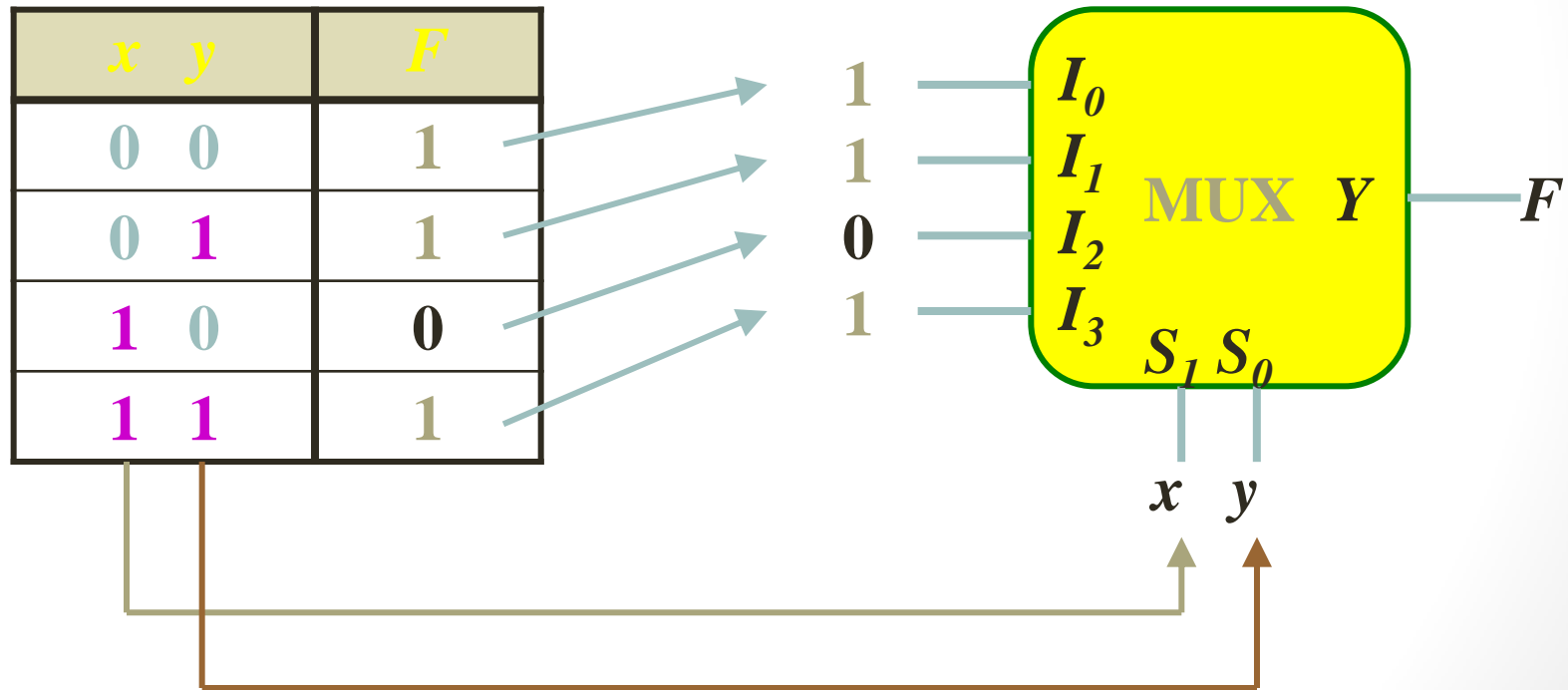


Implementation Using Multiplexers

- Example

$$F(x, y, z) = \sum(1, 2, 6, 7)$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

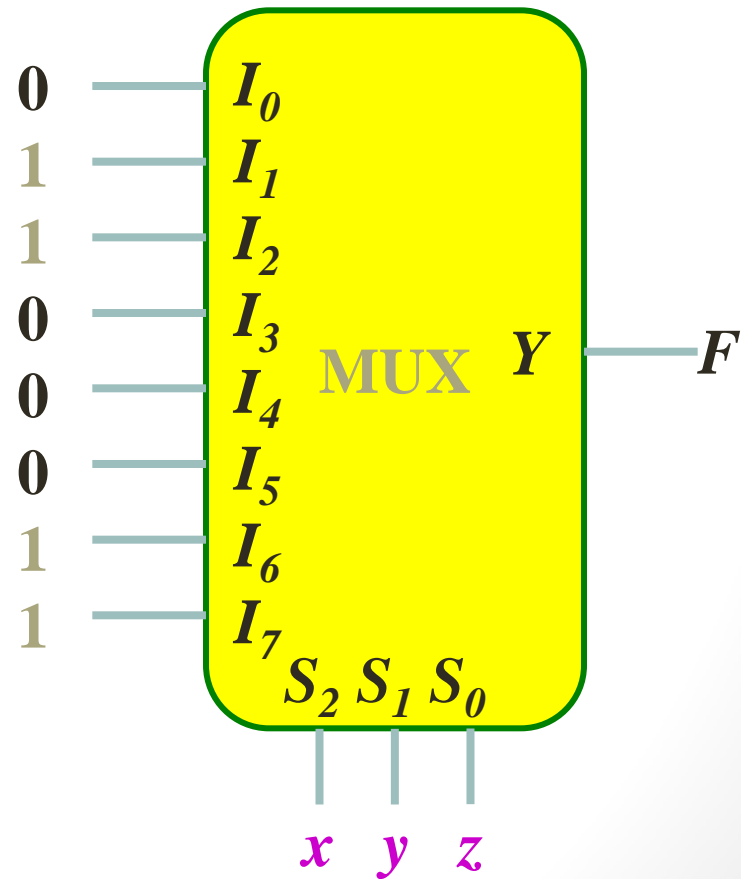


Implementation Using Multiplexers

- Example

$$F(x, y, z) = \sum(1, 2, 6, 7)$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

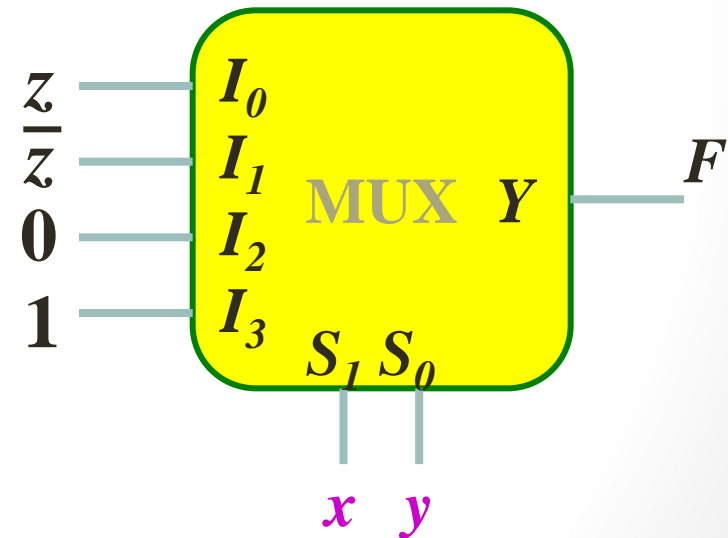
$\left. \begin{array}{l} \text{Row 1} \\ \text{Row 2} \end{array} \right\} F = z$
 $\left. \begin{array}{l} \text{Row 3} \\ \text{Row 4} \end{array} \right\} F = \bar{z}$
 $\left. \begin{array}{l} \text{Row 5} \\ \text{Row 6} \end{array} \right\} F = 0$
 $\left. \begin{array}{l} \text{Row 7} \\ \text{Row 8} \end{array} \right\} F = 1$



Implementation Using Multiplexers

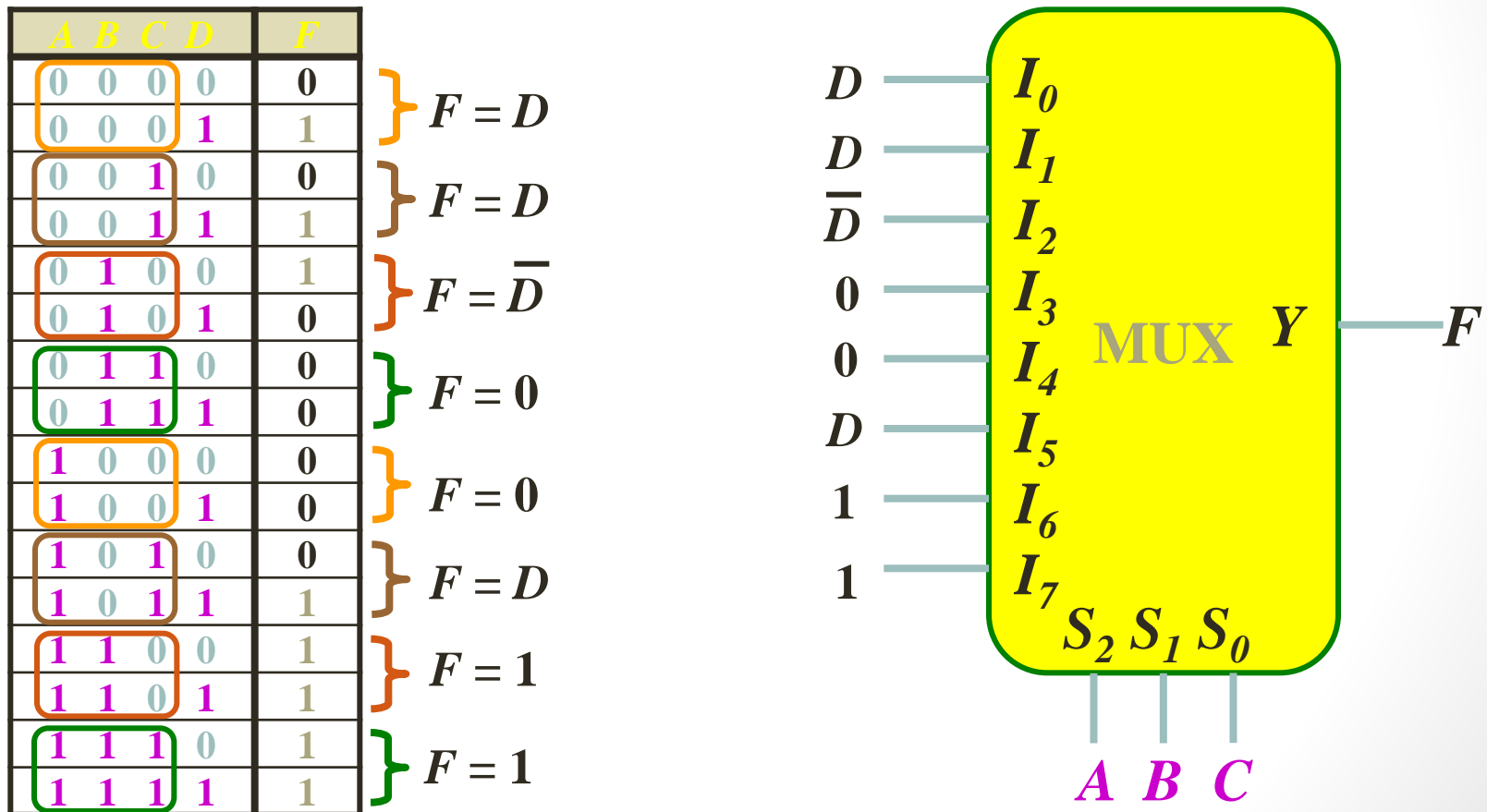Example

$$F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$$



Multiplexer Expansion

- 8-to-1 MUX using Dual 4-to-1 MUX

