

LECTURE 8

COMBINATIONAL DESIGN USING MSI DEVICES

Clock Signal

Sequential logic circuits have memory

Output is a function of input and present state

Sequential circuits are synchronized by a periodic “clock” signal


 
 


Figure 7.33 The clock signal consists of periodic logic-1 pulses.

Clock Signal generator

 Clock signals can be generated using odd number of inverters



$$T = 2 \times t_p \times N$$

Flip Flop

A basic sequential circuit is a flip-flop

Flip-flop has two stable states of complementary output values

 


Figure 7.34 Simple flip-flop.

SR Flip Flop

SR (set-reset) flip-flop based on two nor gates

 


Figure 7.35 An SR flip-flop can be implemented by cross coupling two NOR gates.

SR Flip Flop


 


Figure 7.35 An SR flip-flop can be implemented by cross coupling two NOR gates.

R	S	Q_n
0	0	Q_{n-1}
0	1	1
1	0	0
1	1	Not allowed

(a) Truth table

 

(b) Circuit symbol


Figure 7.36 The truth table and symbol for the SR flip-flop.

Noise Reduction in SR Flip Flop


SR flip flop can reduce a switching noise

When switch is pulled down some oscillations may occur at B

They will be eliminated by the flip-flop

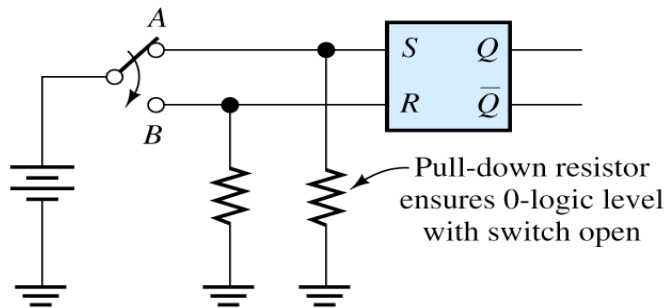

(a) Circuit diagram

 

(b) Waveforms

Figure 7.37 An SR flip-flop can be used to eliminate the effects of switch bounce.

Exercise

For a given S and R inputs to SR flip-flop,
sketch the output signal Q

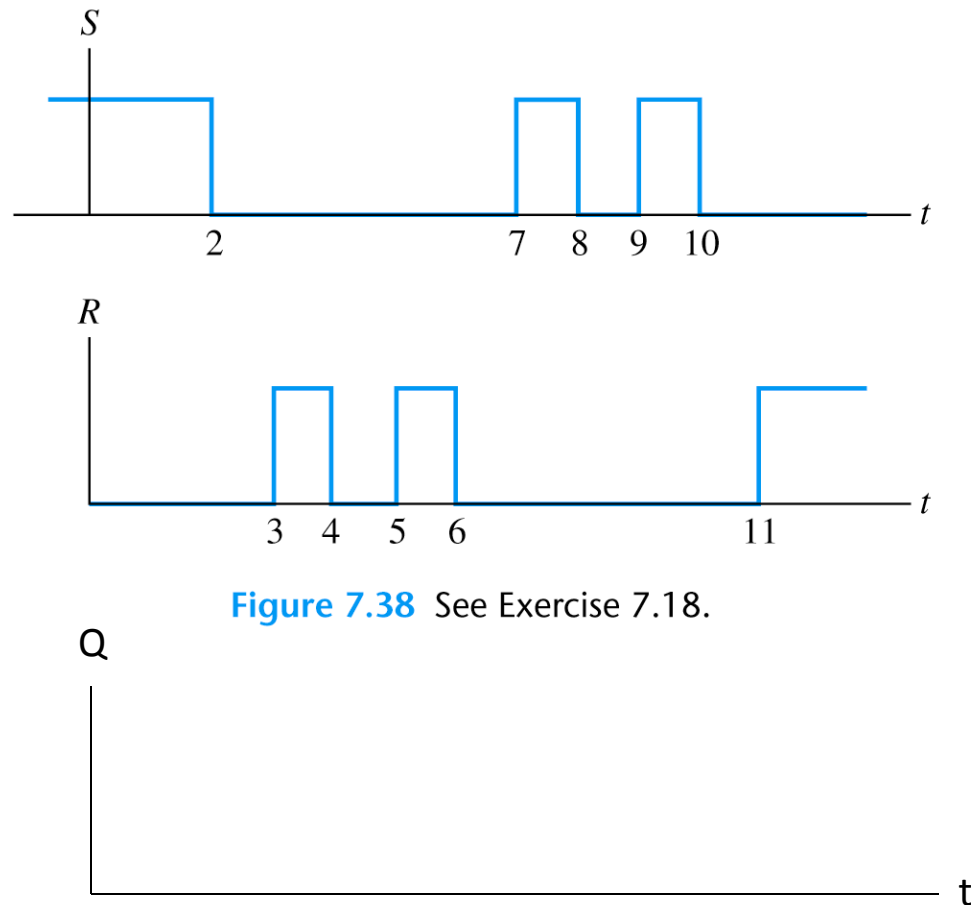


Figure 7.38 See Exercise 7.18.

Exercise

 


Figure 7.39 Answer for Exercise 7.18.

SR Flip Flop

SR (set-reset) flip-flop based on two nand gates


 


Figure 7.40 A flip-flop implemented with NAND gates. See Exercise 7.19.

Clocked SR Flip Flop Circuit

 
Clock controlled flip-flop changes its state only when the clock C is high



(a) Circuit diagram

R	S	C	Q_n
0	0	×	Q_{n-1}
0	1	1	1
1	0	1	0
1	1	1	Not allowed
×	×	0	Q_{n-1}

(b) Truth table

 


(b) Circuit symbol

Figure 7.41 A clocked SR flip-flop.

Clocked SR Flip Flop Circuit with Reset

Some flip-flops have asynchronous preset Pr and clear Cl signals.

 
Output changes once these signals change, however the input signals must wait for a change in clock to change the output



(a) Circuit diagram

Pr	Cl	R	S	C	Q_n
0	0	0	0	×	Q_{n-1}
0	0	0	1	1	1
0	0	1	0	1	0
×	×	1	1	1	Not allowed
0	1	×	×	×	0
1	0	×	×	×	1
1	1	×	×	×	Not allowed

(b) Truth table

 

(c) Circuit symbol

Figure 7.42 A clocked SR flip-flop with asynchronous preset and clear inputs.

Edge Triggered Flip Flop

Edge triggered flip-flop changes only when the clock C changes


 


Figure 7.43 Clock signal.

Positive Edge Triggered Flip Flop

 Positive-edge triggered flip-flop changes only on the rising edge of the clock C



(a) Circuit symbol

C	D	Q_n
0	\times	Q_{n-1}
1	\times	Q_{n-1}
\uparrow	0	0
\uparrow	1	1


(b) Truth table

\uparrow indicates a transition from low to high

Figure 7.44 A positive-edge-triggered D flip-flop.

 Exercise

The input D to a positive-edge triggered flip-flop is shown
Find the output signal Q



(a) Circuit symbol

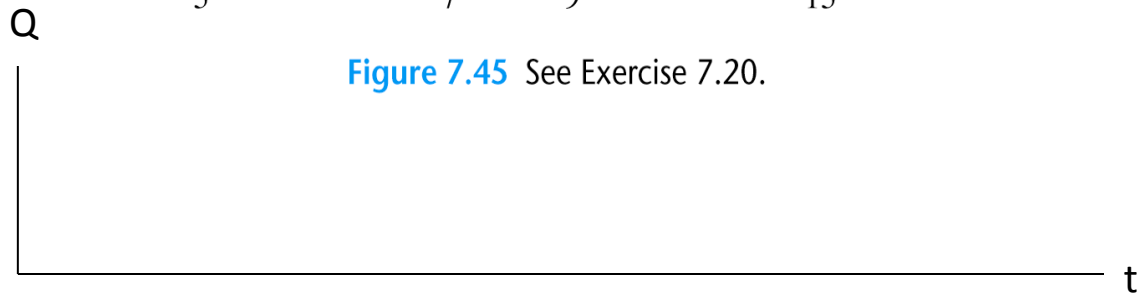
 
 


Figure 7.45 See Exercise 7.20.

Exercise


 


Figure 7.46 Answer for Exercise 7.20.

Negative Edge Triggered JK Flip Flop

 

(a) Circuit symbol


C	J	K	Q_n	Comment
0	×	×	Q_{n-1}	Memory
1	×	×	Q_{n-1}	Memory
↓	0	0	Q_{n-1}	Memory
↓	0	1	0	Reset
↓	1	0	1	Set
↓	1	1	\bar{Q}_{n-1}	Toggle

(b) Truth table


↓ indicates a transition
from low to high

Figure 7.47 Negative-edge-triggered JK flip-flop.



Other Flip Flops

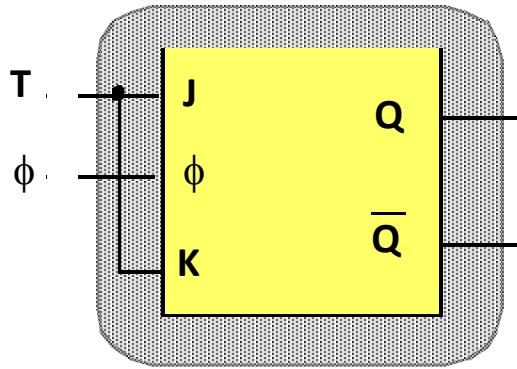



Toggle Flip-Flop

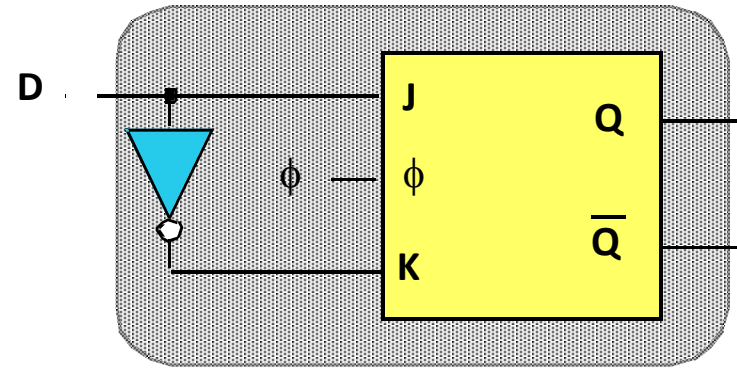

Delay Flip-Flop (D-latch)

 
 


Race Problem

  

Signal can race around during $\phi = 1$

Master-Slave Flip Flop Implementation

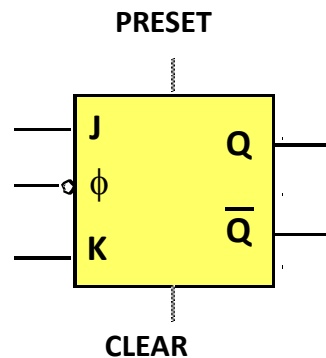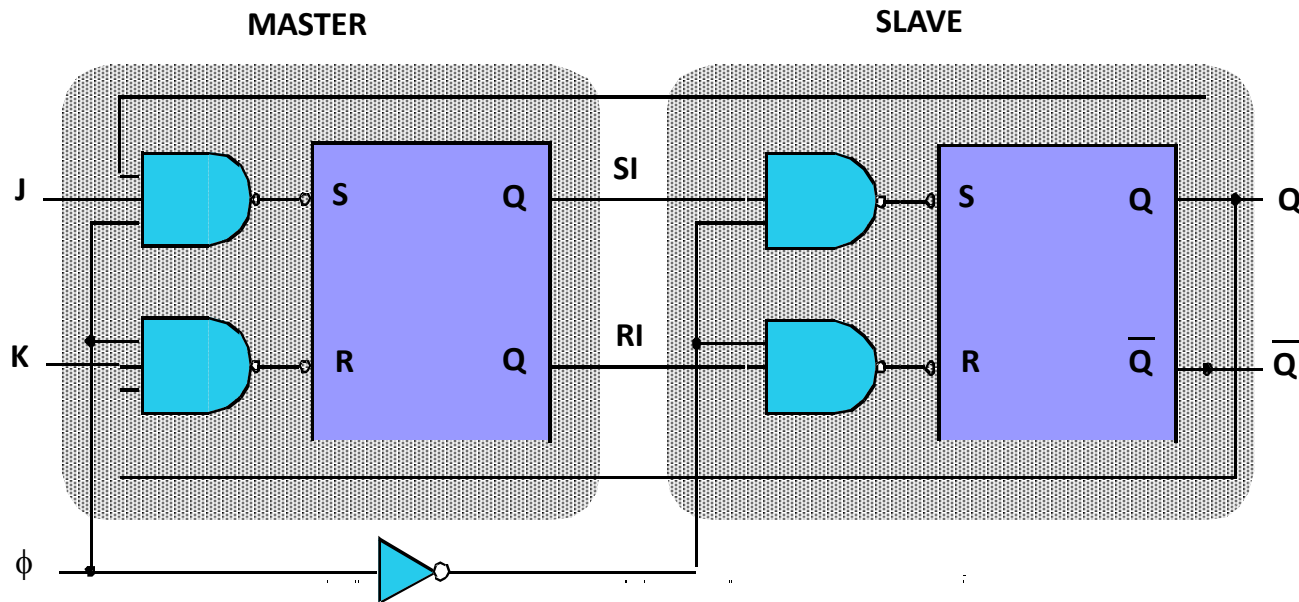

Master transmits the signal to the output during the high clock phase and **slave is waiting** for the clock to change this prevents race conditions

Shift Registers

 


Figure 7.48 Serial-input parallel-output shift register.

Shift Registers

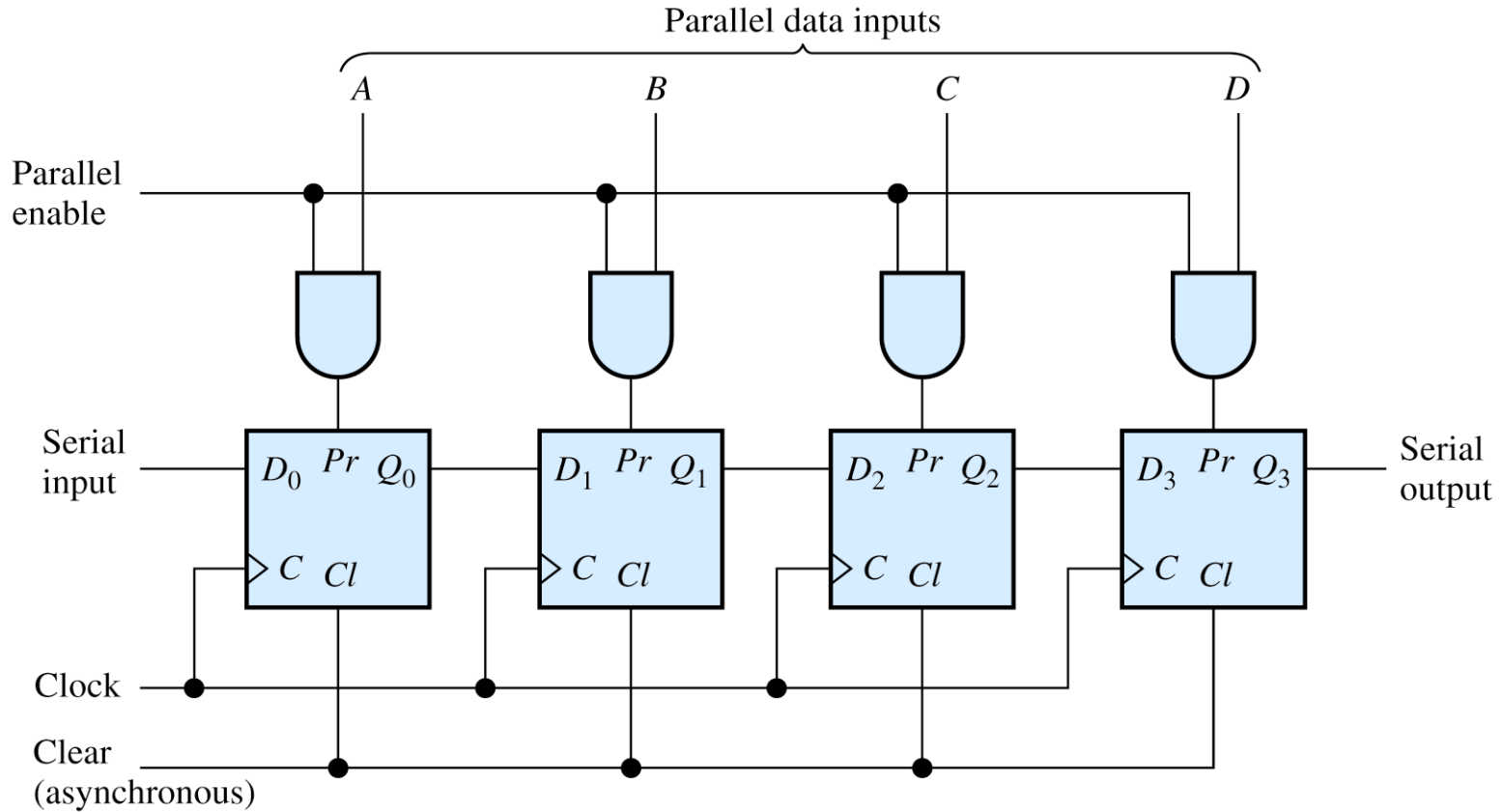


Figure 7.49 Parallel-input serial-output shift register.

Counter

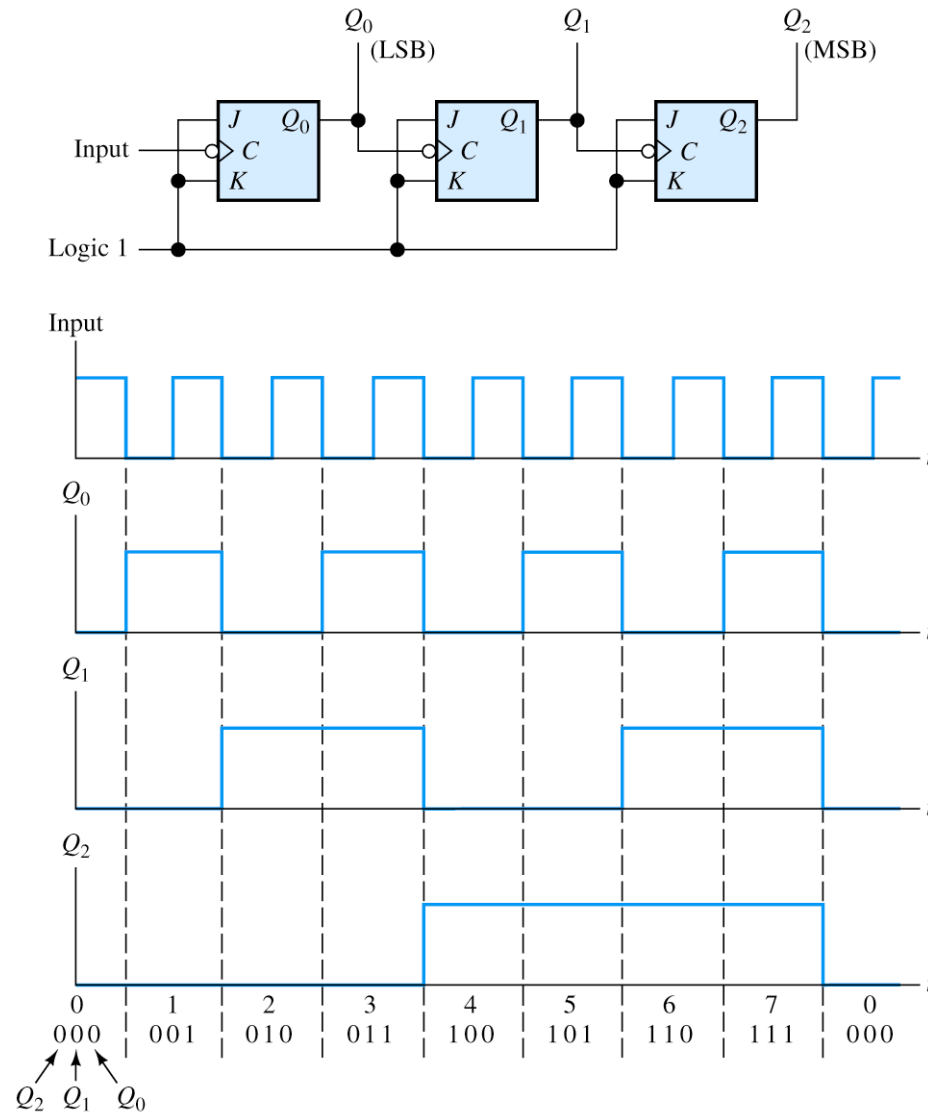


Figure 7.50 Ripple counter.