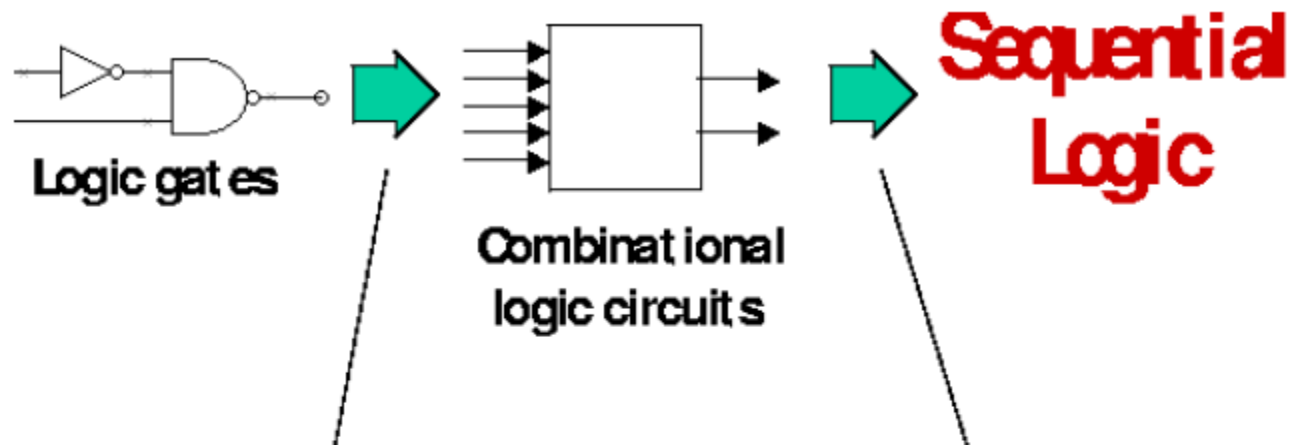


LECTURE 9

COMBINATIONAL DESIGN USING MSI DEVICES

Sequential Circuits Problems



Acyclic connections

Composable blocks

Design:

- ◆ truth tables
- ◆ sum-of-products
- ◆ simplification
- ◆ muxes, ROMs, PLAs

Storage & state

Dynamic discipline

Finite-state machines


Metastability

Throughput & latency

Pipelining


Static
discipline

- A **combinational device** is a circuit element that has
 - one or more digital *inputs*
 - one or more digital *outputs*
 - a *functional specification* that details the value of each output for every possible combination of valid input values
 - a *timing specification* consisting (at minimum) of an upper bound t_{pd} on the required time for the device to compute the specified output values from an arbitrary set of stable, valid input values

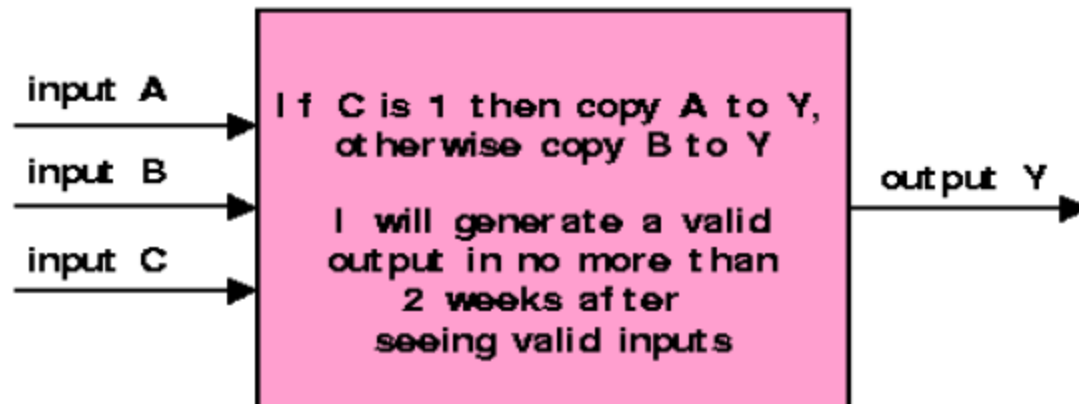

SR Master-Slave Flip-Flop

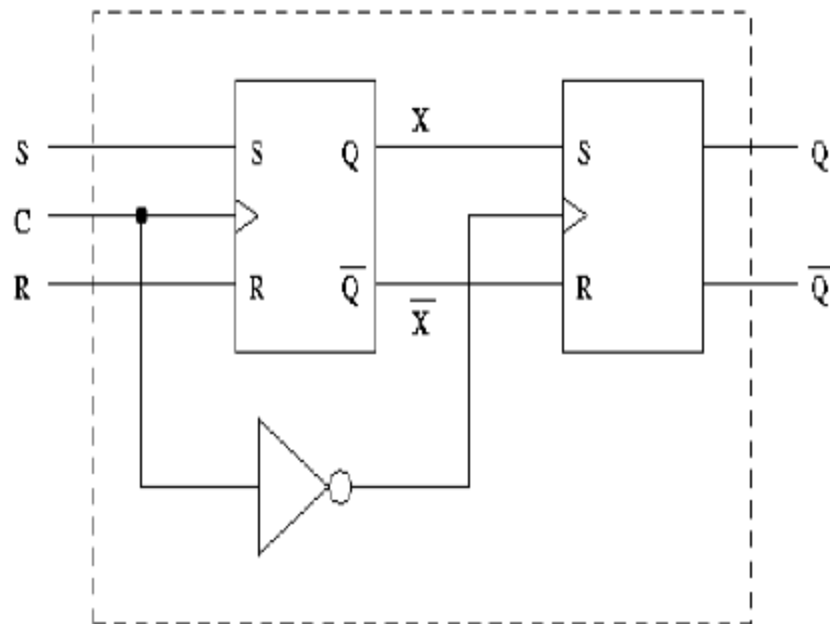
The SR Master-Slave Flip-Flop is constructed from two SR latches and an inverter.



The left hand latch is called the *master* and the right hand latch the *slave*.

JK Flip-Flop

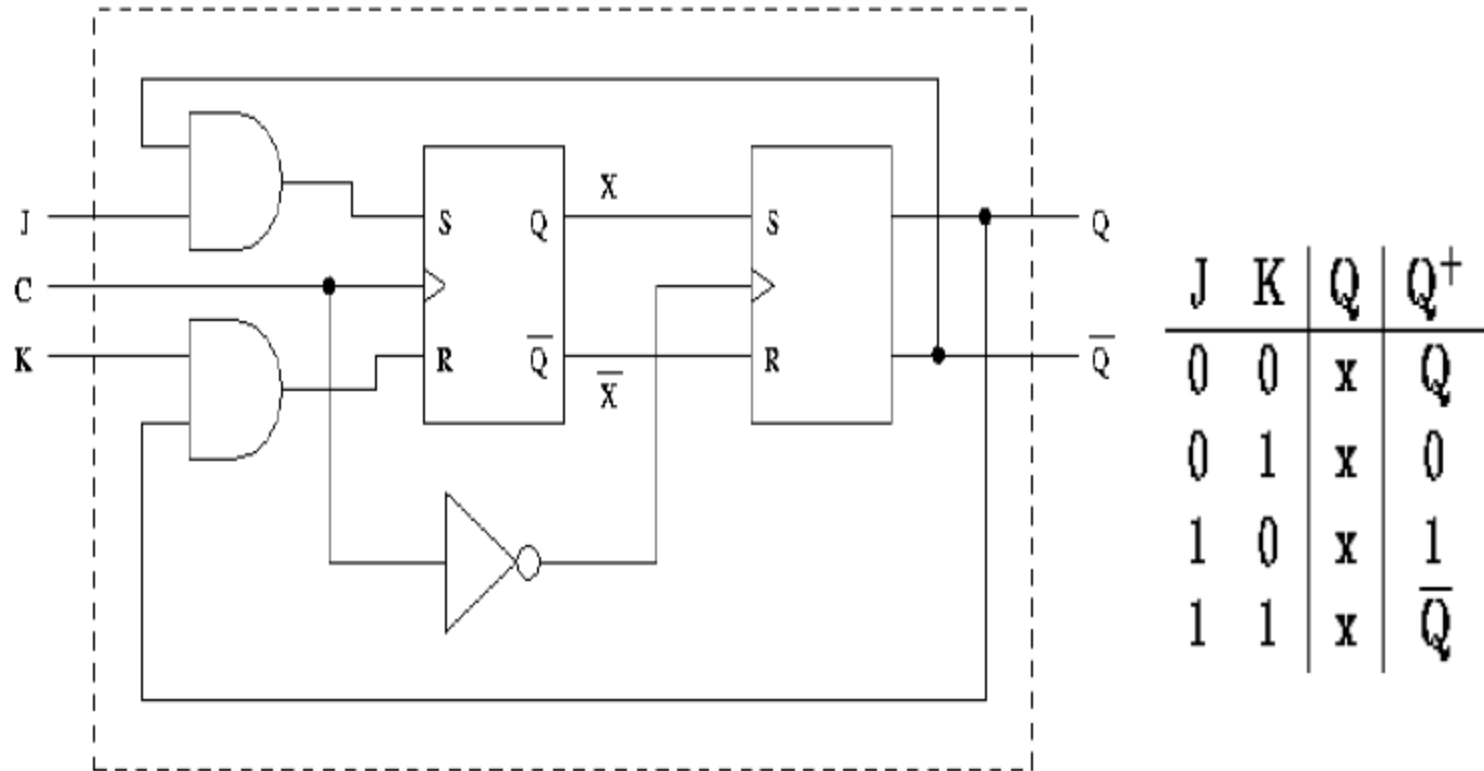The JK flip-flop is constructed from and is similar in operation to the SR flip-flop. The circuit is



For three of the four possible input combinations the operation is identical to the SR. The difference lies in the case where the two inputs are both 1. In