
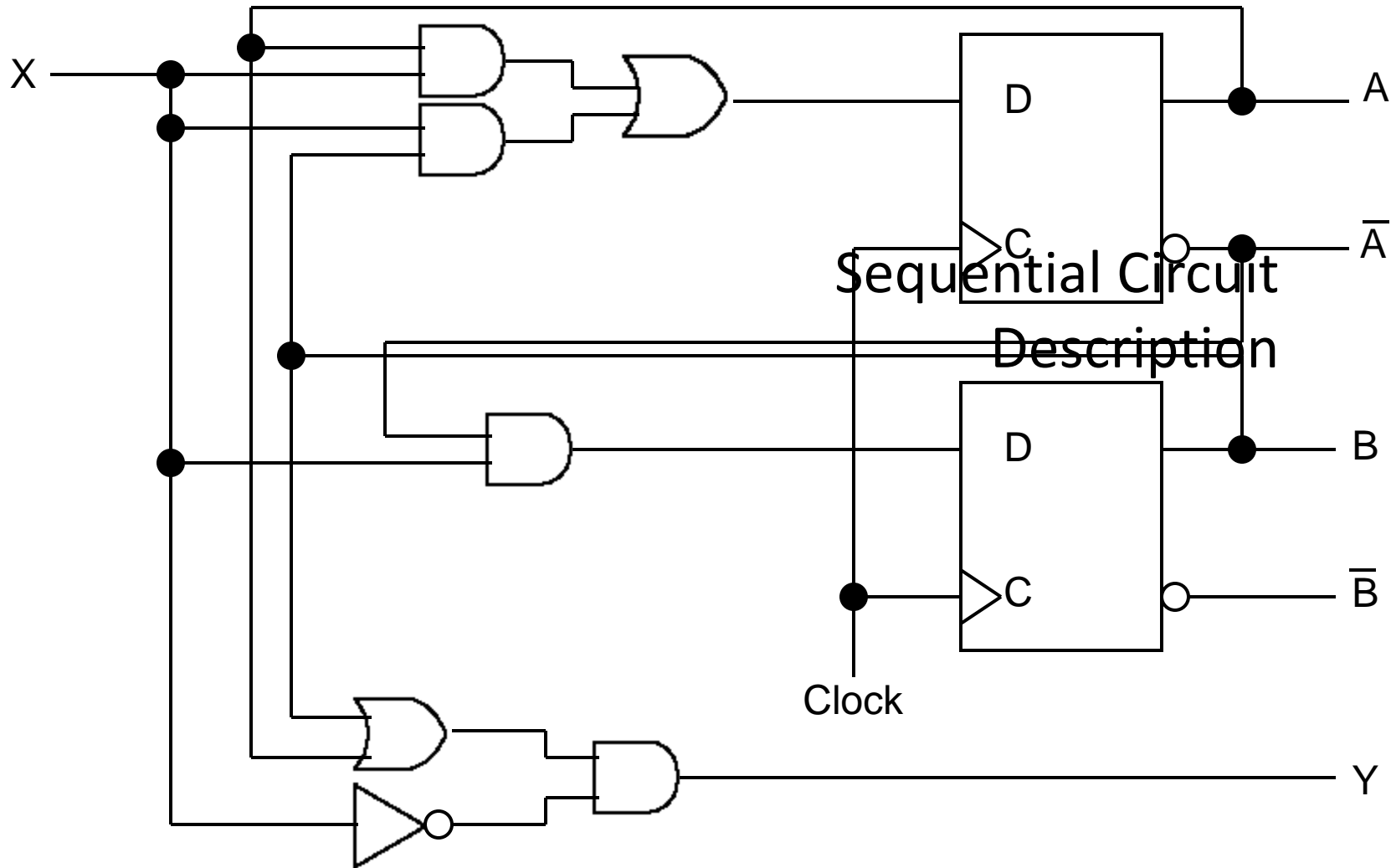


# LECTURE 12

## Digital Logic Families

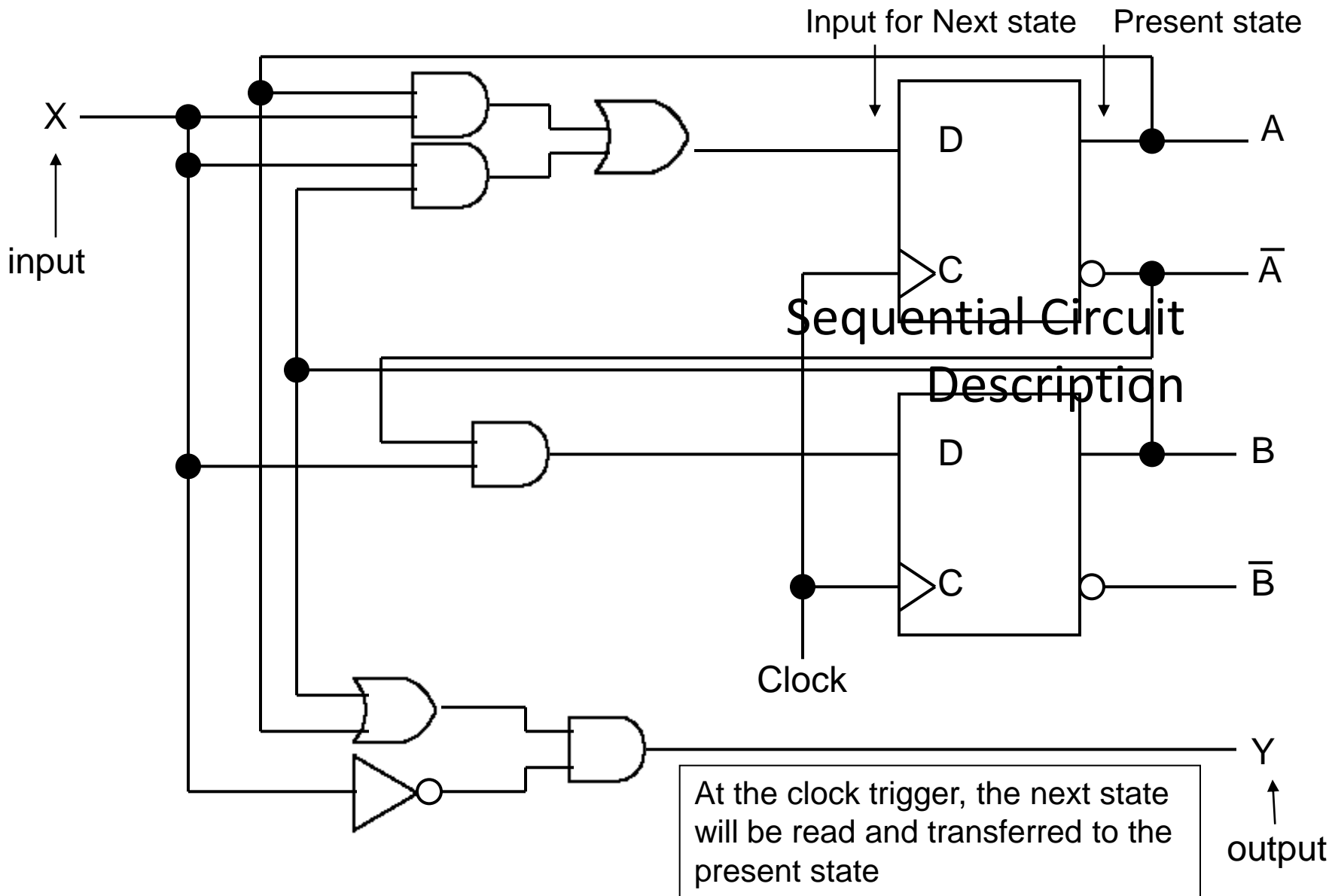



$$A_{\text{next}} = A_{\text{present}}X + B_{\text{present}}X$$

$$B_{\text{next}} = A'_{\text{present}}X$$


$$Y = (A_{\text{present}} + B_{\text{present}})X'$$

} **Input Equations**  
Next state in terms of  
input and present state

← Output in terms of input  
and present state


Present State		Input	Next State		Output
A	B	X	A	B	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

State Table

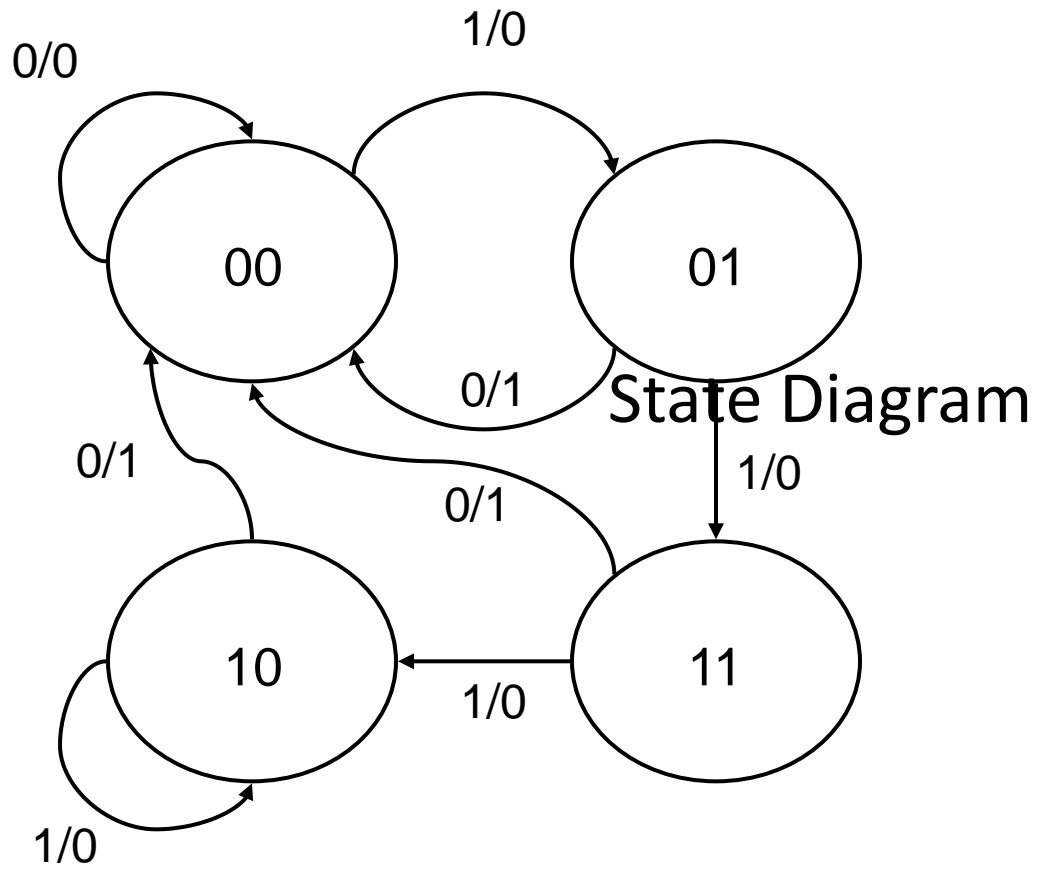

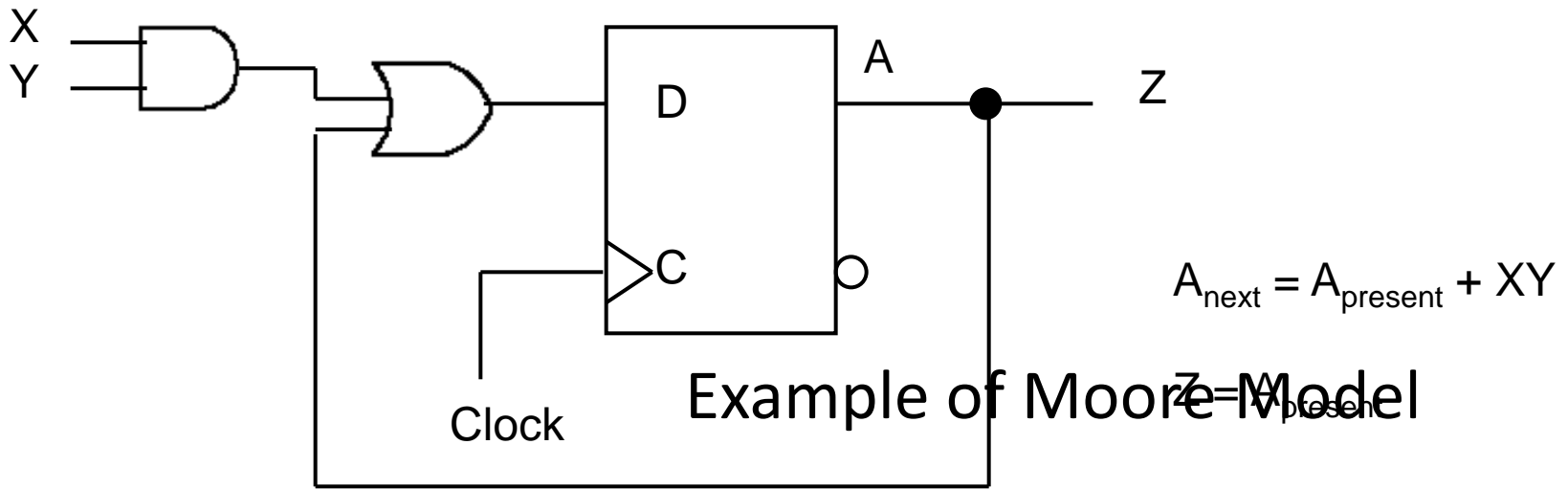
# Mealy and Moore Models

- Preceding Example: Output depends on present state and input. This is called the Mealy Model
- Another kind of circuit: Output only depends on present state. This is called the Moore Model





Example of Moore Model

X	Y	$A_{\text{present}}$	$A_{\text{next}}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

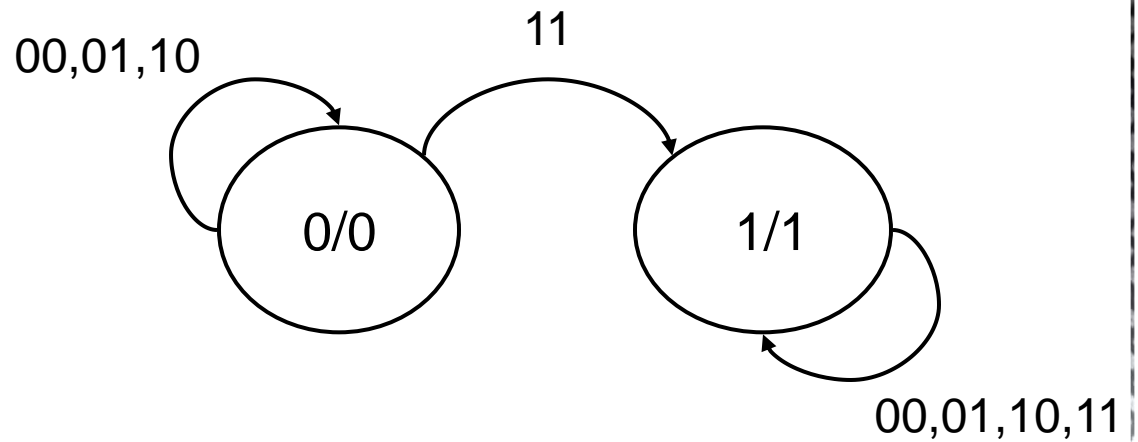





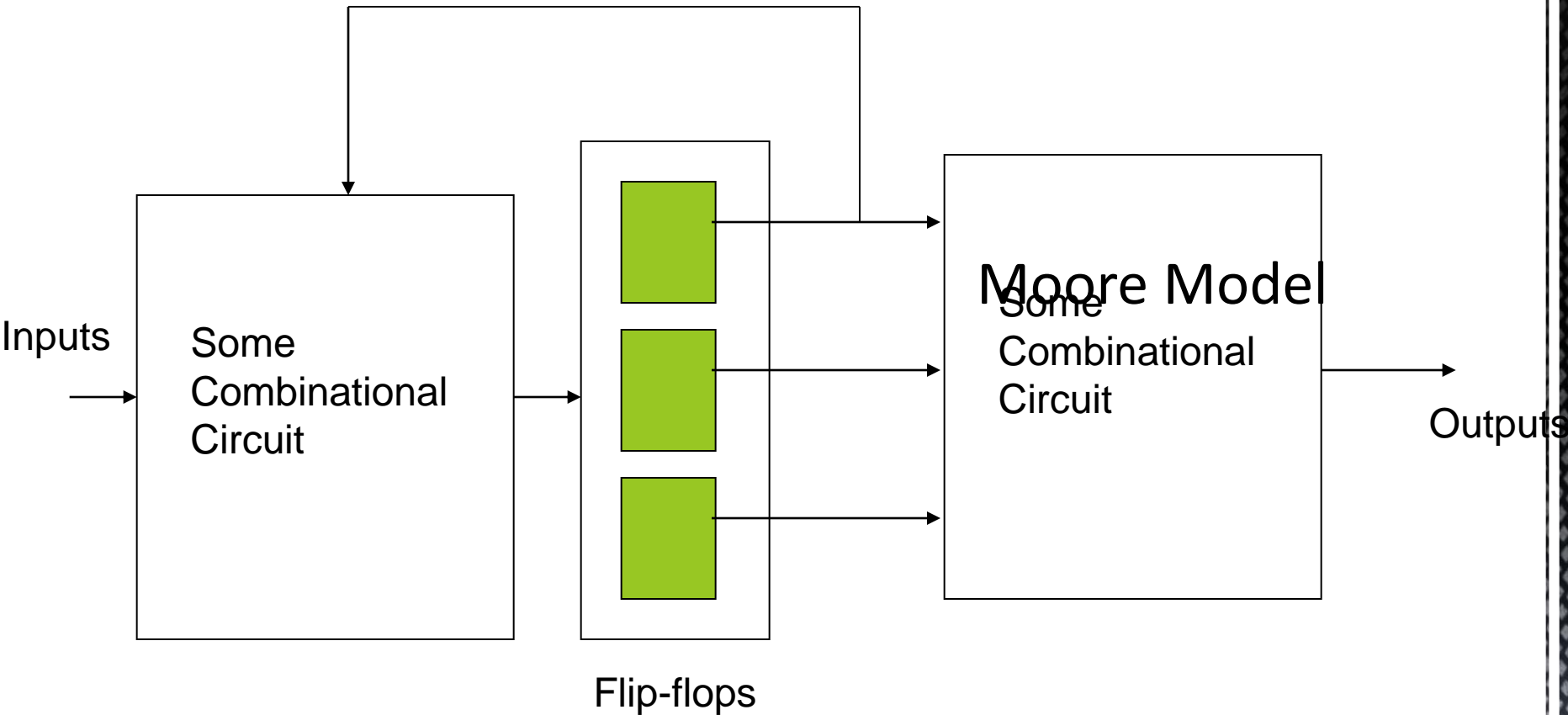

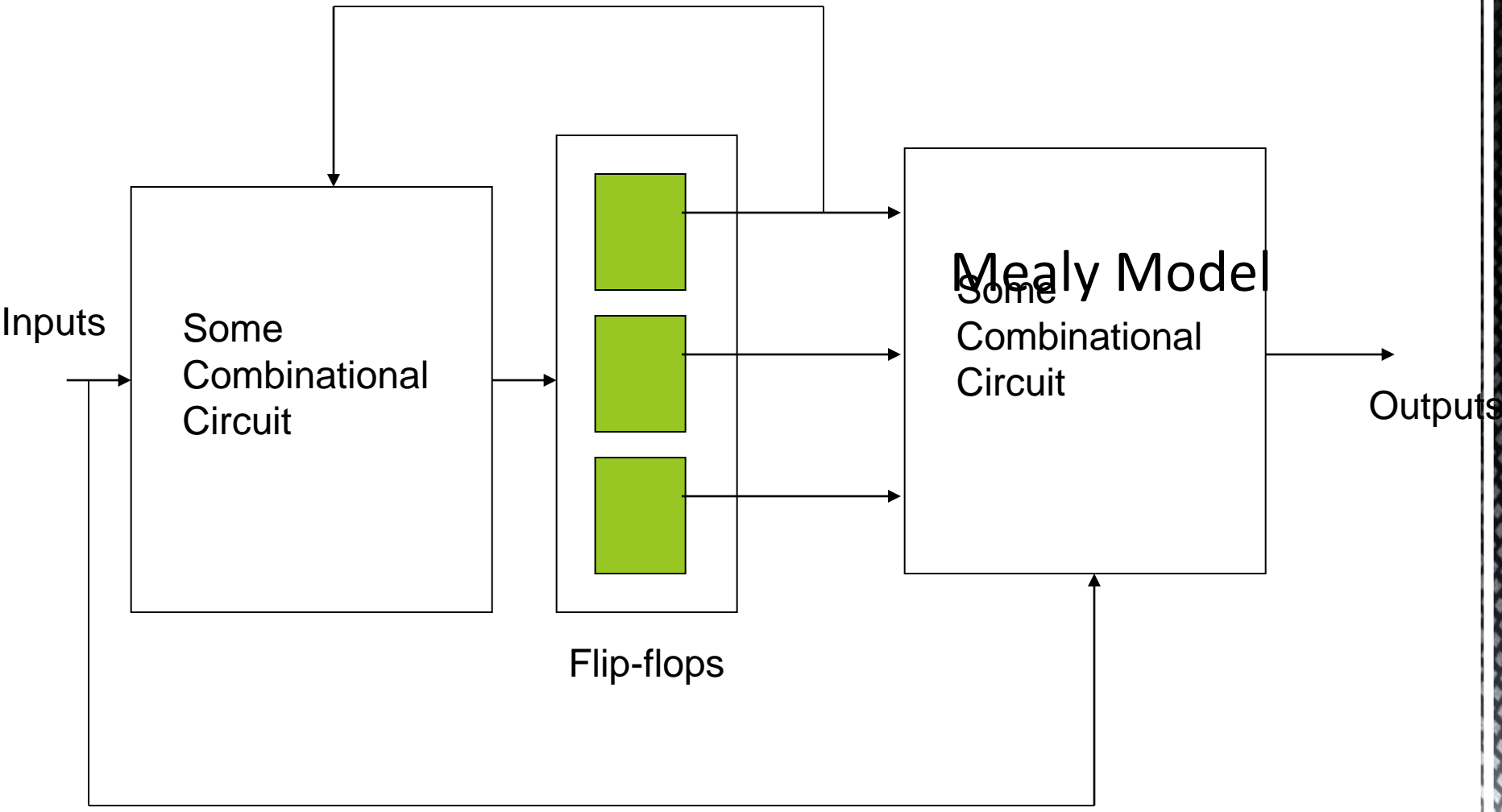

# Mealy and Moore State Diagrams

Moore

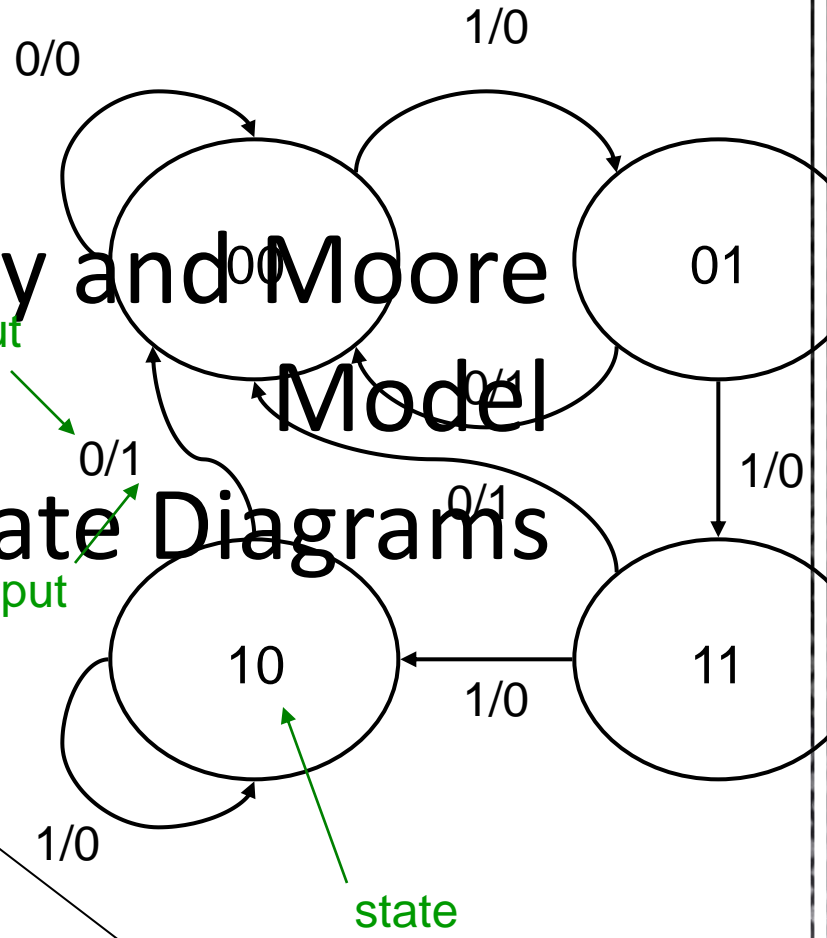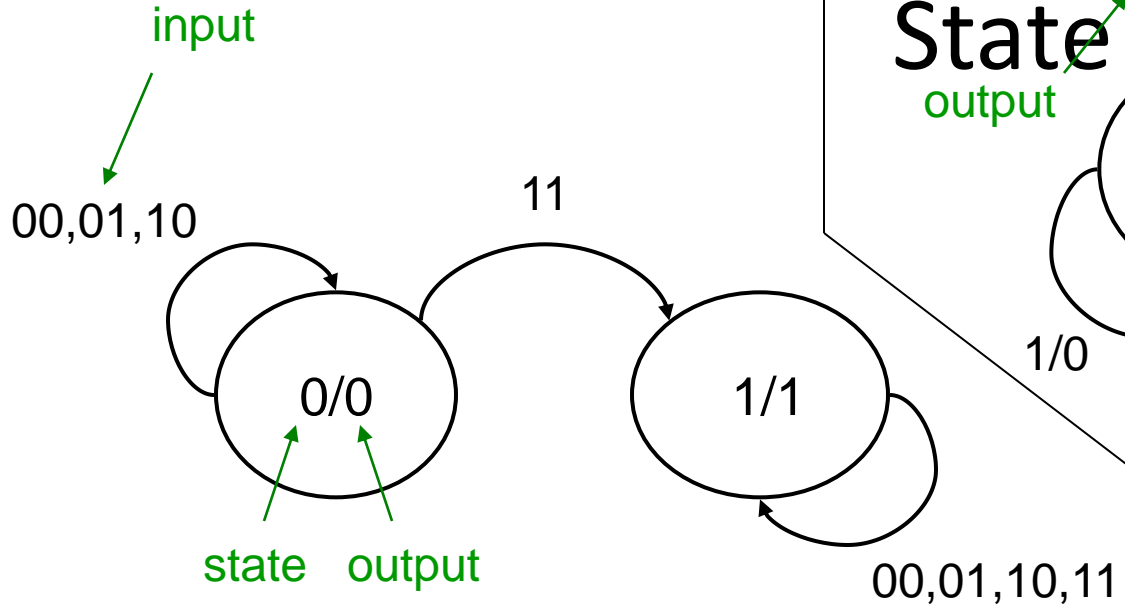


Mealy

- 1. Specification
- 2. Formulation: Draw a state diagram
- 3. Assign state number for each state
- 4. Draw state table
- 5. Derive input equations
- 5. One D flip-flop for each state bit


# How to Design a Sequential Circuit

- Design a sequential circuit to recognize the input sequence 1101.
- That is, output 1 if the sequence 1101 has been read, output 0 otherwise.

## Example

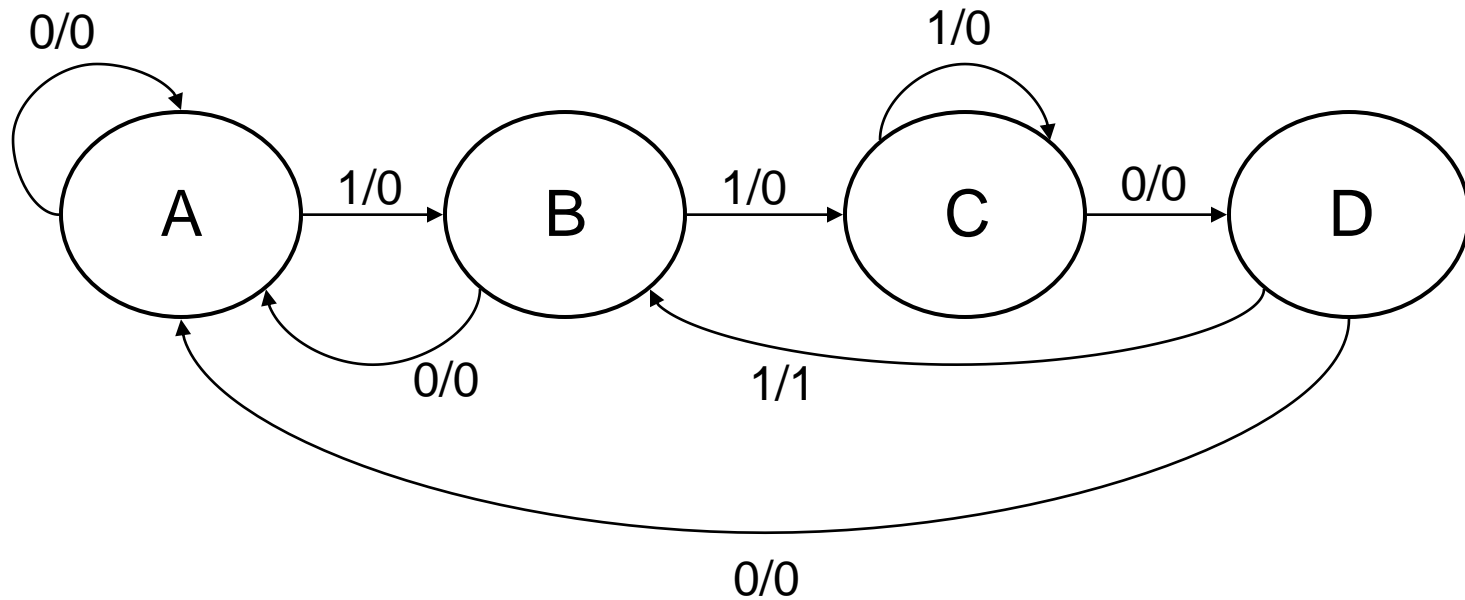

- 4 states, so we need 2 bits

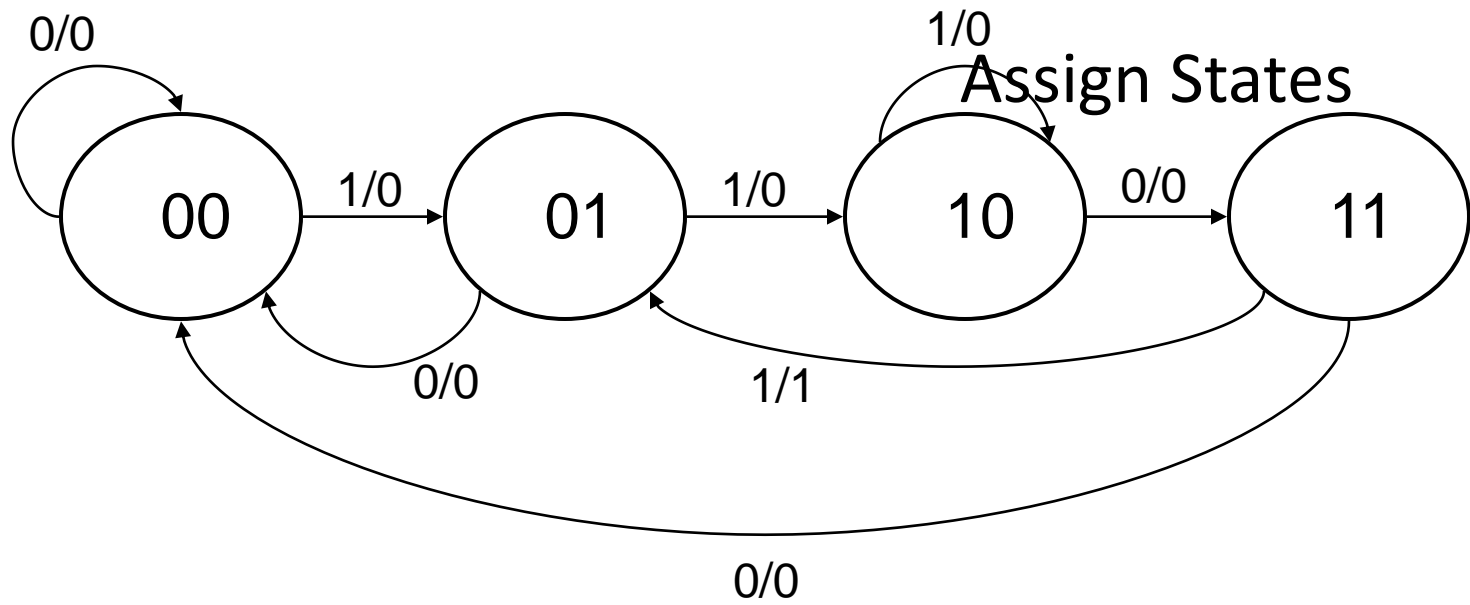

Present State		Input	Next State		Output
A	B	X	A	B	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	1	1

Draw State Table

$$A_{\text{next}} = A'BX + AB'$$

Derive Input Equations

$$B_{\text{next}} = A'B'X + AB'X' + ABX$$

$$Y = ABX$$



