 


LECTURE 14


Digital Logic Families

Map to Technology

- Library: D-type Flip-Flops with Reset input
 - Reset input is used to reset to start state: $Y_1 Y_2 = '00'$



Circuit Implementation with NAND

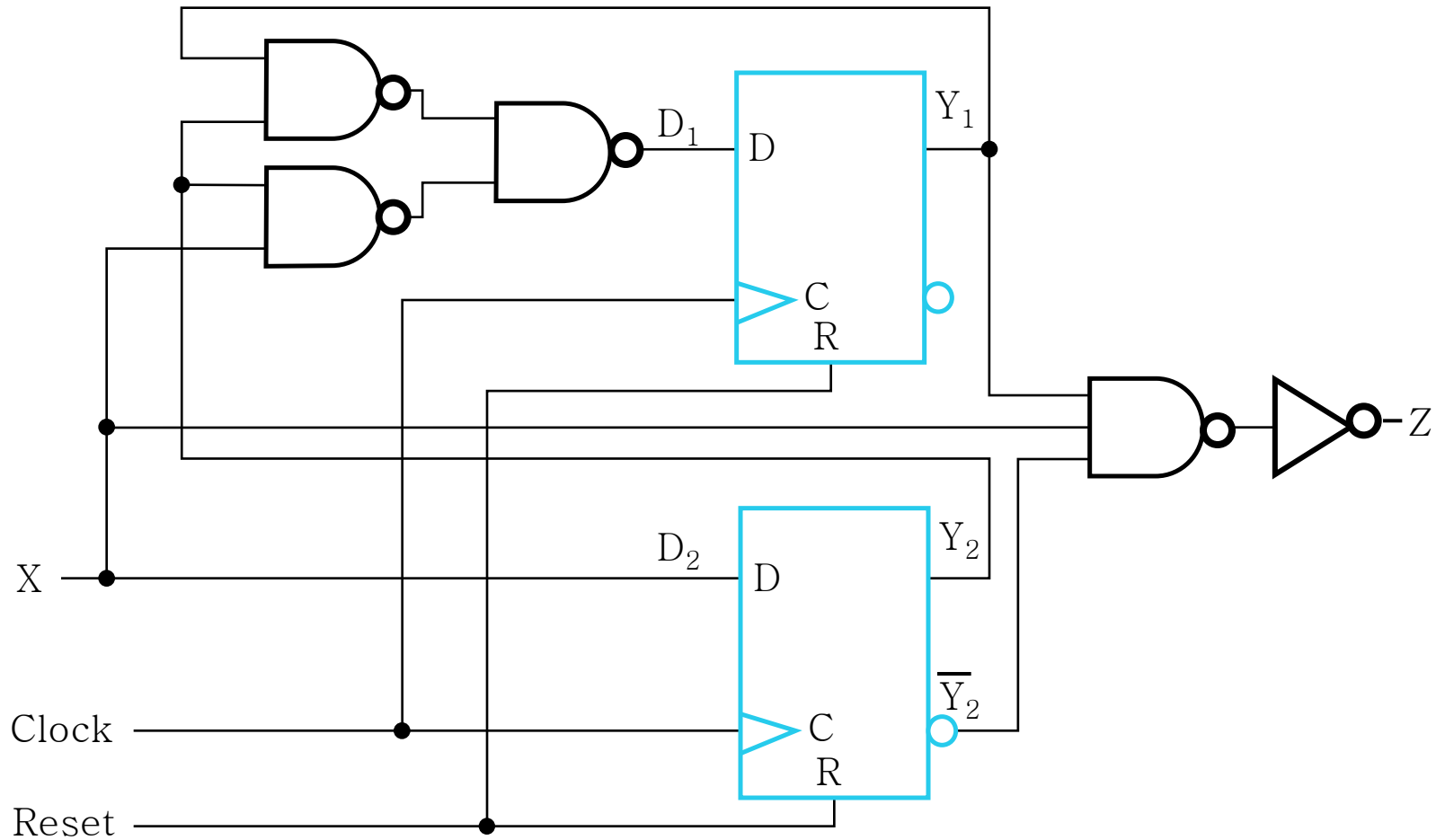

Using SR, JK, and T Flip-Flop Types

- Characteristic table (used in analysis)
 - Defines the next state of the flip-flop in terms of flip-flop inputs and current state
- Characteristic equation (used also in analysis)
 - Obtained from characteristic table
 - Defines the next state of the flip-flop as a Boolean function of the flip-flop inputs and the current state
- Excitation table (used in design)
 - Defines the flip-flop input variable values as function of the current state and next state

SR Flip-Flop

■ Characteristic Table

S	R	Q(t+1)	Operation
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Undefined

■ Excitation Table


Q(t)	Q(t+1)	S	R	Operation
0	0	0	X	No change
0	1	1	0	Set
1	0	0	1	Reset
1	1	X	0	No change

■ Characteristic Equation

$$Q(t+1) = S + \bar{R} Q(t)$$

S R = 0 (S and R cannot be 1 simultaneously)

Symbol

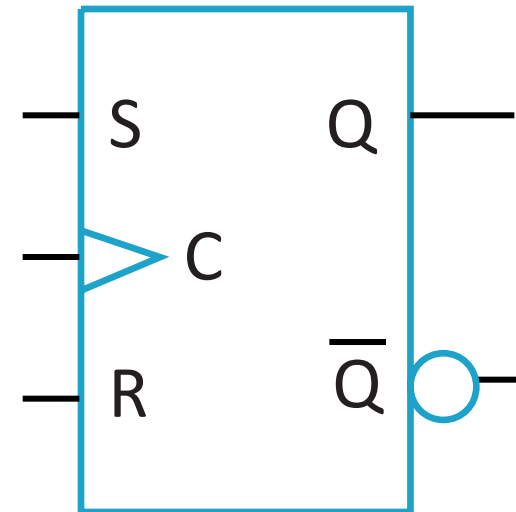

One-Hot Assignment

- Use one flip-flop per state: m states $\Rightarrow m$ flip-flops
 - $Y_3 Y_2 Y_1 Y_0 = 0001$ (state A), 0010 (B), 0100 (C), 1000 (D)
- Flip-flop cost is higher but combinational logic might be simpler
- Provides simplified analysis and design
 - In equations, need to include only the variable that is 1 for the state, e. g., state with code ~~0001~~, is represented in equations by Y_0 instead of $Y_3 Y_2 Y_1 Y_0$ because if Y_0 is '1' then the remaining state variables will be '0'

One-Hot State Assignment

- A = 0001, B = 0010, C = 0100, D = 1000
- The resulting coded state table:

Present State $Y_3 Y_2 Y_1 Y_0$	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
0001	0001	0010	0	0
0010	0001	0100	0	0
0100	1000	0100	0	0
1000	0001	0010	0	1

Optimization: One Hot Assignment

- No need for K-map, flip-flop input equations can be obtained directly from the state table

- Assume D Flip-Flops

$$D_0 = \overline{X}(\overline{Y_0} + Y_1 + Y_3) \text{ or } X \overline{Y_2}$$

$$D_1 = X(\overline{Y_0} + Y_3) = X \overline{Y_1} \overline{Y_2}$$

$$D_2 = X(\overline{Y_1} + Y_2) = X \overline{Y_0} Y_3$$

$$D_3 = X \overline{Y_2}$$

$$Z = XY_3$$


Gate Input Cost = 12

- Total cost = combinational circuit cost + cost of four flip-flops

- Two ways to design clocked sequential circuits
 - Mealy and Moore type sequential circuits

- Mealy type sequential circuit

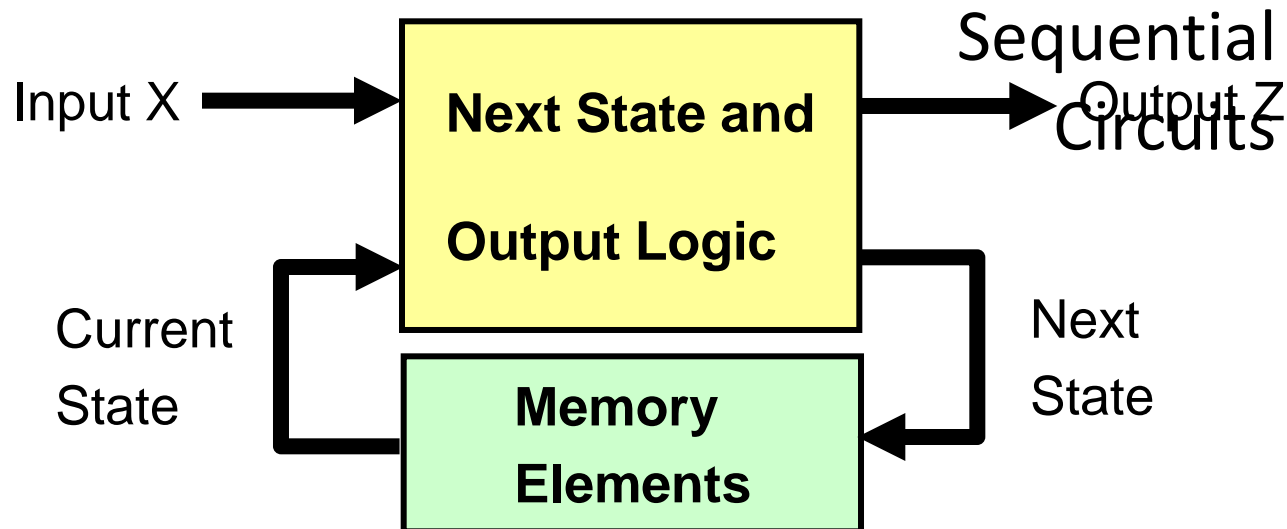
- Output is a function of current state and input



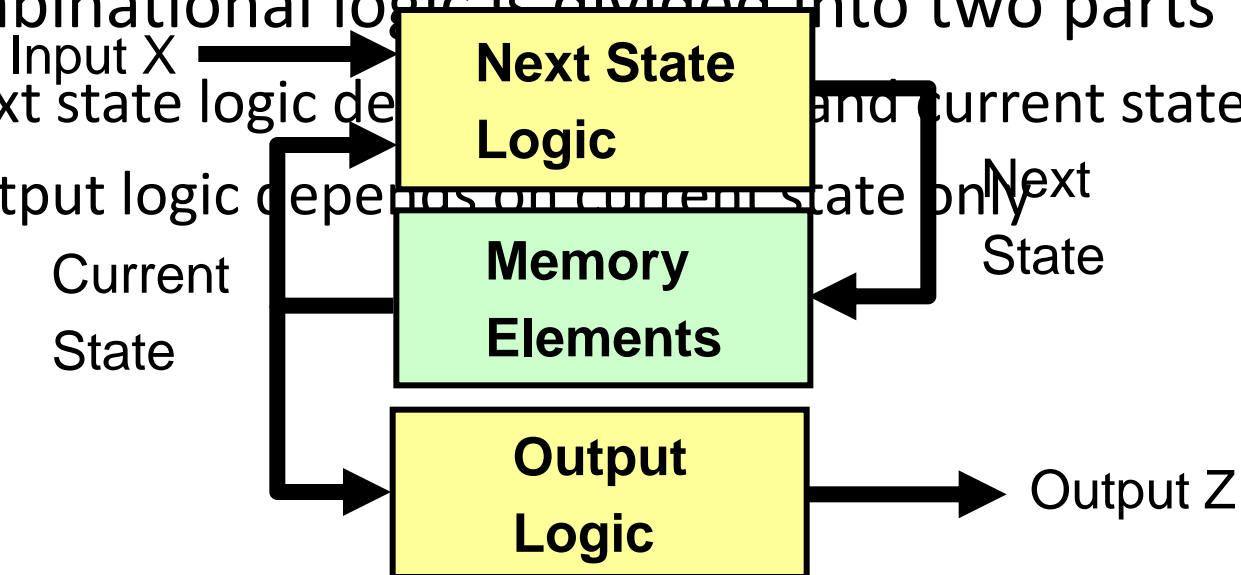- Example: 1101 sequence detector discussed above

Moore Type Sequential Circuits

- Output depends on current state only
 - Output does not depend on input
- Combinational logic is divided into two parts
 - Next state logic depends on current state and current input
 - Output logic depends on current state only




Moore Model for Sequence 1101 Detector


- For the Moore Model, outputs depend on states
- We need to add a state E with output value '1' for the final '1' in the recognized input sequence
 - This new state E, though similar to B, would generate an output of '1' and thus be different from state B
- The Moore model for a sequence recognizer usually has *more states* than the Mealy model

Moore State Diagram

 - We mark **outputs on states** for Moore model
- For Mealy, outputs were marked on arcs
- Arcs now show state transitions and input only
- Add a new state E to produce the output 1
- Note that the new state E produces the same behavior as state B, but gives a different output: '1' rather than '0'



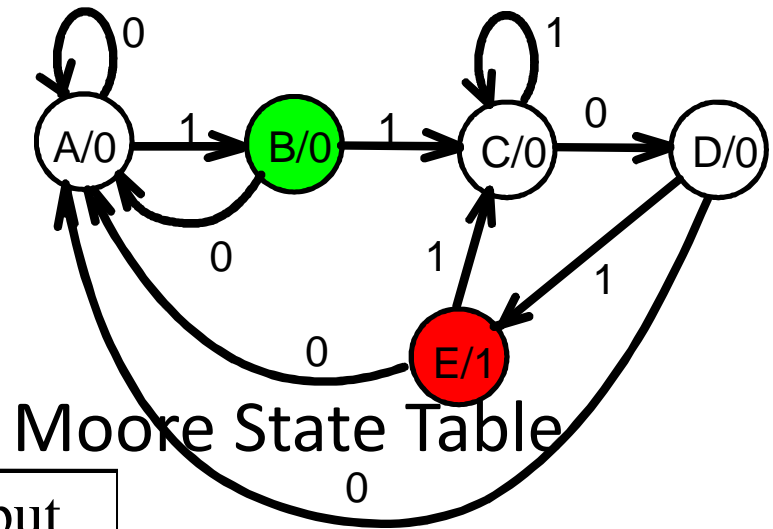- State and output tables are shown below



Moore State Table

Present State	Next State		Output y
	x=0	x=1	
A	A	B	0
B	A	C	0
C	D	C	0
D	A	E	0
E	A	C	1

- Observe that output y does not depend on input x

Moore state diagram typically results in More states

State Assignment for Moore Detector

- As in the previous slide, the sequence of states required to detect the sequence 10000 and output 1 is A-B-C-D-E.
- Using the state assignment

Present State $Y_4 Y_3 Y_2 Y_1 Y_0$	Next State		Output Z
	$x=0$	$x=1$	
A = 0 0 0 0 1	0 0 0 0 1	0 0 0 1 0	0
B = 0 0 0 1 0	0 0 0 0 1	0 0 1 0 0	0
C = 0 0 1 0 0	0 1 0 0 0	0 0 1 0 0	0
D = 0 1 0 0 0	0 0 0 0 1	1 0 0 0 0	0
E = 1 0 0 0 0	0 0 0 0 1	0 0 1 0 0	1

sequence
assignment
required

Equations for Moore Sequence Detector

- Using D Flip Flops, input equations:

$$D_0 = X (Y_0 + Y_1 + Y_3 + Y_4)$$

$$= X Y_2$$

$$D_1 = X Y_0$$

$$D_2 = X (Y_1 + Y_2 + Y_4) = X$$

$$Y_0 Y_3$$

$$D_3 = X Y_2$$


$$D_4 = X Y_3$$

- Output Equation Z

$$Z = Y_4$$

- Gate input cost = 11

Circuit Implementation

 


- Sequential circuits should be verified by showing that the circuit produces the original state diagram
- Verification can be done manually, or with the help of a simulation program
- All possible input combinations are applied at each state and the state variables and outputs are observed
- A reset input is used to reset the circuit to its initial state
- Apply a sequence of inputs to test all the state-input combinations, i.e., all transitions in the state diagram
- Observe the output and the next state that appears after each clock edge in the timing diagram


Input Test Sequence

- An **input test sequence** is required to verify the correct operation of a sequential circuit
- It should **test each state transition** of the state diagram
- Test sequences can be generated from the state diagram
- Consider the Moore sequence detector. Starting at A (after reset), we can generate an input test sequence:

$X = 0101110110011010$

 



Verifying the Moore Sequence Detector

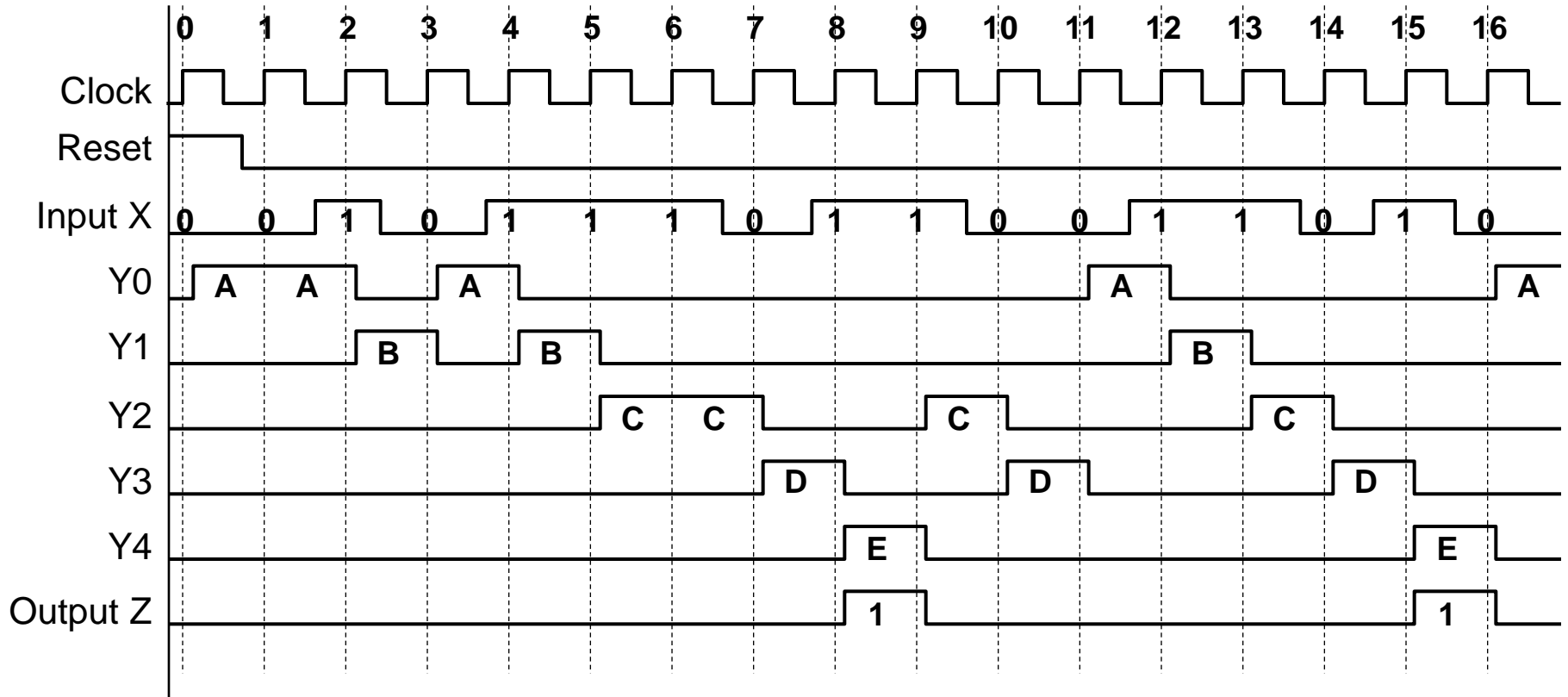

Moore versus Mealy Sequential Circuits

- Output in a Moore sequential circuit is associated with a state, while output in a Mealy circuit is associated with a transition between states
- In general, Moore state diagrams **have more states** than corresponding Mealy state diagrams and the Moore sequential circuit implementation might have higher cost
- Since the output in a Mealy machine is a combination of present state and input values, an **unsynchronized input may result in an invalid output** (drawback of Mealy)
- A Moore state diagram produces a unique output for every state irrespective of inputs. **Output of a Moore machine is synchronized** with the clock (better)

  - To illustrate the drawback of the Mealy machine, consider the design of a '111' sequence detector



State Assignment and Equations

- A minimum of 2 state variables are required
- Using **Gray Code** state assignment and D flip flops

Mealy State Table

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
$Y_1 Y_0$				
A = 0 0	0 0	0 1	0	0
B = 0 1	0 0	1 1	0	0
C = 1 1	0 0	1 1	0	1

- $D_1 = X Y_0$
- $D_0 = X$
- $Z = X Y_1$

Moore State Table

Present State	Next State		Output
	x=0	x=1	Z
$Y_1 Y_0$			
A = 0 0	0 0	0 1	0
B = 0 1	0 0	1 1	0
C = 1 1	0 0	1 0	0
D = 1 0	0 0	1 0	1

- $D_1 = X (Y_0 + Y_1)$
- $D_0 = X \bar{Y}_1 \quad Z = Y_1 \bar{Y}_0$

