 


LECTURE 17


COMBINATIONAL DESIGN USING MSI DEVICES

- PLDs
 - Programmable Logic Devices (PLD)
 - General purpose chip for implementing circuits
 - Can be customized using programmable switches
 - Programmable devices have their functionality programmed before they are first used.
 - Range in complexity from 100's to 10,000's of logic gates.
 - Main types of PLDs
 - ROM
 - PLA
 - PAL Simple/Sequential Prog Logic Devices
 - CPLD (Complex Prog. Logic Devices)
 - FPGA (Field Prog Gate Array)
 - Custom chips: standard cells, sea of gates



- PLD as a Black Box


Inputs
(logic variables)

 


Outputs
(logic functions)


PLD's

 ***Most of these devices
are based on a two level
structure
(sum of products form).***




 

(a) Programmable read-only memory (PROM)

 


(b) Programmable array logic (PAL)

 

 
(c) Programmable logic array (PLA)

- ROM
 - A ROM (Read Only Memory) has a fixed AND plane and a programmable OR plane
 - Size of AND plane is 2^n where n = number of input pins
 - Has an AND gate for every possible minterm so that all input combinations access a different AND gate
 - OR plane dictates function mapped by the ROM




- P input lines: address lines
- 2^P distinct addresses = M locations
- N of bits at each location = Data
- n output lines: word (no of bits stored data)
- CS Signal – Chip Select Signal
- RD Signal – Read Signal

 Address Lines (P) such that $2^P \geq M$ (M is no of locations)




$$F(A,B,C) = \Sigma(0,3,5,6)$$

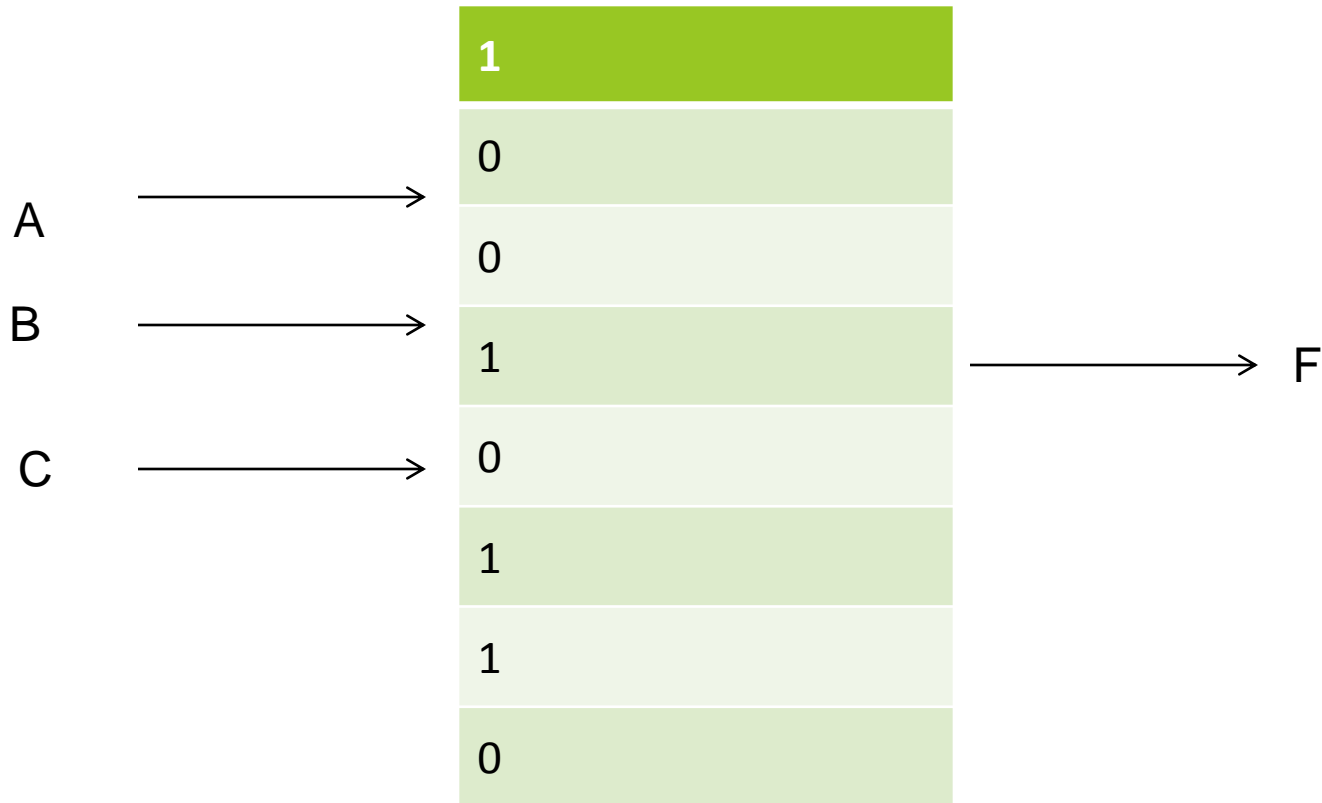


- a $M \times N$ decoder is used to select the location
- plus m OR gates
- can be used to implement any Boolean functions of n input variables
- a fixed AND array and a programmable OR array

- 4x4 ROM

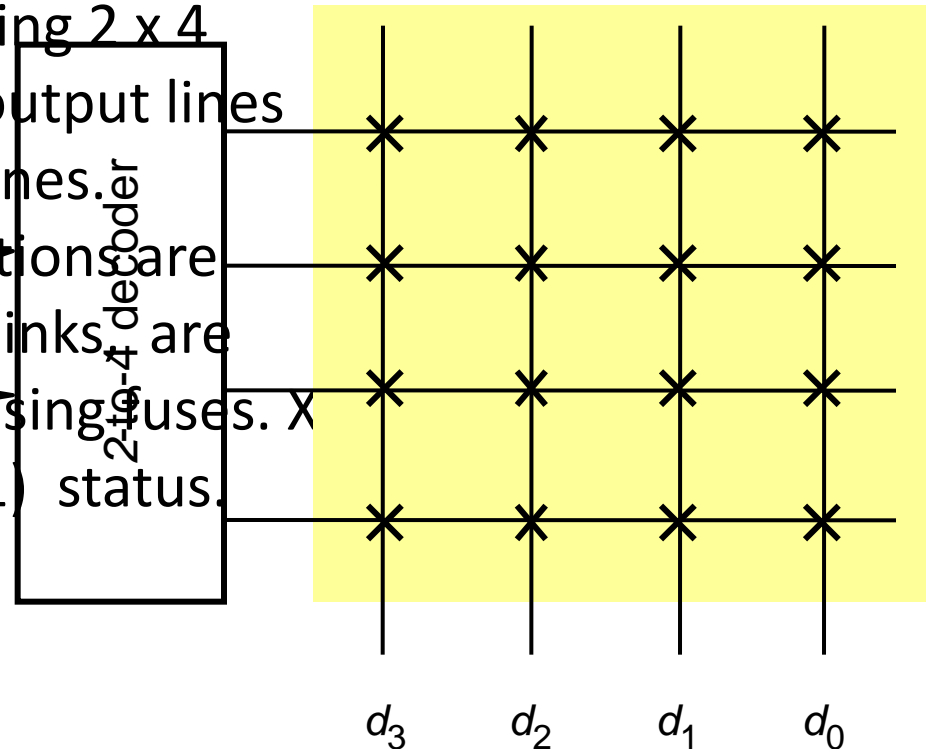- 4x4 ROM has 4 addresses that are decoded using 2 x 4 Decoder, 4 output lines and 4 data lines. Interconnections are called Crosslinks, are connected using fuses. X shows ON (1) status.



▪ A 32x4 ROM

 

- combinational logic Circuit implementation

- store the truth table in a ROM

A_1	A_0	F_1	F_2
0	0	0	1
0	1	1	0
1	0	1	1
1	1	1	0

(a) Truth table


 
 


TABLE 5-5
Truth Table for Circuit of Example 5-3

Inputs			Outputs							Decimal
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0		
0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	1	1
0	1	0	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	0	1	9
1	0	0	0	1	0	0	0	0	0	16
1	0	1	0	1	1	0	0	0	1	25
1	1	0	1	0	0	1	0	0	0	36
1	1	1	1	1	0	0	0	0	1	49

 

(a) Block diagram


A_2	A_1	A_0	F_1	F_2	F_3	F_4
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table

- Types of ROMs
 - mask programming ROM
 - IC manufacturers
 - is economical only if large quantities
 - PROM: Programmable ROM
 - fuses
 - universal programmer
 - EPROM: erasable PROM
 - floating gate
 - ultraviolet light erasable
 - EEPROM: electrically erasable PROM
 - longer time is needed to write
 - flash ROM
 - limited times of write operations


- Programmable Logic Array (PLA) – (Both Array are programmable)

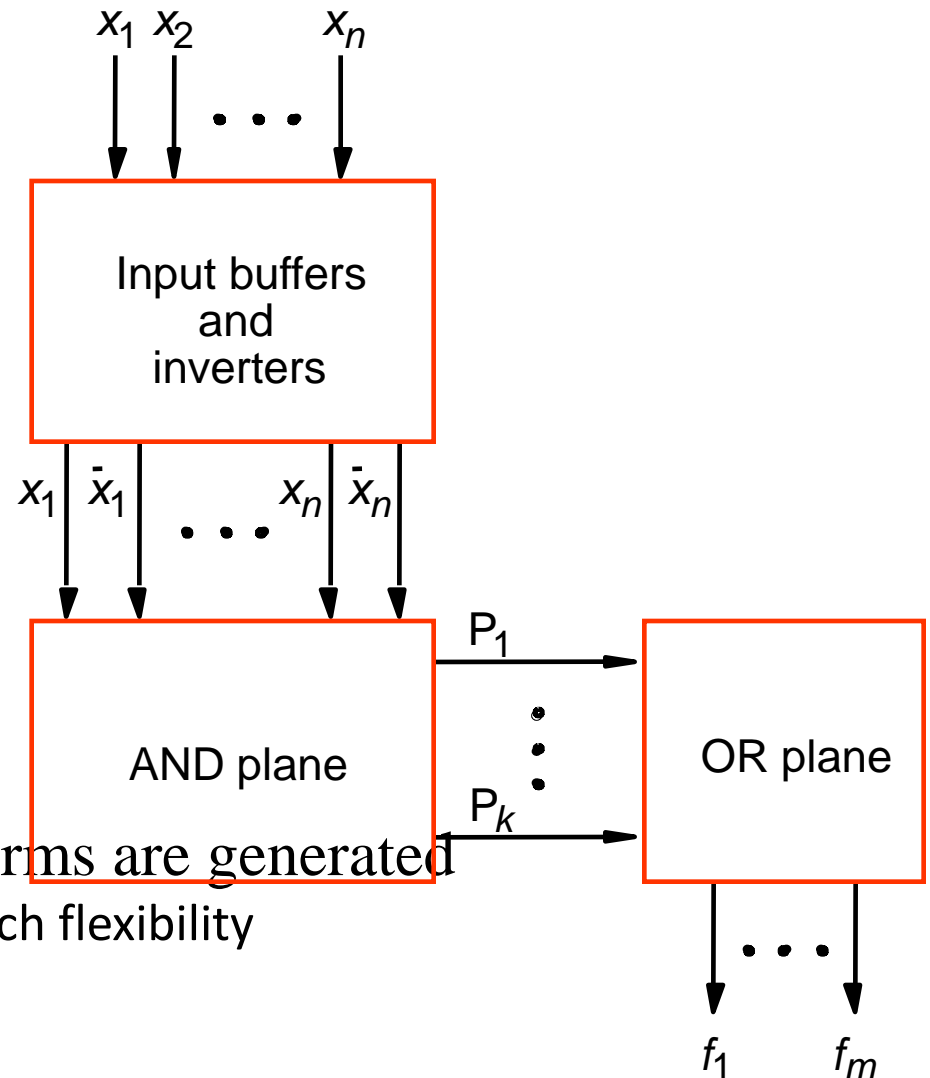- Use to implement circuits in SOP form
- The connections in the AND plane are programmable
- The connections in the OR plane are programmable



- Many applications don't require such flexibility


PLA

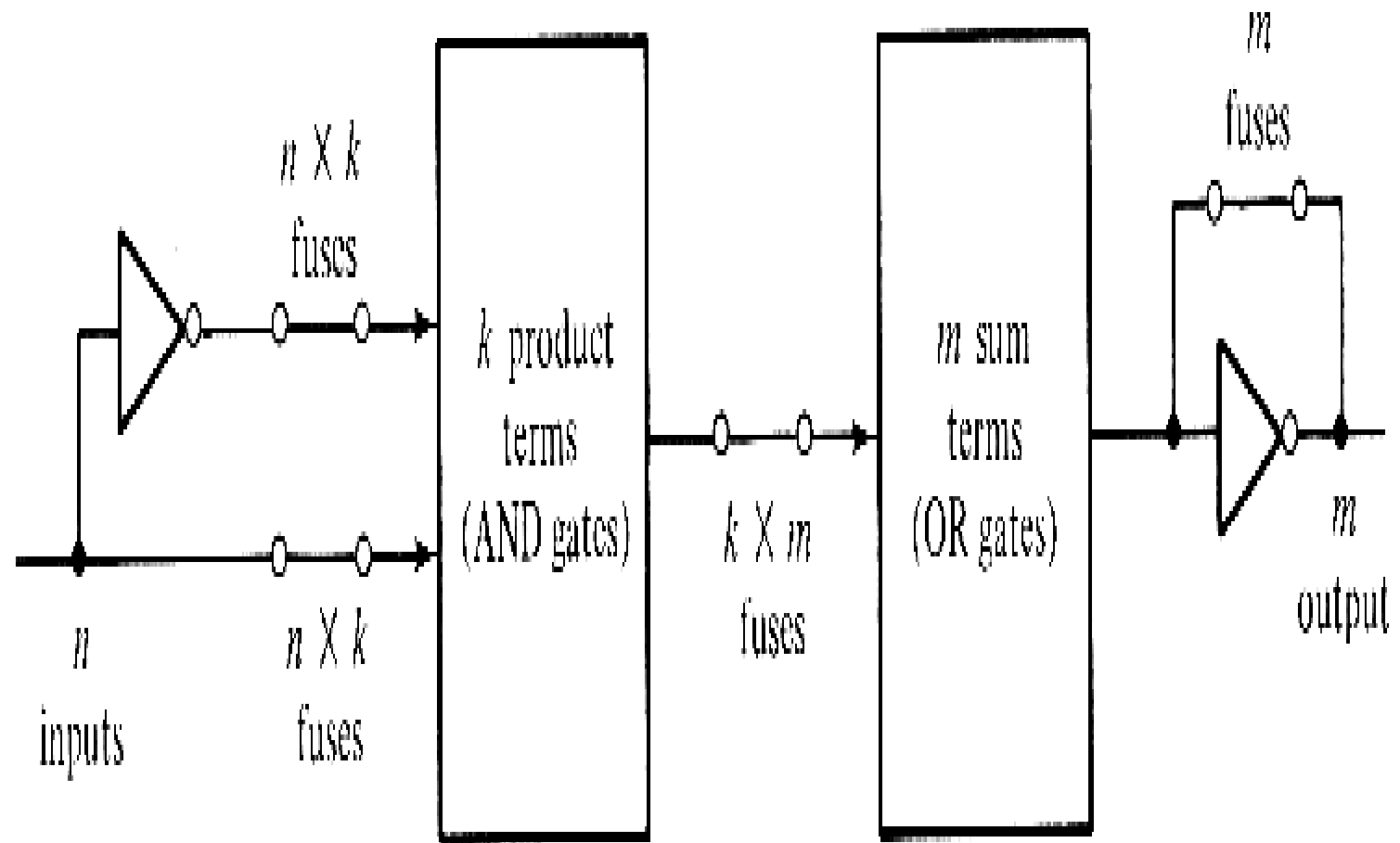

$$f_1 = x_1x_2 + x_1x_3' + x_1'x_2'x_3$$

▪ Gate Level Version of PLA


$$f_2 = x_1x_2 + x_1'x_2'x_3 + x_1x_3$$

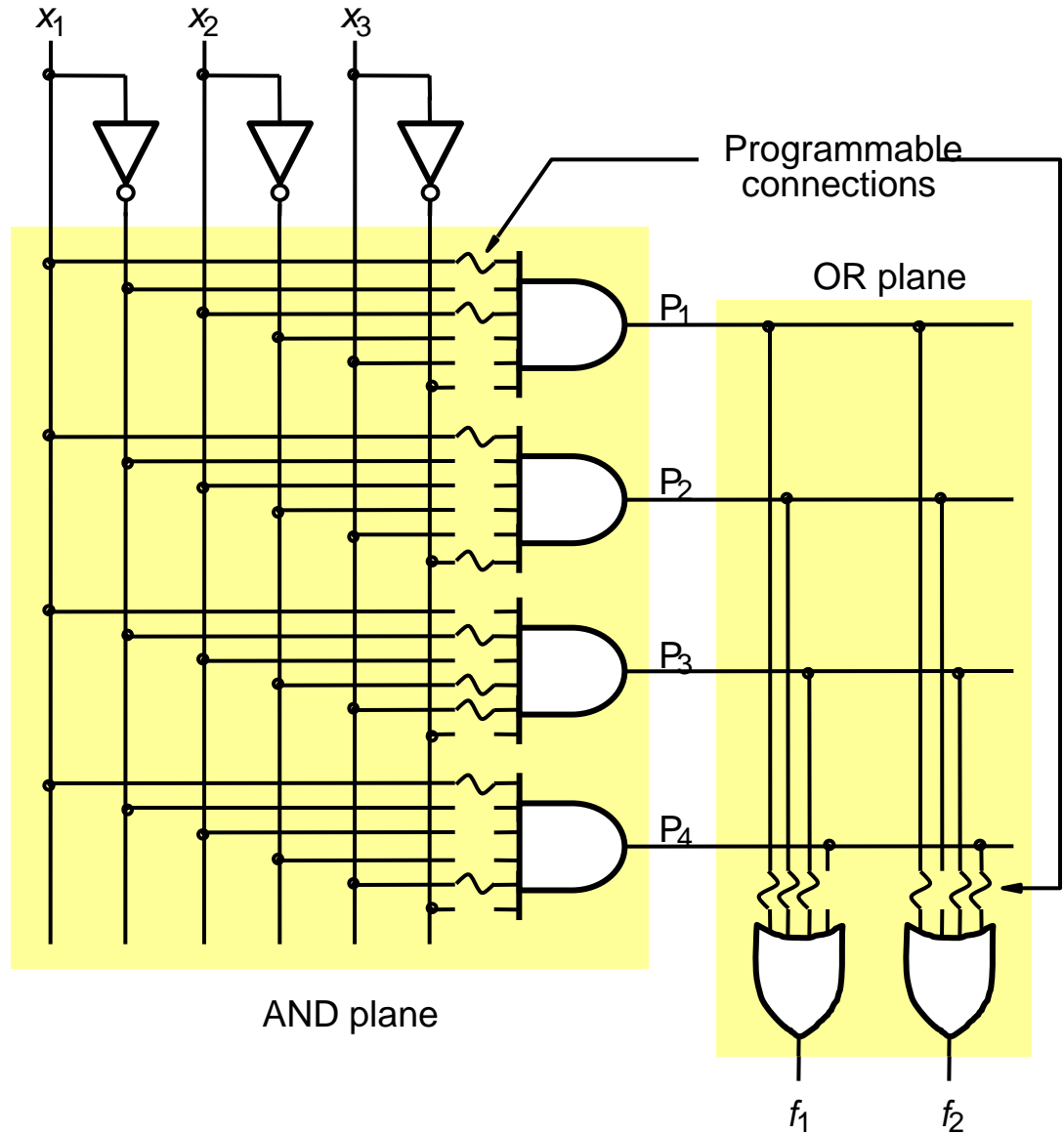

$$f_1 = x_1x_2 + x_1x_3' + x_1'x_2'x_3$$

▪ Customary Schematic of

$$f_2 = x_1x_2 + x_1'x_2'x_3 + x_1x_3$$

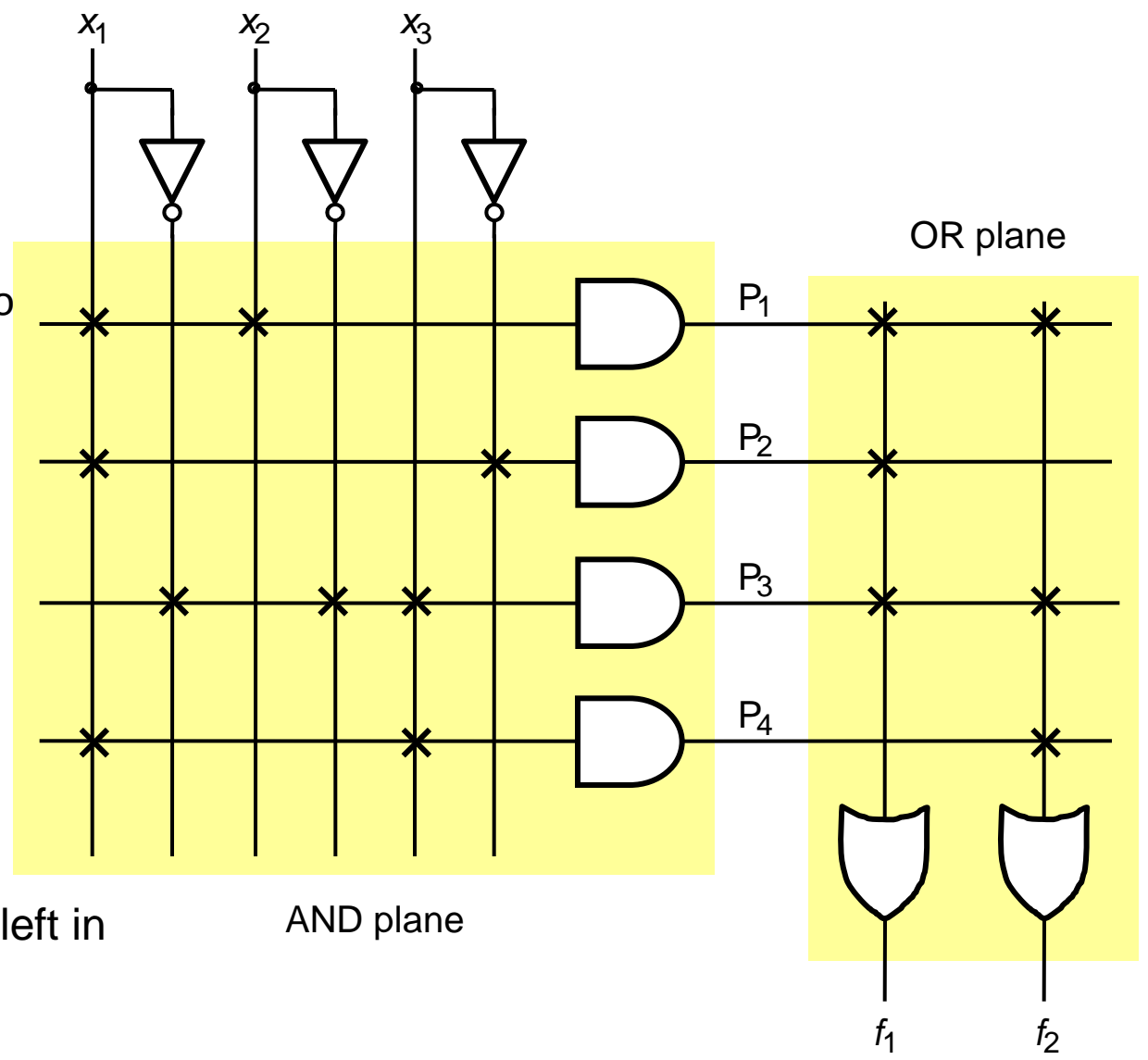

x marks the connections left in place after programming

Advantages of PLA:

- Both AND and OR array are programmable,
- It gives flexibility for implementation of Logic design.
- Included as a part of larger chips such as microprocessors.
- Power requirement is less than ROM.
- Cost is also less.

Disadvantages:

Simplification of boolean expression is required.