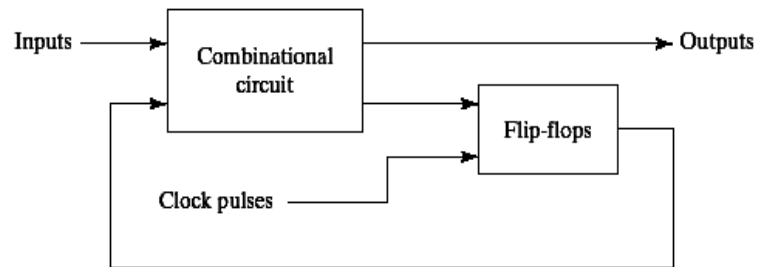


LECTURE 18

Digital Logic Families

Synchronous Sequential Circuits

- The change of internal state occurs in response to the synchronized clock pulses.
- The memory elements are flip-flops.



(a) Block diagram



Asynchronous Sequential Circuits


Asynchronous sequential circuits

- Internal states can change at any instant of time when there is a change in the input variables
- No clock signal is required
- Have better performance but hard to design due to timing

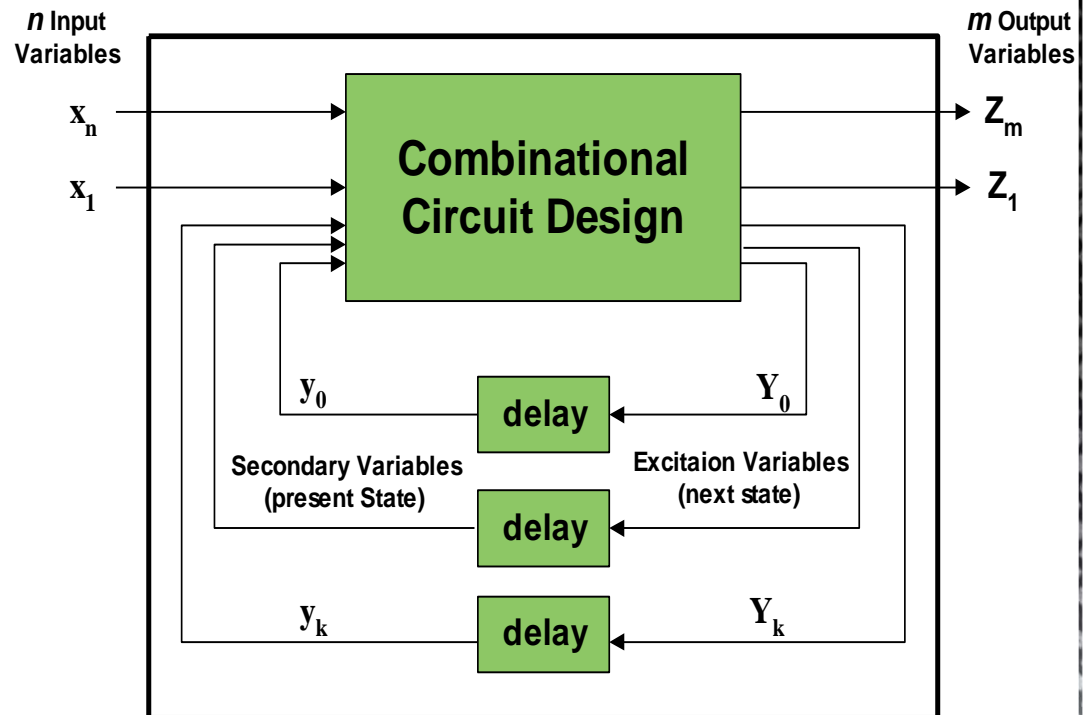problems.

The memory elements are either unclocked FF's or time-delay elements.

-The design of these circuits is more difficult than the design of synchronous circuits due to the timing problem.




Why Asynchronous Circuits?

- 1- Accelerate the speed of the machine (no need to wait for the next clock pulse).
- 2-Used when the input signals change independently of the clock pulses.
- 3- Simplify the circuit in the small independent circuits.
- 4- Used to communicate two circuits each have its own clock.

Asynchronous Circuits

- The delay elements provide short-term memory for the sequential circuits.
- Present state variables $[y_1..y_k]$ are called secondary variables
- Next state variables $[Y_1..Y_k]$ are called excitation variables.
- When an input variable changes, it takes a certain time to propagate through the combinational circuit to change Y , and then Y takes a certain time to propagate through the delay element to become a new state.

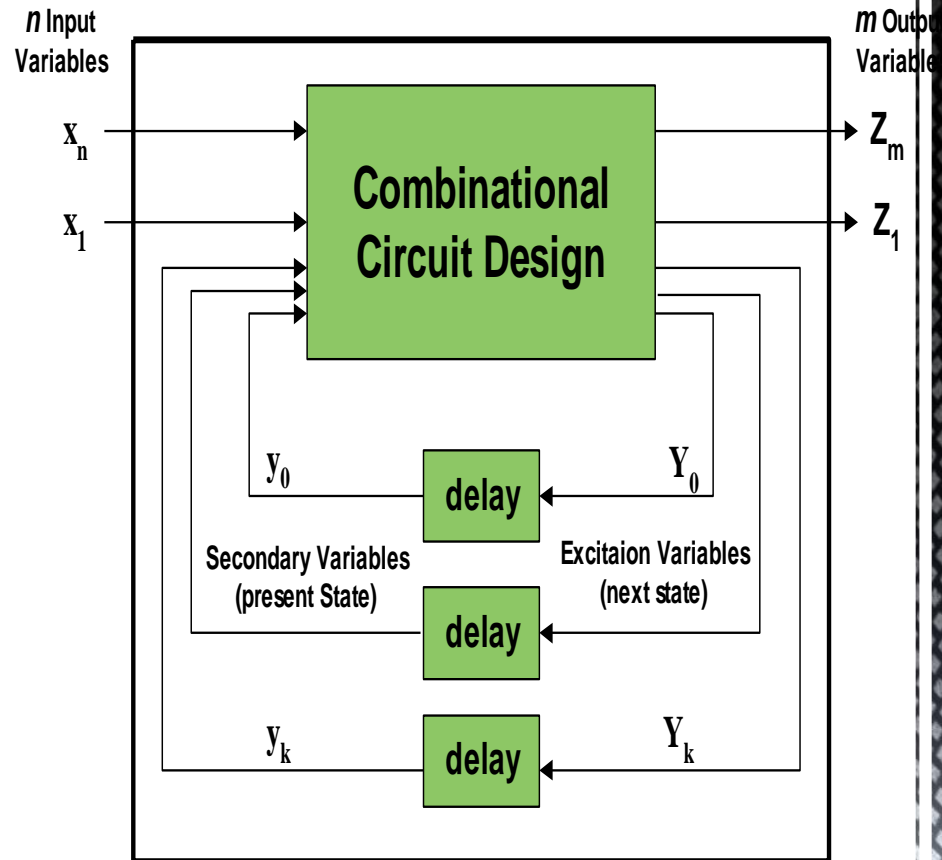

Asynchronous Circuits

- The circuit reaches a steady-state condition when $y_i = Y_i$ for $i=1,2,\dots,K$.
- Stable System:
for a given value of input variables, the system is stable if the circuit reaches a steady state condition.
- Fundamental-mode operation:
this mode assumes that the one input signal changes at a time and only when the circuit is in stable condition.
- The time between two input changes must be longer than the time it takes the circuit to reach a stable state.

Analysis Procedure

The analysis consists of obtaining a table or a diagram that describes the sequence of internal states and outputs as a function of changes in the input variables.

Transition Table

Flow Table

Stability Consideration

Transition Table

Transition table is useful to analyze an asynchronous circuit from the circuit diagram Procedure to obtain transition table:

1. Determine all feedback loops in the circuits
2. Mark the input (y_i) and output (Y_i) of each feedback loop
3. Derive the Boolean functions of all Y 's
4. Plot each Y function in a map and combine all maps into one table
5. Circle those values of Y in each square that are equal to the value of y in the same row


Transition Table

$y_1 y_2$	x	
	0	1
00	0	0
01	1	0
11	1	1
10	0	1

(a) Map for
 $Y_1 = xy_1 + x'y_2$


$y_1 y_2$	x	
	0	1
00	0	1
01	1	1
11	1	0
10	0	0

(b) Map for
 $Y_2 = xy'_1 + x'y_2$

 


$$Y_1 = xy_1 + x'y_2$$

$$Y_2 = xy'_1 + x'y_2$$

- If $y=00$ and $x=0$  $Y == 00$
(Stable)
- If x changes from 0 to 1 while $y=00$, the circuit changes Y to 01 which is temporary unstable condition ($Y \neq y$)
- As soon as the signal propagates to make $Y = 01$, the feedback path causes a change in y to 01. (transition from the first row to the second row)
- If the input repeatedly alternates between 0 and 1, the circuit will repeat the sequence of states

		x	
		0	1
$y_1 y_2$	00	00	01
	01	11	01
	11	11	10
	10	00	10


 $00 \rightarrow 01 \rightarrow 11 \rightarrow 10$

Transition Table

In an asynchronous sequential circuit, the internal state can change immediately after a change in the input.

It is sometimes convenient to combine the internal state with input

value together and call it the **Total State of the circuit.**

(Total state = Internal state + Inputs)

In the last example , the circuit has

- **4 stable total states: ($y_1y_2x= 000, 011, 110, \text{ and } 101$)**
- **4 unstable total states: ($y_1y_2x= 001, 010, 111, \text{ and } 100$)**

Flow Table

- A flow table is similar to a transition table except that the internal state are symbolized with letters rather than binary numbers.

- It also includes the output values of the circuit for each stable state.

	x	
	0	1
a	a	b
b	c	b
c	c	d
d	a	d

(a) Four states with one input

	$x_1 x_2$			
	00	01	11	10
a	$a, 0$	$a, 0$	$a, 0$	$b, 0$
b	$a, 0$	$a, 0$	$b, 1$	$b, 0$

(b) Two states with two inputs and one output

Flow Table


- In order to obtain the circuit described by a flow table, it is necessary to convert the flow table into a transition table from which we can derive the logic diagram .

		$x_1 x_2$			
		00	01	11	10
y	0	0	0	0	1
	1	0	0	1	1

(a) Transition table
 $Y = x_1 x_2' + x_1 y$

		$x_1 x_2$			
		00	01	11	10
y	0	0	0	0	0
	1	0	0	1	0

(b) Map for output
 $z = x_1 x_2 y$

 

(c) Logic diagram

- This can be done through the assignme of a distinct binary value to each state.

Two or more binary state variables will change value when one input variable changes.

Cannot predict state sequence if unequal delay is encountered.

Non-critical race: The final stable state does not depend on the change order of state variables

Critical race: The change order of state variables will result in different stable states
Should be avoided !!

F

		x	
		0	1
y ₁ y ₂	00	00	11
	01		11
	11		11
	10		11

(a) Possible transitions:

00 → 11
00 → 01 → 11
00 → 10 → 11

		x	
		0	1
y ₁ y ₂	00	00	11
	01		01
	11		01
	10		11

(b) Possible transitions:

00 → 11 → 01
00 → 01
00 → 10 → 11 → 01

		x	
		0	1
y ₁ y ₂	00	00	11
	01		01
	11		11
	10		10

(a) Possible transitions:

00 → 11
00 → 01
00 → 10

		x	
		0	1
y ₁ y ₂	00	00	11
	01		11
	11		11
	10		10

(b) Possible transitions:

00 → 11
00 → 01 → 11
00 → 10

Race Solution

It can be solved by making a proper binary assignment to the state variables.

The state variables must be assigned binary numbers in such a way that only one state variable can change at any one time when a state transition occurs in the flow table.

It will be discussed later.

		x	
		0	1
y ₁ y ₂	00	00	01
	01		11
	11		10
	10		10

(a) State transition:
00 → 01 → 11 → 10

		x	
		0	1
y ₁ y ₂	00	00	01
	01		11
	11		11
	10		10

(b) State transition:
00 → 01 → 11

		x	
		0	1
y ₁ y ₂	00	00	01
	01		11
	11		10
	10		01

(c) Unstable
→ 01 → 11 → 10 →

Stability Check

Asynchronous sequential circuits may oscillate between unstable states due to the feedback


-Must check for stability to ensure proper operations

Can be easily checked from the transition table

-Any column has no stable state  unstable

-Ex: when $x_1x_2=11$ in Fig. 9-9(b), Y and y are never the same

$$Y = x_1'x_2 + x_2y'$$

 

(a) Logic diagram


		$x_1 x_2$			
		00	01	11	10
y	0	0	1	1	0
	1	0	1	0	0

(b) Transition table

Latches in Asynchronous Circuits

- The traditional configuration of asynchronous circuits is using one or more feedback loops
 - No real delay elements.
- It is more convenient to employ the SR latch as a memory element in asynchronous circuits
 - Produce an orderly pattern in the logic diagram with the memory elements clearly visible.
- SR latch is also an asynchronous circuit
 - Will be analyzed first using the method for asynchronous circuits.


SR Latch with NOR Gates

 

(a) Crossed-coupled circuit

S	R	Q	Q'	
1	0	1	0	
0	0	1	0	(After $SR = 10$)
0	1	0	1	
0	0	0	1	(After $SR = 01$)
1	1	0	0	

(b) Truth table

 

(c) Circuit showing feedback

		SR			
		00	01	11	10
y	0	0	0	0	1
	1	1	0	0	1

$S=1, R=1$ ($SR = 1$)
should not be used
 $\Rightarrow SR = 0$ is
normal mode


$$Y = SR' + R'y$$

$$Y = S + R'y \text{ when } SR = 0$$

*** should be carefully checked first**

(d) Transition table

SR Latch with NAND Gates

 


(a) Crossed-coupled circuit

S	R	Q	Q'
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1

(After $SR = 10$)

(After $SR = 01$)

(b) Truth table

 

(c) Circuit showing feedback

		SR			
		00	01	11	10
y	0	1	1	0	0
	1	1	1	1	0

$Y = S' + Ry$ when $S'R' = 0$

(d) Transition table

$S=1, R=1$ ($SR = 1$)
 should not be used
 $\Rightarrow SR = 0$ is
 normal mode


* **should be carefully checked first**

Analysis Procedure

Analysis Procedure for NOR latch based asynchronous circuit

- (i) Label each latch o/p with Y_i and feed back path with y_i
- (ii) Derive Boolean functions for S_i and R_i
- (iii) Check $SR = 0$ for each NOR latch
- (iv) Evaluate $Y = S + R'y$ for each latch
- (v) Construct the transition table
- (vi) Circle all stable states

Analysis Example

 

Analysis Example

The procedure for analyzing an asynchronous sequential circuit with SR latches can be summarized as follows:

1. Label each latch output with Y_i and its external feedback path with y_i for $i=1,2,\dots,k$
2. Derive the Boolean functions for the S_i and R_i inputs in each latch.

$$S_1 = x_1 y_2 \qquad S_2 = x_1 x_2$$

$$R_1 = x_1' x_2' \qquad R_2 = x_2' y_1$$

Analysis Example

3. Check whether $SR = 0$ for each NOR latch or whether $S'R' = 0$ for each NAND latch. (if either of these two conditions is not satisfied, there is a possibility that the circuit may not operate properly)
- $$S_1 R_1 = x_1 y_2 x_1 x_2 = 0$$
- $$S_2 R_2 = x_1 x_2 x_2 y_1 = 0$$

4. Evaluate $Y = S + R'y$ for each NOR latch or $Y = S' + Ry$ for each NAND latch.
- $$Y_1 = S_1 + R_1' y_1 = x_1 y_2 + (x_1 + x_2) y_1 = x_1 y_2 + x_1 y_1 + x_2 y_2$$

$$Y_2 = S_2 + R_2' y_2 = x_1 x_2 + (x_2 + y_1') y_2 = x_1 x_2 + x_2 y_2 + y_1' y_2$$

Analysis Example

- Construct a map, with the y 's representing the rows and the x inputs representing the columns.
- Plot the value of $Y=Y_1Y_2\dots Y_k$ in the map.
- Circle all stable states such that $Y=y$. the result is then the transition table.

- The transition table shows that the circuit is **stable**
- Race Conditions: there is a **critical race** condition when the circuit is initially in total state $y_1y_2x_1x_2 = \underline{1101}$ and x_2 changes from 1 to 0.
 - The circuit should go to the total state 0000.
 - If Y_1 changes to 0 before Y_2 , the circuit goes to total state 0100 instead of 0000.

	x_1x_2			
y_1y_2	00	01	11	10
00	00	00	01	00
01	01	01	11	11
11	00	11	11	10
10	00	10	11	10

Transition Table

Implementation Procedure

Procedure to implement an asynchronous sequential circuits with SR latches:

1. Given a transition table that specifies the excitation function $Y = Y_1Y_2...Y_k$, derive a pair of maps for each S_i and R_i using the latch excitation table
2. Derive the Boolean functions for each S_i and R_i (do not to make S_i and R_i equal to 1 in the same minterm square)
3. Draw the logic diagram using k latches together with the gates required to generate the S and R (for NAND latch, use the complemented values in step 2)

Implementation Procedure

Latch Excitation Table

- During the implementation process, the transition table of the circuit is available and we wish to find the values of S and R .
- Excitation table: Lists the required inputs S and R for each of the possible transition from y to Y .

y	Y	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	1

Implementation Example

- Given a transition table that specifies the excitation function procedure for implementing a circuit summarized as follows:

	x_1x_2			
y	00	01	11	10
0	0	0	0	1
1	0	0	1	1

(a) Transition table

$$Y = x_1x'_2 + x_1y$$

Implementation Example

1. Derive a pair of maps for S_i and R_i for each $i = 1, 2, \dots, k$. (This is done by using the latch excitation table)

		x_1x_2			
		00	01	11	10
y	0	0	0	0	1
	1	0	0	X	X

(c) Map for $S = x_1x'_2$


		x_1x_2			
		00	01	11	10
y	0	X	X	X	0
	1	1	1	0	0

(d) Map for $R = x'_1$


Implementation Example

	NOR Latch	NAND Latch
S=	$x_1x'_2$	$(x_1x'_2)'$
R=	x'_1	x_1

 2. Draw the logic diagram, using k latches together with the gates required to generate the S and R Boolean functions obtained in step1 (for NAND latches, use the complemented value



(e) Circuit with NOR latch

 

(f) Circuit with NAND latch