

Dronacharya College of Engineering, Gurgaon

Department of Electronics and Computers Engineering

Subject: Digital Electronics(EC-412-F)

Semester/Branch: IV ECS

Short Answer questions

Section A

- Q1 Combinational circuits are adders, subtractors, multiplexers, demultiplexer, magnitude comparator, parity generator/checker etc.
- Q2. Arithmetic circuits are used for addition, subtraction multiplication division
- Q3. Half adder is used for addition of two binary numbers.
- Q4. Full adder is used to perform addition of more than 2 bits
- Q5. Serial adder require one full adder for one additional bit while parallel adders requires N full adders for n bit addition.

Section B

- Q1 Two more adders are look ahead carry adder why?.
- Q2 Half subtractor subtracts two numbers we get 2 output variables i e difference and borrow give demonstration.
- Q3 Full subtractor is subtraction of 3 bits how?.
- Q4 Encoder converts human language into machine language give examples.
- Q5 Decoder is used to convert machine language to human language give examples.
- Q6 Multiplexers are universal circuits which selects one input out of multiple inputs and give it as a result, prove it by taking an example.
- Q7 Demultiplexer receives information on single line and distribute to the 2 lines where n are selection lines.


Section C

Q 1. List the applications of decoders.

- Ans.**
- 1 Decoders are used in counter systems
 2. Decoders are used for A/D conversion.
 - 3 Decoders are used for D/A conversion
 4. Decoders are used in seven segment digital displays.


Q 2 Give functional block diagram of 2 1 MUX

Ans.

 

 Q 3 Explain half subtractor with the help of its internal circuit

Ans. To subtract two numbers i e two Input variables A and B we get two output variable i e difference 'D' and borrow 'Bo' It is known as half subtractor Functional diagram is shown:



Its truth table is as shown:


Inputs		Outputs	
A	B	D	B ₀
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Thus, the minimized logic functions are:

$$D = \bar{A}B + A\bar{B} = A \oplus B$$

$$B_0 = \bar{A}B$$


The circuit diagram is as shown:

 

Q 4. Implement half adder circuit using 4 : 1 MUX or multiplexers only.

Ans. Truth table of half adder is as shown:

Inputs		Outputs	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

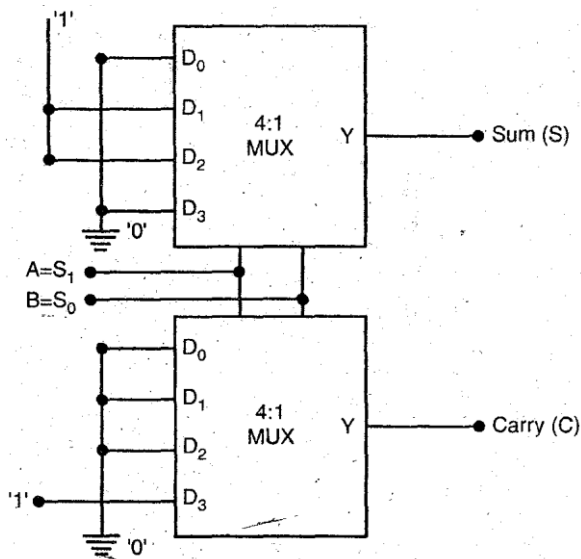

Section D

Q1. Design 3 bit Gray Code to binary converters

Ans. The truth table for 3 bit Gray Code to binary conversion is as shown:

Decimal Equipment	Gray Code			Binary Code		
	G ₂	G ₁	G ₀	B ₂	B ₁	B ₀
0	0	0	0	0	0	0
1	0	0	1	0	0	1
3	0	1	1	0	1	0
2	0	1	0	0	1	1
6	1	1	0	1	0	0
7	1	1	1	1	0	1
5	1	0	1	1	1	0
4	1	0	0	1	1	1

K-Maps:

For B₂:

		G ₁ G ₀				
		$\bar{G}_1\bar{G}_0$	\bar{G}_1G_0	G_1G_0	$G_1\bar{G}_0$	
G ₂	\bar{G}_2	0 0	0 1	0 3	0 2	∴ B ₂ = G ₂
	G ₂	1 4	1 5	1 7	1 6	


For B₁:

		G ₁ G ₀				
		$\bar{G}_1\bar{G}_0$	\bar{G}_1G_0	G_1G_0	$G_1\bar{G}_0$	
G ₂	\bar{G}_2	0 0	0 1	1 3	1 2	∴ B ₁ = $\bar{G}_2G_1 + G_2\bar{G}_1$ B ₁ = G ₁ ⊕ G ₂
	G ₂	1 4	1 5	0 7	0 6	

For B₀:

		G ₁ G ₀				
		$\bar{G}_1\bar{G}_0$	\bar{G}_1G_0	G_1G_0	$G_1\bar{G}_0$	
G ₂	\bar{G}_2	0 0	1 1	0 3	1 2	∴ B ₀ = $\bar{G}_2\bar{G}_1G_0 + \bar{G}_2G_1\bar{G}_0 + G_2\bar{G}_1\bar{G}_0 + G_2G_1G_0$ = $\bar{G}_2(\bar{G}_1G_0 + G_1\bar{G}_0) + G_2(\bar{G}_1\bar{G}_0 + G_1G_0)$ = $\bar{G}_2(G_1 \oplus G_0) + G_2(G_1 \odot G_0)$ = $\bar{G}_2(G_1 \oplus G_0) + G_2(\overline{G_1 \oplus G_0})$ ∴ B ₀ = G ₁ ⊕ G ₀ ⊕ G ₂
	G ₂	1 4	0 5	1 7	0 6	

Circuit Implementation is as shown:

 

Q 2. Design BCD to Excess-3 code converter.

Ans. BCD to Excess-3 Code Converter:

The input variables are BCD's (A, B, C and D) and output variables are excess-3 code (E3, E2, E1 and E0)

