



# Control Systems




# **Lecture: 2**

# **Mathematical Modelling**
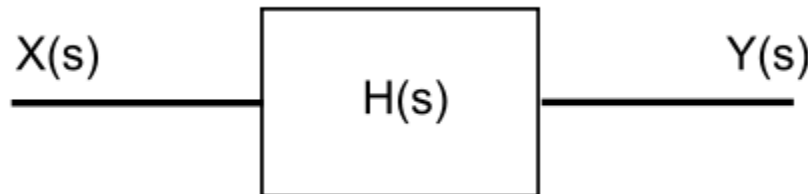
## Definition of Transfer Function

- Transfer Function reveals how the circuit modifies the input amplitude in creating output amplitude.
- Therefore, transfer function describes how the circuit processes the input to produce output.



$$H(s) = \frac{Y(s)}{X(s)}$$

Transfer Function is the ratio of the output of a system to the input of a system, in the Laplace domain considering its initial conditions to be zero.

# Frequency Domain

Resistor

$$V(s) = RI(s)$$

$$V = RI$$



Inductor

$$V(s) = sLI(s)$$


$$V = sLI$$



Capacitor

$$V(s) = \frac{1}{sC}I(s)$$

$$V = \frac{1}{sC}I$$

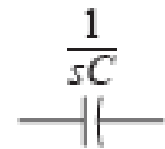

$$v_R(t) = Ri(t)$$

$$V_R(s) = RI(s)$$

$$v_L(t) = L \frac{di}{dt}$$

$$V_L(s) = sLI(s)$$

$$v_C(t) = \frac{1}{C} \int idt$$

$$V_C(s) = \frac{1}{sC} I(s)$$

**Time constants:**

$$T_{RC} = RC = \frac{V}{A} \frac{Q}{V} = \frac{VQ}{\frac{Q}{\text{sec}} V} = \text{sec}$$

$$T_{RL} = \frac{L}{R} = \frac{\frac{V}{A}}{\frac{\text{sec}}{V}} = \text{sec}$$

# Frequency Domain

Resistor

$$V(s) = RI(s)$$

$$V = RI$$



Inductor

$$V(s) = sLI(s)$$


$$V = sLI$$



Capacitor


$$V(s) = \frac{1}{sC}I(s)$$

$$V = \frac{1}{sC}I$$

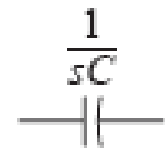
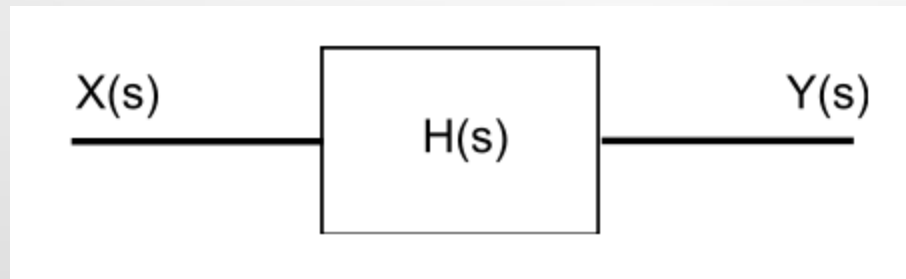
# Definition of Transfer Function

Transfer Function is the ratio of the output of a system to the input of a system, in the Laplace domain considering its initial conditions to be zero.



$$H(s) = \frac{Y(s)}{X(s)}$$

# Frequency Domain

Resistor

$$V(s) = RI(s)$$

$$V = RI$$



Inductor

$$V(s) = sLI(s)$$


$$V = sLI$$



Capacitor

$$V(s) = \frac{1}{sC}I(s)$$

$$V = \frac{1}{sC}I$$

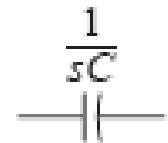


$$\frac{V(s)}{I(s)} = R$$

$$\frac{V(s)}{I(s)} = sL$$

$$\frac{V(s)}{I(s)} = \frac{1}{sC}$$




# Impedances in series

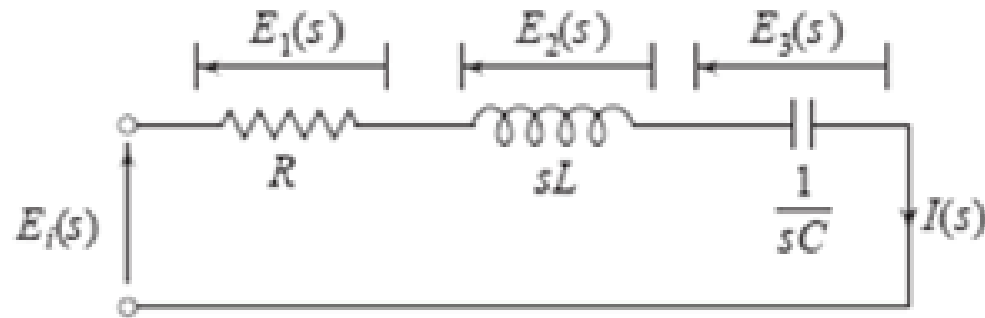

(a)


$$Z(s)_{eq} = \frac{E_i(s)}{I(s)} = R + \frac{1}{sC} + Ls$$

# Impedances in parallel

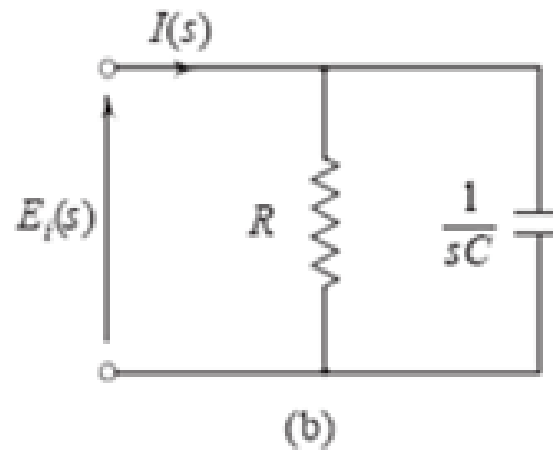

$$Z(s)_{\text{eq}} = \frac{E_i(s)}{I(s)} = \frac{R}{C \left( R + \frac{1}{Cs} \right) s}$$

# Impedance Approach

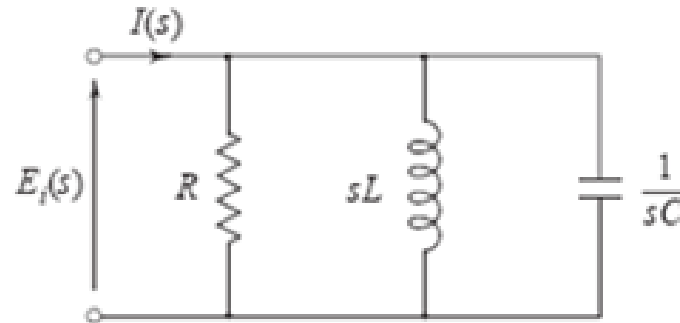

(c)

$$\frac{1}{Z(s)_{eq}} = Y(s)_{eq} = \frac{I(s)}{E_i(s)} = \frac{1}{R} + Cs + \frac{1}{Ls} \quad \text{or}$$

$$Z(s)_{eq} = \frac{E_i(s)}{I(s)} = \frac{LR}{C \left( R + \frac{1}{Cs} \right) \left( \frac{R}{C \left( R + \frac{1}{Cs} \right) s} + Ls \right)}$$

# Derivation of Transfer Function


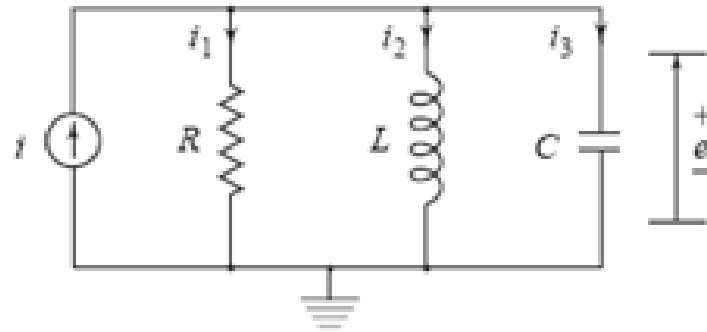


Fig. 2.28 An RLC circuit

$$H(s) = \frac{\frac{L}{C \left( \frac{1}{Cs} + Ls \right)}}{R + \frac{L}{C \left( \frac{1}{Cs} + Ls \right)}}$$


# Derivation of Transfer Function

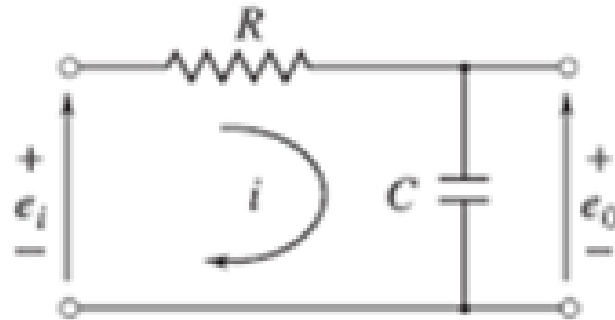

(a)

$$H(s) = \frac{1}{C \left( R + \frac{1}{Cs} \right) s}$$


# Derivation of Transfer Function

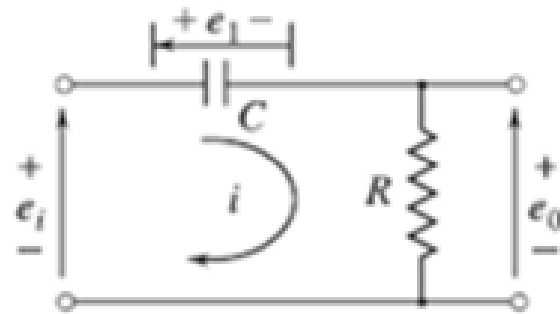

(b)

$$H(s) = \frac{R}{R + \frac{1}{Cs}}$$

# Derivation of Transfer Function

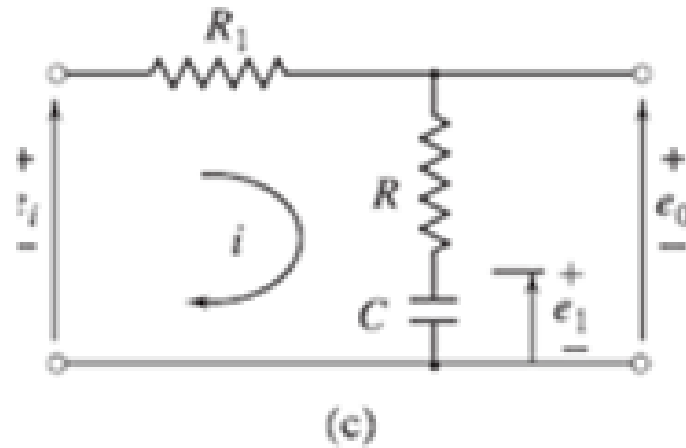

$$H(s) = \frac{R + \frac{1}{Cs}}{R + R_1 + \frac{1}{Cs}}$$