



# ANALOG ELECTRONICS

LECTURE NO. 5

# CLAMPER

The clamping network is to “clamp” a signal to a different dc level. Also known as dc restorers. The clamping ckt is often used in TV receivers as a dc restorer.

- The network consists of:

- a) Capacitor

- b) Diode



- c) Resistive element

- d) Independent dc supply (option)

- The magnitude of R and C must be chosen such that the time constant


- $\tau = RC$  is large enough to ensure that the voltage across the capacitor does not discharge significantly during the interval the diode is non conducting.

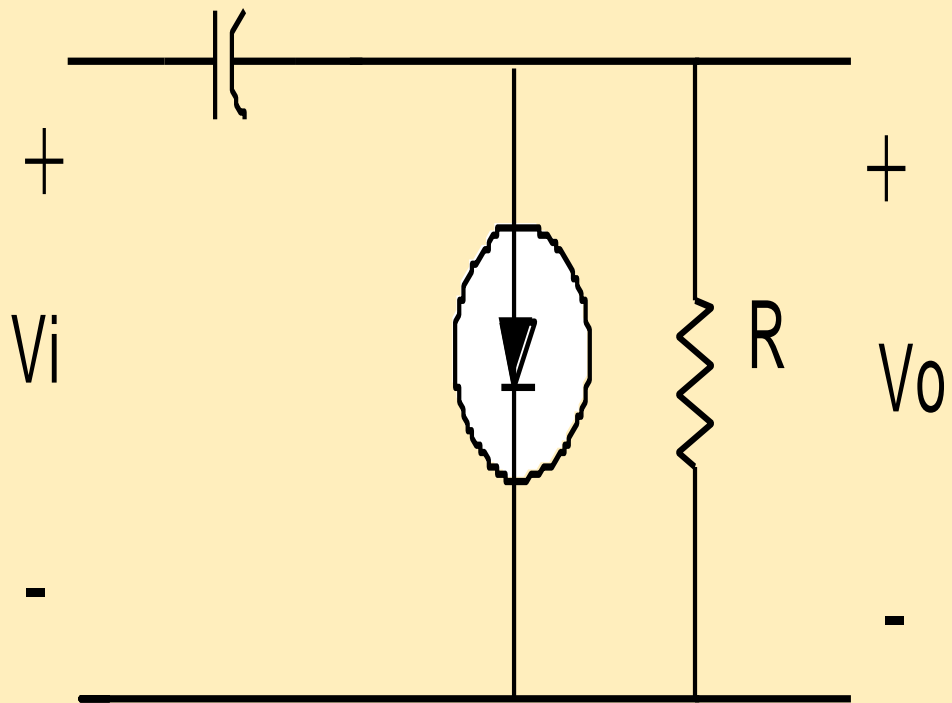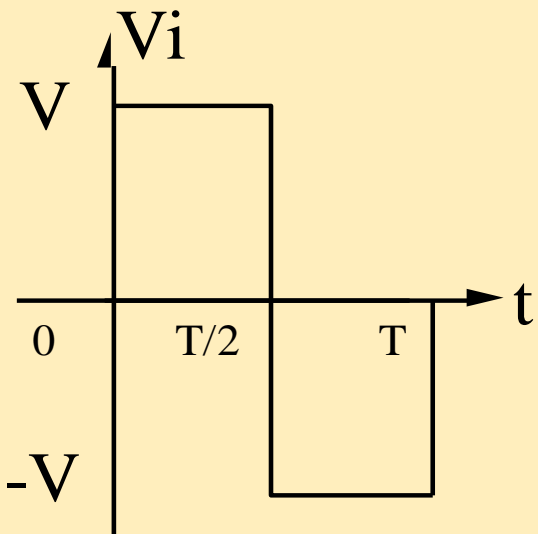- Our analysis basis that all capacitor is fully charge and discharge in 5 time constant.




# OPERATION OF CLAMPER

**+ ve region**

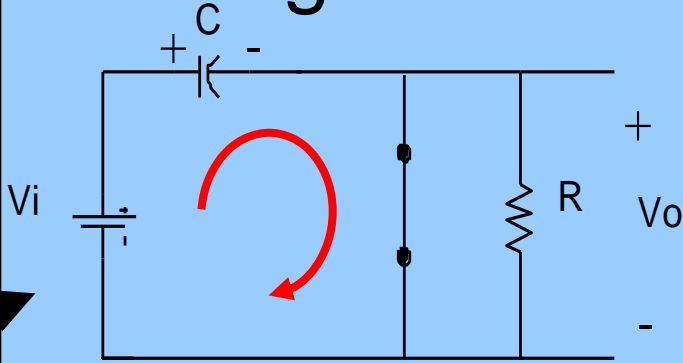


- 0 - T/2: Diode is ON state (short-cct equivalent)
- Assume RC time is small and capacitor charge to V volts very quickly
- $V_o = 0$  V (ideal diode)

**- ve region**

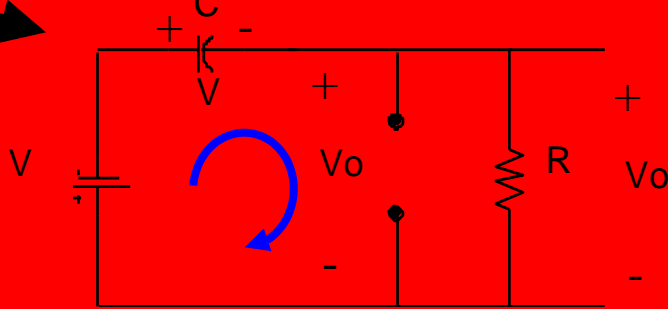

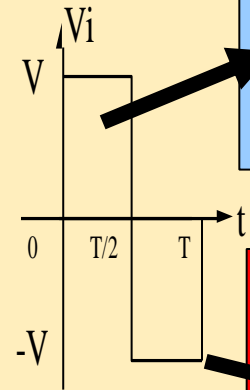
- T/2  $\rightarrow$  T: Diode is OFF state (open-cct equivalent)
- Both for the stored voltage across capacitor and applied signal current through cathode to anode
- KVL:  $-V - V - V_o = 0$  and  $V_o = -2V$





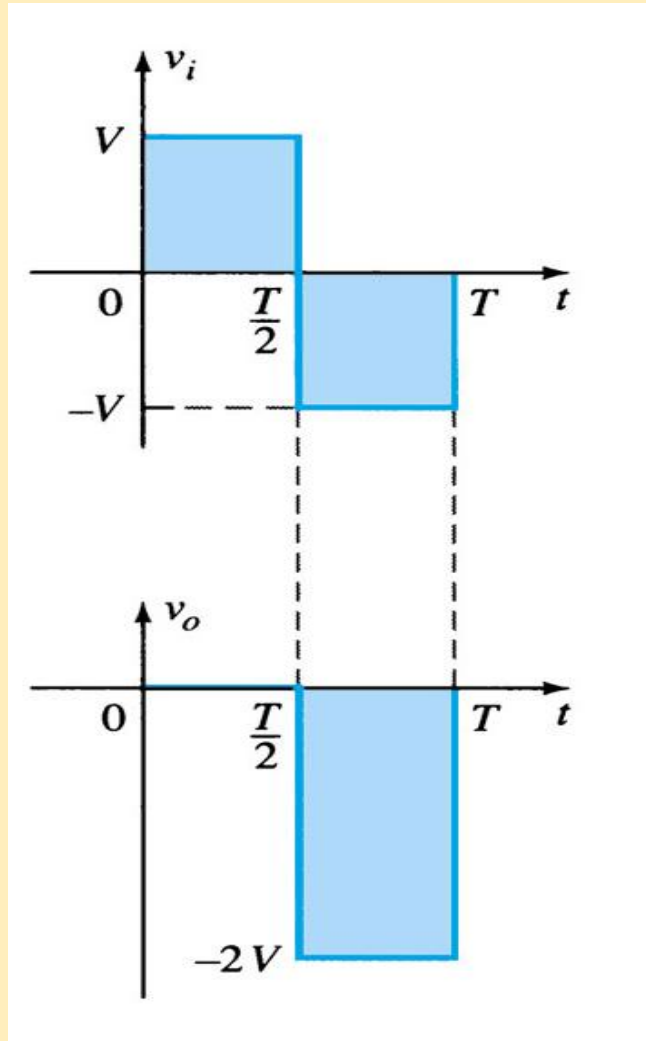
# Tips : Clamping network

*Total swing o/p signal = the total swing i/p signal*


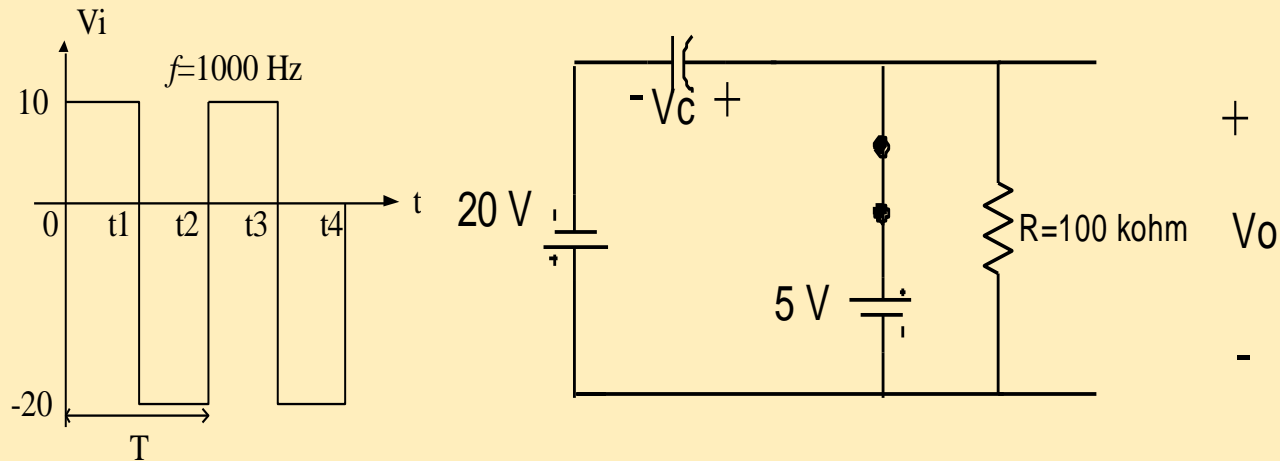
# Solution:

**Step 1:** Consider the part of i/p signal that will forward bias the diode. From network ( $t_1 - t_2$ : -ve region)




**Step 2:** During ON state assume capacitor will charge to a voltage level determined by the network. Find the store voltage capacitor & obtained  $V_o$

$$\text{KVL: } -20 + V_c - 5 = 0$$
$$V_c = 25\text{v}$$

$$V_o = 5$$

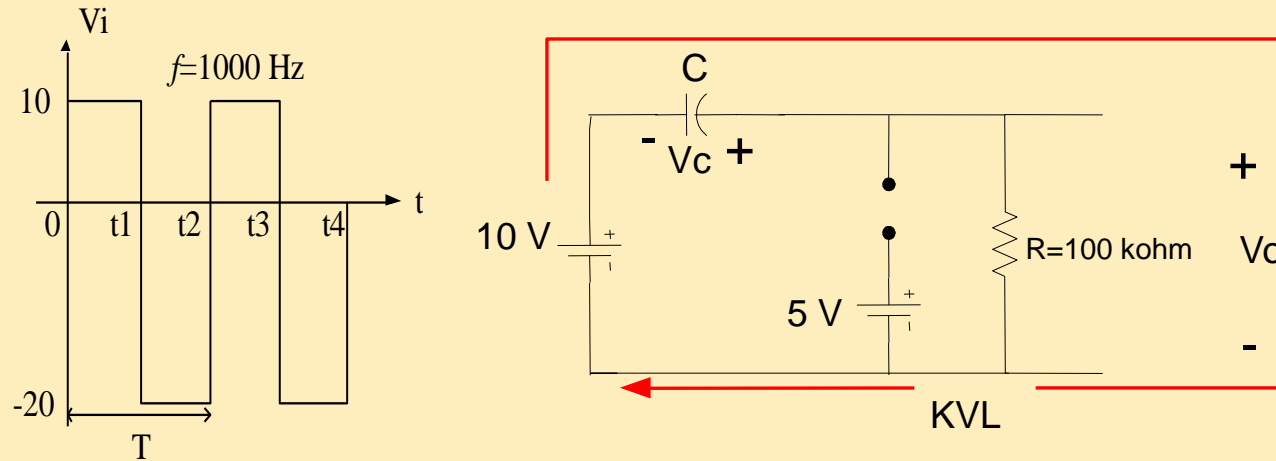**Step 3:** During OFF state assume capacitor will hold on its established voltage level. From network ( $t_2 - t_3$ : +ve region)



**Step 4:** Obtained  $V_o$

$$\begin{aligned} \text{KVL: } 10. \quad V_c \quad V_o \quad 0 \\ 10. \quad 25. \quad V_o \quad 0 \\ V_o \quad \underline{\underline{35V}} \end{aligned}$$



Time constant of discharging is determined

by:  $\tau = RC = (100k)(1\mu) = 100 \text{ ms}$

The total discharge time is  $5 \tau = 5(100 \text{ ms}) = 500 \text{ ms}$
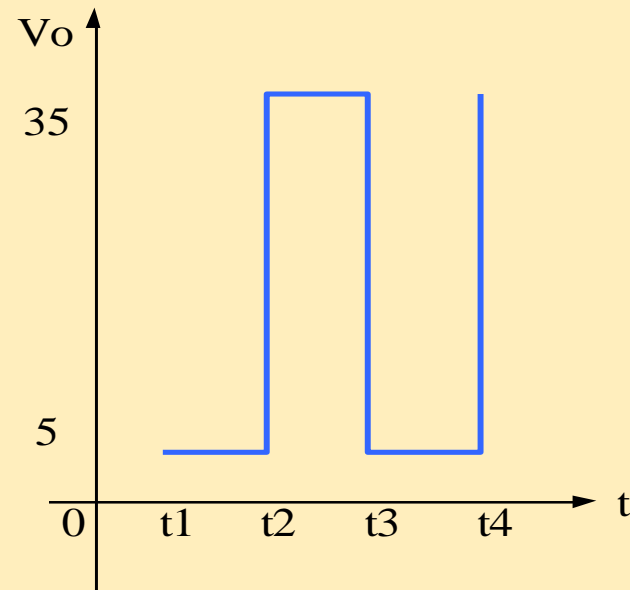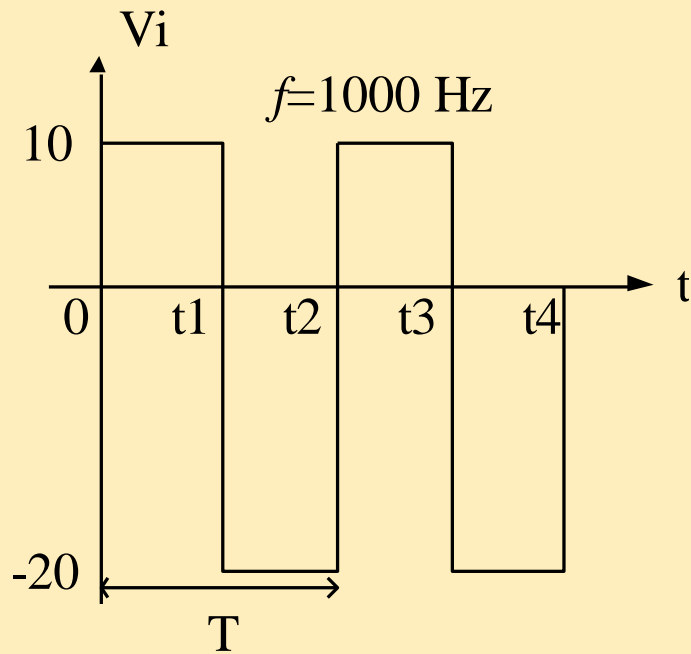
# Solution (cntd):

**Step 5:** Checking!!! total swing o/p signal = total swing i/p signal  
From network ( $t_2 - t_3$ : +ve region)





# SUMMARY OF CLAMPER CIRCUITS

## Clamping Networks

