

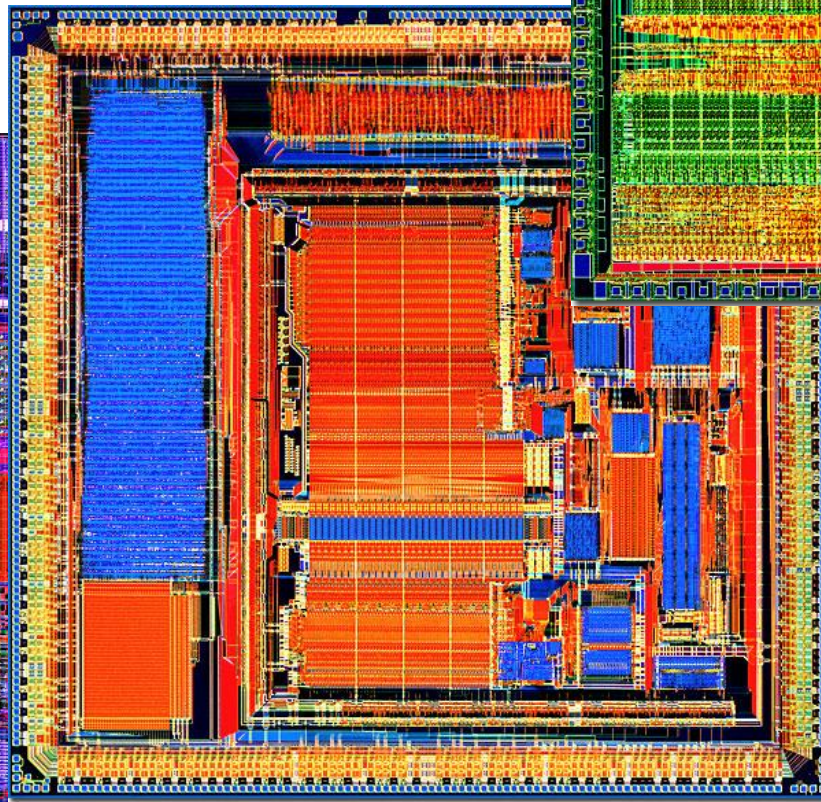


# Field Effect Transistors Circuit Analysis


HP PA8000

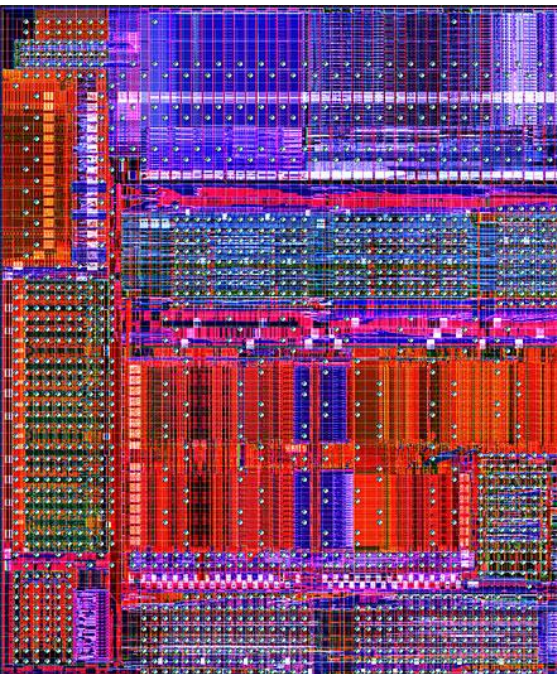


Fujitsu 68903

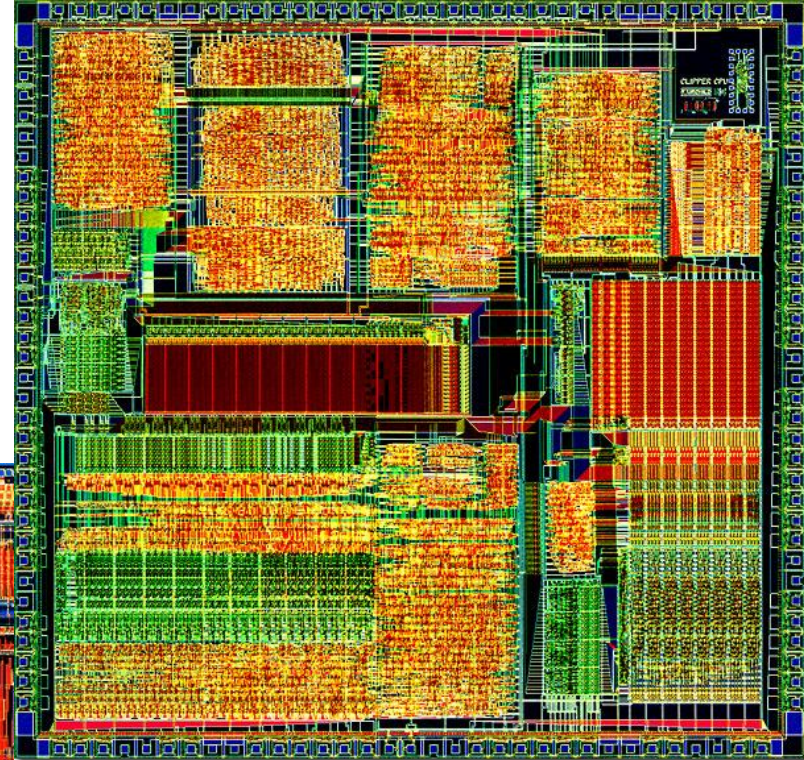

Fairchild Clipper  
C100

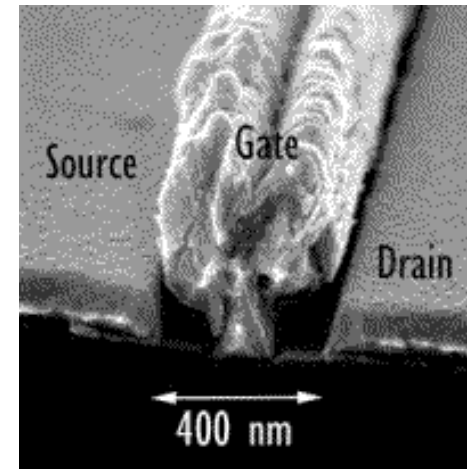

# FET Circuit Analysis

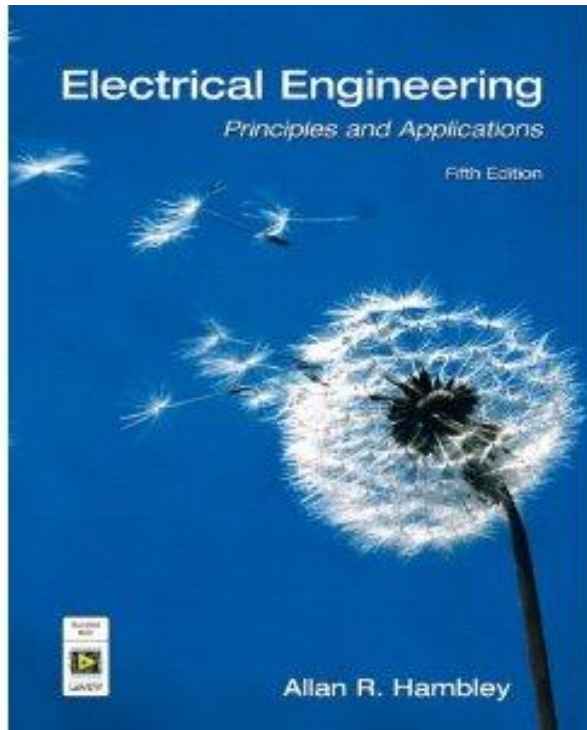

Chapter 12: Field  
Effect Transistors

- 1. MOS Small Signal Equivalent*
- 2. Transconductance*
- 3. Common-Source Amplifiers*
- 4. Source Follower*
- 5. Logic gates*

# Small-Signal Equivalent Circuit for FETs

Output signal from an amplifier using FET can be effectively modulated by small changes of input signal current. In this way it is possible to make small changes from the Q point.

Symbols:

The total quantities:  $i_D(t)$ ,  $v_{GS}(t)$

The dc point values:  $I_{DQ}$ ,  $V_{GSQ}$

The signal  $i_d(t)$ ,  $v_{gs}(t)$

$$v_{GS}(t) = V_{GSQ} + v_{gs}(t)$$

$$i_D(t) = I_{DQ} + i_d(t)$$

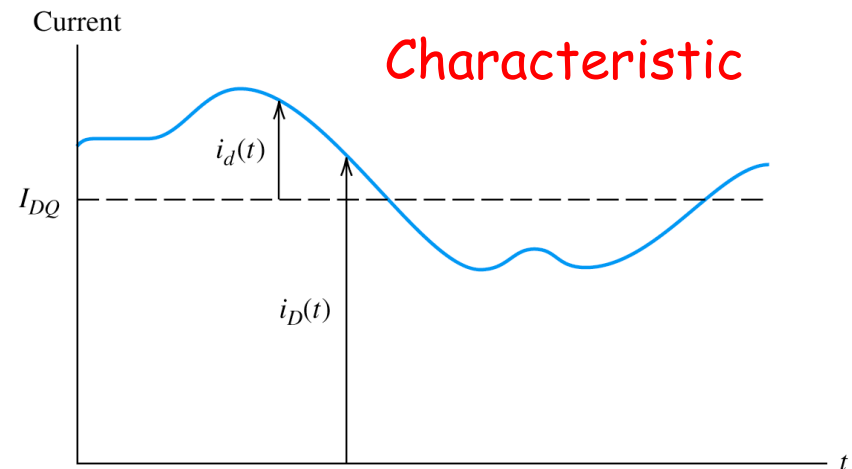


Figure 12.18 Illustration of the terms in Equation 12.15.

# Small-Signal Equivalent Circuit - Transconductance

Schematic

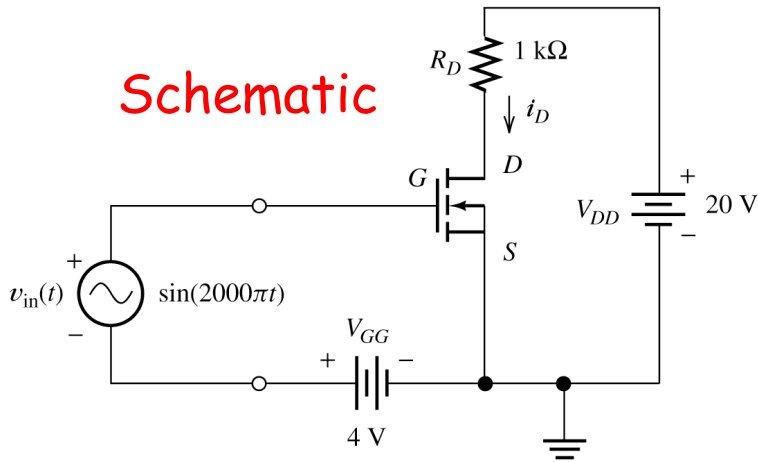


Figure 12.10 Simple NMOS amplifier circuit.

Analysis... (a little bit of math)

$$i_D = K(v_{GS} - V_{t0})^2$$

$$I_{DQ} + i_d(t) = K[V_{GSQ} + v_{gs}(t) - V_{t0}]^2$$

$$I_{DQ} + i_d(t) = K(V_{GSQ} - V_{t0})^2 + 2K(V_{GSQ} - V_{t0})v_{gs}(t) + Kv_{gs}^2(t)$$

We know that

$$I_{DQ} = K(V_{GSQ} - V_{t0})^2 *$$

Also we assume that

$$|v_{gs}(t)| \ll |(V_{GSQ} - V_{t0})|$$

# Small-Signal Equivalent Circuit - Transconductance

Schematic

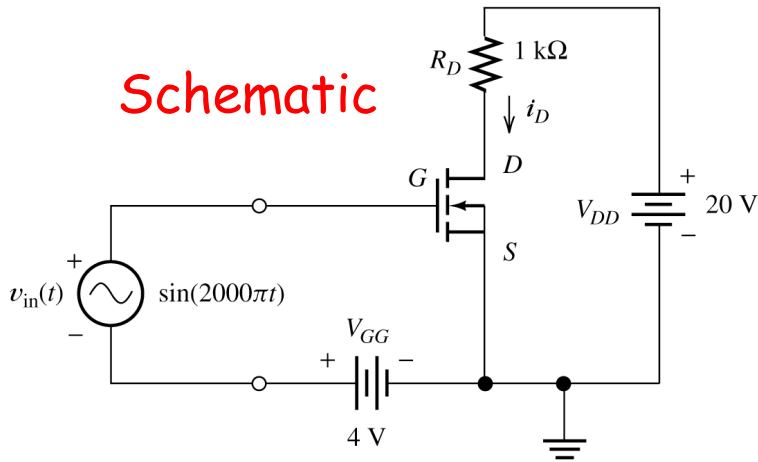


Figure 12.10 Simple NMOS amplifier circuit.

~~$$I_{DQ} + i_d(t) = K(V_{GSQ} - V_{t0})^2 + 2K(V_{GSQ} - V_{t0})v_{gs}(t) + Kv_{gs}^2(t)$$~~


We know that

$$I_{DQ} = K(V_{GSQ} - V_{t0})^2 *$$

Also we assume that

$$|v_{gs}(t)| \ll |(V_{GSQ} - V_{t0})|$$

Drain current generated  
by signal

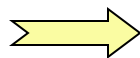

$$i_d(t) = 2K(V_{GSQ} - V_{t0})v_{gs}(t)$$

# Small-Signal Equivalent Circuit - Transconductance

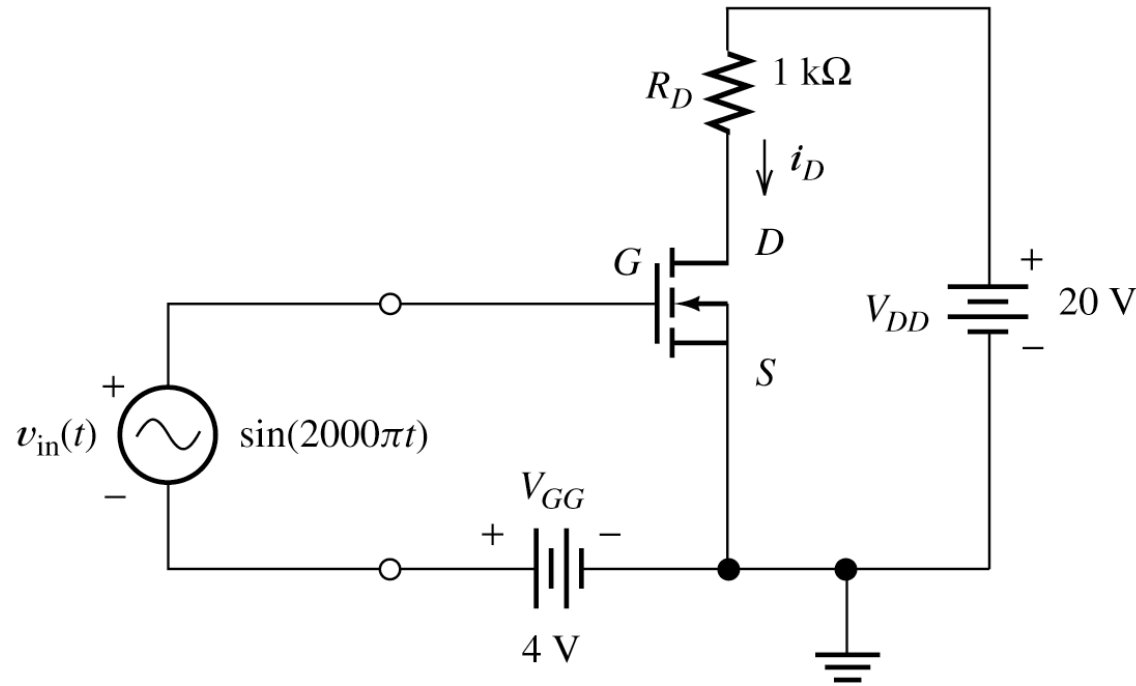


Figure 12.10 Simple NMOS amplifier circuit.

We define the transconductance as

$$g_m = \frac{i_d(t)}{v_{gs}(t)}$$

or

$$i_d(t) = g_m v_{gs}(t)$$

so

$$g_m = 2K(V_{GSQ} - V_{t0})$$

# Small-Signal Equivalent Circuit - Transconductance

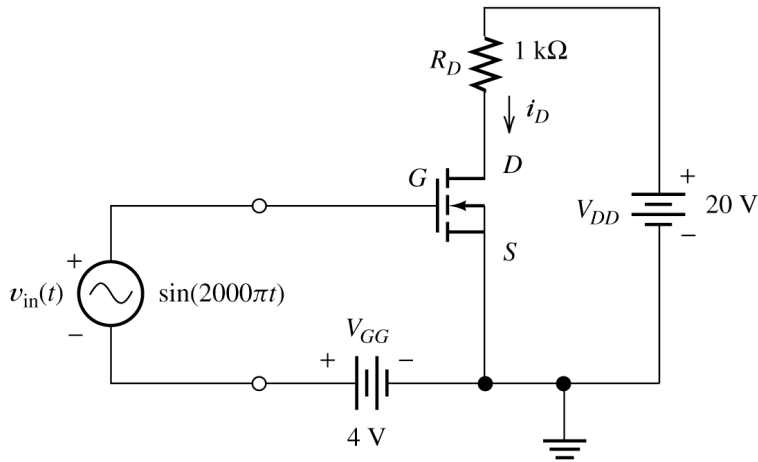


Figure 12.10 Simple NMOS amplifier circuit.

$$i_D = K(v_{GS} - V_{t0})^2$$

so

$$(v_{GS} - V_{t0}) = \sqrt{\frac{I_{DQ}}{K}}$$


Thus the  
transconductance

$$g_m = 2K(v_{GSQ} - V_{t0}) = 2\sqrt{KI_{DQ}}$$

# Small-Signal Equivalent Circuit - Transconductance
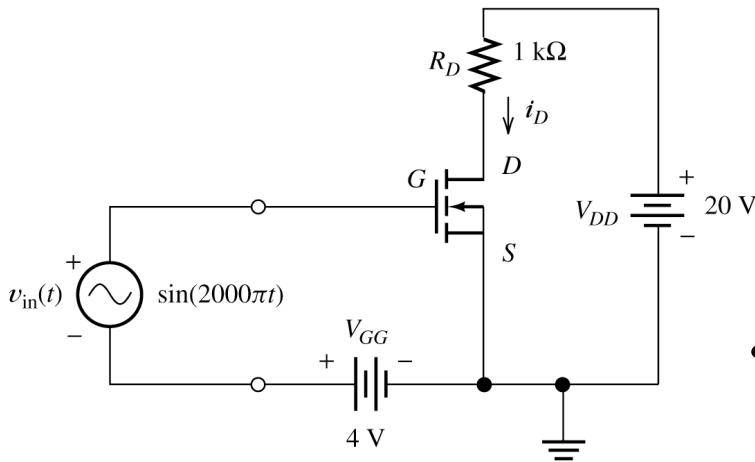
## Exercise

The transistor has  $KP=50\mu\text{A}/\text{V}^2$ ,  $V_{t0}=2\text{V}$ ,  $L=10\mu\text{m}$ , and  $W=400\mu\text{m}$



$$K = \left(\frac{W}{L}\right) \frac{KP}{2} = 1\text{mA}/\text{V}^2$$


$$g_m = 2K(V_{GSQ} - V_{t0}) = 2(4 - 2) = 4\text{mS}$$

Figure 12.10 Simple NMOS amplifier circuit.



# Small-Signal Equivalent Circuit

Also we assume that  $i_g(t) = 0$

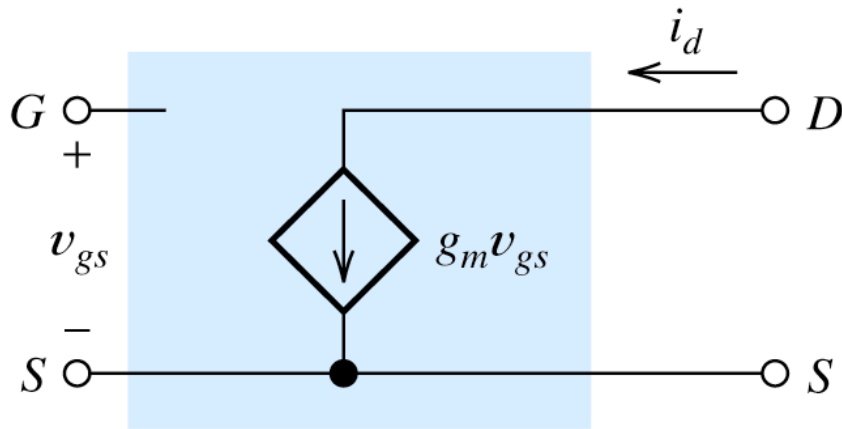

$$g_m = 2\sqrt{KI_{DQ}}$$

$$K = \left(\frac{W}{L}\right) \frac{KP}{2}$$

**Figure 12.19** Small-signal equivalent circuit for FETs.


Better performance is obtained with higher values of  $g_m$ . Please notice that  $g_m$  is proportional to the square root of the Q point drain current. Simply, we can increase  $g_m$  by choosing a higher value of  $I_{DQ}$ .

# More Complex Equivalent Circuits

For more accurate analyses of FET transistor we have to add more components to an equivalent circuit.

Small capacitance: for high response FET amplifiers

Drain resistor: account for the effect of  $v_{DS}$  on the drain current

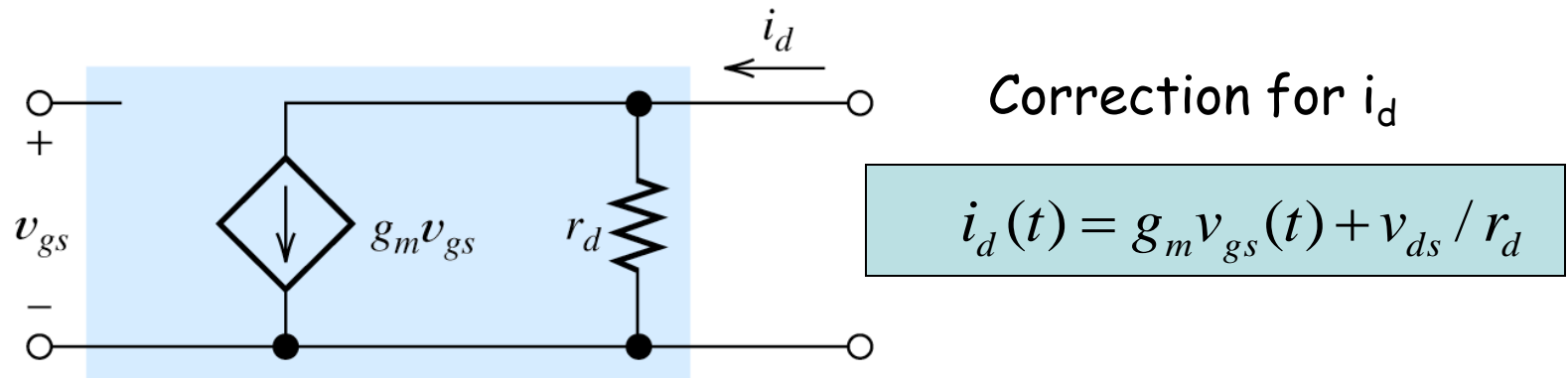

**Figure 12.20** FET small-signal equivalent circuit that accounts for the dependence of  $i_D$  on  $v_{DS}$ .

Please read section: Transconductance and ... pp.591  
Example 12.3

# Drain Resistance Calculation

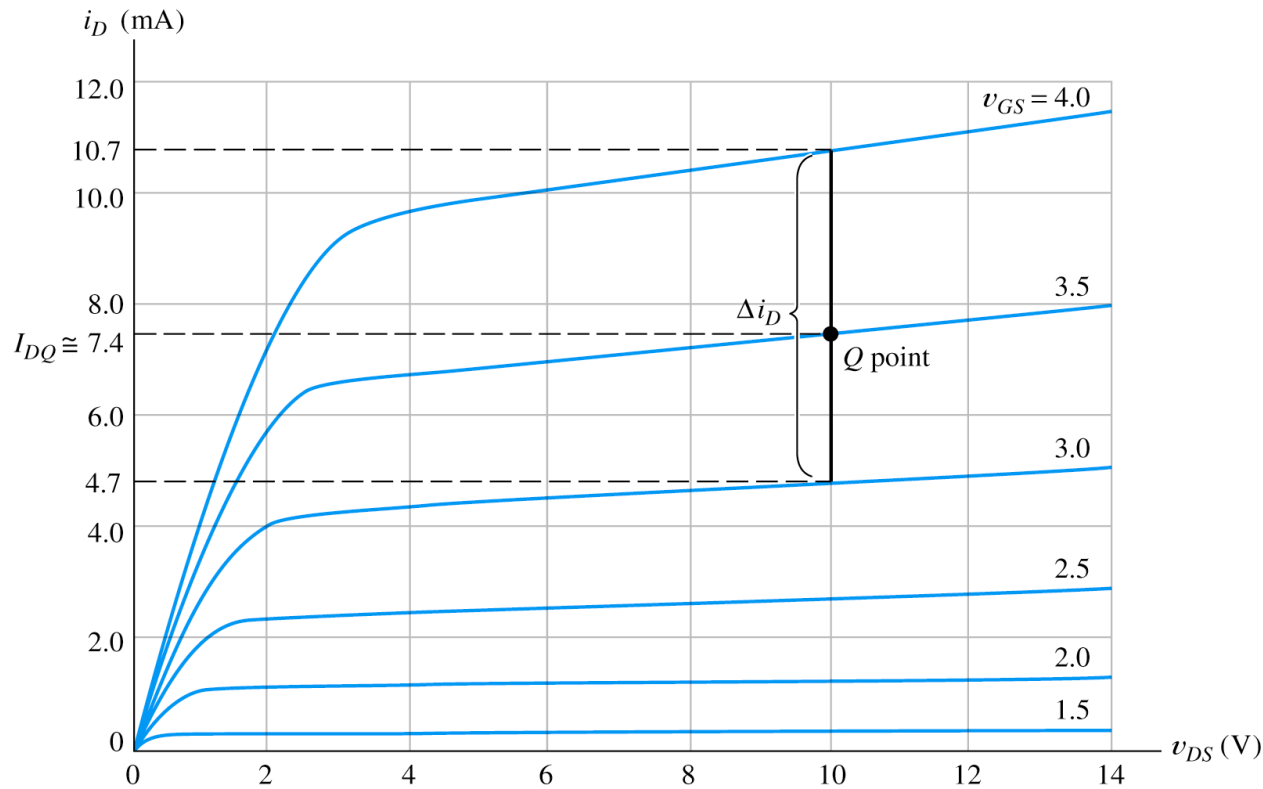


Figure 12.21 Determination of  $g_m$  and  $r_d$ . See Example 12.3.


so at  $v_{GS}=4V$

$$\frac{1}{r_d} = \frac{\Delta i_D}{\Delta v_{DS}} = \frac{(10.7 - 10) \text{ mA}}{(10 - 6) \text{ V}} = \frac{0.7}{4} \text{ mS} = 0.175 \text{ mS}$$

$$r_d = 5.7 \text{ k}\Omega$$

$$\frac{1}{r_d} = \frac{\Delta i_D}{\Delta v_{DS}}$$

# Common-Source Amplifier

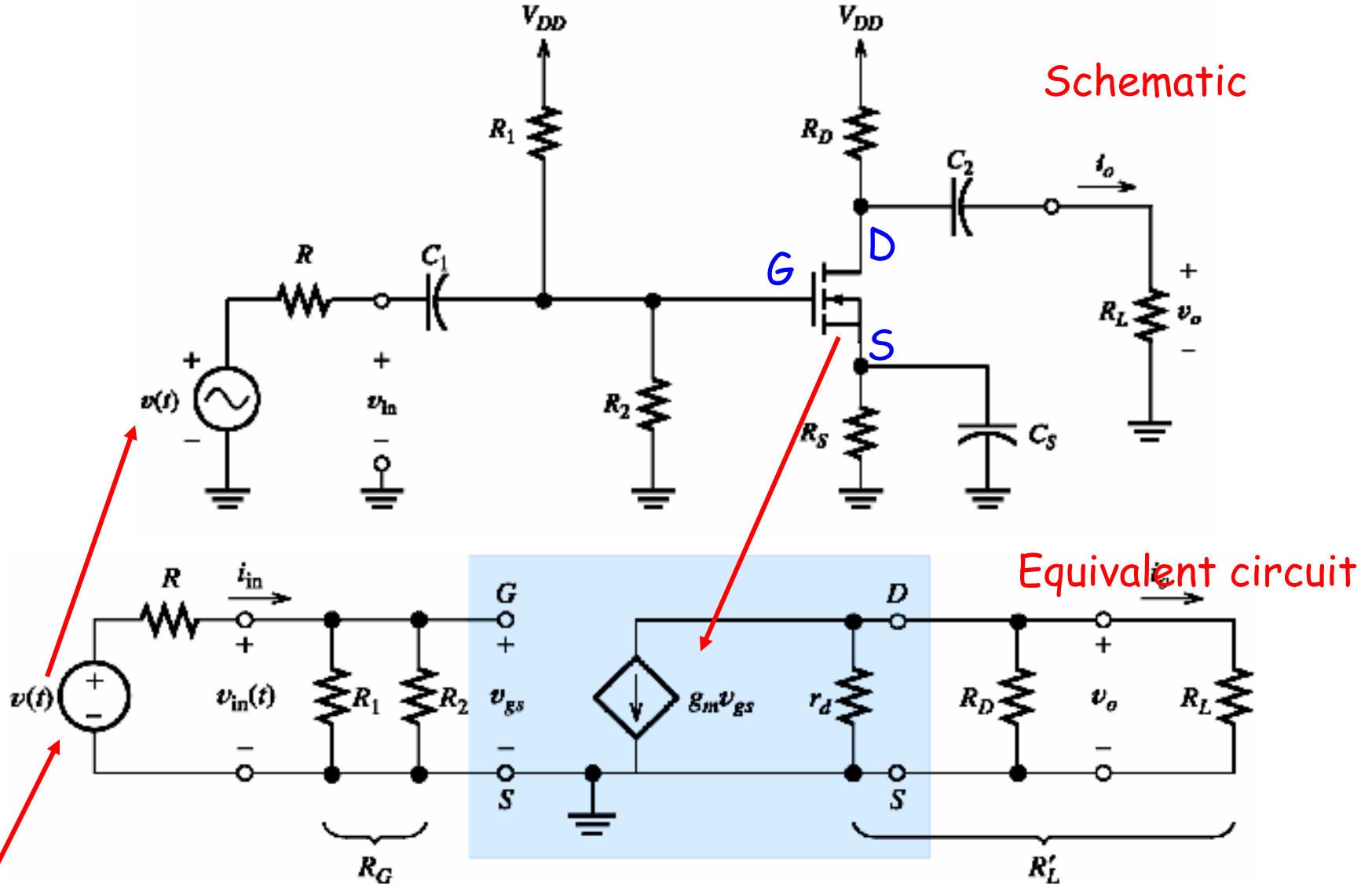

The dc supply voltage acts as a short circuit for the ac current.


# Common-Source Amplifier

$C_1, C_2$  -coupling C


$C_s$  -bypass C

ac signal

Schematic

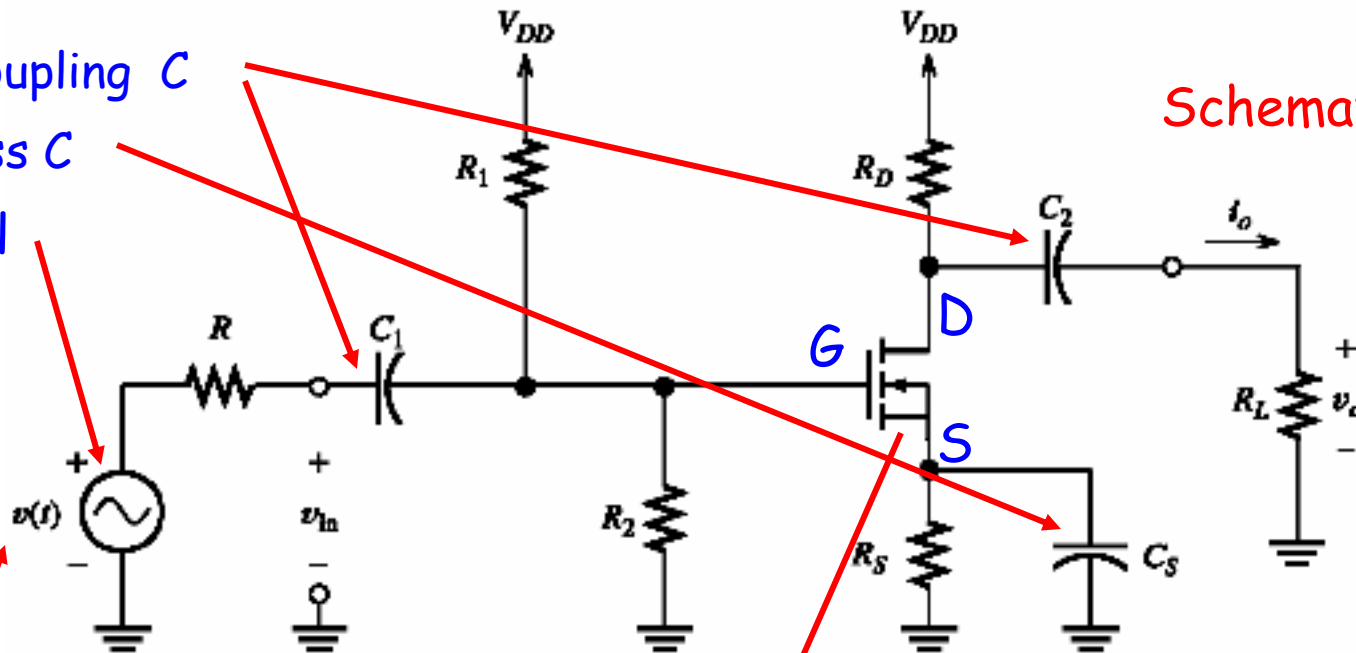


Equivalent circuit

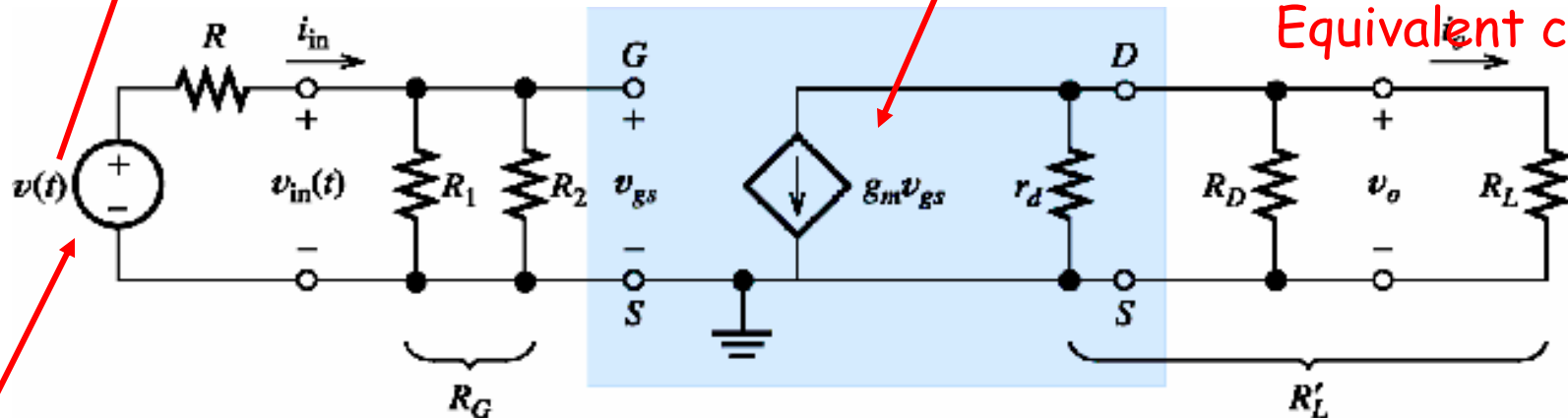

The dc supply voltage acts as a short circuit for the ac current.

# Common-Source Amplifier: Gain, $R_{in}$ and $R_{out}$

Equivalent circuit (once more)

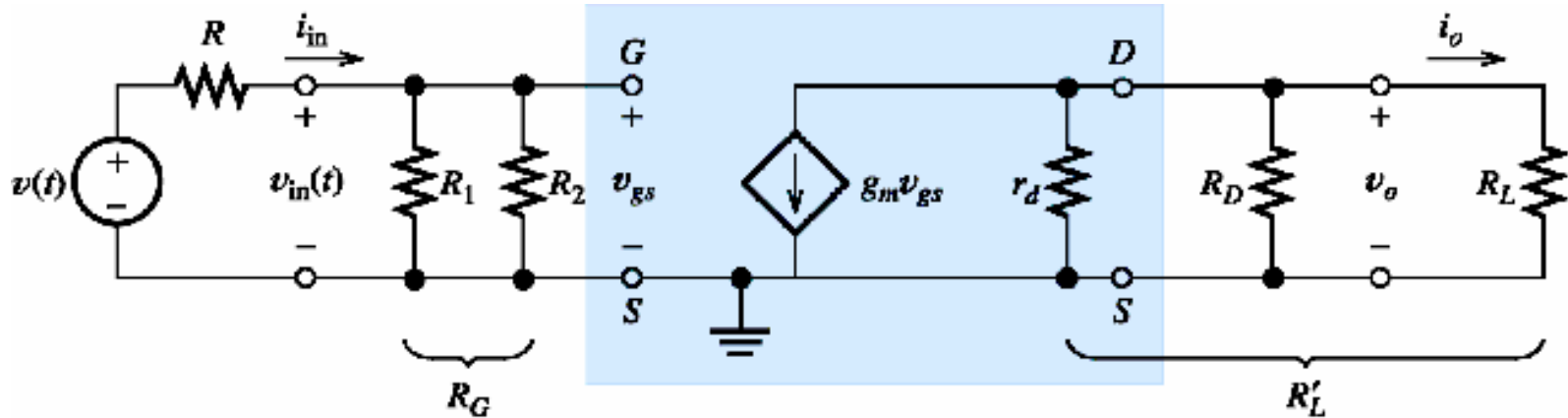

$$R'_L = \frac{1}{1/r_d + 1/R_D + 1/R_L}$$

Voltage gain

$$v_o = -(g_m v_{gs}) R'_L \quad v_{in} = v_{gs}$$

$$A_v = \frac{v_o}{v_{in}} = -g_m R'_L$$


Input resistance

$$R_{in} = \frac{v_{in}}{i_{in}} = R_G = R_1 || R_2$$

From bias point analysis
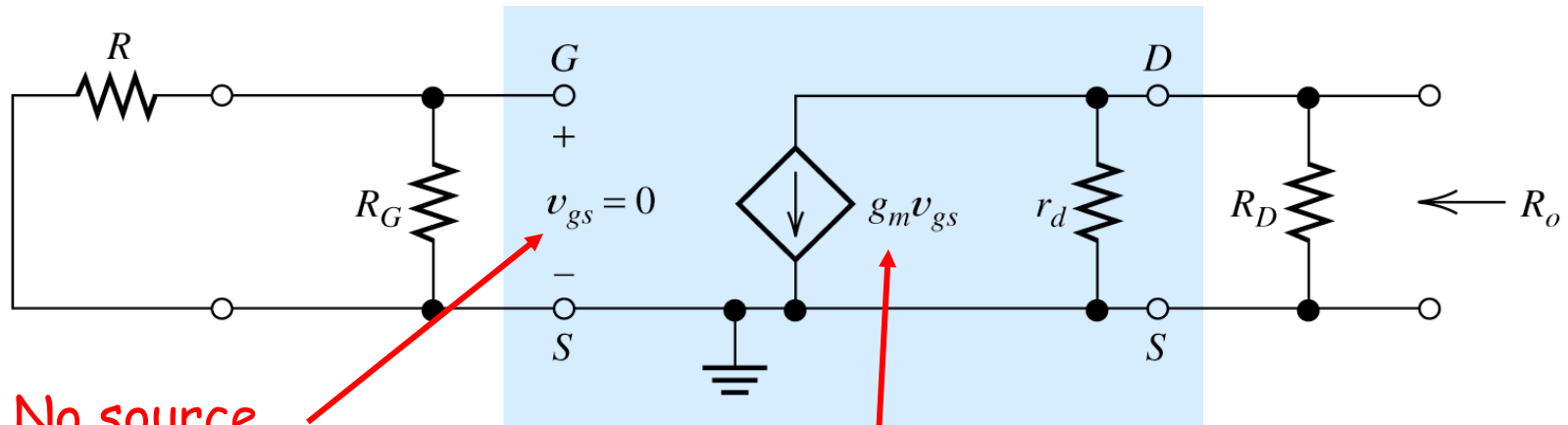
# Common-Source Amplifier: Gain, $R_{in}$ and $R_{out}$

To find out the  $R_{out}$  we have to: disconnect the load, replace the signal source by short circuit - Thevenin equivalent resistance



No source connected to the input

Figure 12.24 Circuit used to find  $R_o$ .

if  $v_{gs}=0$  then  $g_m v_{gs}=0$

Output resistance

Example 12.4

$$R_{out} = \frac{1}{1/R_D + 1/r_d}$$

# Source Follower


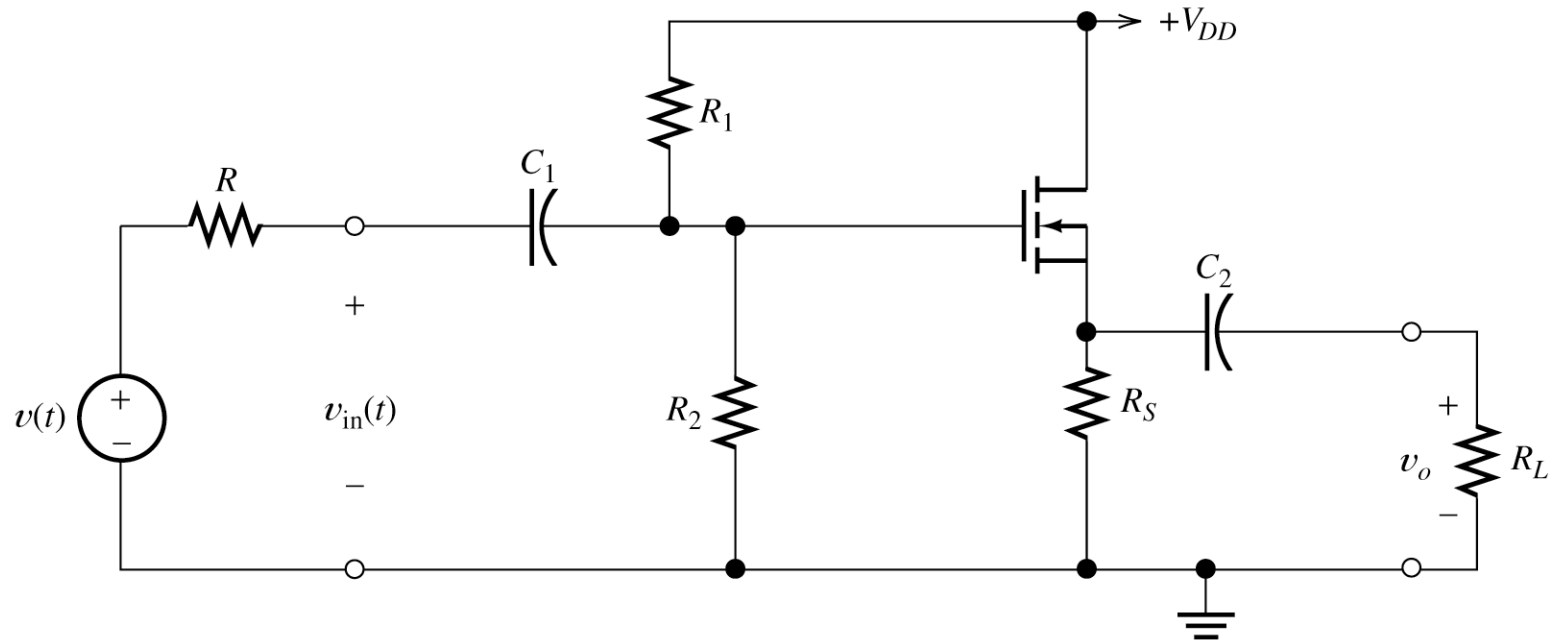


Figure 12.26 Source follower.

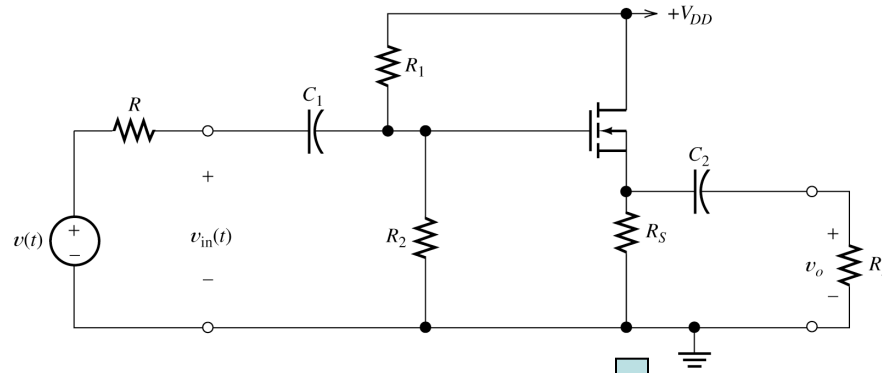

# Small-Signal Equivalent Circuit - Source Follower



Notice that small signal  $I_{DS}$  goes up. Why?

Figure 12.26 Source follower.

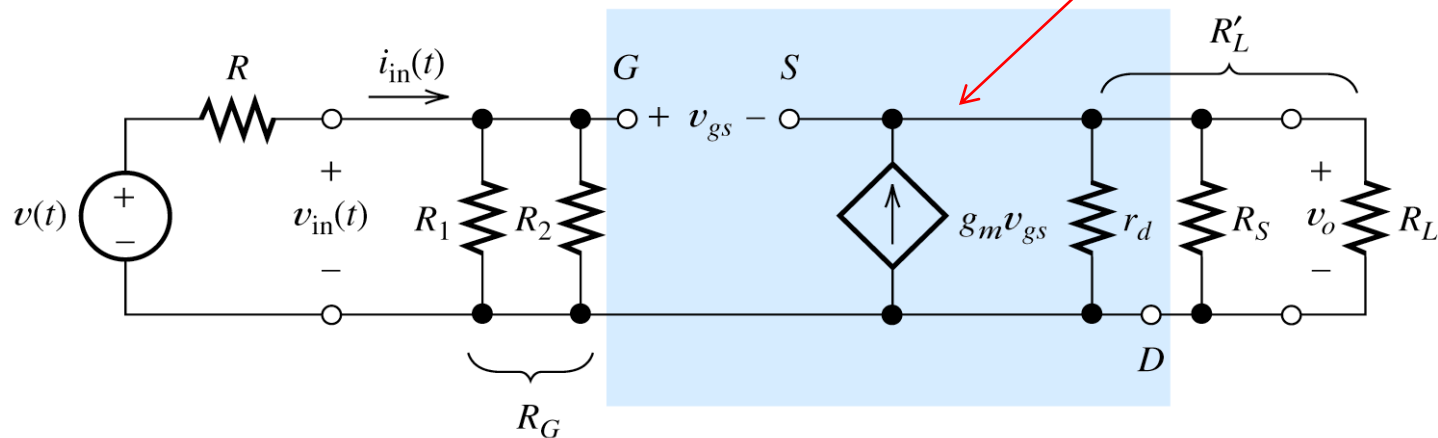


Figure 12.27 Small-signal ac equivalent circuit for the source follower.

# Small-Signal Equivalent Circuit - Source Follower

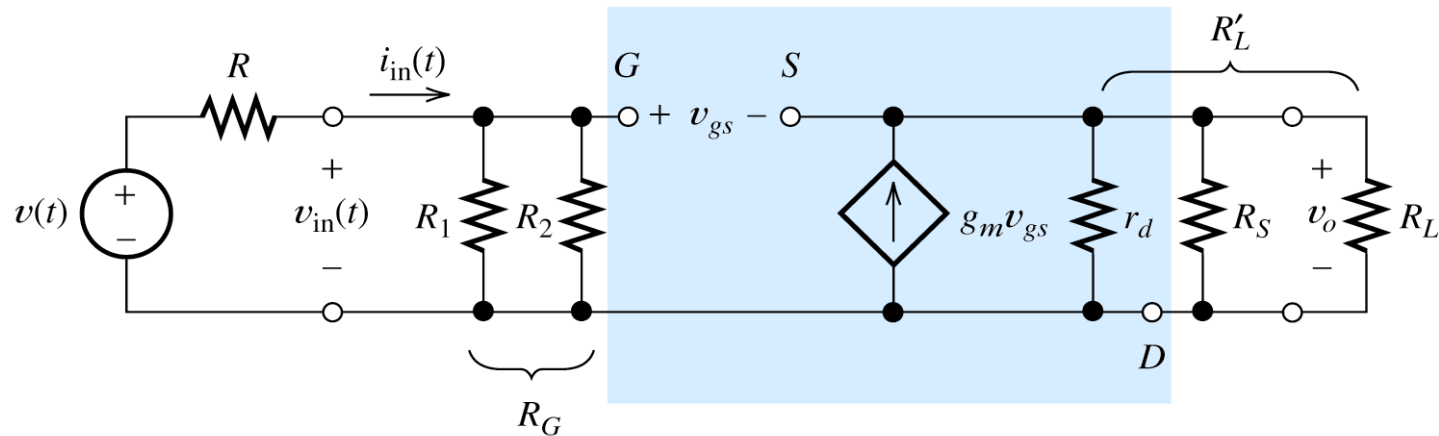


Figure 12.27 Small-signal ac equivalent circuit for the source follower.

$$R'_L = \frac{1}{1/r_d + 1/R_S + 1/R_L}$$

Input resistance

$$R_{in} = \frac{v_{in}}{i_{in}} = R_G = R_1 \parallel R_2$$


Voltage gain

$$v_o = g_m v_{gs} R'_L \quad v_{in} = v_{gs} + v_o = v_{gs} (1 + g_m R'_L)$$


$$A_v = \frac{v_o}{v_{in}} = \frac{g_m R'_L}{1 + g_m R'_L} \leq 1$$

Since the output voltage is almost equal to the input - hence the name source follower

# Logic gates - CMOS Inverter

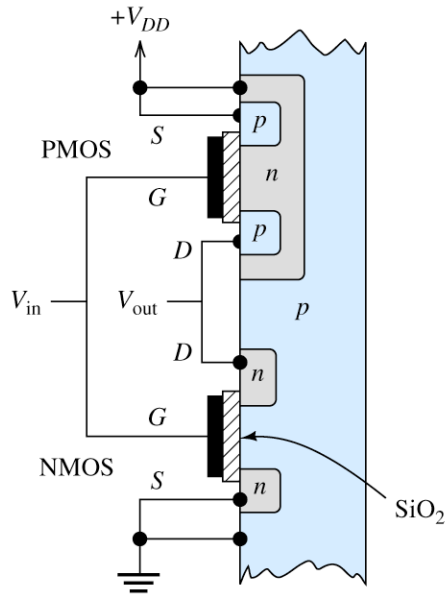


(a) Physical structure

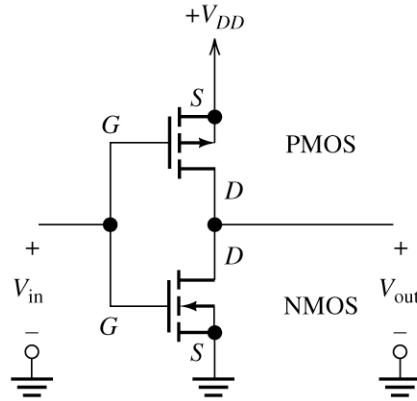


(b) Circuit diagram

Logic truth table

V <sub>in</sub>	V <sub>out</sub>
0	1
1	0

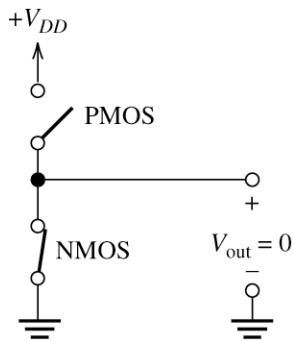

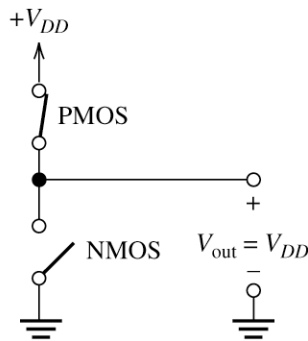(c) Equivalent circuit with V<sub>in</sub> high




(d) Equivalent circuit with V<sub>in</sub> low


Switch level equivalent circuits

Figure 12.31 CMOS inverter.


# Logic gates - CMOS NAND gate

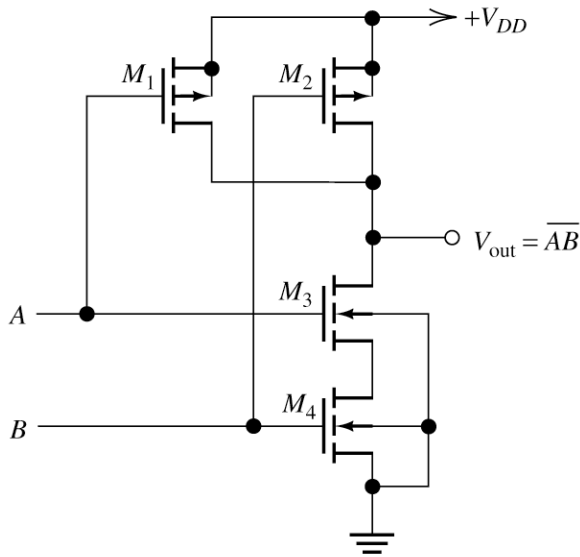

(a) Circuit diagram

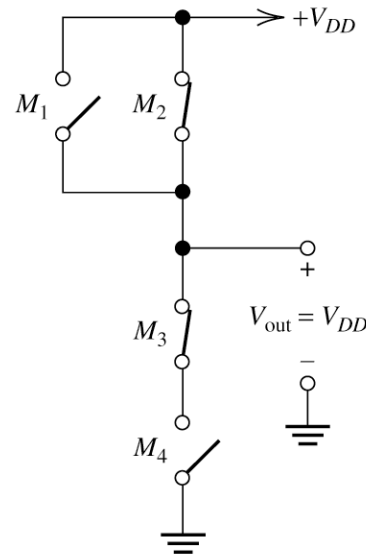

(b) A high and B low

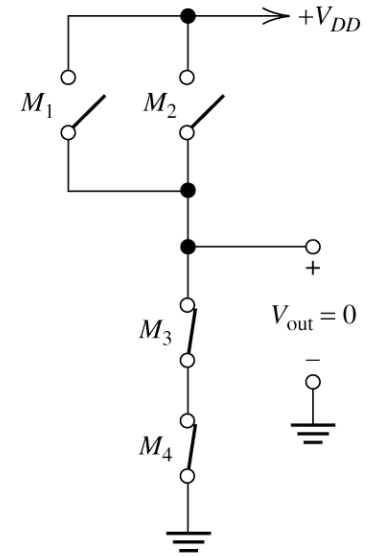

(c) Both A and B are high

Figure 12.32 Two-input CMOS NAND gate.

Logic truth table

A	B	V <sub>out</sub>
0	0	1
0	1	1
1	0	1
1	1	0

# Logic gates - CMOS NOR gate


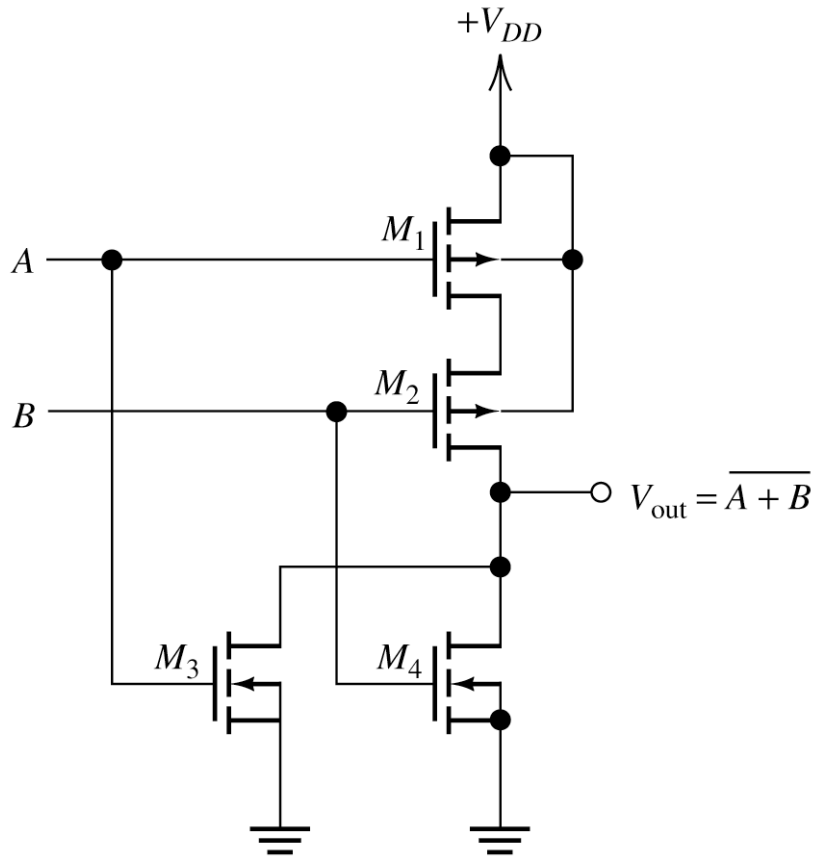


Figure 12.33 Two-input CMOS NOR gate.


Exercise

Draw switch level circuits for different inputs and derive the truth table for this gate


# Logic gates - CMOS NOR gate

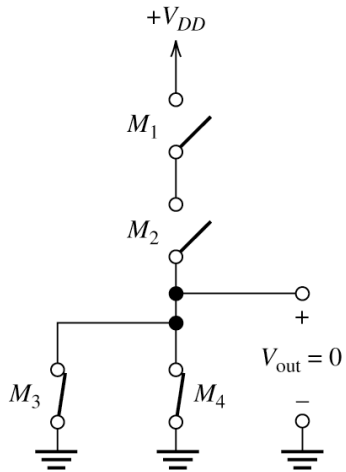

(a) A and B both high

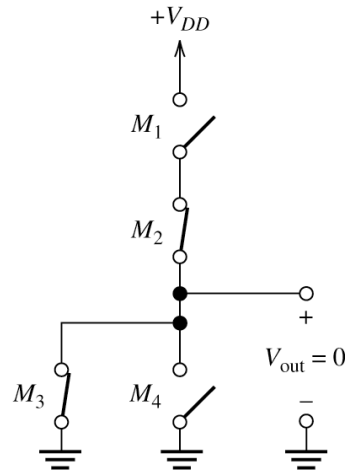

(b) A high and B low

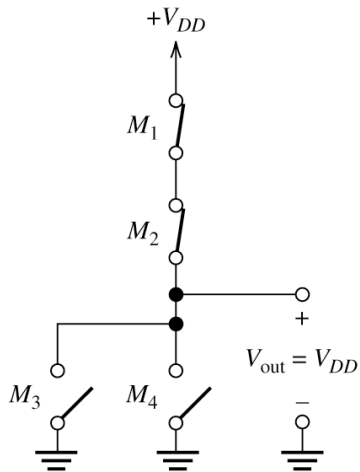

(c) A and B both low

A	B	$V_{out}$
Low	Low	High
Low	High	Low
High	Low	Low
High	High	Low

(d) Truth table

Logic truth table

A	B	$V_{out}$
0	0	1
0	1	0
1	0	0
1	1	0

Figure 12.34 Answers for Exercise 12.14.