

# Lecture 13

MOSFET


# The Transfer Characteristics – *Graphical Derivation*

## *Operation as a Switch*

- Operate the MOSFET at the Extreme points of the Transfer Curve
- $v_i < V_t$ : switch is turned off and  $v_o = V_{DD}$  (operate between  $X$  and  $A$ )
- $v_i = V_{DD}$ : switch is turned on and  $v_o$  is very small (operate at point  $C$ )

**SWITCH OFF**

**SWITCH ON**

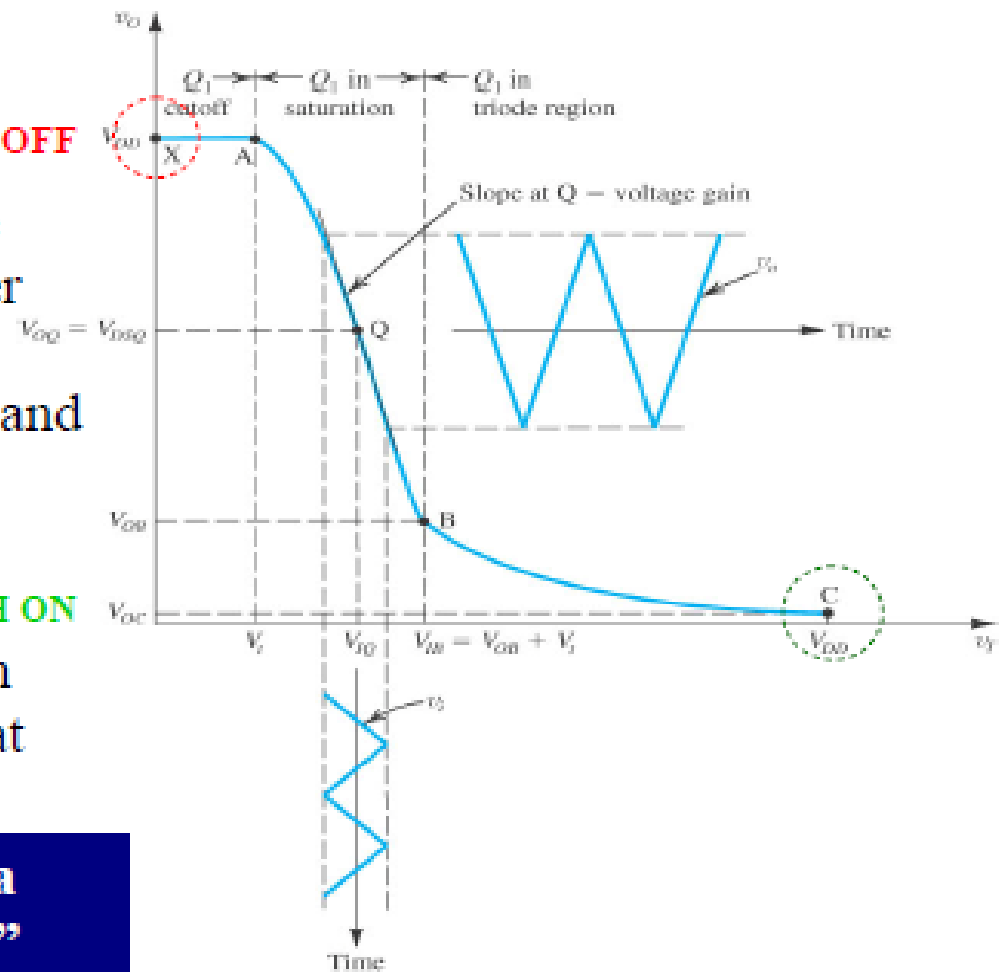


**MOSFET Operates as a  
“Digital Logic Inverter”**

# The Transfer Characteristics – Graphical Derivation

## Operation as a Linear Amplifier

- We make use of the Saturation-mode segment of the curve (A Through B)
- The MOSFET is biased somewhere in the middle, e.g. point Q
- The AC signal to be amplified is then superimposed on the DC Voltage  $V_{IQ}$
- By keeping  $v_i$  sufficiently small, we restrict operation to the almost linear region between A and B
- **Gain ( $A_v$ ):**


$$A_v = \left. \frac{dv_o}{dv_i} \right|_{v_i = V_{IQ}}$$

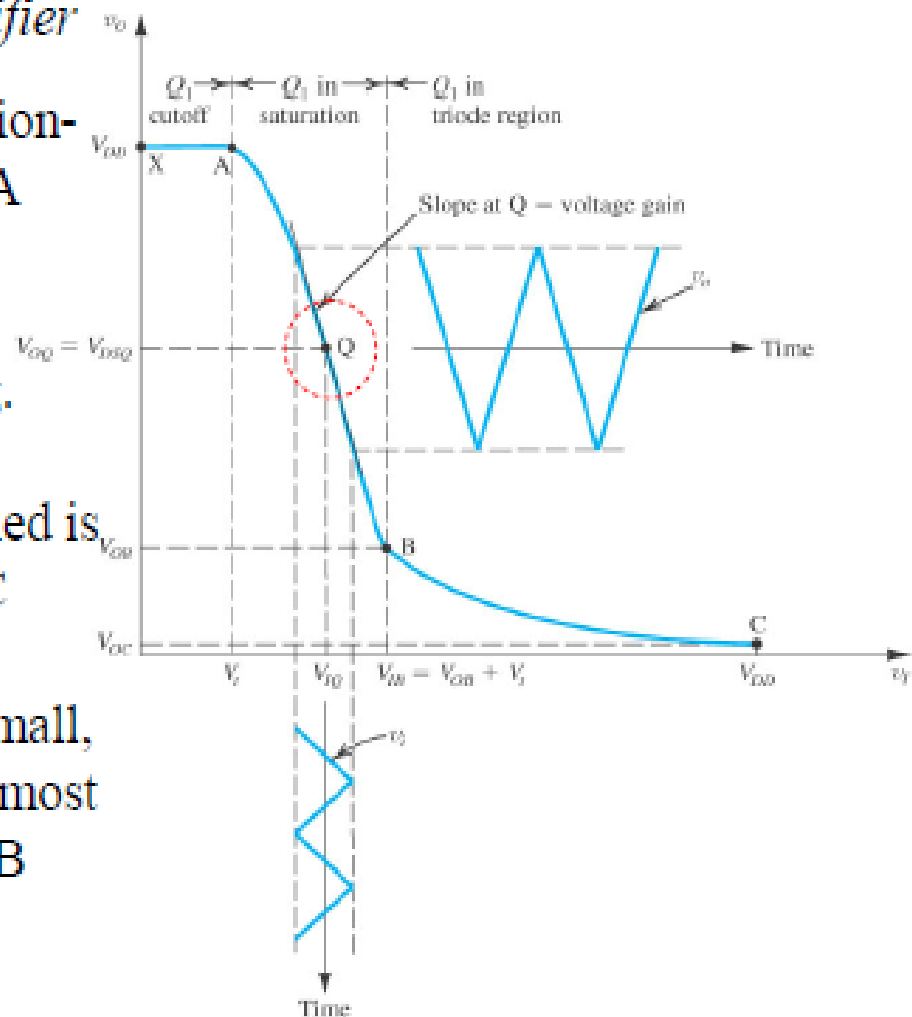


# The Transfer Characteristics – Graphical Derivation
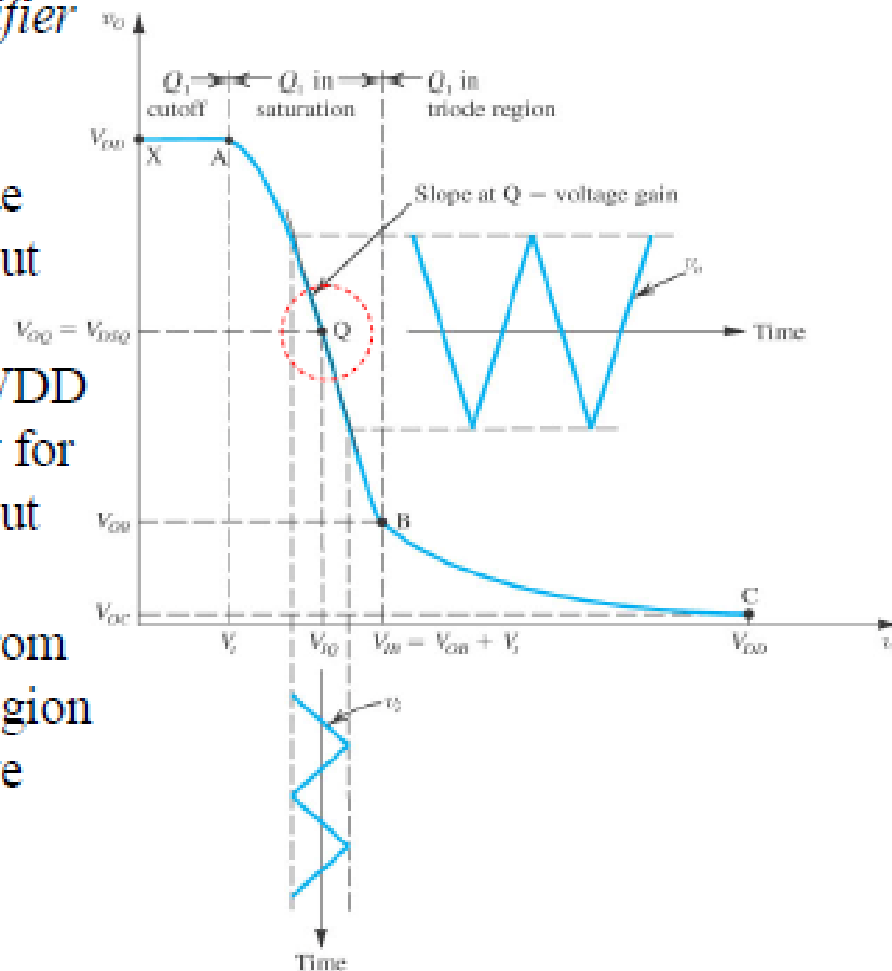
## Operation as a Linear Amplifier

- $V_{DSQ}$  should be of such value to allow for the required output signal swing
- $V_{DSQ}$  should be lower than VDD by sufficient amount to allow for the positive peaks of the output signal (sufficient *headroom*)
- $V_{DSQ}$  should also be away from the boundary of the Triode region (point B) to allow for negative peaks (sufficient *legroom*)



## How to Bias a MOSFET Amplifier?

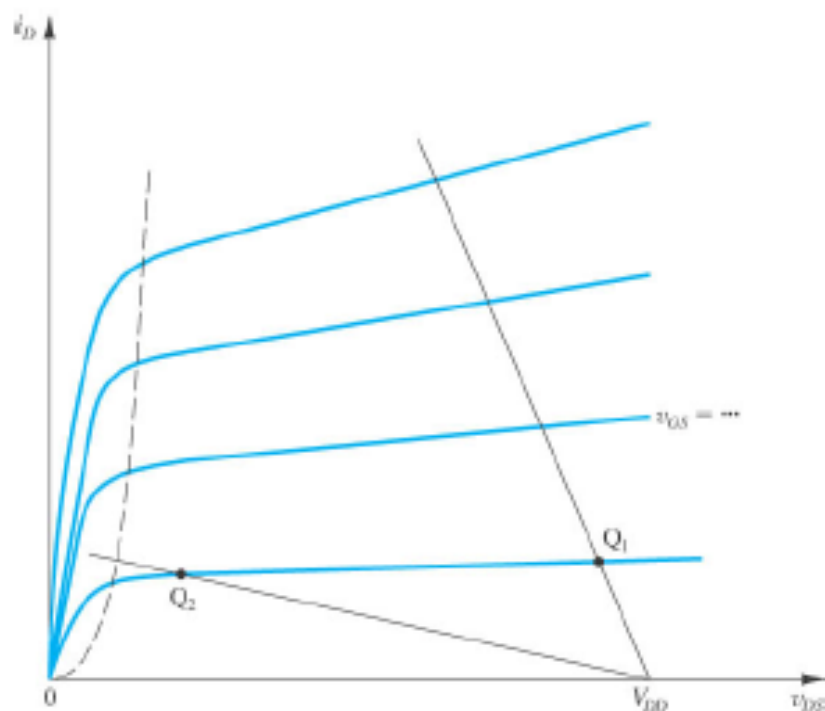

- **Bias Point Q1:** does not leave sufficient room for positive signal swing at the drain (too close to  $V_{DD}$ )
- **Bias Point Q2:** too close to the boundary of the Triode region and might not allow for sufficient negative signal swing

# Analytical Expressions for the Transfer Characteristics

- Derive  $v_o = f(v_i)$

- Cut-off Segment:

$$V_i \leq V_t \text{ and } v_o = V_{DD}$$

- Saturation Segment:

$$v_o = V_{DD} - \frac{1}{2} R_D \mu_n C_{ox} \frac{W}{L} (v_i - V_t)^2$$

$$A_v = -R_D \mu_n C_{ox} \frac{W}{L} (V_{IQ} - V_t)$$

- Triode Segment:

$$v_o = V_{DD} - R_D \mu_n C_{ox} \frac{W}{L} \left[ (v_i - V_t)v_o - \frac{1}{2} v_o^2 \right]$$