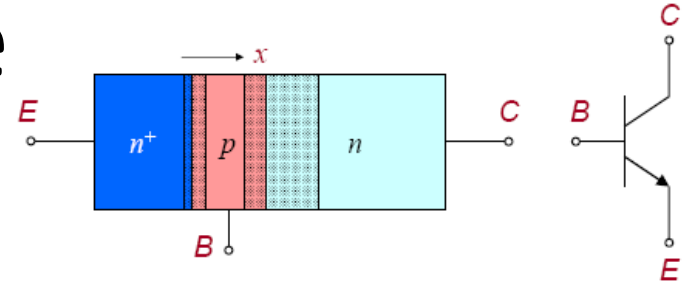


Lecture 16



BJT

Terminals & Ope



- Three terminals:
 - Base (B): very thin and lightly doped central region (little recombination).
 - Emitter (E) and collector (C) are two outer regions sandwiching B.
- Normal operation (linear or active region):
 - B-E junction forward biased; B-C junction reverse biased.
 - The emitter emits (injects) majority charge into base region and because the base very thin, most will ultimately reach the collector.
 - The emitter is highly doped while the collector is lightly doped.
 - The collector is usually at higher voltage than the emitter.

Terminals & Operations

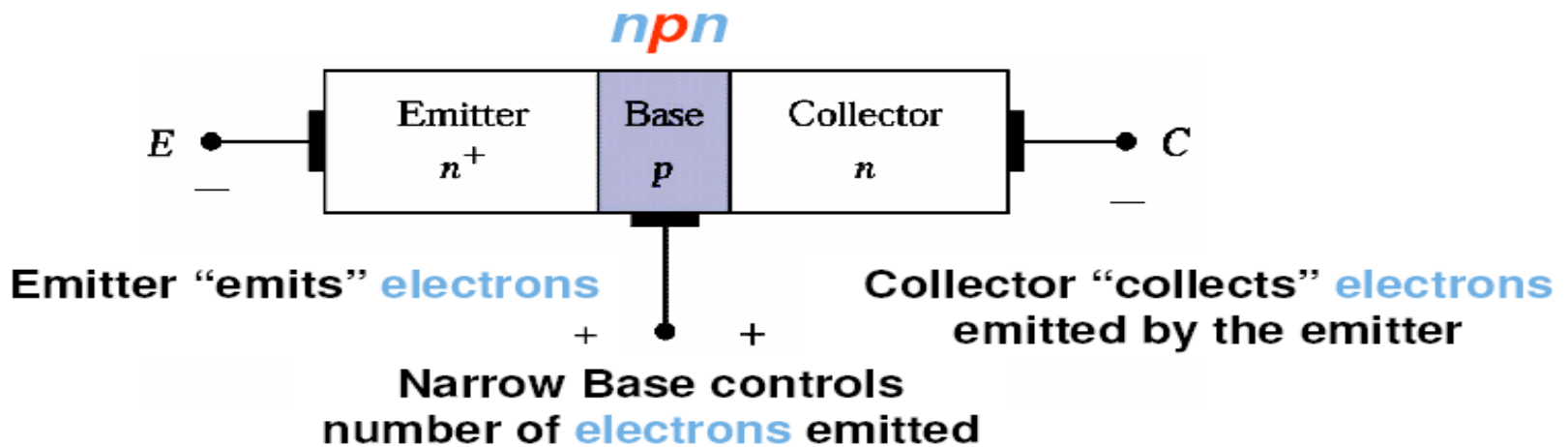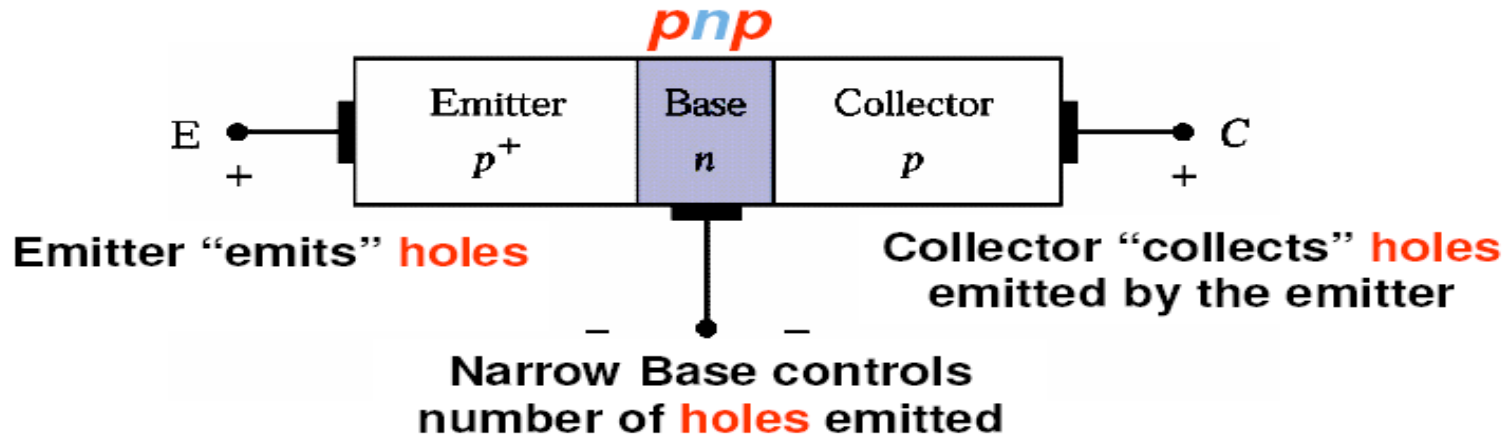


Operation Mode

Operation mode	Biasing polarity <i>B-E</i> junction	Biasing polarity <i>B-C</i> junction
<u>Active</u>	<u>Forward</u>	<u>Reverse</u>
Saturation	Forward	Forward
Cutoff	Reverse	Reverse

* Note: There is also a mode of operation called inverted (active), which is rarely used.

- Active:** Most widely encountered operation, e.g., as **amplifiers**.
Large signal gain, small signal distortion ($i-v$: flat region)
- Saturation:** Equivalent to an **on state** when BJT is used as a **Switch**
High current flow, Low voltage (in digital circuit “zero” logic level)
- Cutoff:** Equivalent to an **off state** when BJT is used as a **Switch**
Low current flow, High voltage (in digital circuit “one” logic level)

Operati

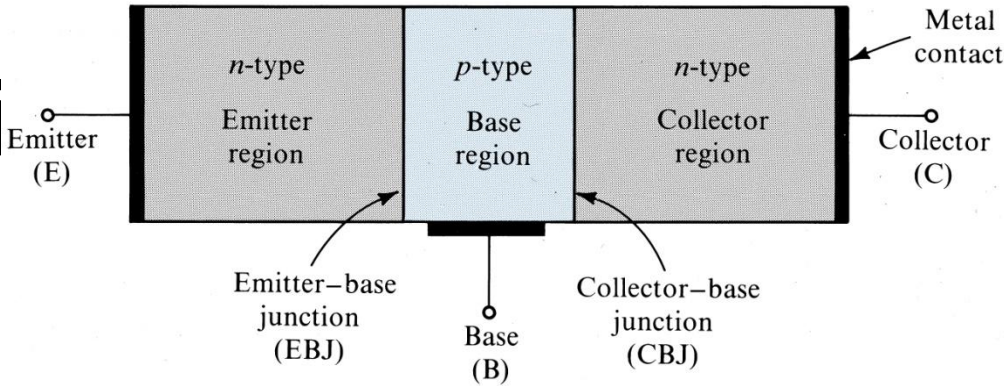


- **Active:**
 - Most importance mode, e.g. for amplifier operation.
 - The region where current curves are practically flat.
- **Saturation:**
 - Barrier potential of the junctions cancel each other out causing a virtual short.
 - Ideal transistor behaves like a closed switch.
- **Cutoff:**
 - Current reduced to zero
 - Ideal transistor behaves like an open switch.

Operation Mode


Four BJT operation modes vs. input and output voltage combinations

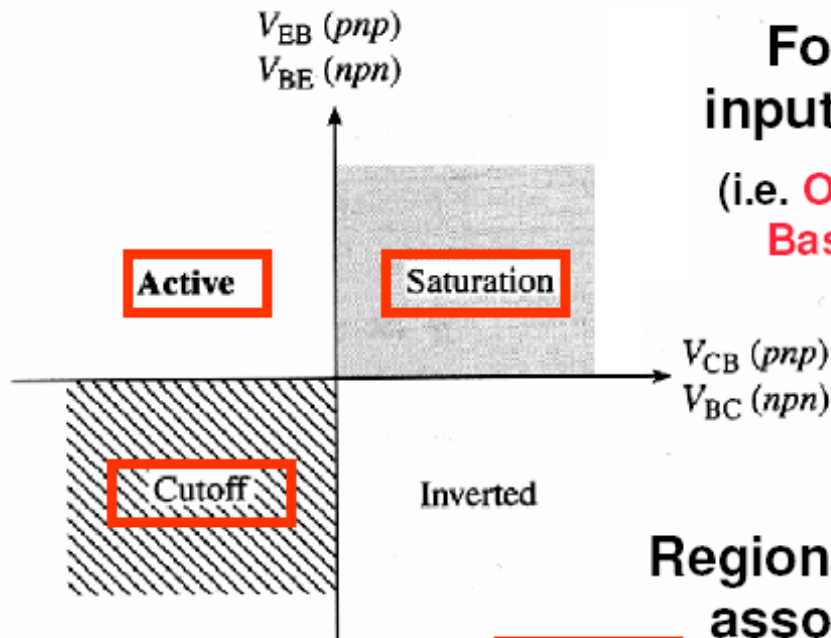(i.e. **Operational modes** can be defined based on **Base-Emitter voltage** and **Base-Collector voltage**)



Note: the inverted (active) mode is rarely used

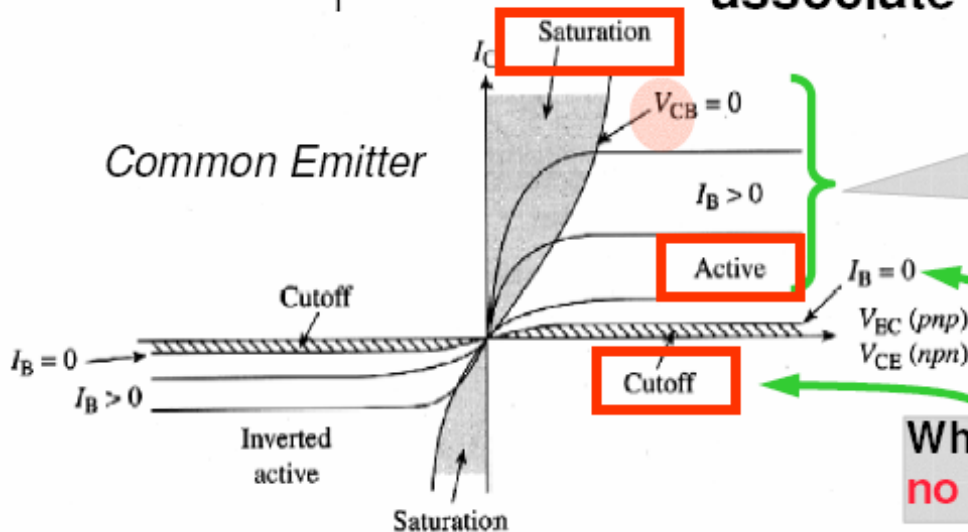
Regions of the BJT CE output characteristics associate with the four operation modes.



When **Base current flows**, a **Collector current can flow**.
The device is then a **current controlled current device**.

When there is **no Base current**, almost **no Collector current flows**.


BJT in Active Mode

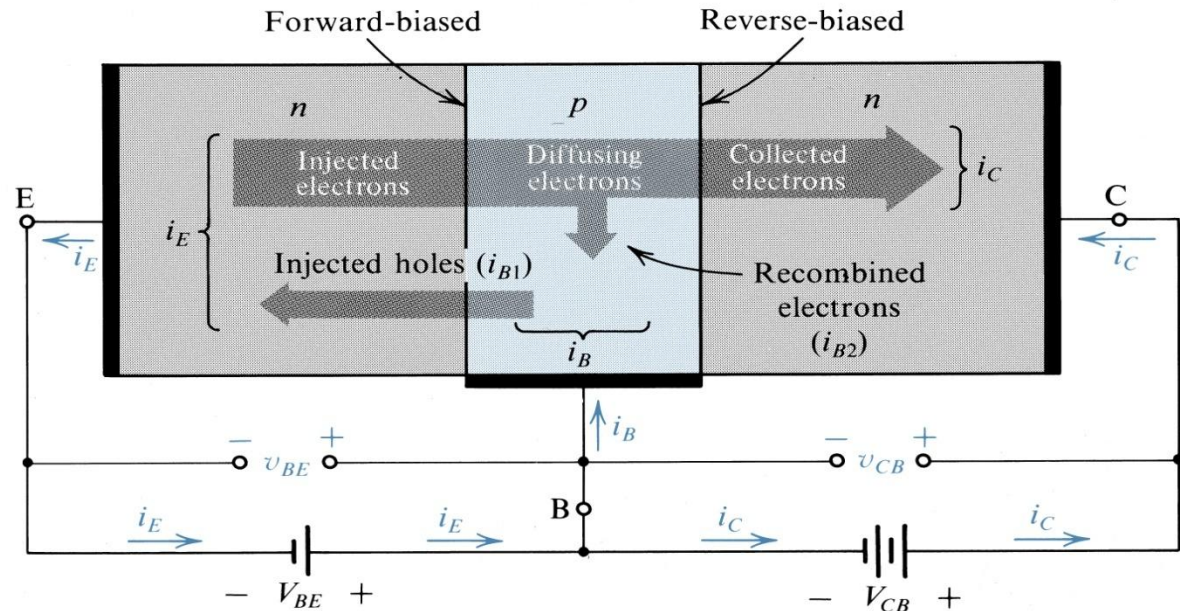


- Operation

- Forward bias of EBJ **injects electrons from emitter into base** (small number of holes injected from base into emitter)
- Most electrons shoot through the base into the collector across the reverse bias junction (think about band diagram)
- **Some electrons recombine with majority carrier** in (P-type) base region

Circuit Symbols

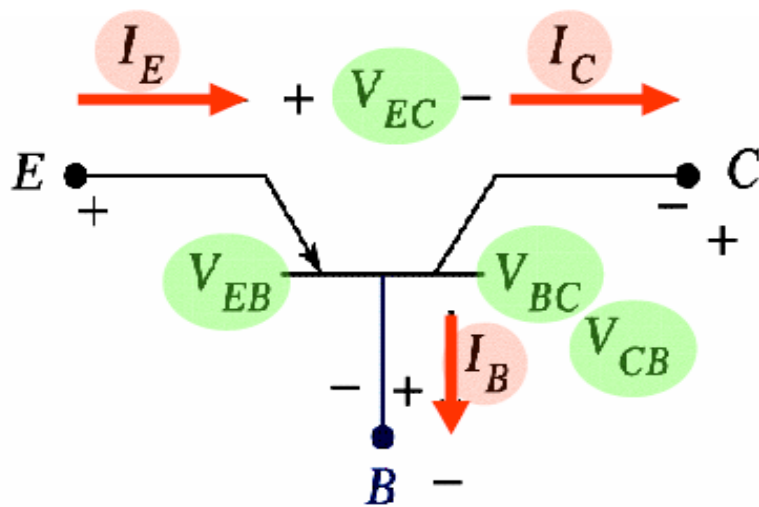

pnp

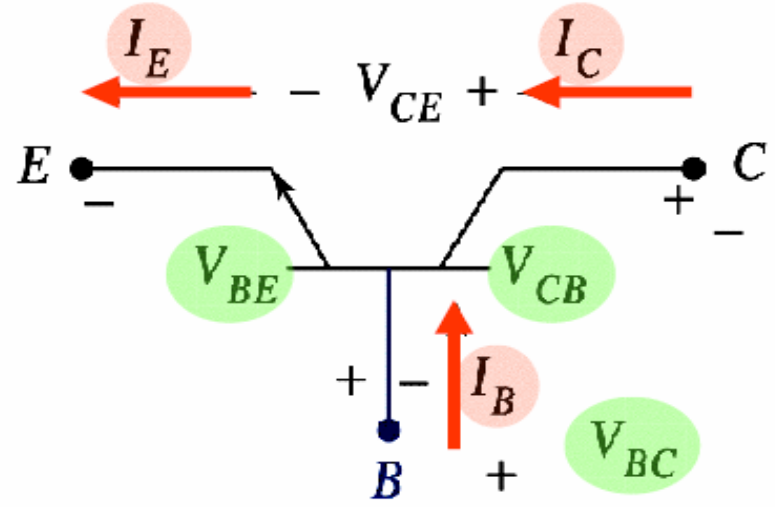

npn

Two of the currents and two of the voltages are independent.

If two of the currents or voltages are known, third terminal current or voltage is determined.

$$I_E = I_B + I_C$$

$$V_{EB} + V_{BC} + V_{CE} = 0$$

Current flowing into a device
= current flowing out of device


$$(V_{CE} = -V_{EC})$$

Circuit Configuration

Common-Base (CB)

input = V_{EB} & I_E


output = V_{CB} & I_C

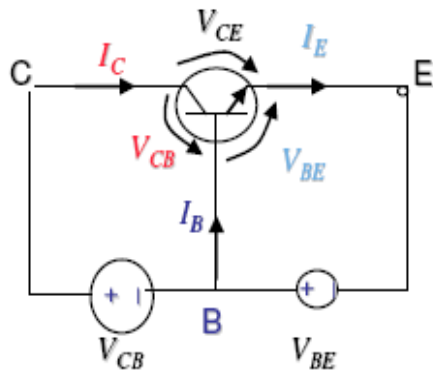

Common-Emitter (CE)

input = V_{BE} & I_B

output = V_{CE} & I_C

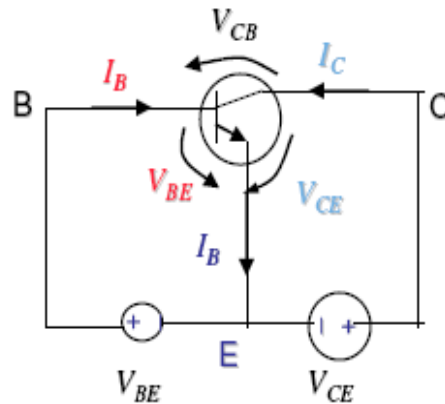

Common-Collector (CC)

input = V_{CB} & I_B

output = V_{CE} & I_E

