

# Lecture 21

BJT



## Ch6 Basic BJT Amplifiers Circuits

### 6.2 Single-Stage BJT Amplifiers

#### Small-Signal Models Analysis

Steps for using small-signal models

1. Determine the DC operating point of the BJT
  - in particular, the collector current
2. Calculate small-signal model parameters:  $r_{be}$
3. Eliminate DC sources
  - replace voltage sources with short circuits and current sources with open circuits
4. Replace BJT with equivalent small-signal models
5. Analysis




# Ch6 Basic BJT Amplifiers Circuits

## 6.2 Single-Stage BJT Amplifiers

### Small-Signal Models Analysis

#### Example 1

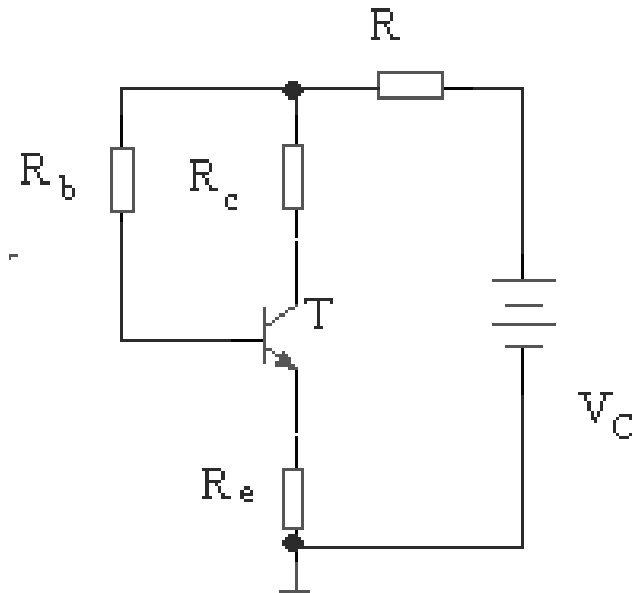

$$V_C = (I_B + I_C)R + I_B R_b + V_{BE} + I_E R_e$$

$$\rightarrow I_B = \frac{V_C - V_{BE}}{R_b + (1 + \beta)(R + R_e)}$$

$$I_C \approx \beta I_B,$$

$$I_E = I_C + I_B = (1 + \beta)I_B$$

$$V_{CE} = V_C - I_C R_C - I_E (R + R_e)$$




# Ch6 Basic BJT Amplifiers Circuits

## 6.2 Single-Stage BJT Amplifiers

### Small-Signal Models Analysis

#### Example 2

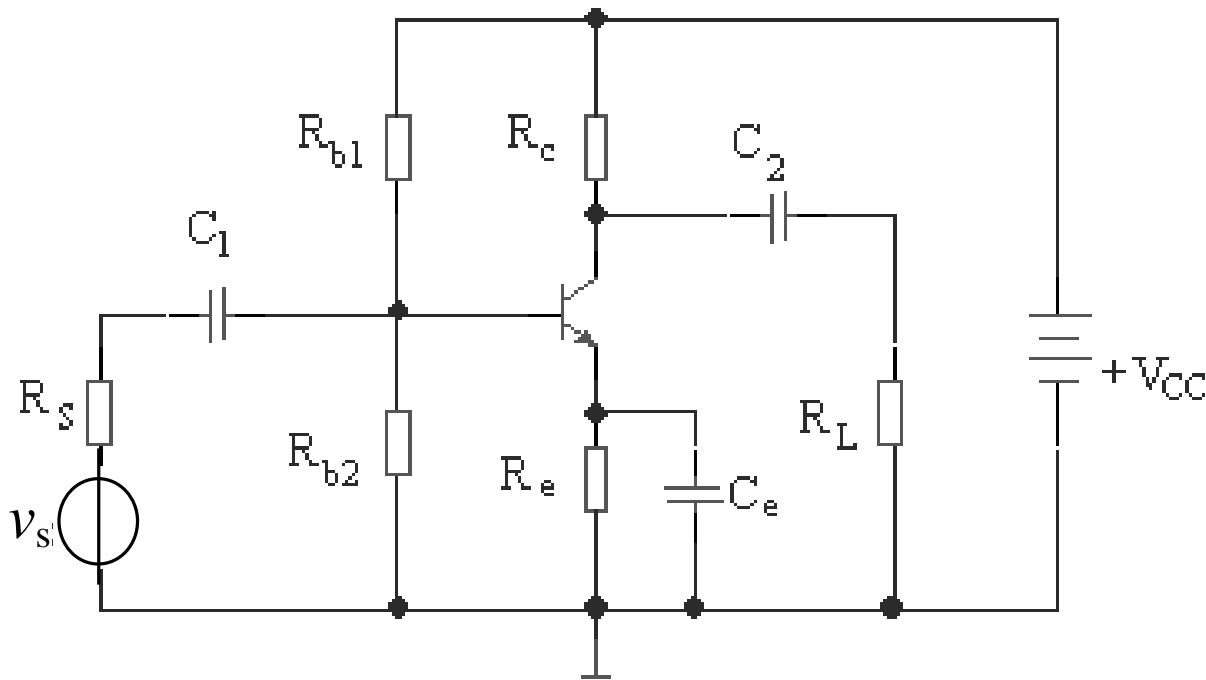

$$V_B = \frac{R_{b2}}{R_{b1} + R_{b2}} V_{CC}$$

$$I_C \approx I_E = \frac{V_B - V_{BE}}{R_e} \approx V_B / R_e$$

$$I_B = \frac{I_C}{\beta}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_e)$$




# Ch6 Basic BJT Amplifiers Circuits

## 6.2 Single-Stage BJT Amplifiers

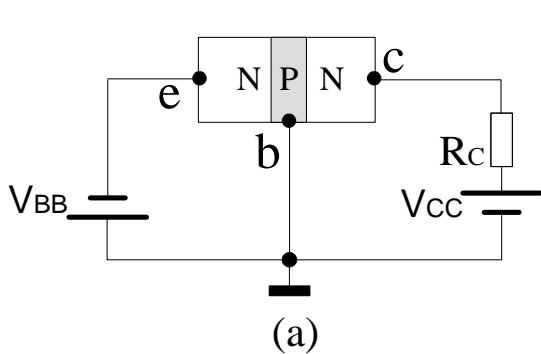
### Small-Signal Models Analysis

There are three basic configurations for single-stage BJT amplifiers:


- Common-Emitter
- Common-Base
- Common-Collector



$$V_E < V_B < V_C$$

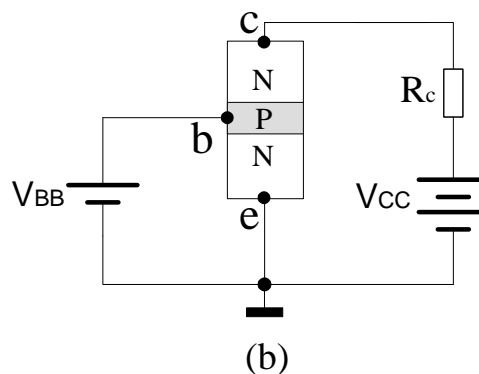

$$V_E < V_B < V_C$$

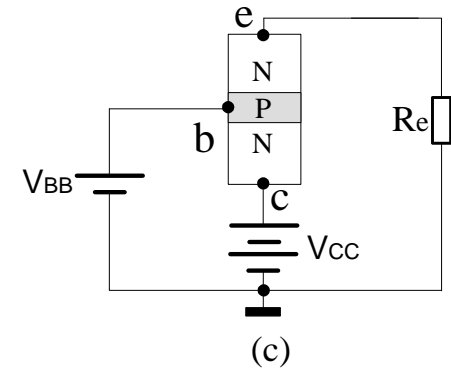


$$V_E < V_B < V_C$$



# Ch6 Basic BJT Amplifiers Circuits

## 6.2 Single-Stage BJT Amplifiers

### Common-Collector Amplifier

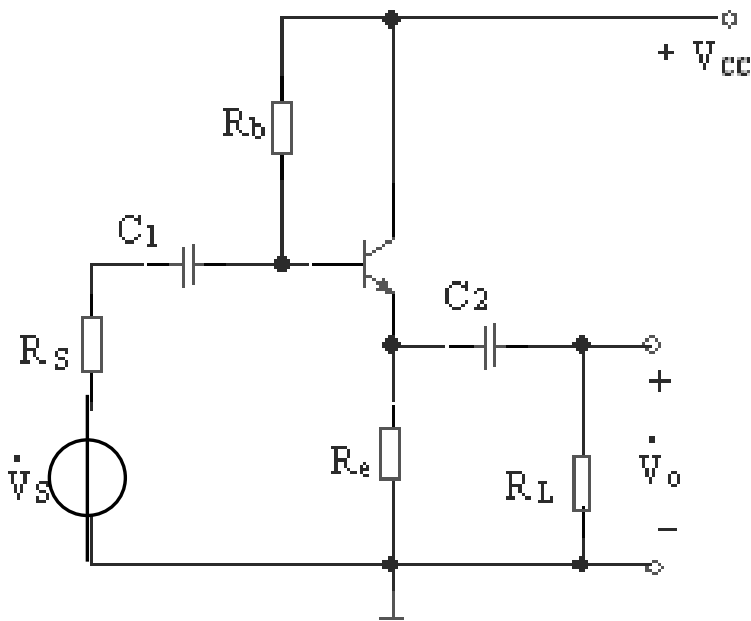

$$V_{CC} = I_B R_b + V_{BE} + I_E R_e = I_B R_b + V_{BE} + (1 + \beta) I_B R_e$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_b + (1 + \beta) R_e} \approx \frac{V_{CC}}{R_b + (1 + \beta) R_e}$$

$$I_C = \beta I_B$$

$$V_{CC} = V_{CE} + I_E R_e \approx V_{CE} + I_C R_e$$

$$V_{CE} \approx V_{CC} - I_C R_e$$

Note :  $\dot{V}_o$  is slightly less than  $\dot{V}_i$  due to the voltage drop introduced by  $V_{BE}$

$$A_V \cong 1$$





# Ch6 Basic BJT Amplifiers Circuits

## 6.2 Single-Stage BJT Amplifiers
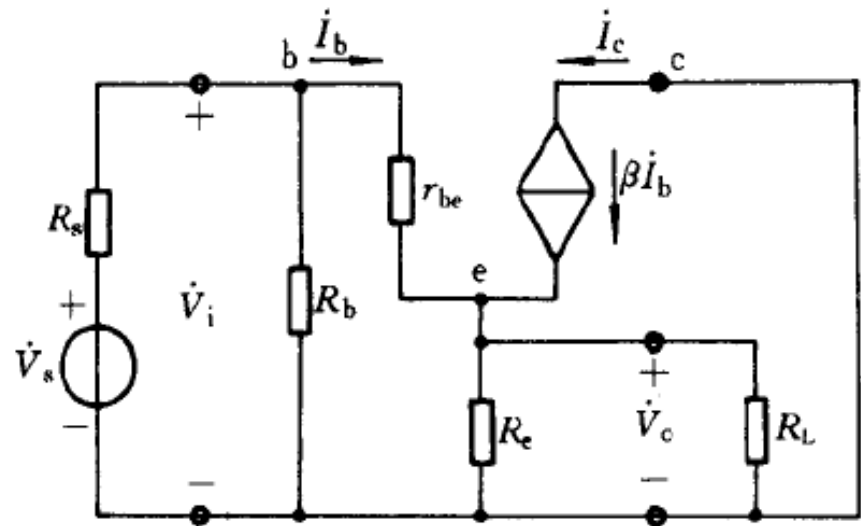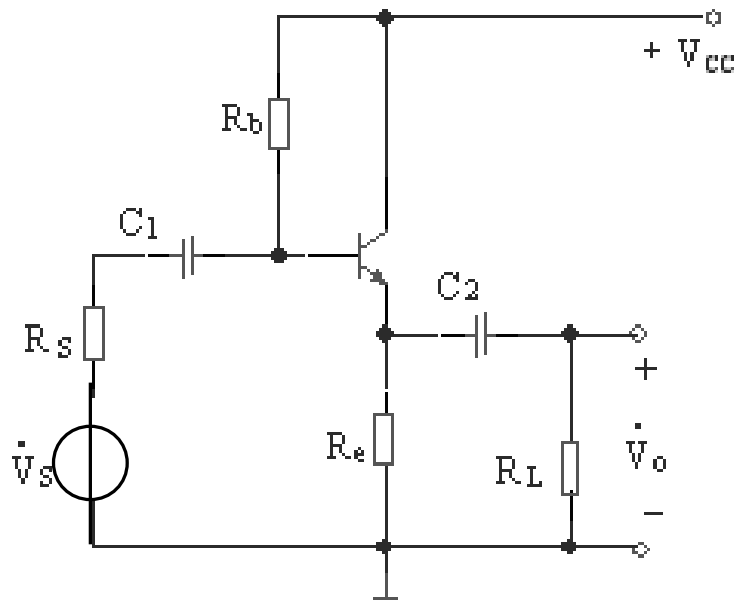
### Common-Collector Amplifier

The last basic configuration is to tie the collector to a fixed voltage, drive an input signal into the base and observe the output at the emitter.





# Ch6 Basic BJT Amplifiers Circuits

## 6.2 Single-Stage BJT Amplifiers


### Common-Collector Amplifier

Let's find  $A_v$ ,  $A_i$ :

$$\dot{V}_o = I_e (R_e \parallel R_L) = I_b (1 + \beta) (R_e \parallel R_L)$$

$$\dot{V}_i = I_b [r_{be} + (1 + \beta) (R_e \parallel R_L)] = I_b r_{be} + I_e (R_e \parallel R_L)$$
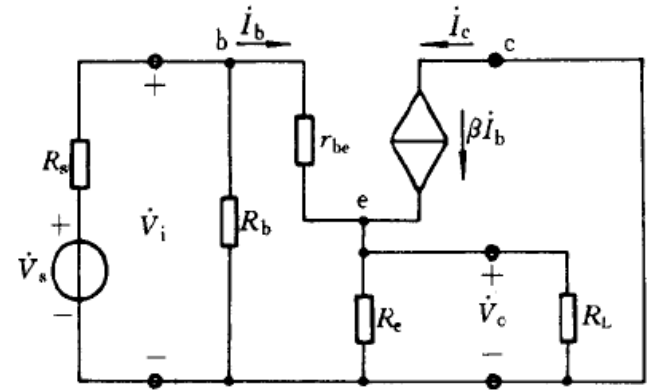
$$\therefore A_v = \frac{\dot{V}_o}{\dot{V}_i} = \frac{(1 + \beta) (R_e \parallel R_L)}{r_{be} + (1 + \beta) (R_e \parallel R_L)} \approx \frac{\beta (R_e \parallel R_L)}{r_{be} + (1 + \beta) (R_e \parallel R_L)} < 1$$







# Ch6 Basic BJT Amplifiers Circuits

## 6.2 Single-Stage BJT Amplifiers

### Common-Collector Amplifier

Let's find  $A_v$ ,  $A_i$ :

$$I_o R_L = I_e (R_e \parallel R_L) = (1 + \beta) I_b (R_e \parallel R_L)$$


$$I_o = I_b \frac{(1 + \beta)(R_e \parallel R_L)}{R_L}$$

$$I_b (r_{be} + (1 + \beta)(R_e \parallel R_L)) = (I_i - I_b) R_b$$

$$I_i = I_b \frac{r_{be} + (1 + \beta)(R_e \parallel R_L) + R_b}{R_b} \approx I_b \frac{(1 + \beta)(R_e \parallel R_L) + R_b}{R_b}$$

$$A_i = \frac{(1 + \beta)(R_e \parallel R_L)}{R_L} \times \frac{R_b}{(1 + \beta)(R_e \parallel R_L) + R_b} \approx \frac{(1 + \beta)(R_e \parallel R_L)}{R_L}$$
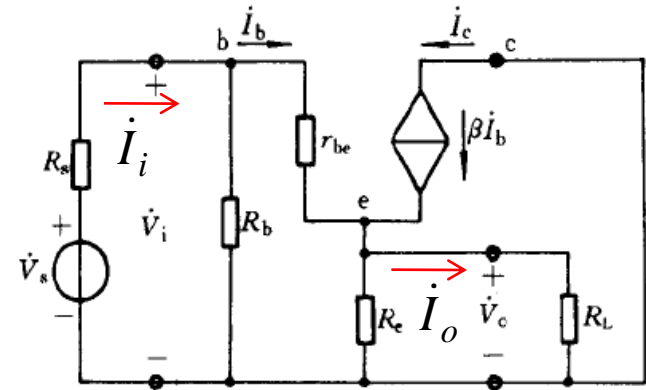
$$A_i \approx \frac{(1 + \beta)(R_e \parallel R_L)}{R_L} \gg 1$$



$(1 + \beta)(R_e \parallel R_L) \ll R_b$




# Ch6 Basic BJT Amplifiers Circuits

## 6.2 Single-Stage BJT Amplifiers

### Common-Collector Amplifier

Let's find  $R_i$ :

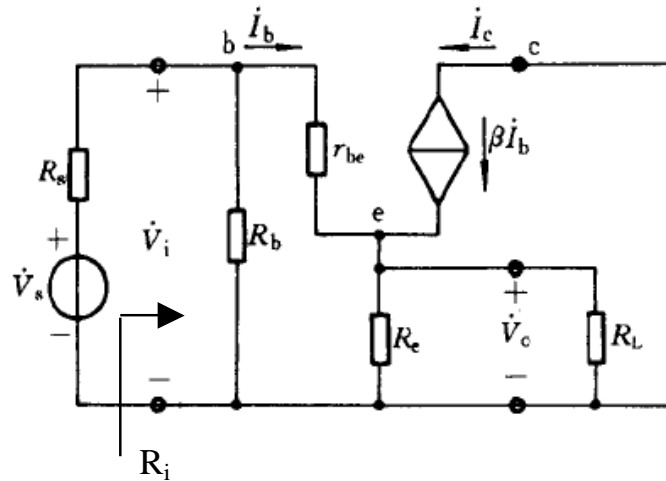

$$v_i = i_b r_{be} + i_e (R_e // R_L) = i_b [r_{be} + (1 + \beta)(R_e // R_L)]$$

$$R'_i = \frac{v_i}{i_b} = r_{be} + (1 + \beta)(R_e // R_L)$$

$$R_i = R'_i // R_b = [r_{be} + (1 + \beta)(R_e // R_L)] // R_b \approx R_b // \beta(R_e // R_L)$$





# Ch6 Basic BJT Amplifiers Circuits

## 6.2 Single-Stage BJT Amplifiers

### Common-Collector Amplifier

Let's find  $R_o$ :

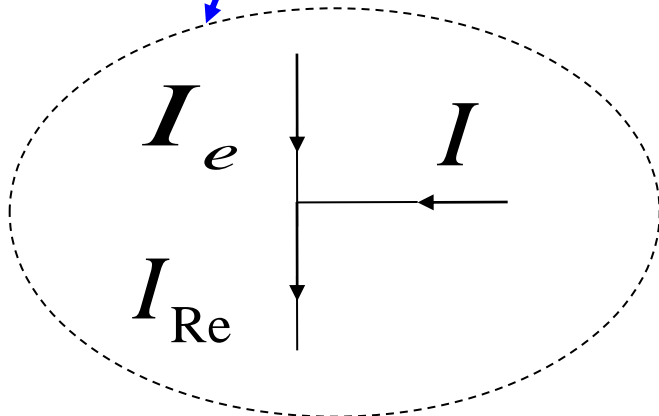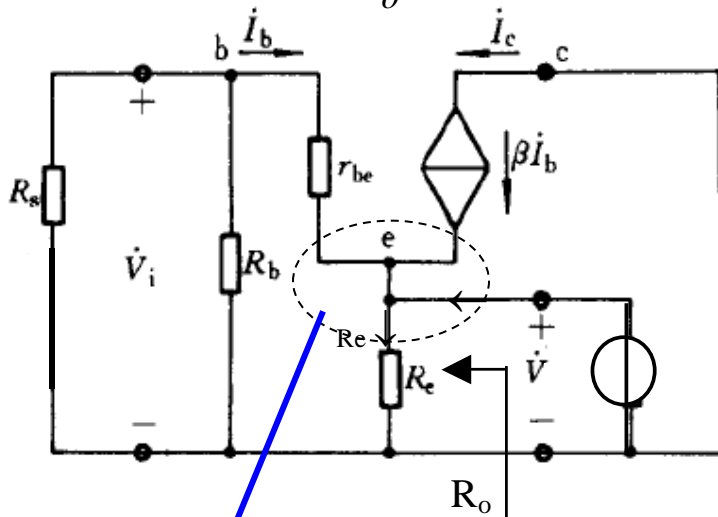

$$I_{Re} = I + I_e \quad I = I_{Re} - I_e$$

$$I = I_{Re} - I_e = I_{Re} - (1 + \beta)I_b$$

$$I = I_{Re} - I_b - \beta I_b$$

$$= \frac{v}{R_e} + (1 + \beta) \frac{v}{r_{be} + R_s // R_b}$$

$$R_o = \frac{v}{i} = \frac{1}{\frac{1}{R_e} + \frac{1}{(r_{be} + R_s // R_b)/(1 + \beta)}}$$



$$= R_e // \frac{(r_{be} + R_s // R_b)}{1 + \beta}$$



# Ch6 Basic BJT Amplifiers Circuits

## 6.2 Single-Stage BJT Amplifiers

### Common-Collector Amplifier

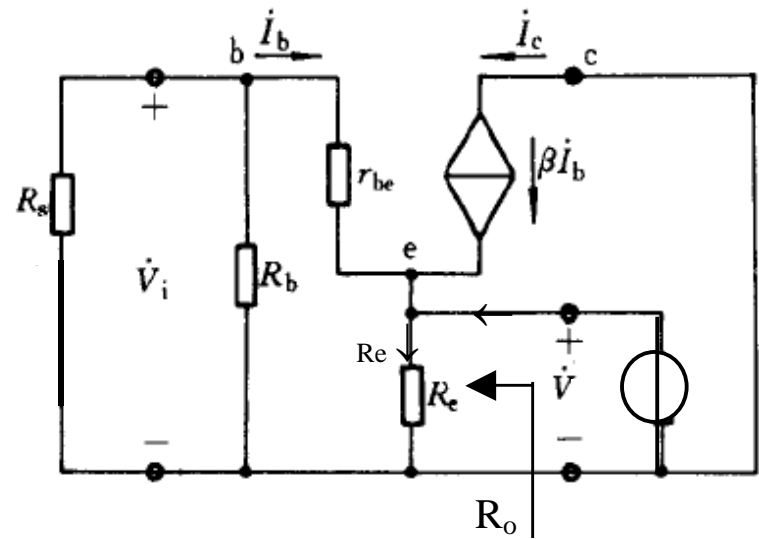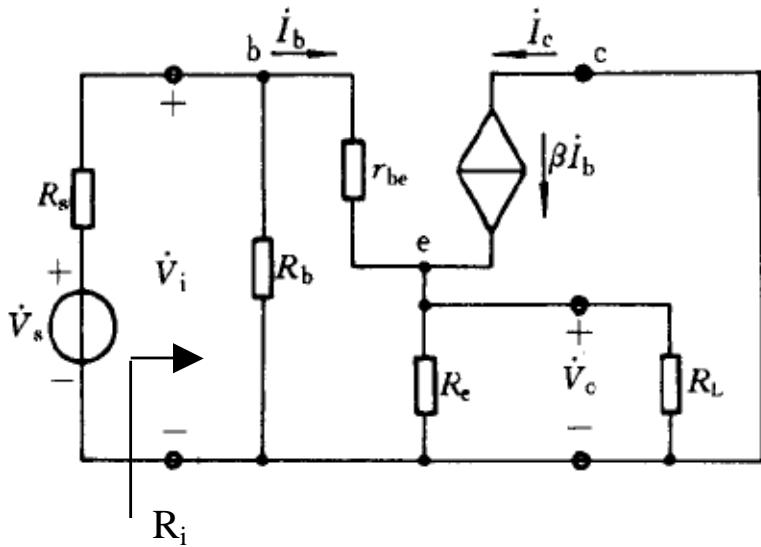

$$R_i = [r_{be} + (1 + \beta)(R_e // R_L)] // R_b$$


$$R_o = R_e // \frac{(r_{be} + R_s // R_b)}{1 + \beta}$$



# Ch6 Basic BJT Amplifiers Circuits

## 6.2 Single-Stage BJT Amplifiers

### Common-Collector Amplifier

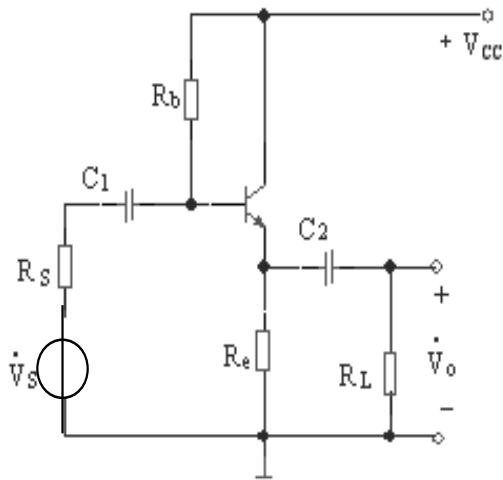

$$A_v = \frac{V_o}{V_i} \approx \frac{\beta(R_e // R_L)}{r_{be} + (1 + \beta)(R_e // R_L)} \approx 1$$

$$A_i \approx \frac{(1 + \beta)(R_e // R_L)}{R_L} \gg 1$$

$$R_i = [r_{be} + (1 + \beta)(R_e // R_L)] // R_b$$

$$R_o = R_e // \frac{(r_{be} + R_s // R_b)}{1 + \beta}$$

C-C amp characteristics:

- Voltage gain is less than unity, but close (to unity) since  $\beta$  is large and  $r_{be}$  is small.
- Also called an emitter follower since the emitter follows the input signal.
- Input resistance is higher, output resistance is lower.
  - Used for connecting a source with a large  $R_s$  to a load with low resistance.