

# Lecture 27

Op- Amp

# Input Impedance

Input Impedance can be regarded as,

$$R_{in} = R_a + R_{\pi} // R'$$


where  $R'$  is the equivalent impedance of the red box circuit, that is

$$R' = \frac{V_{\pi}}{i_f}$$


However, with the below circuit,

$$V_{\pi} - (-AV_{\pi}) = i_f (R_f + R_o)$$
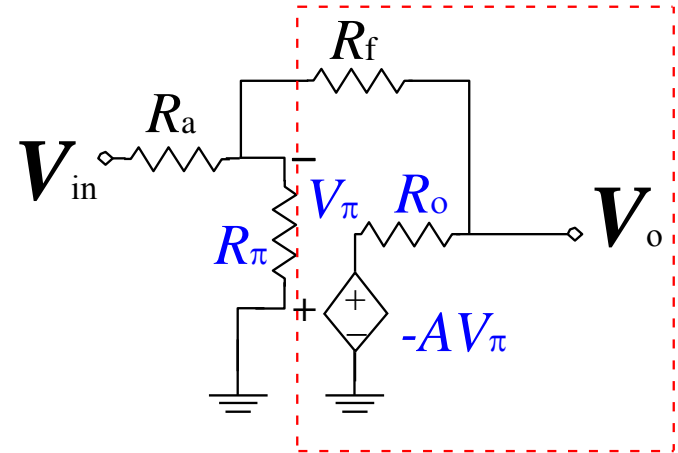
$$\Rightarrow R' = \frac{V_{\pi}}{i_f} = \frac{R_f + R_o}{1 + A}$$



$R'$

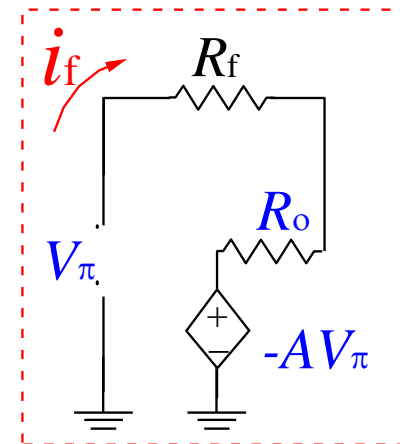

# Input Impedance

Finally, we find the input impedance as,

$$R_{in} = R_a + \left[ \frac{1}{R_\pi} + \frac{1+A}{R_f + R_o} \right]^{-1} \Rightarrow R_{in} = R_a + \frac{R_\pi (R_f + R_o)}{R_f + R_o + (1+A)R_\pi}$$

Since,  $R_f + R_o \ll (1+A)R_\pi$ ,  $R_{in}$  become,

$$R_{in} \sim R_a + \frac{(R_f + R_o)}{(1+A)}$$

Again with  $R_f + R_o \ll (1+A)$

$$R_{in} \sim R_a$$

Note: The op-amp can provide an impedance isolated from input to output

# Output Impedance

Only source-free output impedance would be considered, i.e.  $V_i$  is assumed to be 0

Firstly, with figure (a),

$$V_\pi = \frac{R_a \parallel R_\pi}{R_f + R_a \parallel R_\pi} V_o \Rightarrow V_\pi = \frac{R_a R_\pi}{R_a R_f + R_a R_\pi + R_f R_\pi} V_o$$

By using KCL,  $i_o = i_1 + i_2$

$$i_o = \frac{V_o}{R_f + R_a \parallel R_f} + \frac{V_o - (-AV_\pi)}{R_o}$$

By substitute the equation from Fig. (a),

The output impedance,  $R_{out}$  is

$$\frac{V_o}{i_o} = \frac{R_o (R_a R_f + R_a R_\pi + R_f R_\pi)}{(1 + R_o)(R_a R_f + R_a R_\pi + R_f R_\pi) + (1 + A)R_a R_\pi}$$

$\therefore R_\pi$  and  $A$  comparably large,

$$R_{out} \sim \frac{R_o (R_a + R_f)}{AR_a}$$

