

# Response of First and Second order Systems

# Response of First-Order Systems

- **Initial and final value formulae**

- increasing or decreasing exponential waveforms (for either voltage or current) are given by:


$$v = V_f + (V_i - V_f)e^{-t/T}$$

$$i = I_f + (I_i - I_f)e^{-t/T}$$

- where  $V_i$  and  $I_i$  are the *initial* values of the voltage and current
- where  $V_f$  and  $I_f$  are the *final* values of the voltage and current
- the first term in each case is the **steady-state response**
- the second term represents the **transient response**
- the combination gives the **total response** of the arrangement

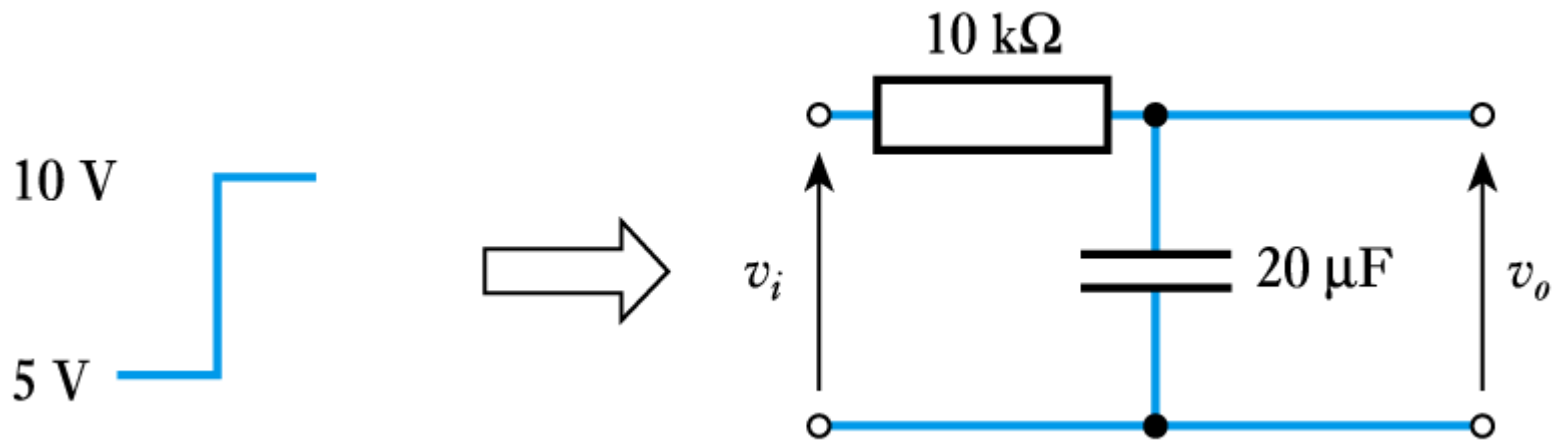
## Example – see **Example 18.3** from course text

The input voltage to the following  $CR$  network undergoes a step change from 5 V to 10 V at time  $t = 0$ . Derive an expression for the resulting output voltage.




Here the initial value is 5 V and the final value is 10 V. The time constant of the circuit equals  $CR = 10 \times 10^3 \times 20 \times 10^{-6} = 0.2\text{s}$ . Therefore, from above, for  $t \geq 0$

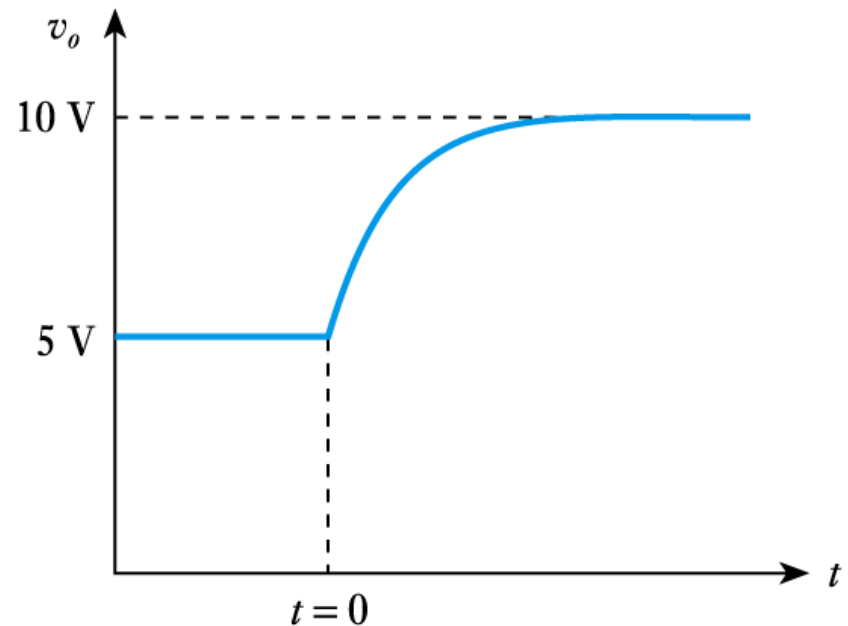
$$\begin{aligned}v &= V_f + (V_i - V_f)e^{-t/T} \\&= 10 + (5 - 10)e^{-t/0.2} \\&= 10 - 5e^{-t/0.2} \text{ volts}\end{aligned}$$



# The nature of exponential curves

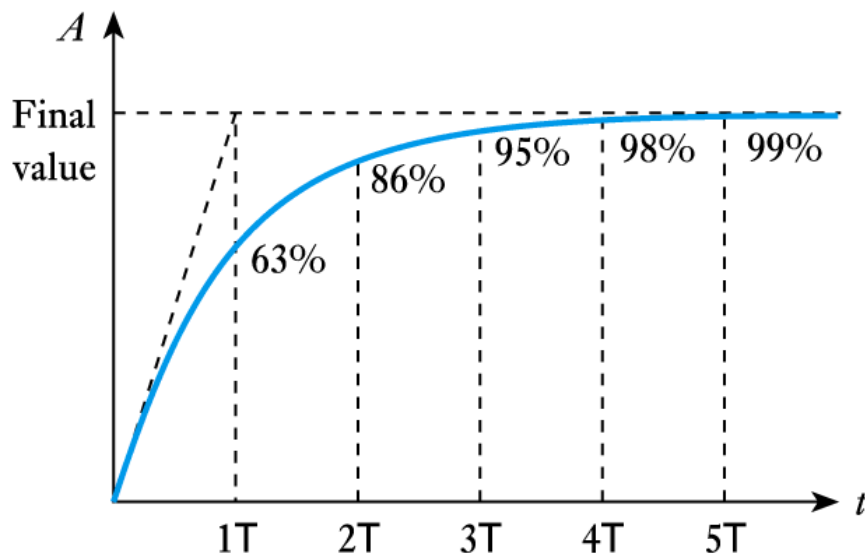


(a)  $A(1 - e^{-t/T})$

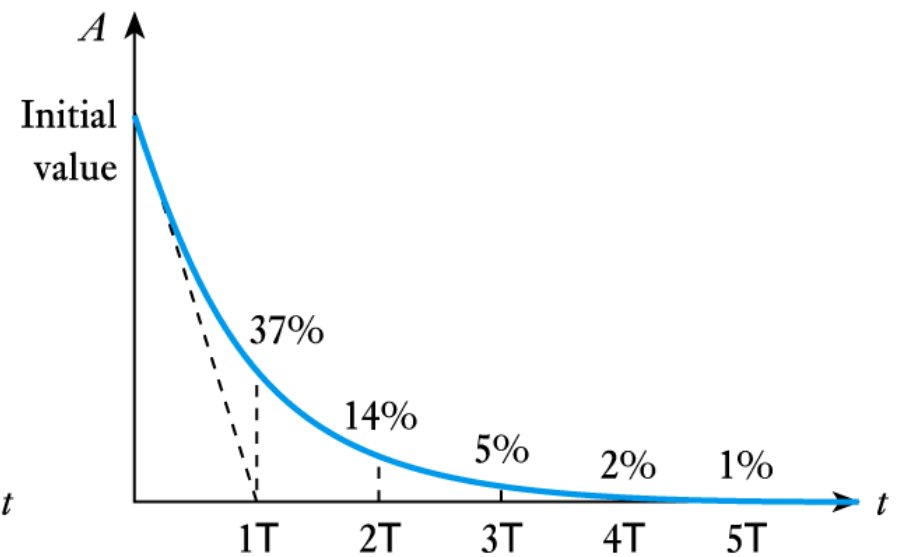

(b)  $A e^{-t/T}$





# Response of first-order systems to a square waveform

— see **Section 18.4.3**

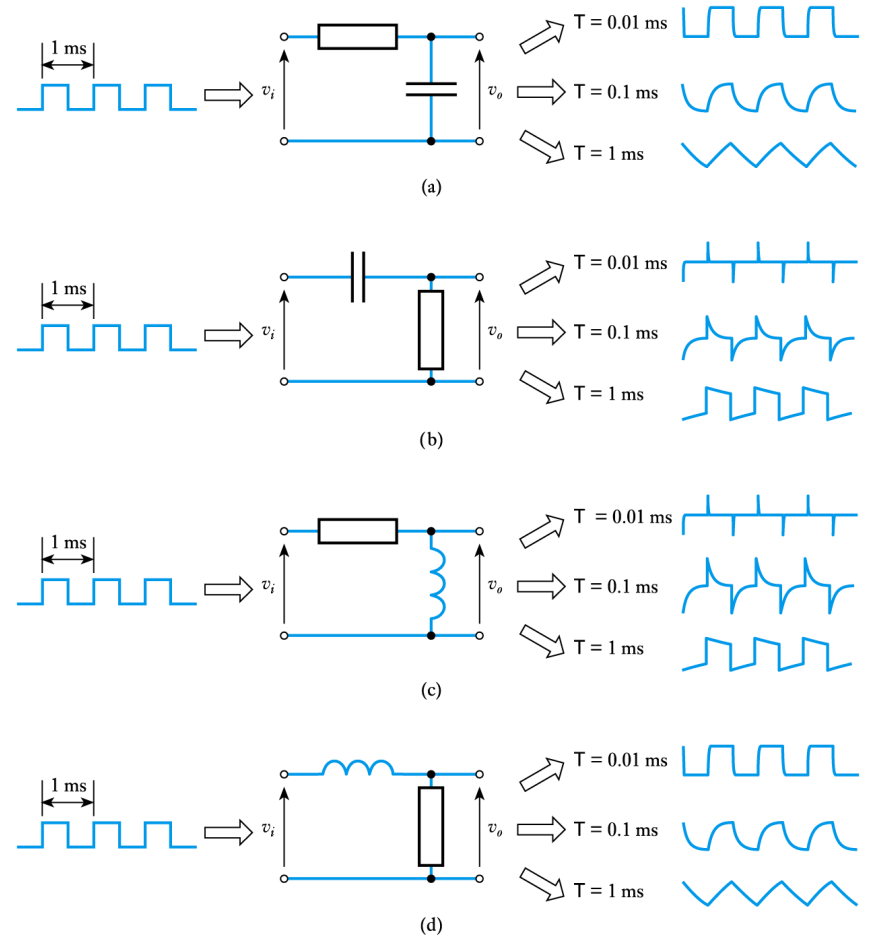

# Response of first-order systems to a square waveform of different frequencies

— see **Section 18.4.3**

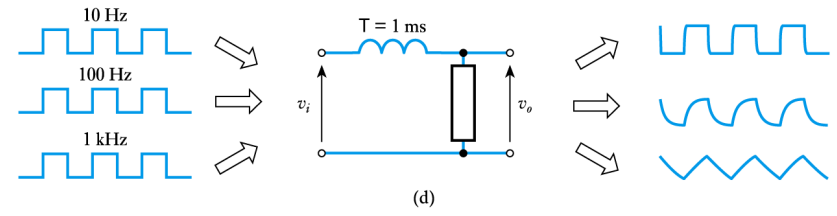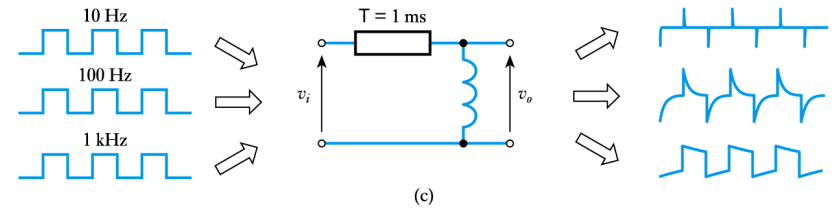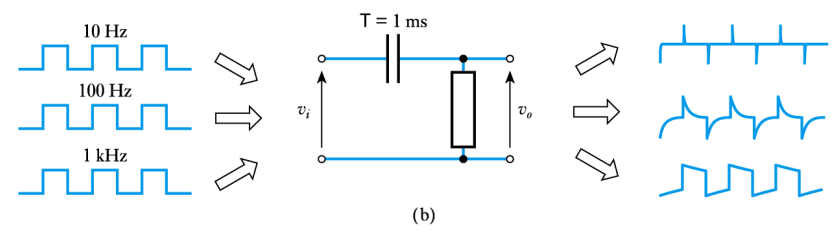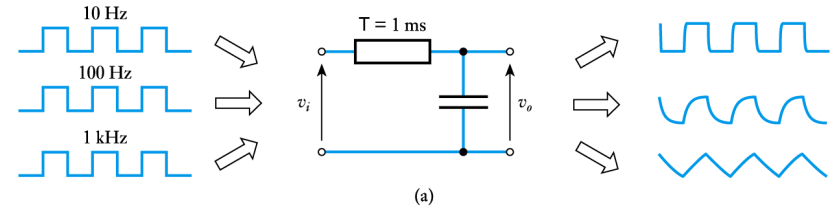


# Second-Order Systems

- Circuits containing both capacitance and inductance are normally described by second-order differential equations. These are termed **second-order systems**

– for example, this circuit
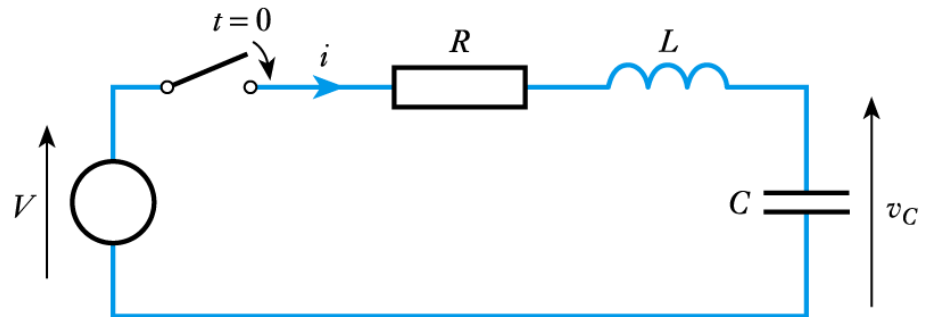
$$LC \frac{d^2 v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C = V$$






- When a step input is applied to a second-order system, the form of the resultant transient depends on the relative magnitudes of the coefficients of its differential equation. The general form of the response is

$$\frac{1}{\omega_n^2} \frac{d^2 y}{dt^2} + \frac{2\zeta}{\omega_n} \frac{dy}{dt} + y = x$$

- where  $\omega_n$  is the **undamped natural frequency** in rad/s and  $\zeta$  (Greek Zeta) is the **damping factor**
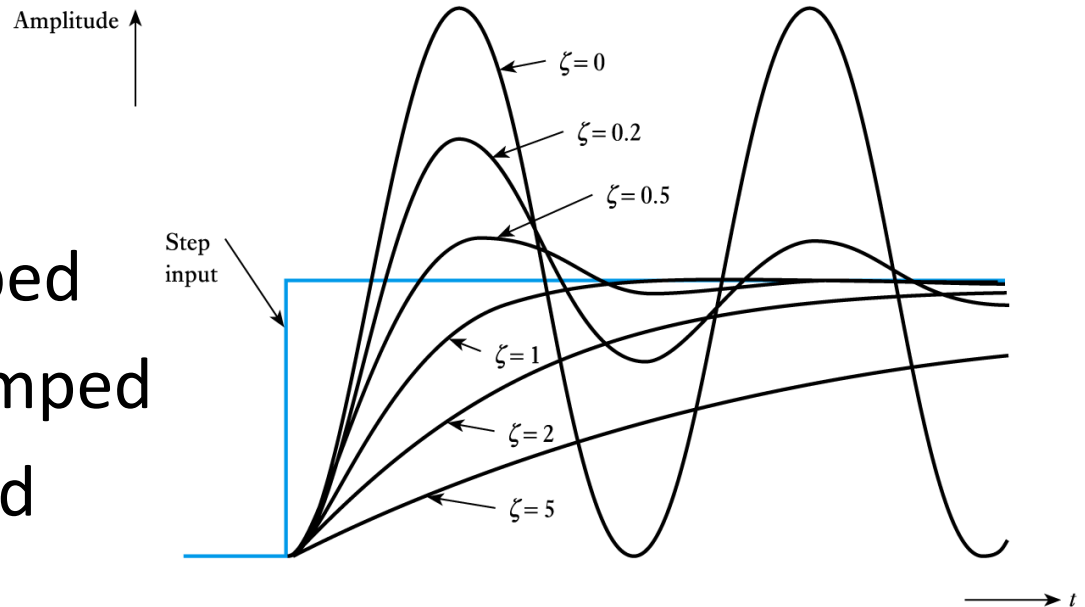
# Response of second-order systems

- $\zeta = 0$  undamped
- $\zeta < 1$  under damped
- $\zeta = 1$  critically damped
- $\zeta > 1$  over damped



# Higher-Order Systems

- Higher-order systems are those that are described by third-order or higher-order equations
- These often have a transient response similar to that of the second-order systems described earlier
- Because of the complexity of the mathematics involved, they will not be discussed further here

# Key Points

- The charging or discharging of a capacitor, and the energising and de-energising of an inductor, are each associated with exponential voltage and current waveforms
- Circuits that contain resistance, and either capacitance or inductance, are termed first-order systems
- The increasing or decreasing exponential waveforms of first-order systems can be described by the initial and final value formulae
- Circuits that contain both capacitance and inductance are usually second-order systems. These are characterised by their undamped natural frequency and their damping factor