Realization of Digital Filters

Discrete Time Systems: Overview

- The difference equation, the impulse response and the system function are equivalent characterization of the input/output relation of a LTI Discrete-time systems.
- LTI system can be modeled using :
 - 1. A Difference/Differential equation, y(n) = x[n] + x[n-1] + ...
 - 2. Impulse Response, h(n)
 - 3. Transfer Function, H(z)
- The systems that are described by the difference equations, can be represented by structures consisting of an interconnection of the basic operations of addition, multiplication by a constant or signal multiplication, delay and advance.

 The Adder, Multiplier, Delay & Advance is shown below:

1. Adder:

$$x[n]$$

$$y[n] = x[n] + y[n]$$

2. Multiplier:


Modulator:

$$x[n] \longrightarrow \bigvee^{A} w[n] = Ax[n]$$

$$x[n]$$

$$y[n] = x[n] y[n]$$

3. Delay:

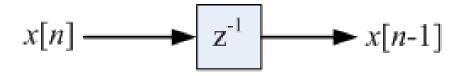


4. Advance:

$$x[n] \longrightarrow z \longrightarrow x[n+1]$$

 Consider a first-order causal LTI IIR digital filter described by

$$y[n] = -d_1y[n-1] + p_0x[n] + p_1x[n-1]$$

The block diagram representation is

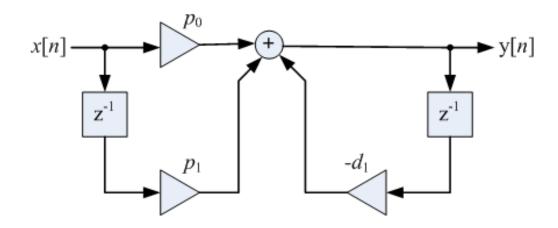

□ Example 1:


Given an LTI system is described by the difference equation below:

$$y(n) - 0.25y(n-1) = 0.5x(n) + 0.5x(n-1)$$

Draw the block diagram representation


- The implementation of LTI system can be realized in terms of Block Diagram and Signal Flow Graph.
- The LTI system can be represented in 2 manner:
 - a. Block Diagram
 - b. Mathematical Model

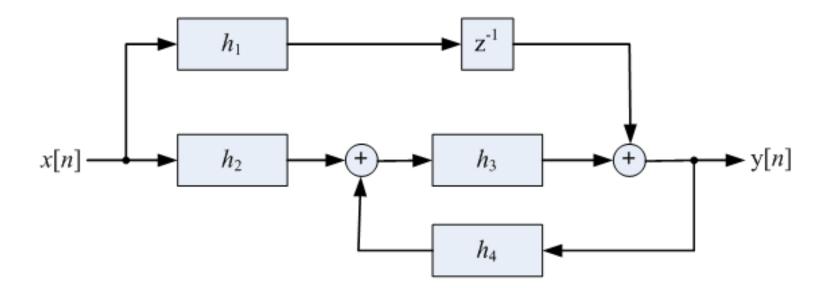• Example of Block diagram is shown below:



Block Diagrams

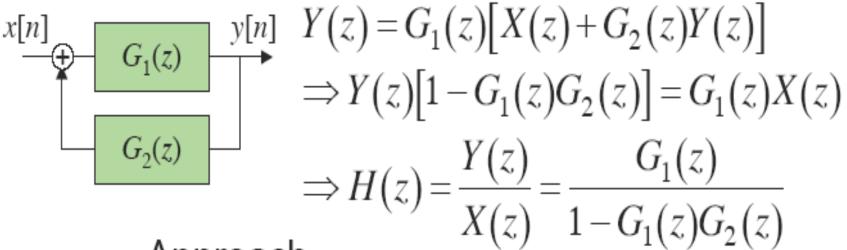- Useful way to illustrate implementations
- Z-transform helps analysis:




- Approach
 - Output of summers as dummy variables
 - Everything else is just multiplicative

Equivalent Structures

- Modifications to block diagrams that do not change the filter
- e.g. Commutation H = AB = BA


$$\longrightarrow A \longrightarrow B \longrightarrow A \longrightarrow A \longrightarrow$$

■ Factoring $AB+CB=(A+C)\cdot B$

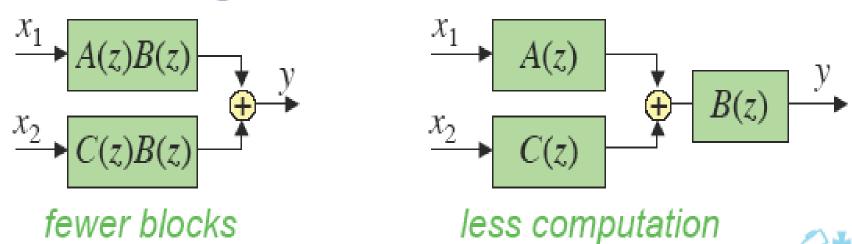

 The Transfer Function of LTI system can be connected in 2 ways :

a. Parallel Connection:

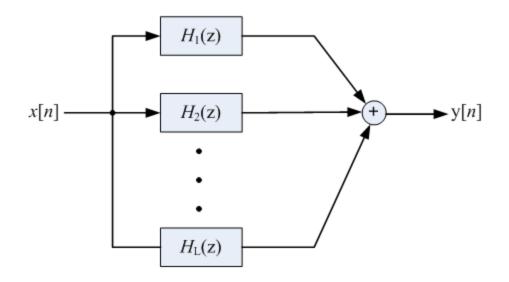

The overall transfer function,

$$H(z) = H_1(z) + H_2(z) + ... + H_L(z)$$

• b. Cascade connection:



The overall transfer function:

$$H(z) = H_1(z).H_2(z)....H_L(z)$$

Each one of them can be implemented using any of the Direct Forms

Canonic

 number of delays in the block diagram representation is equal to the order of the difference equation

- Non-canonic
 - otherwise

FIR FILTER STRUCTURES

FIR FILTERS

- These are realized using only two Forms:
- (as it only has the Numerator part i.e. ALL ZERO SYSTEMS)


 1. Direct Form 1 or Tapped delay Line or Transversal delay Line Filter.

2. Cascade form

FIR Filter Structures


- Direct form
 - An FIR filter of order N requires N + 1 multipliers, N adders and N delays.
 - An FIR filter of order 4
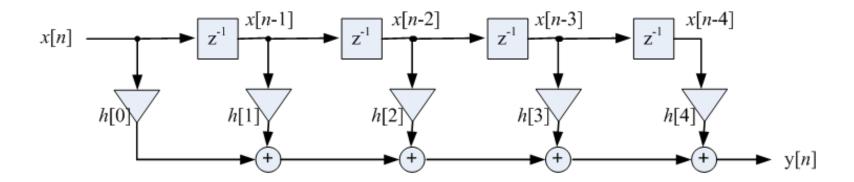
$$y[n] = h[0]x[n] + h[1]x[n-1] + h[2]x[n-2] + h[3]x[n-3] + h[4]x[n-4]$$




FIR Filter Structures

Direct form "Tapped Delay Line"

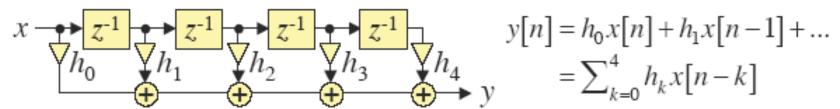

Transpose

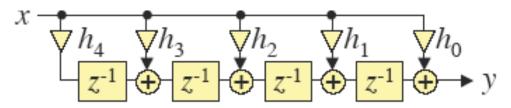

Re-use delay line if several inputs x_i for single output y?

- Cascade form
 - Transfer function H(z) of a causal FIR filter of order N

$$H(z) = \sum_{k=0}^{N} h[k]z^{-k}$$

Factorized form

$$H(z) = h[0] \prod_{k=1}^{k} (1 + \beta_{1k} z^{-1} + \beta_{2k} z^{-2})$$

Where k = N/2 if N is even and k = (N + 1)/2 if N is odd, with $\beta_{2k} = 0$

Example...

 Determine the Direct Form & Cascade Form Realization for the transfer Function of an FIR Digital filter which is given by

$$H(z)=(1-1/4 Z +3/8 Z^2)(1-1/8Z-1/2Z^2)$$


Direct Form

We Simply Expand the equation to get this form as

no as expand one oransier rancoron mas, oras, equation (v) as under


$$H(z) = 1 - \frac{3}{8}z^{-1} - \frac{3}{32}z^{-2} + \frac{5}{64}z^{-3} - \frac{3}{16}z^{-4}$$

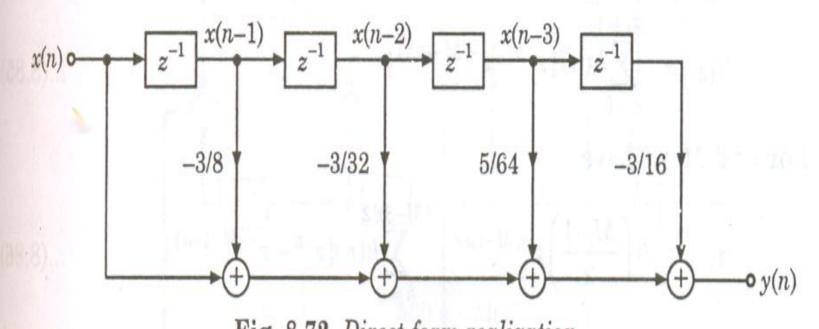This function can be realised in FIR direct form as depicted in figure 8.72.



Cascade Form

• H(z)=H1(z)* H2(z) & hence

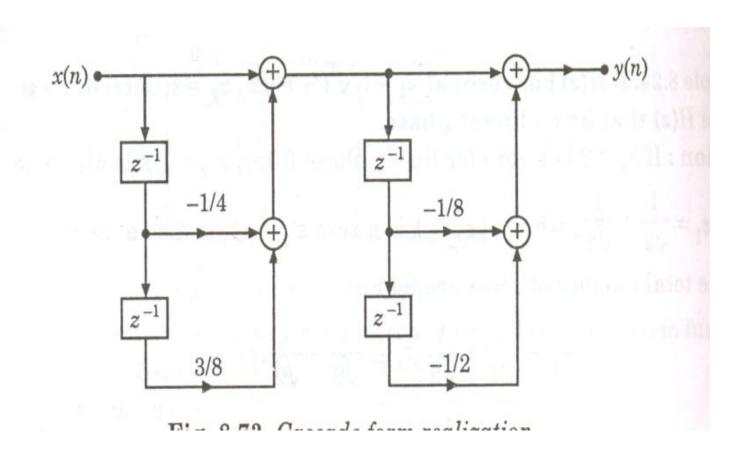


Equivalent Structures


Transpose

- reverse paths
- adders ← nodes
- input↔output

$$Y = b_1 X + b_2 z^{-1} X + b_3 z^{-2} X$$

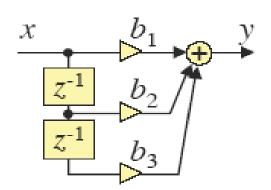= $b_1 X + z^{-1} (b_2 X + z^{-1} b_3 X)$



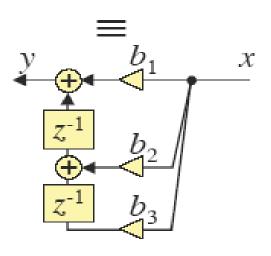

IIR FILTER STRUCTURES

 IIR system/filter can be realized in several structures:

- 1. DIRECT FORM I
- 2. DIRECT FORM II (CANONIC)
- 3. CASCADE FORM
- 4. PARALLEL FORM

IIR System Function


$$H(z) = \frac{Y(z)}{S(z)} = \frac{\sum_{k=0}^{M-1} B_k z^{-k}}{\sum_{k=0}^{N-1} 1 + \sum_{k=1}^{N-1} A_k z^{-k}}$$

where M and N are integer numbers.

Bifurcation of H(z) into H1(z) & H2(z)

247 $H(z) = \frac{\sum_{k=0}^{M-1} B_k z^{-k}}{\sum_{k=0}^{N-1} A_k z^{-k}} = H_1(z) \cdot H_2(z)$ $H_1(z) = \sum_{k=0}^{M-1} B_k z^{-k}$...(7.4) $H_2(z) = \frac{1}{N-1}$ $1 + \sum_{k=1}^{\infty} A_k z^{-k}$ $= \left[1 + \sum_{k=1}^{N} A_k z^{-k}\right]^{-1}$ $= 1 - \sum_{k=1}^{N} A_k z^{-k} = 1 + \sum_{k=1}^{N} (-A_k) z^{-k}$...(7.5)

Block Diagram of Direct Form I & II

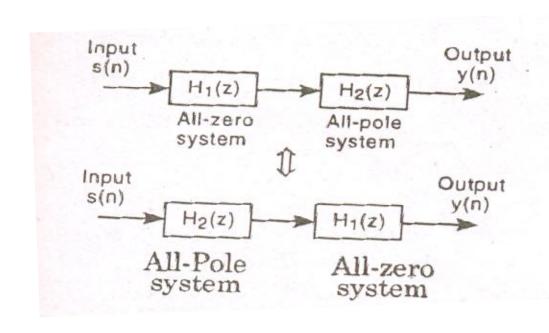

IIR Filter Structures

IIR: numerator + denominator

$$H(z) = \frac{p_0 + p_1 z^{-1} + p_2 z^{-2} + \dots}{1 + d_1 z^{-1} + d_2 z^{-2} + \dots}$$

$$= P(z) \cdot \frac{1}{D(z)}$$
FIR
$$\frac{z^{-1}}{z^{-1}} = \frac{p_1}{p_2}$$

$$\frac{z^{-1}}{z^{-1}} = \frac{p_1}{z^{-1}}$$

$$\frac{z^{-1}}{z^{-1}} = \frac{p_2}{z^{-1}}$$

$$\frac{z^{-1}}{z^{-1}} = \frac{p_2}{z^{-1}}$$


$$\frac{z^{-1}}{z^{-1}} = \frac{p_2}{z^{-1}}$$

$$\frac{z^{-1}}{z^{-1}} = \frac{p_2}{z^{-1}}$$


$$\frac{z^{-1}}{z^{-1}} = \frac{z^{-1}}{z^{-1}}$$

IIR Filter Structures

Hence, Direct form I

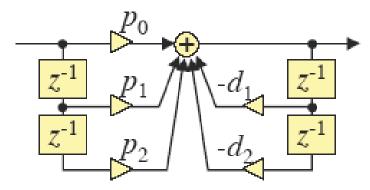


■ Commutation → Direct form II (DF2)

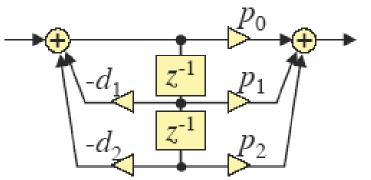


- same signal
 delay lines merge
- "canonical"min. memory usage


Direct Form I Realization

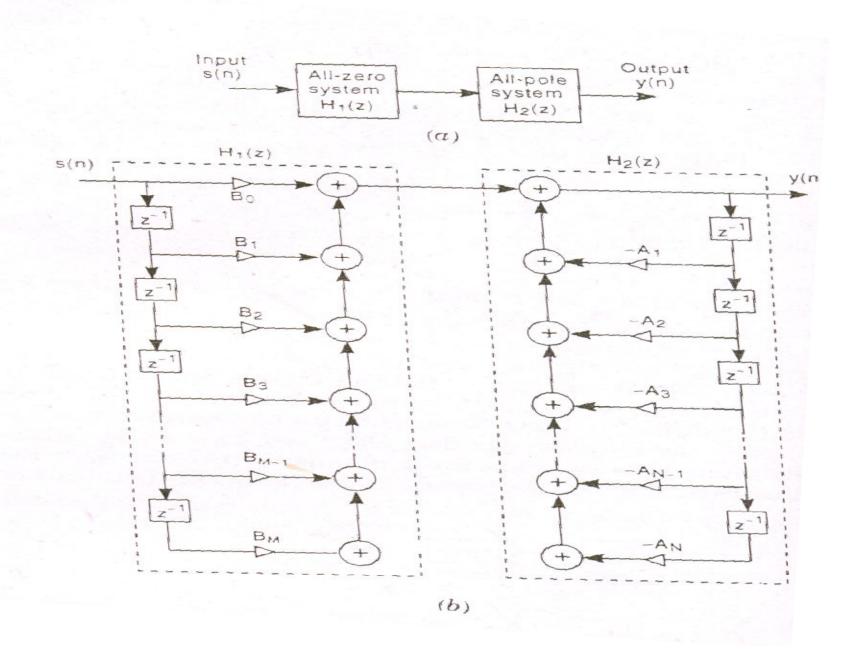

Direct Form II Realization

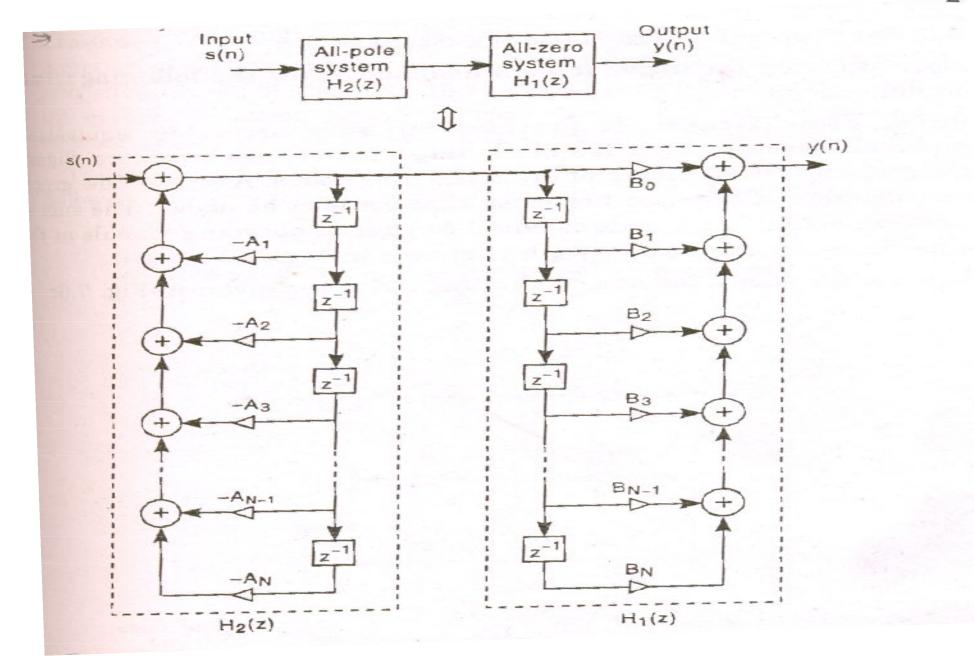

Canonic Direct Form II Realization

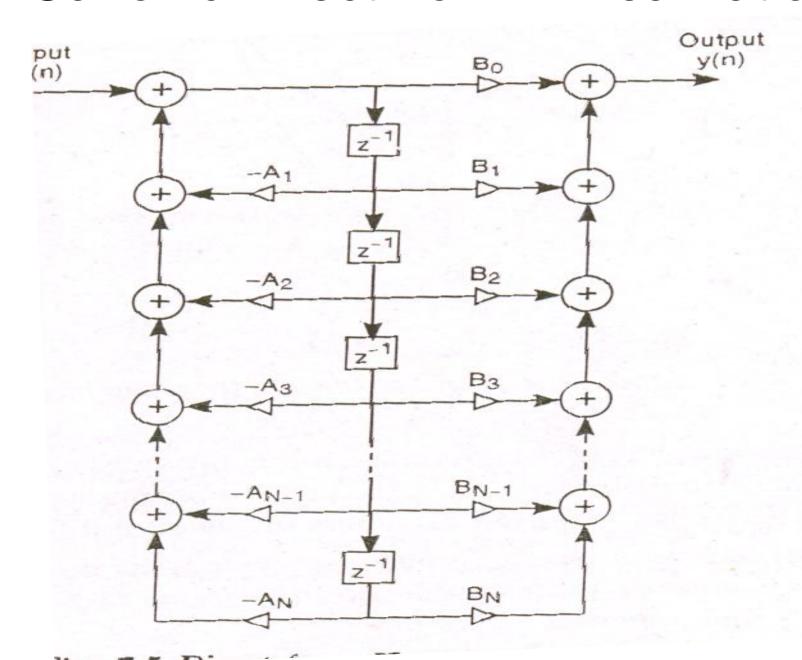

Parallel Form Realization

$$H_k(z) = \frac{B_{k0} + B_{k1}z^{-1}}{1 + A_{k1}z^{-1} + A_{k2}z^{-2}} \qquad \dots (7.9)$$

Coefficients B_{ki} and A_{ki} real-valued system parameters.

Parallel form network structures are shown in Fig. 7.9 and Fig. 7.10.

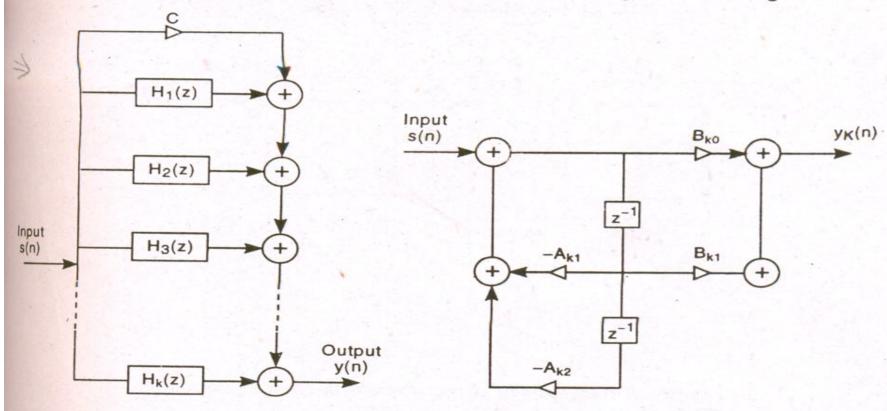


Fig. 7.9 Paralled-form network structure of IIR system.


Fig. 7.10 Structure of IInd order section in a parallel-form network structure realization.

Example..

Example 7.2 Sketch the direct form-I, direct form-II, cascade and parallel-form network structures for the system characterized by following difference equations.


$$y(n) = \frac{3}{4}y(n-1) - \frac{1}{8}y(n-2) + s(n) + \frac{1}{3}s(n-1)$$

Direct Form I

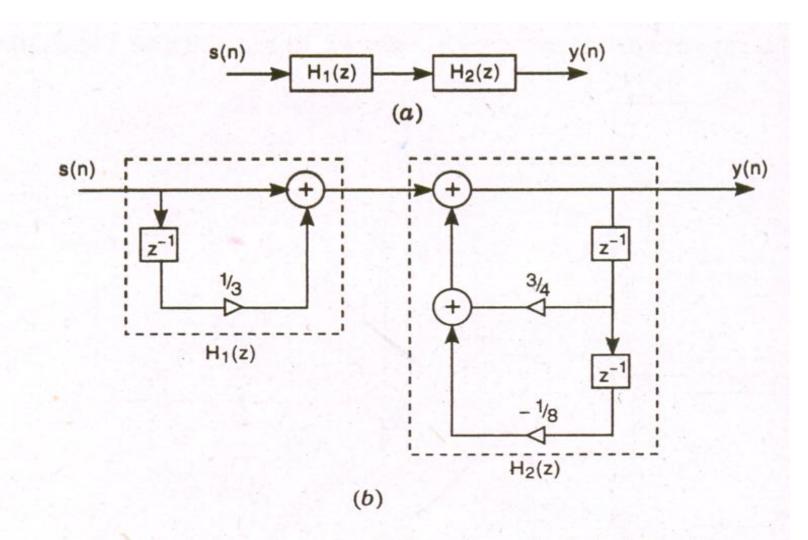

- (a) Block diagram of direct form-I of above problem.
- (b) Direct form-I, network structure of above filter.

Direct Form II & Cascade Form

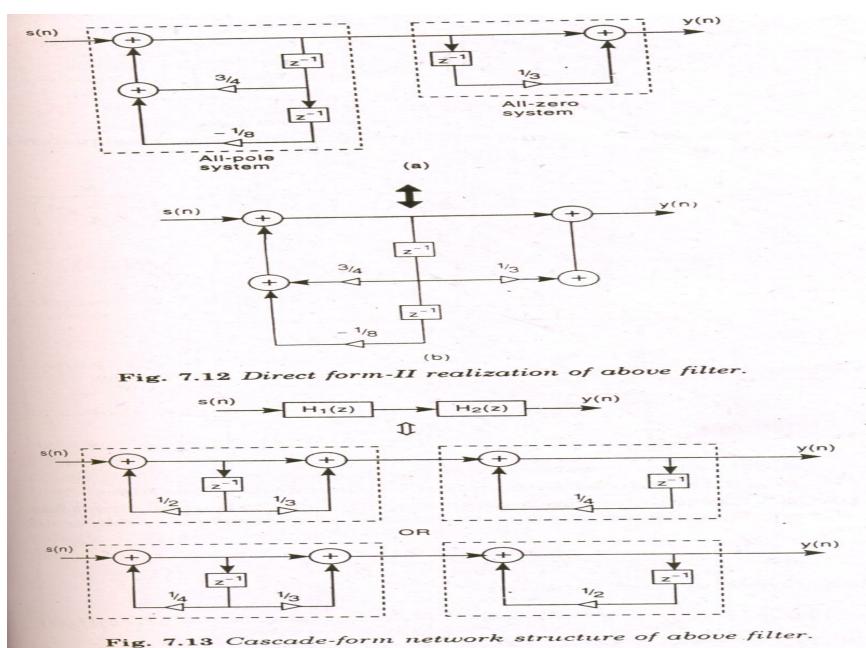

Parallel Form

To get this we use PFE method :

•
$$H(z) = Y(z)/X(z)$$

 Giving us A1=-7/3 & A2= 10/3 so implementing it we have -----

Parallel Form


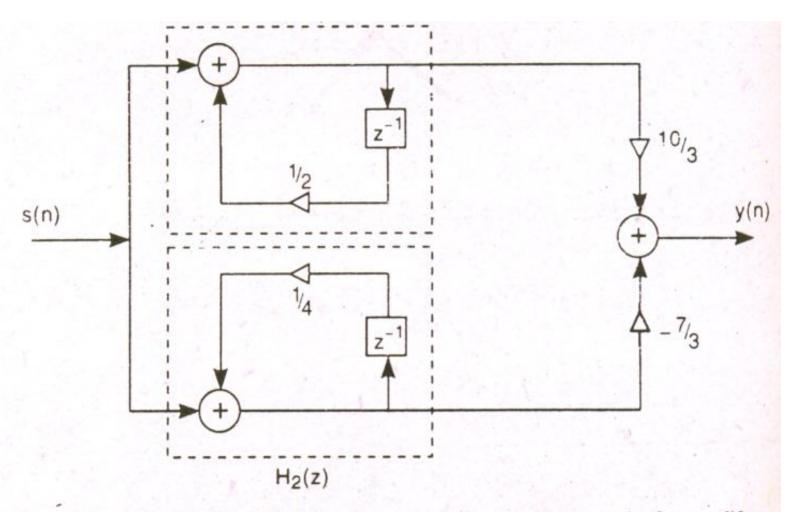


Fig. 7.14 Parallel form network structure of above filter.

 

- Direct Form I
 - Consider a third order IIR described by transfer function

$$H(z) = \frac{P(z)}{D(z)} = \frac{p_0 + p_1 z^{-1} + p_3 z^{-3}}{1 + d_1 z^{-1} + d_3 z^{-3}}$$

Implement as a cascade of two filter section

$$X(z)$$
 \longrightarrow $H_1(z)$ \longrightarrow $H_2(z)$ \longrightarrow $Y(z)$


Where

$$H_1(z) = \frac{W(z)}{X(z)} = P(z) = p_0 + p_1 z^{-1} + p_2 z^{-2} + p_3 z^{-3}$$


and

$$H_2(z) = \frac{Y(z)}{W(z)} = \frac{1}{D(z)} = \frac{1}{1 + d_1 z^{-1} + d_2 z^{-2} + d_3 z^{-3}}$$

Resulting in realization indicated below

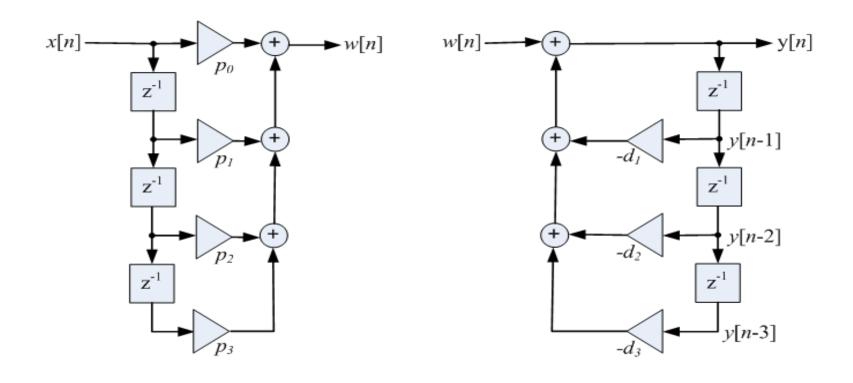


Direct Form I

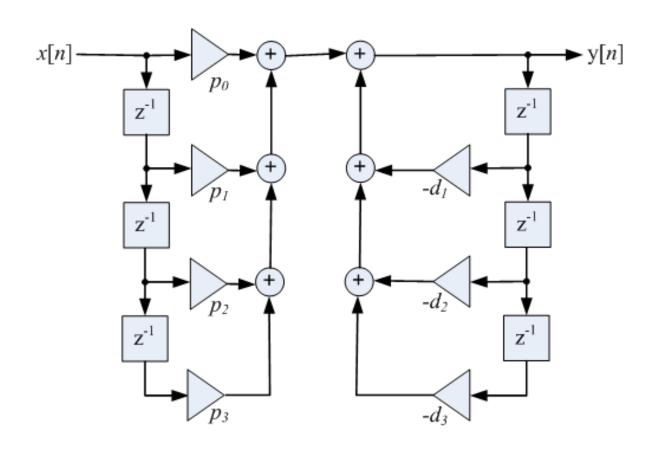

Direct Form II (Canonic)

The two top delays can be shared

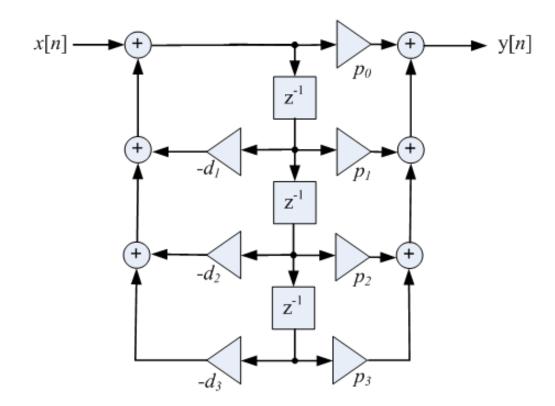


Cascade Form

$$H(z) = p_0 \prod_{k} \left(\frac{1 + \beta_{1k} z^{-1} + \beta_{2k} z^{-2}}{1 + \alpha_{1k} z^{-1} + \alpha_{2k} z^{-2}} \right)$$

A third order transfer function

$$H(z) = p_0 \left(\frac{1 + \beta_{11} z^{-1}}{1 + \alpha_{11} z^{-1}} \right) \left(\frac{1 + \beta_{12} z^{-1} + \beta_{22} z^{-2}}{1 + \alpha_{12} z^{-1} + \alpha_{22} z^{-1}} \right)$$


Cascade Form

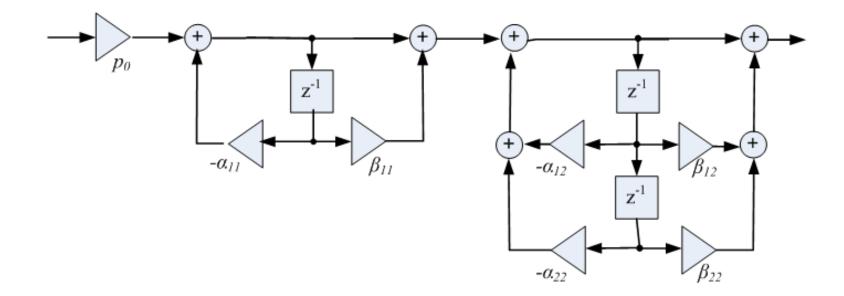

 Parallel Form: Use Partial Fraction Expansion Form to realize them

$$H(z) = \gamma_0 + \sum_{k} \left(\frac{\gamma_{0k} + \gamma_{1k} z^{-1}}{1 + \alpha_{1k} z^{-1} + \alpha_{2k} z^{-2}} \right)$$

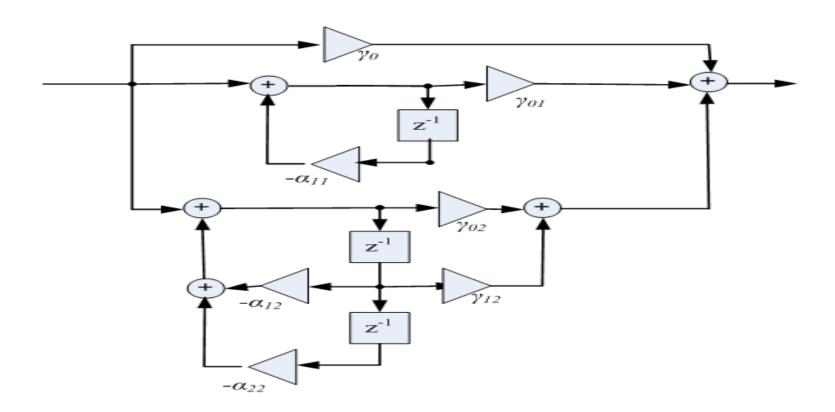 Parallel Form: used in High Speed Filtering applications(as operated parallely)



Parallel IIR Structures

Can express H(z) as sum of terms (IZT)


$$H(z) = \text{consts} + \sum_{\ell=1}^{N} \frac{\rho_{\ell}}{1 - \lambda_{\ell} z^{-1}} \quad \rho_{\ell} = (1 - \lambda_{\ell} z^{-1}) F(z)|_{z = \lambda_{\ell}}$$

Or, second-order terms:

$$H(z) = \gamma_0 + \sum_{k} \frac{\gamma_{0k} + \gamma_{1k} z^{-1}}{1 + \alpha_{1k} z^{-1} + \alpha_{2k} z^{-2}}$$

Suggests parallel realization...

Parallel IIR Structures

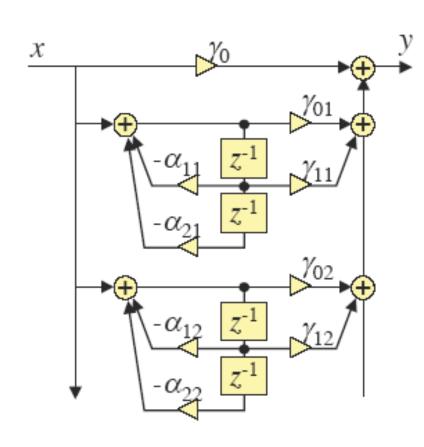

- Sum terms become parallel paths
- Poles of each SOS are from full TF
- System zeros arise from output sum
- Why do this?
 - stability/sensitivity
 - reuse common terms