

Introduction to CMOS VLSI Design

CMOS Transistor Theory

pMOS I-V


- ❑ All dopings and voltages are inverted for pMOS
- ❑ Mobility μ_p is determined by holes
 - Typically 2-3x lower than that of electrons μ_n
 - 120 cm²/V*s in AMI 0.6 μ m process
- ❑ Thus pMOS must be wider to provide same current
 - In this class, assume $\mu_n / \mu_p = 2$

Capacitance

- ❑ Any two conductors separated by an insulator have capacitance
- ❑ Gate to channel capacitor is very important
 - Creates channel charge necessary for operation
- ❑ Source and drain have capacitance to body
 - Across reverse-biased diodes
 - Called diffusion capacitance because it is associated with source/drain diffusion


Gate Capacitance

 - Approximate channel as connected to source
- $C_{gs} = \epsilon_{ox}WL/t_{ox} = C_{ox}WL = C_{permicron}W$
- $C_{permicron}$ is typically about 2 fF/ μm




Diffusion Capacitance

 - ❑ C_{sb} , C_{db}
- ❑ Undesirable, called *parasitic* capacitance
- ❑ Capacitance depends on area and perimeter
 - Use small diffusion nodes
 - Comparable to C_g for contacted diff
 - $\frac{1}{2} C_g$ for uncontacted
 - Varies with process




Pass Transistors

 - ❑ We have assumed source is grounded
- ❑ What if source > 0 ?
 - e.g. pass transistor passing V_{DD}







Pass Transistors




 
- ❑ We have assumed source is grounded
- ❑ What if source > 0 ?
 - e.g. pass transistor passing V_{DD}
- ❑ $V_g = V_{DD}$
 - If $V_s > V_{DD} - V_t$, $V_{gs} < V_t$
 - Hence transistor would turn itself off
- ❑ nMOS pass transistors pull no higher than $V_{DD} - V_{tn}$
 - Called a degraded “1”
 - Approach degraded value slowly (low I_{ds})
- ❑ pMOS pass transistors pull no lower than V_{tp}



Pass Transistor Ckts

    

Pass Transistor Ckts

    

Effective Resistance

- ❑ Shockley models have limited value
 - Not accurate enough for modern transistors
 - Too complicated for much hand analysis
- ❑ Simplification: treat transistor as resistor
 - Replace $I_{ds}(V_{ds}, V_{gs})$ with effective resistance R
 - $I_{ds} = V_{ds}/R$
 - R averaged across switching of digital gate
- ❑ Too inaccurate to predict current at any given time
 - But good enough to predict RC delay

RC Delay Model

- ❑ Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- ❑ Capacitance proportional to width
- ❑ Resistance inversely proportional to width




RC Values

- ❑ Capacitance
 - $C = C_g = C_s = C_d = 2 \text{ fF}/\mu\text{m}$ of gate width
 - Values similar across many processes
- ❑ Resistance
 - $R \approx 6 \text{ K}\Omega \cdot \mu\text{m}$ in $0.6\mu\text{m}$ process
 - Improves with shorter channel lengths
- ❑ Unit transistors
 - May refer to minimum contacted device ($4/2 \lambda$)
 - Or maybe $1 \mu\text{m}$ wide device
 - Doesn't matter as long as you are consistent


Inverter Delay Estimate

 - Estimate the delay of a fanout-of-1 inverter




Inverter Delay Estimate

 - Estimate the delay of a fanout-of-1 inverter




Inverter Delay Estimate

 - Estimate the delay of a fanout-of-1 inverter



Inverter Delay Estimate

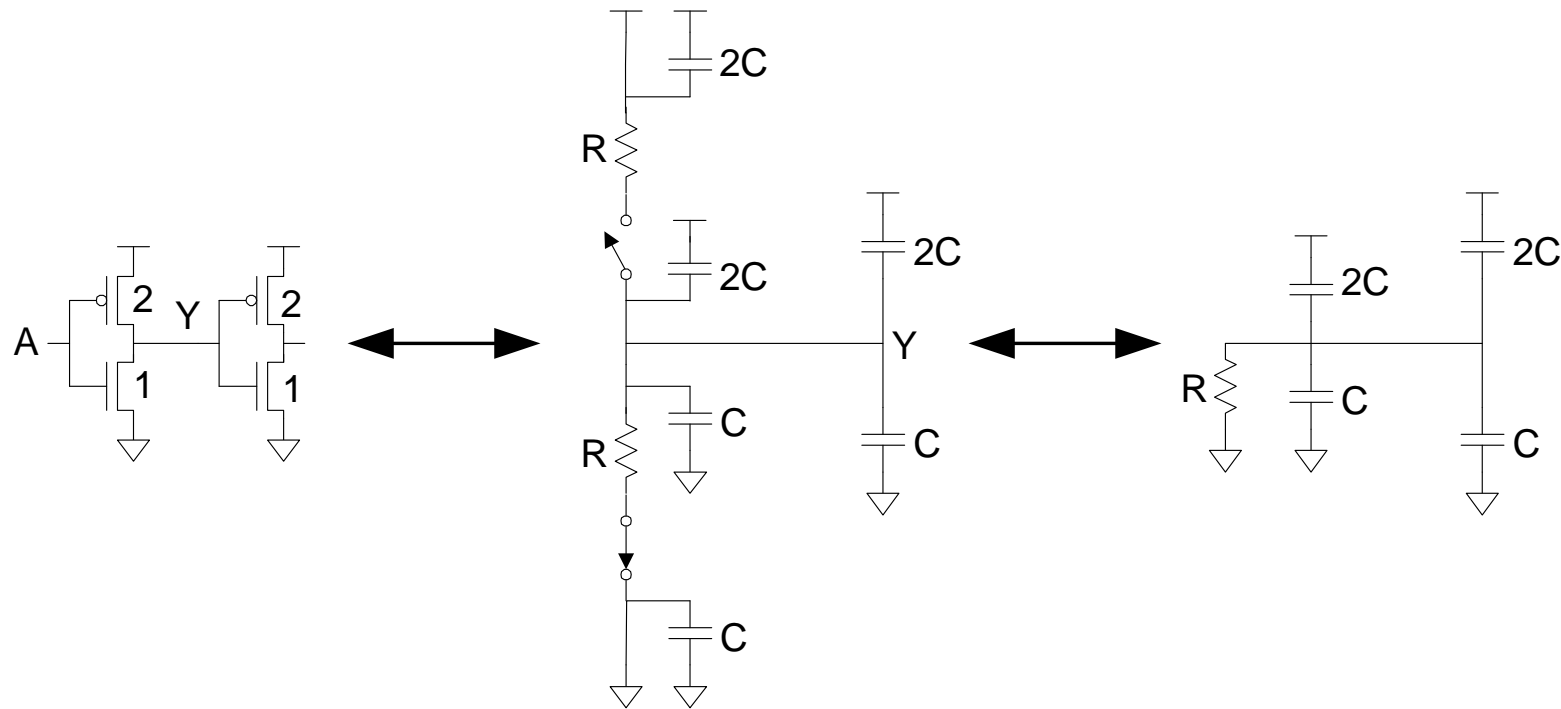- Estimate the delay of a fanout-of-1 inverter



$$d = 6RC$$