

Introduction to CMOS VLSI Design

MOS devices: static and
dynamic behavior

Activity

- 1) If the width of a transistor increases, the current will
increase decrease not change
- 2) If the length of a transistor increases, the current will
increase decrease not change
- 3) If the supply voltage of a chip increases, the maximum transistor current will
increase decrease not change
- 4) If the width of a transistor increases, its gate capacitance will
increase decrease not change
- 5) If the length of a transistor increases, its gate capacitance will
increase decrease not change
- 6) If the supply voltage of a chip increases, the gate capacitance of each transistor will
increase decrease not change

Activity

- 1) If the width of a transistor increases, the current will
increase decrease not change
- 2) If the length of a transistor increases, the current will
increase **decrease** not change
- 3) If the supply voltage of a chip increases, the maximum transistor current will
increase decrease not change
- 4) If the width of a transistor increases, its gate capacitance will
increase decrease not change
- 5) If the length of a transistor increases, its gate capacitance will
increase decrease not change
- 6) If the supply voltage of a chip increases, the gate capacitance of each transistor will
increase decrease **not change**

DC Response

□ DC Response: V_{out} vs. V_{in} for a gate

□ Ex: Inverter

– When $V_{in} = 0$ $\rightarrow V_{out} = V_{DD}$

– When $V_{in} = V_{DD}$ $\rightarrow V_{out} = 0$


– In between, V_{out} depends on transistor size and current

– By KCL, must settle such that

$$I_{dsn} = |I_{dsp}|$$

– We could solve equations

 – But graphical solution gives more insight




Transistor Operation

- ❑ Current depends on region of transistor behavior
- ❑ For what V_{in} and V_{out} are nMOS and pMOS in
 - Cutoff?
 - Linear?
 - Saturation?


nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} <$	$V_{gsn} >$	$V_{gsn} >$
	$V_{dsn} <$	$V_{dsn} >$

 

nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$

 


nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$

$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

 


nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$ $V_{in} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$


$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

 


pMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} >$	$V_{gsp} <$	$V_{gsp} <$
	$V_{dsp} >$	$V_{dsp} <$

 

pMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$

 


pMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$

$$V_{tp} < 0$$

$$V_{dsp} = V_{out} - V_{DD}$$

 


pMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$ $V_{in} > V_{DD} + V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$


$$V_{tp} < 0$$

$$V_{dsp} = V_{out} - V_{DD}$$

 


I-V Characteristics

 - Make pMOS is wider than nMOS such that $\beta_n = \beta_p$




Current vs. V_{out} , V_{in}

 


Load Line Analysis

- For a given V_{in} :
 - Plot I_{dsn} , I_{dsp} vs. V_{out}
 - V_{out} must be where |currents| are equal in

 


Load Line Analysis

□ $V_{in} = 0$

 


Load Line Analysis

□ $V_{in} = 0.2V_{DD}$

 


Load Line Analysis

□ $V_{in} = 0.4V_{DD}$

 


Load Line Analysis

□ $V_{in} = 0.6V_{DD}$

 


Load Line Analysis

□ $V_{in} = 0.8V_{DD}$

 


Load Line Analysis

□ $V_{in} = V_{DD}$


 


Load Line Summary

 

DC Transfer Curve

  
- Transcribe points onto V_{in} vs. V_{out} plot



Operating Regions

- Revisit transistor operating regions


Region	nMOS	pMOS
A		
B		
C		
D		
E		

 

Operating Regions

- Revisit transistor operating regions

Region	nMOS	pMOS
A	Cutoff	Linear
B	Saturation	Linear
C	Saturation	Saturation
D	Linear	Saturation
E	Linear	Cutoff

 

Beta Ratio

- ❑ If $\beta_p / \beta_n \neq 1$, switching point will move from $V_{DD}/2$
- ❑ Called *skewed gate*
- ❑ Other gates: collapse into equivalent inverter

