 


PLD (Programmable Logic Device)

- Can be programmed by the users as per their requirement
- Large circuit is designed on a single chip
- Possible to implement a combinational or sequential circuit using the PLD
- Consist of array of NOT, AND and OR gates
- Any Boolean function can be represented by sum of the product form.

Programmable ROM (PROM)




- Address: m bits; data: n bits
- ROM contains 2^N word of M bit each
- The input bits decide the particular word that becomes available on output lines

- A ROM (Read Only Memory) has a fixed AND plane and a programmable OR plane
- Size of AND plane is 2^n where n = number of input pins
 - Has an AND gate for every possible minterm so that all input combinations access a different AND gate
- OR plane dictates function mapped by the ROM

4x4 ROM

 - ▶ $2^2 \times 4$ bit ROM has 4 addresses that are decoded




ROM Types

- ▶ Programmable PROM
 - Break links through current pulses
 - Write once, Read multiple times
- ▶ Erasable PROM (EPROM)
 - Program with ultraviolet light
 - Write multiple times, Read multiple times
- ▶ Electrically Erasable PROM (EEPROM)/ Flash Memory
 - Program with electrical signal
 - Write multiple times, Read multiple times

Combinational Circuit Implementation using PROM


I0 I1 I2 F0 F1 F2

0	0	0	1	0	0
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	1	0	0
1	1	1	0	1	0

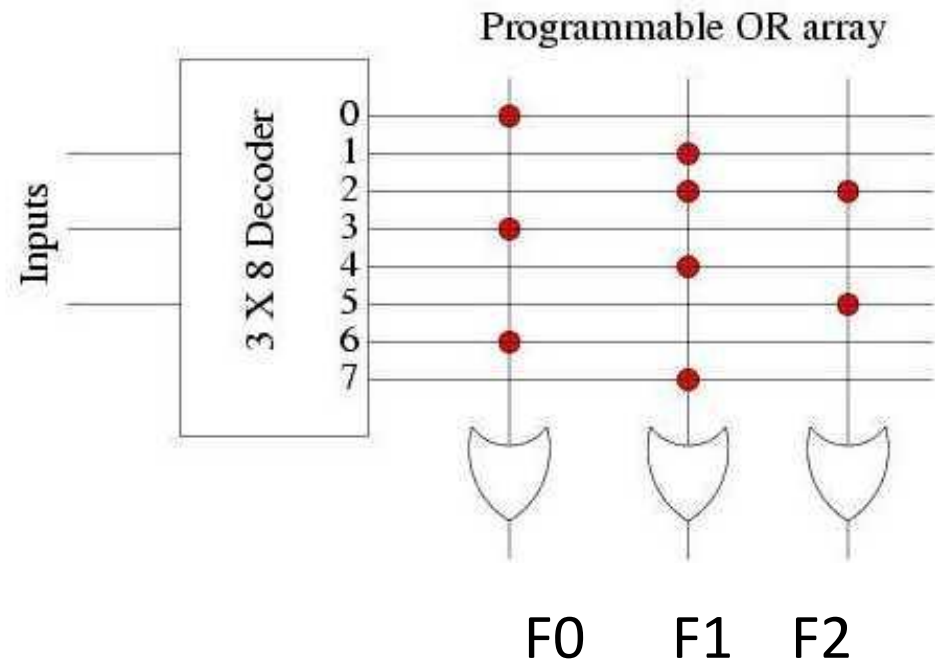


Programmable Logic Array (PLA)

 - Use to implement circuits in SOP form
- The connections in the AND plane are programmable
- The connections in the OR plane are programmable




Gate Level Version of PLA

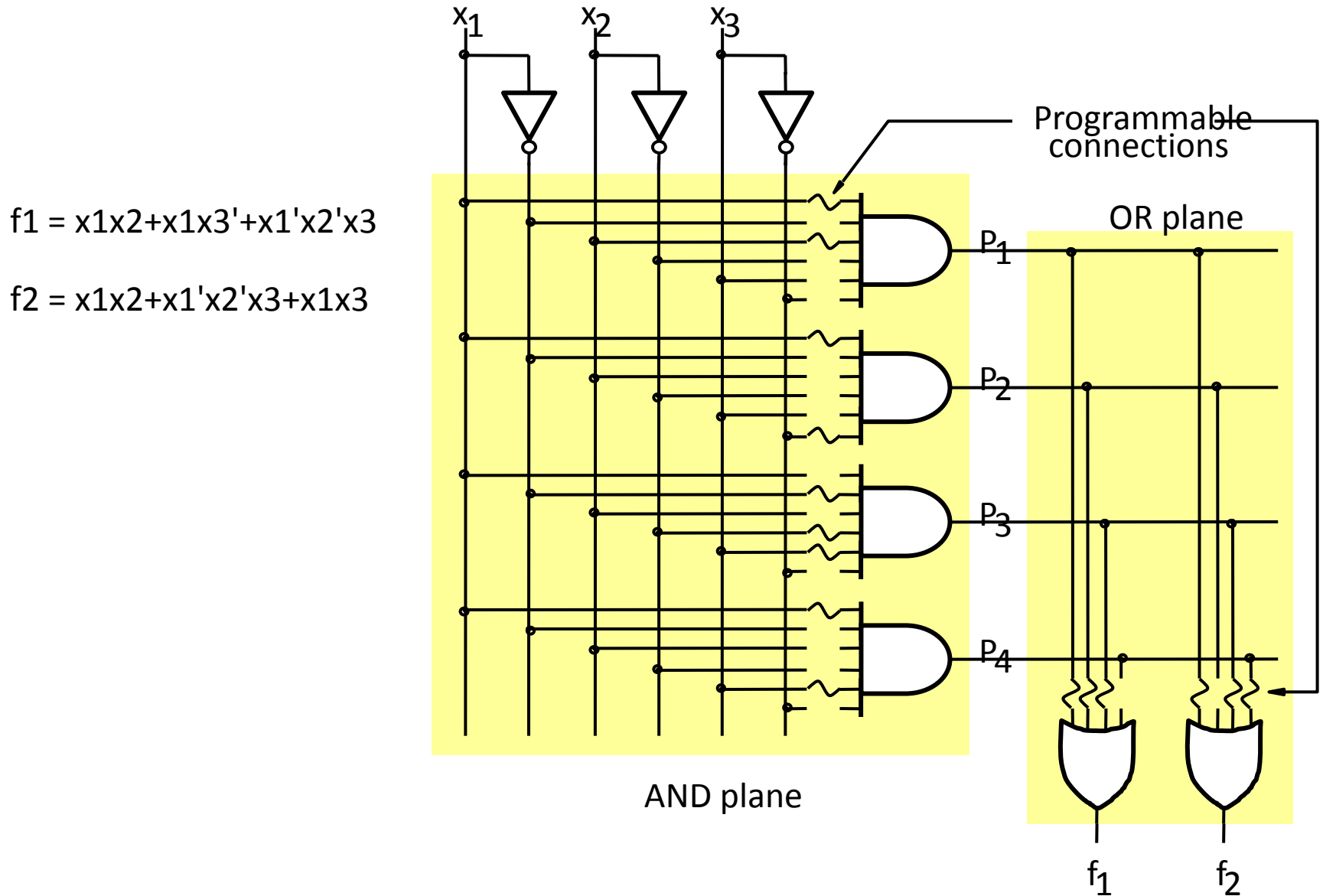

Customary Schematic of a PLA

$$f_1 = x_1x_2 + x_1x_3' + x_1'x_2'x_3$$

$$f_2 = x_1x_2 + x_1'x_2'x_3 + x_1x_3$$

 

x marks the connections left in place after programming