 


# Programmable Array Logic (PAL)


- Also used to implement circuits in SOP form
- The connections in the AND plane are programmable
- The connections in the OR plane are NOT programmable




# Example Schematic of a PAL

$$f_1 = x_1x_2x_3' + x_1'x_2x_3$$

$$f_2 = x_1'x_2' + x_1x_2x_3$$

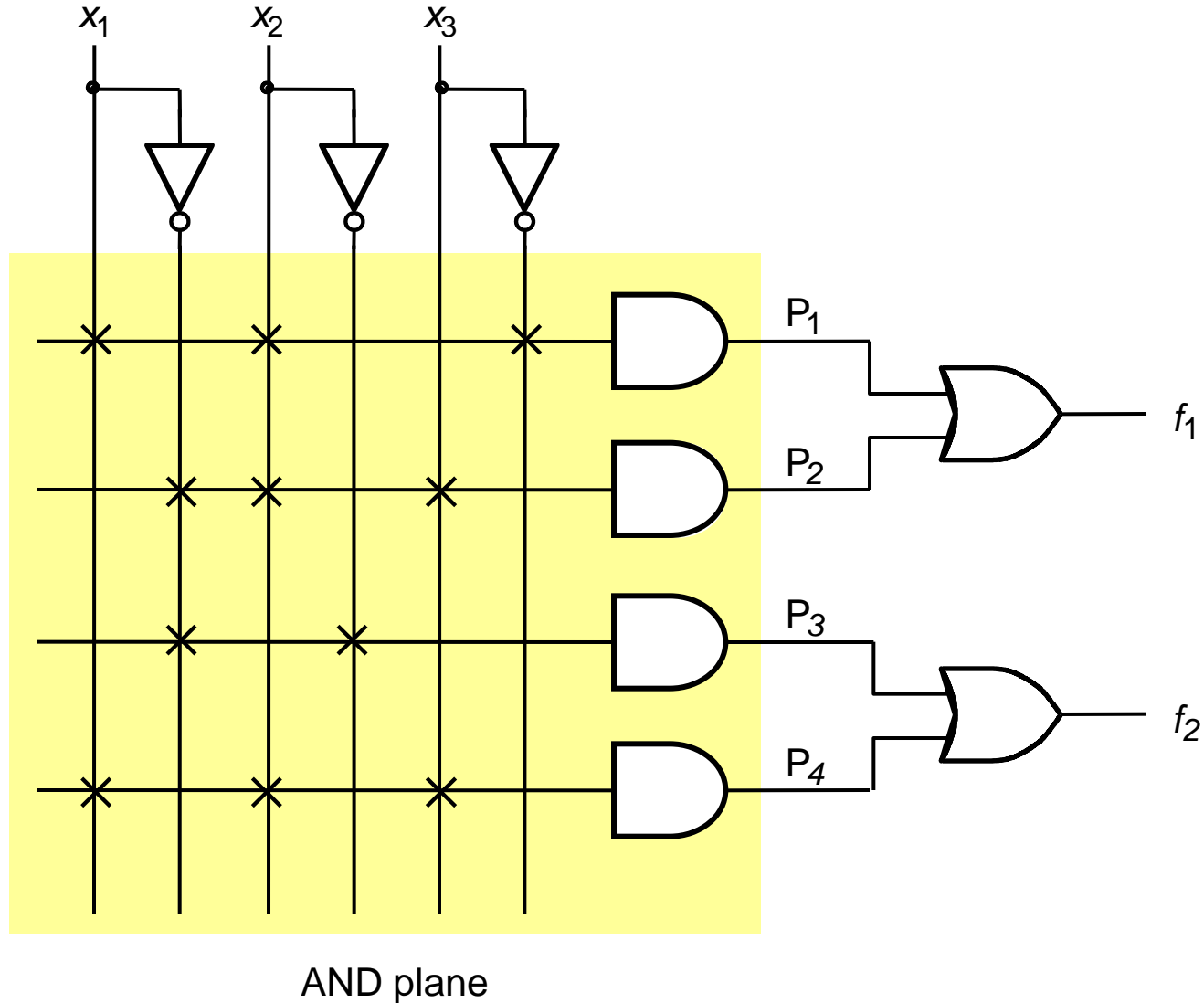

# PLDs

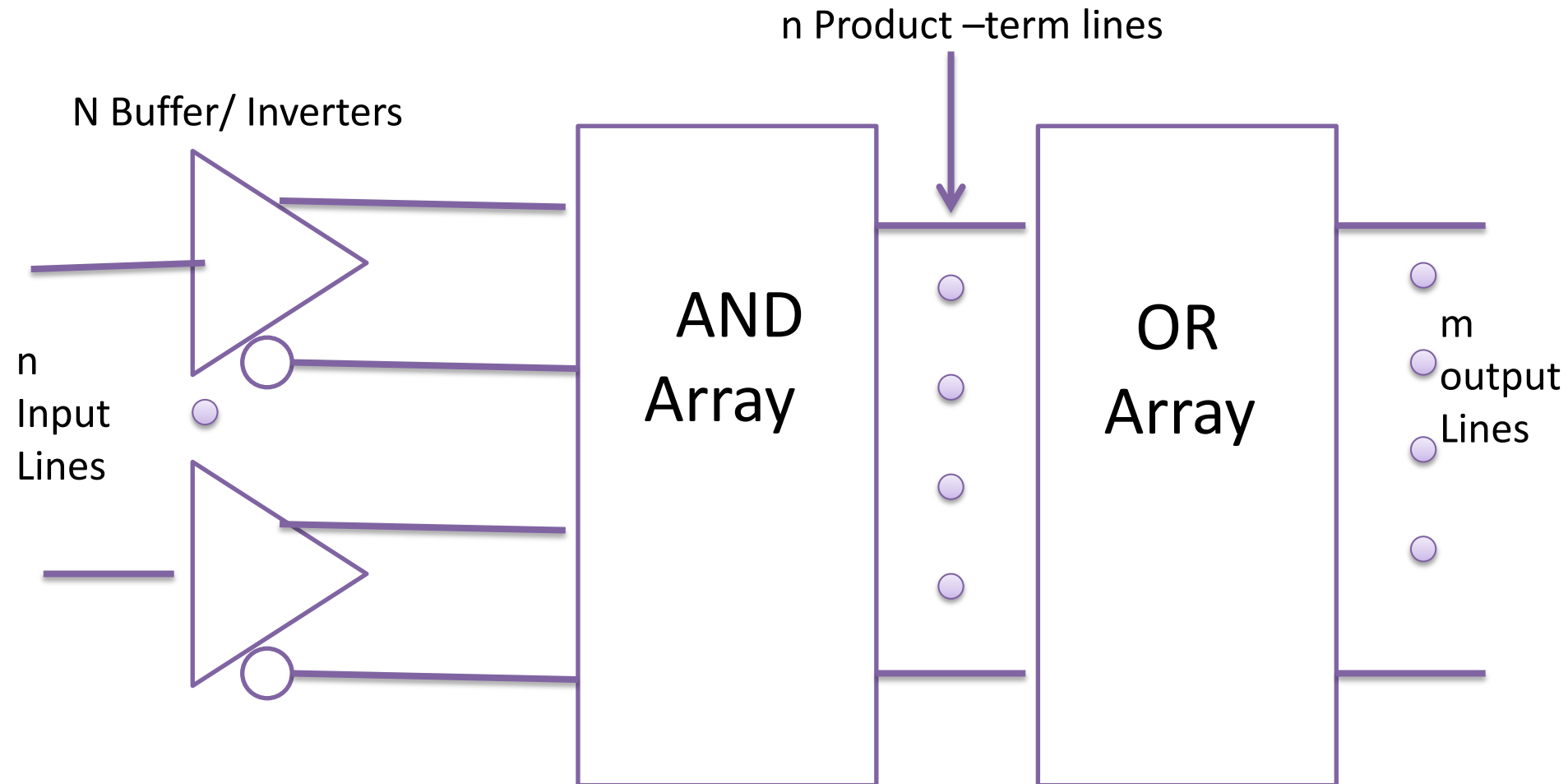

# Types of PLD

- PROM (Programmable read only memory)
- PLA (programmable logic array)
- PAL (Programmable array logic)
- GAL (Generic array logic)
- PEEL (Programmable Electrically Erasable Logic)
- CPLDs (Complex programmable logic device)
- FPGA (Field programmable gate array)

# Programmable Array

<b>Device</b>	<b>AND Array</b>	<b>OR Array</b>
ROM	Fixed	Programmable
PLA	Programmable	Programmable
PAL	Programmable	Fixed
GAL	Programmable	Fixed

# ROM as PLD

- Consider a ROM with  $m$  outputs (the address lines) and  $n$  inputs (the data lines).
- When used as a memory, the ROM contains words of  $n$  bits each

# TYPES

- PROMs (programmable ROMs),
- EPROMs (ultraviolet-erasable PROMs)
- EEPROMs (electrically erasable PROMs)