

# **ELECTRONICS SYSTEM DESIGN**

## **SECTION-5**


### **ASYNCHRONOUS FINITE STATE** **MACHINE**

# Finite State Machines

- Sequential circuits
  - primitive sequential elements
  - combinational logic
- Models for representing sequential circuits
  - finite-state machines (Moore and Mealy)
- Basic sequential circuits revisited
  - shift registers
  - counters
- Design procedure
  - state diagrams
  - state transition table
  - next state functions
- Hardware description languages

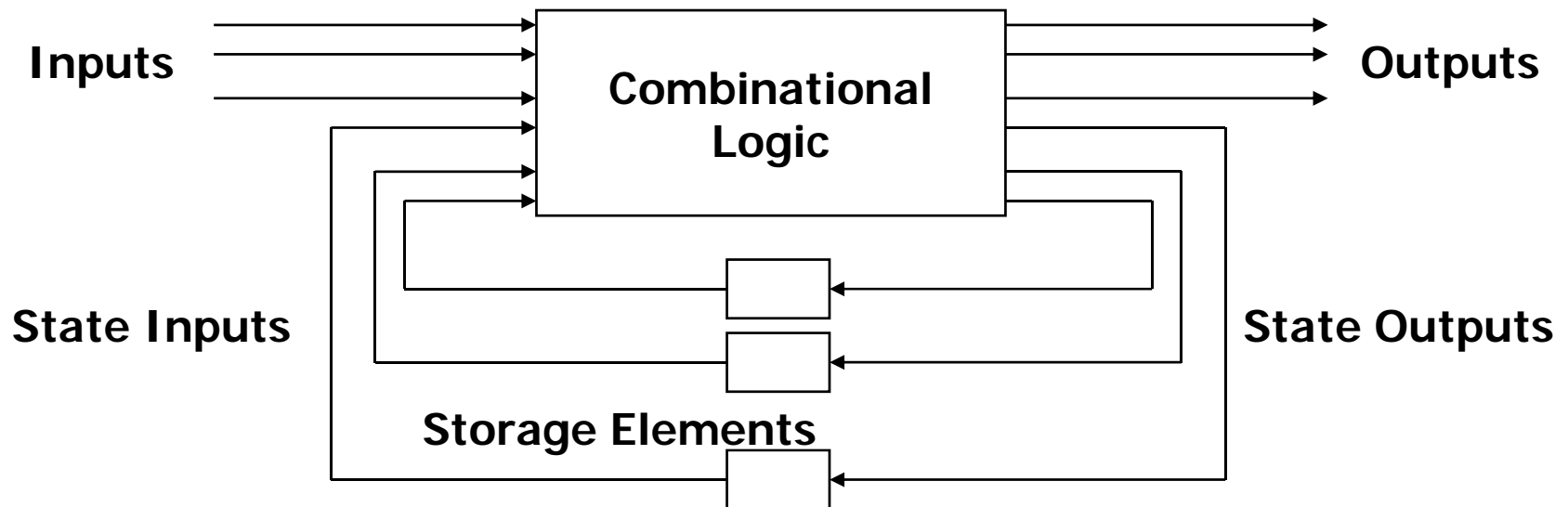
# Abstraction of state elements

- Divide circuit into combinational logic and state
- Localize the feedback loops and make it easy to break cycles
- Implementation of storage elements leads to various forms of sequential logic



 
# Forms of sequential logic

- Asynchronous sequential logic – state changes occur whenever state inputs change (elements may be simple wires or delay elements)
- Synchronous sequential logic – state changes occur in lock step across all storage elements (using a periodic waveform - the clock)



 
# Finite state machine representations

- States: determined by possible values in sequential storage elements
- Transitions: change of state
- Clock: controls when state can change by controlling storage elements
- Sequential logic
  - sequences through a series of states
  - based on sequence of values on input signals
  - clock period defines elements of sequence


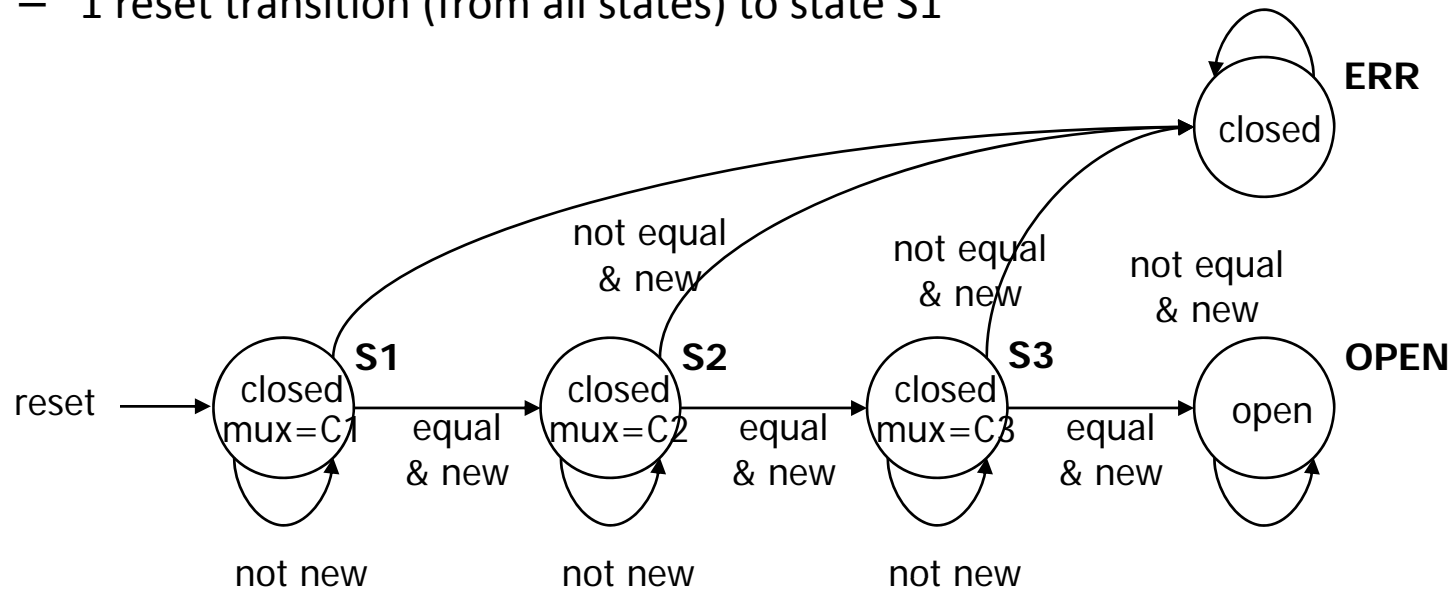
# Example finite state machine diagram



- Combination lock from introduction to course
  - 5 states
  - 5 self-transitions
  - 6 other transitions between states
  - 1 reset transition (from all states) to state S1


  
# Can any sequential system be represented with a state diagram?


- Shift register

- input value shown on transition arcs
- output values shown within state node


 
# Counters are simple finite state machines


- Counters
  - proceed through well-defined sequence of states in response to enable
- Many types of counters: binary, BCD, Gray-code
  - 3-bit up-counter: 000, 001, 010, 011, 100, 101, 110, 111, 000, ...
  - 3-bit down-counter: 111, 110, 101, 100, 011, 010, 001, 000, 111, ...




 
# How do we turn a state diagram into logic?

- Counter
  - 3 flip-flops to hold state
  - logic to compute next state
  - clock signal controls when flip-flop memory can change
    - wait long enough for combinational logic to compute new value
    - don't wait too long as that is low performance




# FSM design procedure

- Start with counters
  - simple because output is just state
  - simple because no choice of next state based on input
- State diagram to state transition table
  - tabular form of state diagram
  - like a truth-table
- State encoding
  - decide on representation of states
  - for counters it is simple: just its value
- Implementation
  - flip-flop for each state bit
  - combinational logic based on encoding
 
# FSM design procedure: state diagram to encoded state transition table

- Tabular form of state diagram
- Like a truth-table (specify output for all input combinations)
- Encoding of states: easy for counters – just use value



	present state	next state
0	000	001   1
1	001	010   2
2	010	011   3
3	011	100   4
4	100	101   5
5	101	110   6
6	110	111   7
7	111	000   0




# Implementation

- D flip-flop for each state bit
- Combinational logic based on encoding

Verilog notation to show function represents an input to D-FF

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

   
$N1 \leq C1'$   
 $N2 \leq C1C2' + C1'C2$   
 $\leq C1 \text{ xor } C2$   
 $N3 \leq C1C2C3' + C1'C3 + C2'C3$   
 $\leq (C1C2)C3' + (C1' + C2')C3$   
 $\leq (C1C2)C3' + (C1C2)'C3$   
 $\leq (C1C2) \text{ xor } C3$




# Back to the shift register

- Input determines next state

In	C1	C2	C3	N1	N2	N3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	0	1
1	0	1	1	1	0	1
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	1

 


 $N1 \leq In$   
 $N2 \leq C1$   
 $N3 \leq C2$


 
# More complex counter example

- Complex counter
  - repeats 5 states in sequence
  - not a binary number representation
- Step 1: derive the state transition diagram
  - count sequence: 000, 010, 011, 101, 110
- Step 2: derive the state transition table from the state transition diagram



Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	–	–	–
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	–	–	–
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	–	–	–

note the don't care conditions that arise from the unused state codes

# More complex counter example (cont'd)

- Step 3: K-maps for next state functions

		C			
C+		0	0	0	X
	A	X	1	X	1
		B			

		C			
B+		1	1	0	X
	A	X	0	X	1
		B			

		C			
A+		0	1	0	X
	A	X	1	X	0
		B			

$$C+ \leq A$$

$$B+ \leq B' + A'C'$$

$$A+ \leq BC'$$

# Self-starting counters (cont'd)


- Re-deriving state transition table from don't care assignment

C+	C		
	0	0	0
A	1	1	1
	B		

B+	C		
	1	1	0
A	1	0	0
	B		

A+	C		
	0	1	0
A	0	1	0
	B		



Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

 


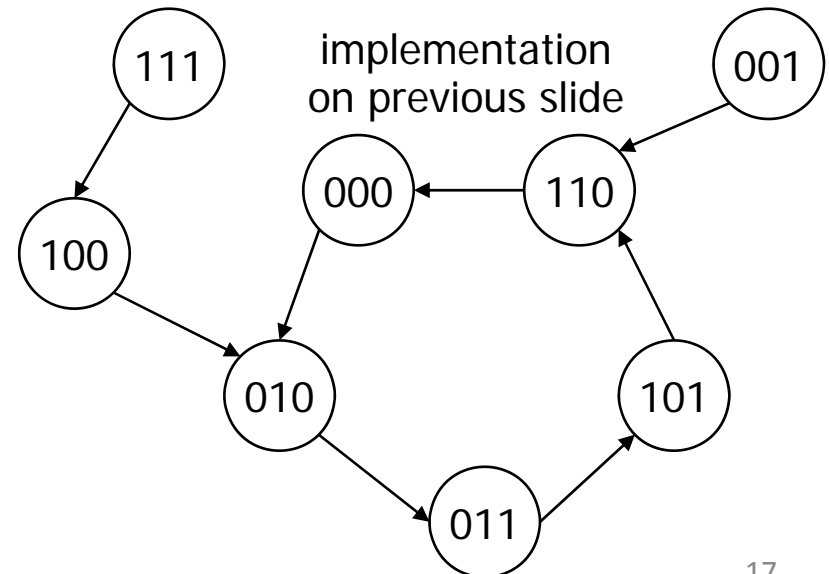 
# Self-starting counters

- Start-up states
  - at power-up, counter may be in an unused or invalid state
  - designer must guarantee that it (eventually) enters a valid state
- Self-starting solution
  - design counter so that invalid states eventually transition to a valid state
  - may limit exploitation of don't cares



# Activity

- 2-bit up-down counter (2 inputs)
  - direction:  $D = 0$  for up,  $D = 1$  for down
  - count:  $C = 0$  for hold,  $C = 1$  for count


# Activity (cont'd)

-

.....

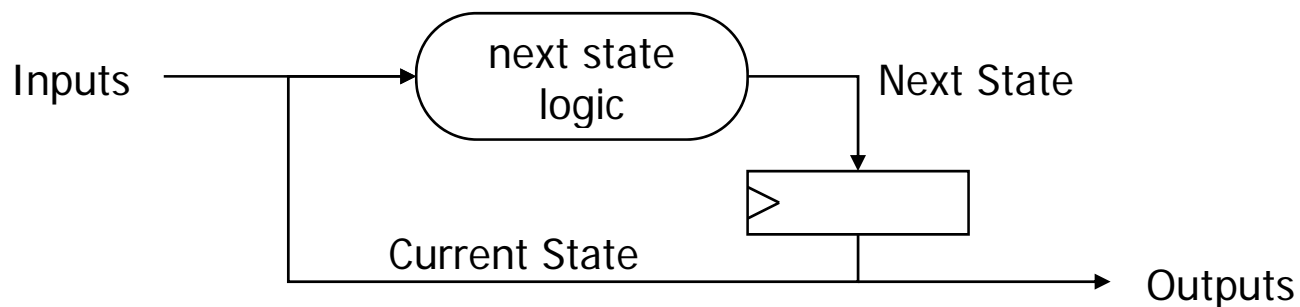
# Counter/shift-register model

- Values stored in registers represent the state of the circuit
- Combinational logic computes:
  - next state
    - function of current state and inputs
  - outputs
    - values of flip-flops




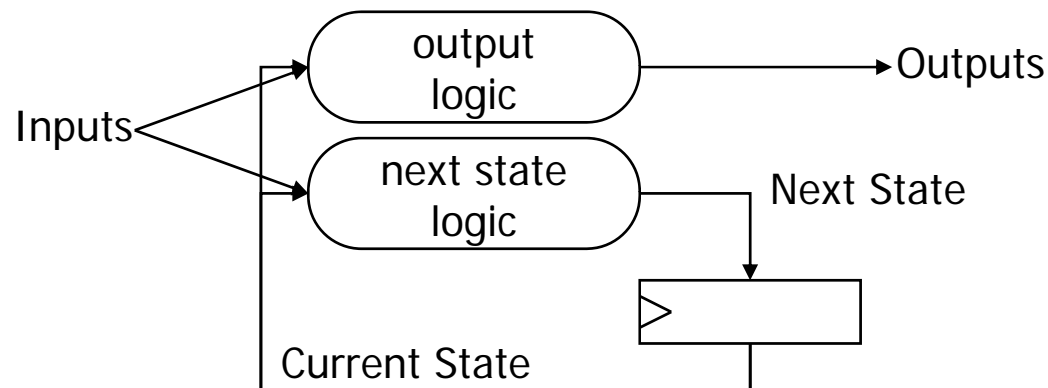
# General state machine model

- Values stored in registers represent the state of the circuit
- Combinational logic computes:
  - next state
    - function of current state and inputs
  - outputs
    - function of current state and inputs (Mealy machine)
    - function of current state only (Moore machine)


 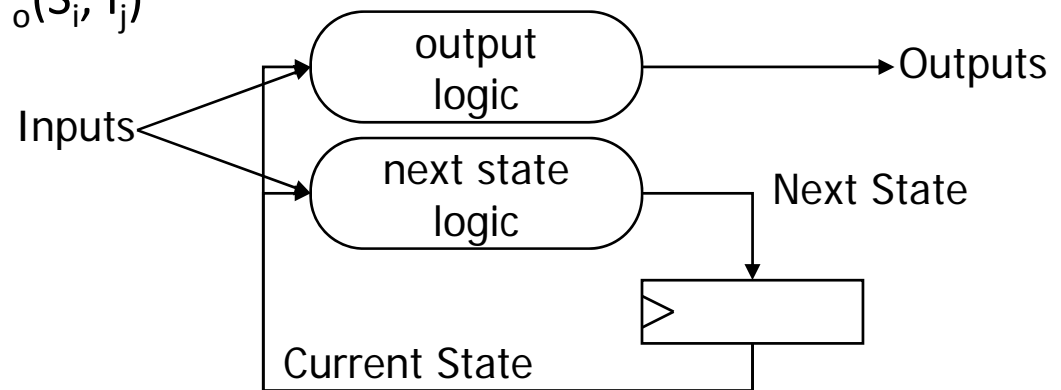
# State machine model (cont'd)

- States:  $S_1, S_2, \dots, S_k$
- Inputs:  $I_1, I_2, \dots, I_m$
- Outputs:  $O_1, O_2, \dots, O_n$
- Transition function:  $F_s(S_i, I_j)$
- Output function:  $F_o(S_i)$  or  $F_o(S_i, I_j)$




# Comparison of Mealy and Moore machines


- Mealy machines tend to have less states
  - different outputs on arcs ( $n^2$ ) rather than states ( $n$ )
- Moore machines are safer to use
  - outputs change at clock edge (always one cycle later)
  - in Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected – asynchronous feedback may occur if one isn't careful
- Mealy machines react faster to inputs
  - react in same cycle – don't need to wait for clock
  - in Moore machines, more logic may be necessary to decode state into outputs
    - more gate delays after clock edge

# Comparison of Mealy and Moore machines (cont'd)


- Moore

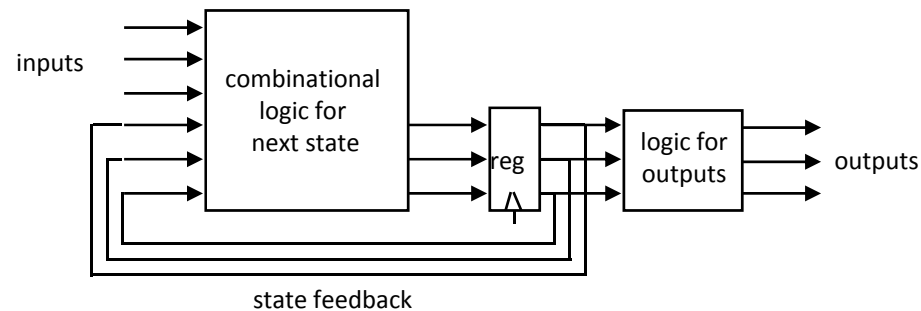

- Mealy

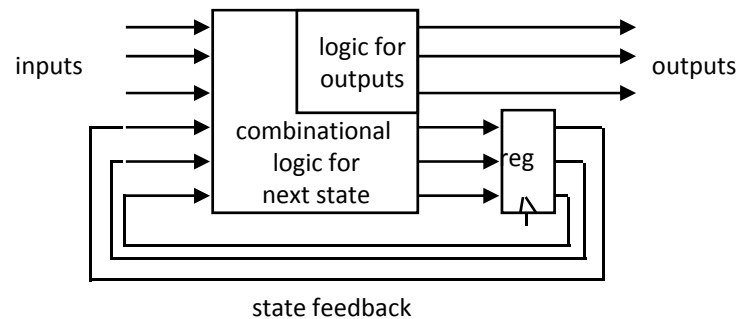


- Synchronous Mealy

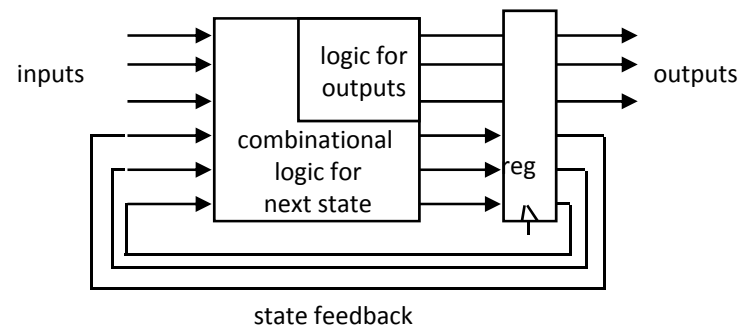


 
# Specifying outputs for a Moore machine


- Output is only function of state
  - specify in state bubble in state diagram
  - example: sequence detector for 01 or 10



reset	input	current state	next state	output
1	–	–	A	
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	1
 
# Specifying outputs for a Mealy machine


- Output is function of state and inputs
  - specify output on transition arc between states
  - example: sequence detector for 01 or 10



reset	input	current state	next state	output
1	–	–	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0

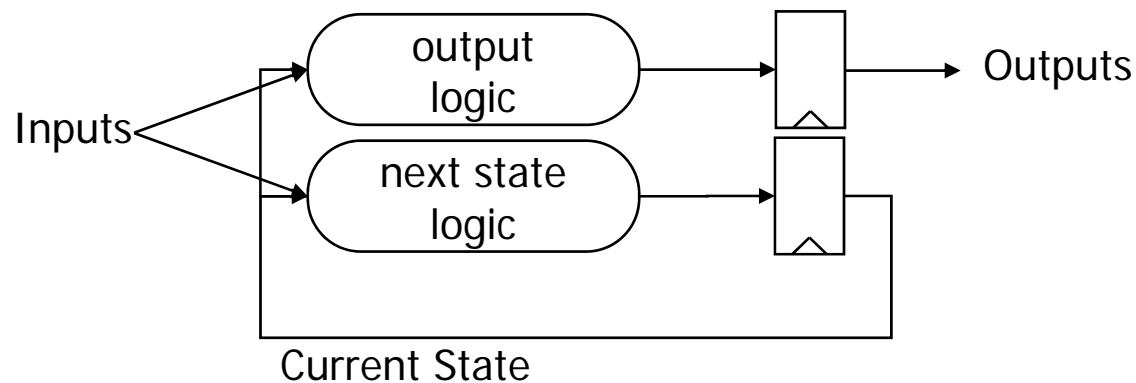
# Registered Mealy machine (really Moore)

- Synchronous (or registered) Mealy machine
  - registered state AND outputs
  - avoids 'glitchy' outputs
  - easy to implement in PLDs
- Moore machine with no output decoding
  - outputs computed on transition to next state rather than after entering
  - view outputs as expanded state vector


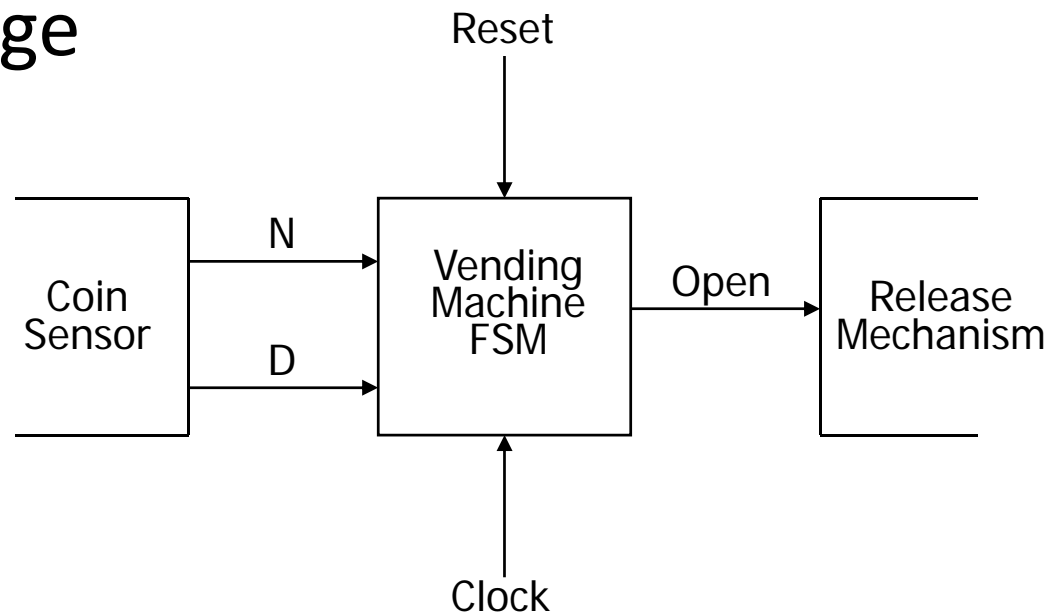
# Example: vending machine

- Release item after 15 cents are deposited
- Single coin slot for dimes, nickels
- No change



# Example: vending machine (cont'd)

- Suitable abstract representation

- tabulate typical input sequences:


- 3 nickels
- nickel, dime
- dime, nickel
- two dimes

- draw state diagram:

- inputs: N, D, reset
- output: open chute


- assumptions:

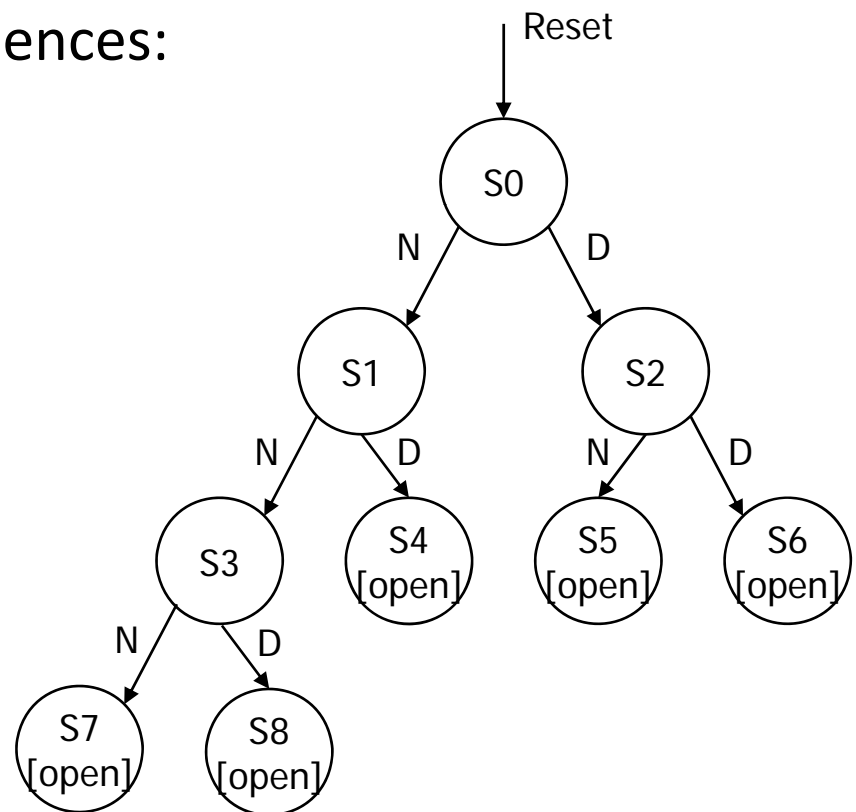- assume N and D asserted for one cycle
- each state has a self loop for  $N = D = 0$  (no coin)


 
# Example: vending machine (cont'd)

- Minimize number of states - reuse states whenever possible



present state	inputs		next state	output open
	D	N		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	—	—
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	—	—
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	—	—
15¢	—	—	15¢	1

symbolic state table

# Example: vending machine (cont'd)

- Uniquely encode states

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	-	-	-
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	-	-	-
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
		1	1	-	-	-
1	1	-	-	1	1	1


# Example: Moore implementation

- Mapping to logic

		Q1			
		0	0	1	1
D	0	0	0	1	1
	0	0	1	1	1
	X	X	X	1	X
	1	1	1	1	1
		Q0			

		Q1			
		0	1	1	0
D	0	0	1	1	0
	1	1	0	1	1
	X	X	X	1	X
	0	0	1	1	1
		Q0			

		Q1			
		0	0	1	0
D	0	0	0	1	0
	0	0	0	1	0
	X	X	X	1	X
	0	0	0	1	0
		Q0			

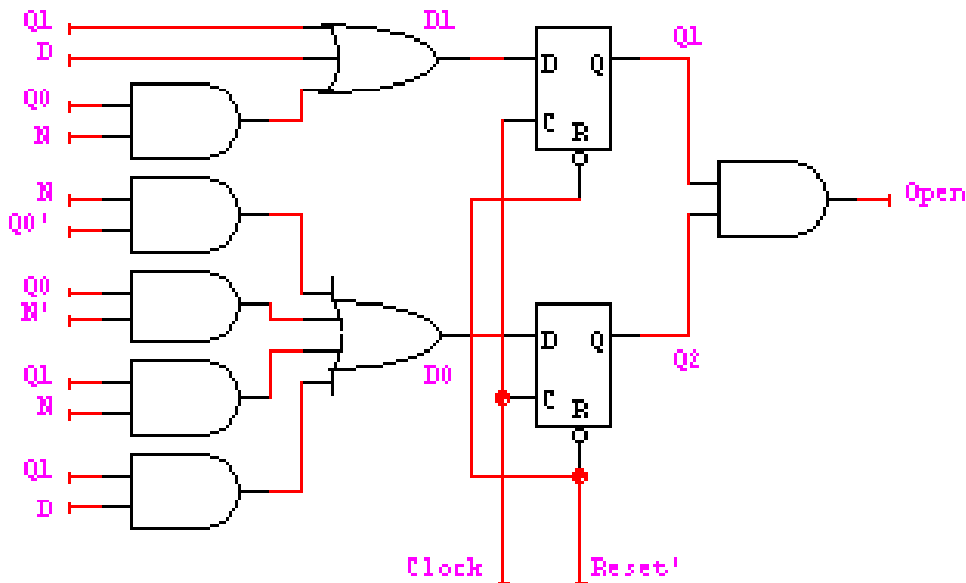

$$D1 = Q1 + D + Q0 N$$

$$D0 = Q0' N + Q0 N' + Q1 N + Q1 D$$

$$OPEN = Q1 Q0$$



# Example: vending machine (cont'd)

- One-hot encoding

present state				inputs		next state output				
Q3	Q2	Q1	Q0	D	N	D3	D2	D1	D0	open
0	0	0	1	0	0	0	0	0	1	0
				0	1	0	0	1	0	0
				1	0	0	1	0	0	0
				1	1	-	-	-	-	-
0	0	1	0	0	0	0	0	1	0	0
				0	1	0	1	0	0	0
				1	0	1	0	0	0	0
				1	1	-	-	-	-	-
0	1	0	0	0	0	0	1	0	0	0
				0	1	1	0	0	0	0
				1	0	1	0	0	0	0
				1	1	-	-	-	-	-
1	0	0	0	-	-	1	0	0	0	1

$$D0 = Q0 D' N'$$

$$D1 = Q0 N + Q1 D' N'$$



$$D2 = Q0 D + Q1 N + Q2 D' N'$$

$$D3 = Q1 D + Q2 D + Q2 N + Q3$$


$$OPEN = Q3$$
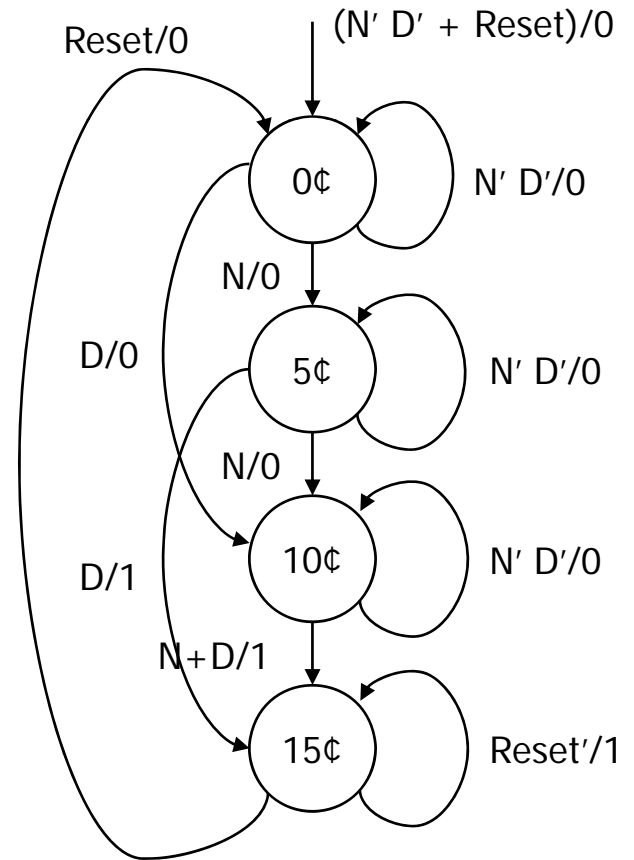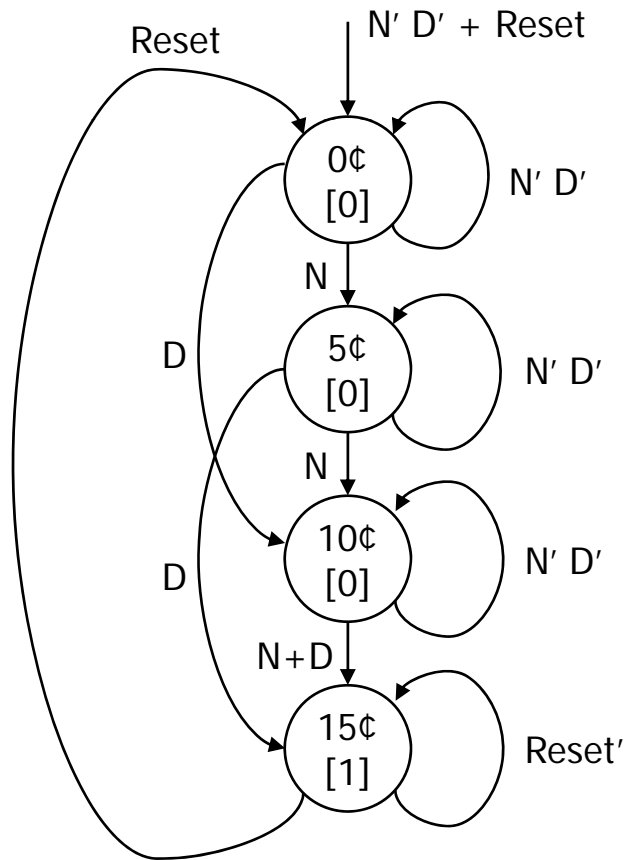
# Equivalent Mealy and Moore state diagrams

- Moore machine
  - outputs associated with state
- Mealy machine
  - outputs associated with transitions



# Example: Mealy implementation

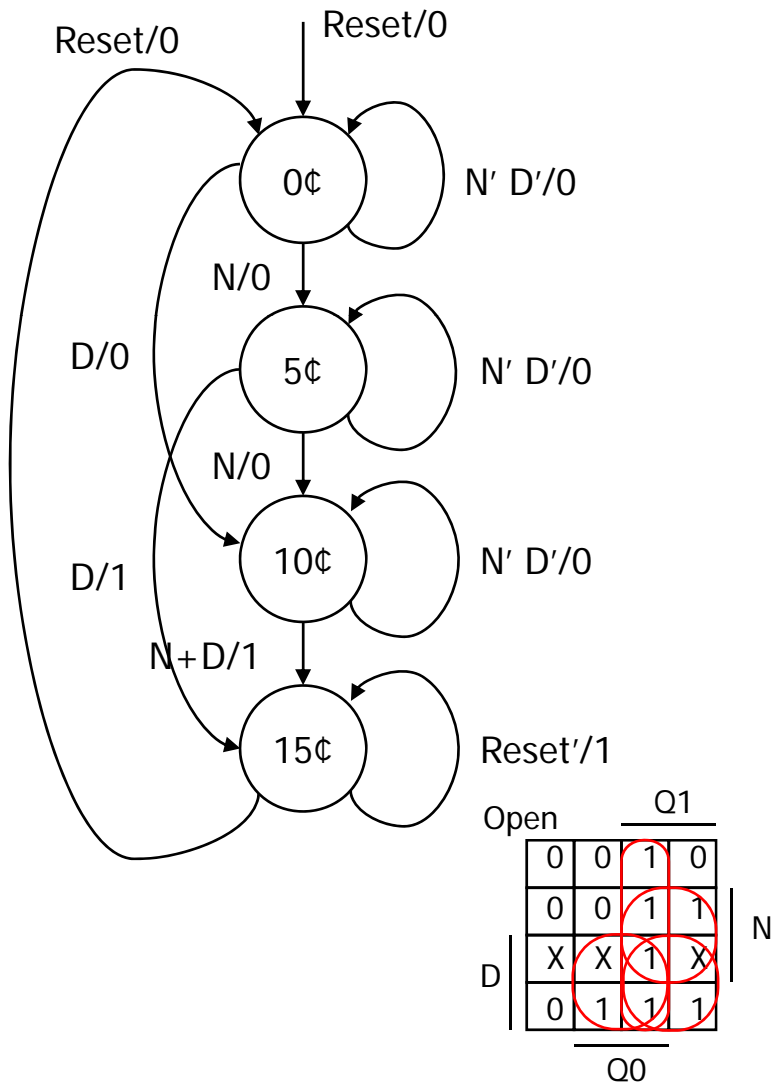

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	-	-	-
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	1
		1	1	-	-	-
1	0	0	0	1	0	0
		0	1	1	1	1
		1	0	1	1	1
		1	1	-	-	-
1	1	-	-	1	1	1

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$

$$OPEN = Q1Q0 + Q1N + Q1D + Q0D$$


# Example: Mealy implementation

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$



$$\text{OPEN} = Q1Q0 + Q1N + Q1D + Q0D$$

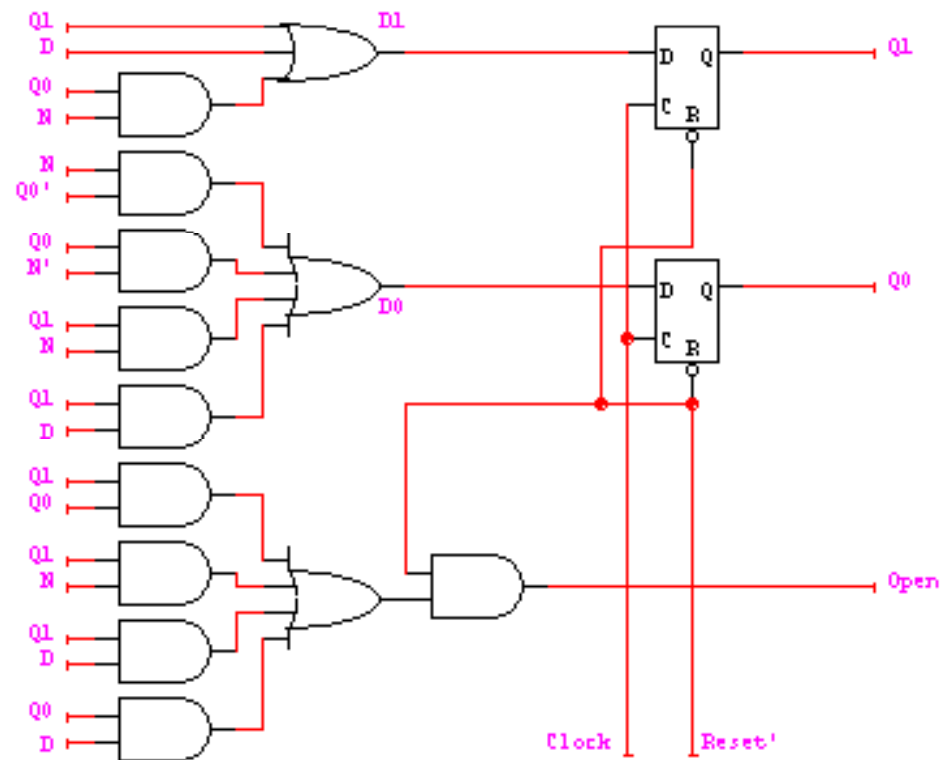make sure OPEN is 0 when reset  
– by adding AND gate


  
# Vending machine: Moore to synch. Mealy




- OPEN = Q1Q0 creates a combinational delay after Q1 and Q0 change in Moore implementation
- This can be corrected by retiming, i.e., move flip-flops and logic through each other to improve delay
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$   
 $= Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$
- Implementation now looks like a synchronous Mealy machine
  - it is common for programmable devices to have FF at end of logic



# Vending machine: Mealy to synch.

 
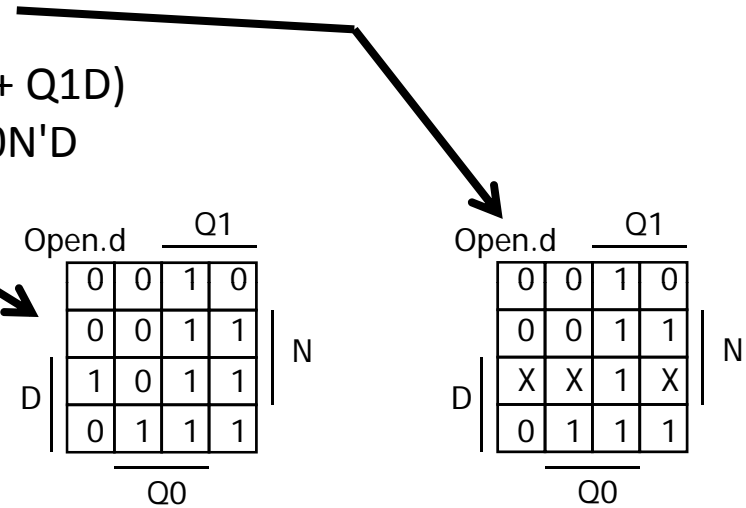
 
## Mealy

- $OPEN.d = Q1Q0 + Q1N + Q1D + Q0D$
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$   
 $= Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$



  
 
# Mealy and Moore examples

- Recognize A,B = 0,1
  - Mealy or Moore?


  
# Mealy and Moore examples (cont'd)

- Recognize A,B = 1,0 then 0,1
  - Mealy or Moore?






# Hardware Description Languages and Sequential Logic

- Flip-flops
  - representation of clocks - timing of state changes
  - asynchronous vs. synchronous
- FSMs
  - structural view (FFs separate from combinational logic)
  - behavioral view (synthesis of sequencers – not in this course)
- Data-paths = data computation (e.g., ALUs, comparators) + registers
  - use of arithmetic/logical operators
  - control of storage elements


# Example: reduce-1-string-by-1

- Remove one 1 from every string of 1s on the input

Moore

 

Mealy

 


# Verilog FSM - Reduce 1s example

- **Moore machine**

```
module reduce (clk, reset, in, out);  
  input clk, reset, in;  
  output out;  
  
  parameter zero = 2'b00;  
  parameter one1 = 2'b01;  
  parameter two1s = 2'b10;  
  
  reg out;  
  reg [2:1] state; // state variables  
  reg [2:1] next_state;  
  
  always @(posedge clk)  
    if (reset) state = zero;  
    else state = next_state;
```

 
state assignment  
(easy to change,  
if in one place)



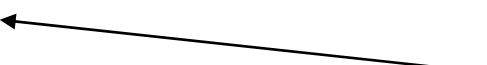
# Moore Verilog FSM (cont'd)

```
always @(in or state)
    case (state)
        zero:
            // last input was a zero
            begin
                if (in) next_state = one1;
                else    next_state = zero;
            end
        one1:
            // we've seen one 1
            begin
                if (in) next_state = twos;
                else    next_state = zero;
            end
        twos:
            // we've seen at least 2 ones
            begin
                if (in) next_state = twos;
                else    next_state = zero;
            end
    endcase
```

crucial to include  
all signals that are  
input to state determination



note that output  
depends only on state



```
always @(state)
    case (state)
        zero: out = 0;
        one1: out = 0;
        twos: out = 1;
    endcase
```


```
endmodule
```

# Mealy Verilog FSM

```
module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg state; // state variables
  reg next_state;

  always @(posedge clk)
    if (reset) state = zero;
    else      state = next_state;

   always @(in or state)
    case (state)
      zero:           // last input was a zero
      begin
        out = 0;
        if (in) next_state = one;
        else   next_state = zero;
      end
      one:           // we've seen one 1
      if (in) begin
        next_state = one; out = 1;
      end else begin
        next_state = zero; out = 0;
      end
    endcase
endmodule
```



# Synchronous Mealy Machine

```
module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg state; // state variables

  always @(posedge clk)
    if (reset) state = zero;
    else
      case (state)
        zero:      // last input was a zero
          begin
            out = 0;
            if (in) state = one;
            else   state = zero;
          end
        one:       // we've seen one 1
          if (in) begin
            state = one; out = 1;
          end else begin
            state = zero; out = 0;
          end
      endcase
endmodule
```

# Finite state machines summary

- Models for representing sequential circuits
  - abstraction of sequential elements
  - finite state machines and their state diagrams
  - inputs/outputs
  - Mealy, Moore, and synchronous Mealy machines
- Finite state machine design procedure
  - deriving state diagram
  - deriving state transition table
  - determining next state and output functions
  - implementing combinational logic
- Hardware description languages

# Hazards

- A **hazard** is a condition in a *logically correct* digital circuit or computer program that may lead to a logically incorrect output
- Static hazards: Output should stay constant, but doesn't
- Static 1 hazard: Output should be a constant 1, but when one input is changed drops to 0 and then recovers to 1.
- Cannot occur in a POS implementation
- Static 0 hazard: Output should be a constant 0, but when one input is changed rises to 1 and then drops back to 0
- Cannot occur in a SOP implementation
- Dynamic Hazards: An input transition is supposed to cause a single transition, but causes two or more transitions.



# Hazards


- **Why do hazards matter?**
- The output of a hazard-prone circuit or program depends on conditions other than the inputs and the state
- The signal passed to another circuit by a hazard-prone circuit depends on exactly when the output is read
- In edge-triggered logic circuits, a momentary glitch resulting from a hazard can be converted into an erroneous output

# Static Hazards

- The circuit  $x'y' + yz$  has a static 1 hazard
- If the input  $y$  is changed from 0 to 1, control of the output of the OR gate shifts from one AND gate to the other
- Any difference in delays between the two AND gates will result in a glitch in the output of the OR
 
# Static Hazards


- The timing diagram below shows the inputs and outputs of a circuit for  $x'y' + yz$  with a static 1 hazard



# Static Hazards


- Static 1 hazard detection using a Karnaugh map:
- Reduce the logic function to a minimal sum of prime implicants
- A Karnaugh map that contains adjacent, disjoint prime implicants is subject to a static 1 hazard
- Adjacent prime implicants: Only one variable needs to change value to move from one prime implicant to the other
- Disjoint prime implicants
- No prime implicant covers cells of both of the disjoint prime implicants
- Correspond to AND gates that must both change their outputs when a particular input is changed

# Static Hazards

 


$$F(x,y,z) = \bar{x}\bar{y} + yz$$

# Static Hazards

 


$$F(x, y, z) = \bar{x}\bar{y} + yz + \bar{x}z$$

# Static Hazards

 
 
# Dynamic Hazards

- B changes from 0 to 1 (1,0,1,0 output change)





# Dynamic Hazards

- There are also two types of Dynamic hazards: the 0 output transitions to a 1 back to 0 and then 1 again. Or the 1 output transitions to a 0 back to 1 and then 0 again.
- Dynamic hazards happen because of multiple paths in a multilevel network, each with its own asymmetric delay. Circuits which contain multiple paths of the same signal should be re-clocked before the signal is used by a circuit.

# Dynamic Hazards

- If Static Hazards are removed from the design, Dynamic Hazards will not occur. A **Karnaugh map** [K-map] is the easiest way to eliminate a Static Hazard or glitches. These timing hazards will develop as random or intermittent circuit failures. The type of circuit failure will depend on the signals used in the AND / OR gate circuit, and perhaps how often they change state.

# Dynamic Hazards

- Another method to eliminate timing hazards from effecting an IC down the line is to re-clock the final output signals. Re-clocking the signal does not eliminate the glitch, but stops it from causing circuit failure. Re-clocking the signal seems to be common for designers unsure of why the glitch occurs, or how to stop the glitch from developing. Solving the problem via a K-map results in an additional AND gate, re-clocking requires an additional flip flop.

# Function Hazards

- XOR function

