

ELECTRONICS SYSTEM DESIGN

SECTION-3


SEQUENTIAL MACHINES

Lecture 11: Sequential Logic Latches & Flip-flops

- [Introduction](#)
- [Memory Elements](#)
- Pulse-Triggered Latch
 - ❖ [S-R Latch](#)
 - ❖ [Gated S-R Latch](#)
 - ❖ [Gated D Latch](#)
- [Edge-Triggered Flip-flops](#)
 - ❖ [S-R Flip-flop](#)
 - ❖ [D Flip-flop](#)
 - ❖ [J-K Flip-flop](#)
 - ❖ [T Flip-flop](#)
- [Asynchronous Inputs](#)

Introduction

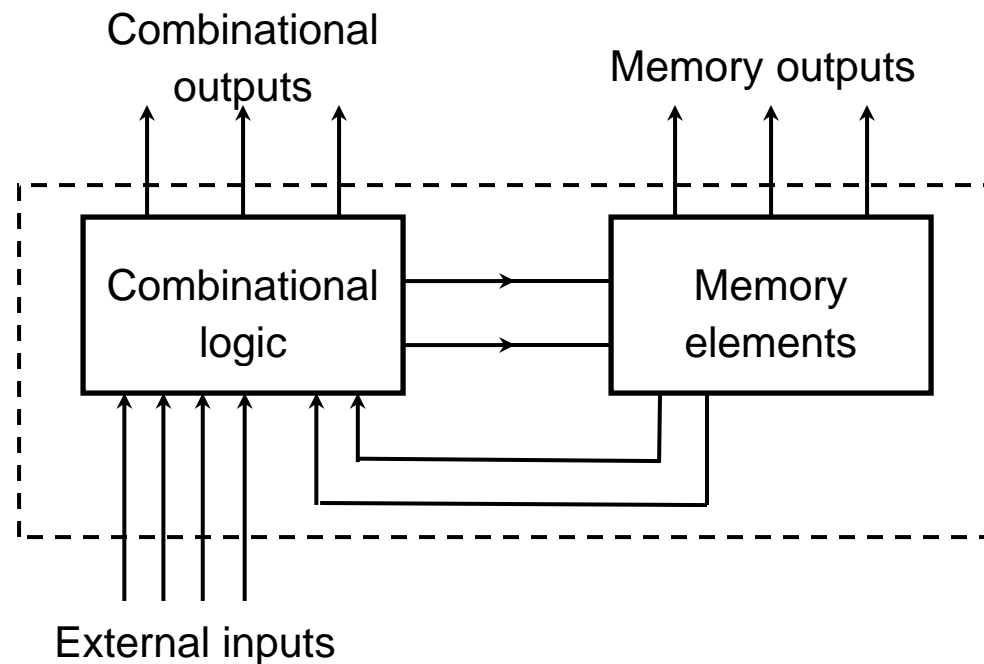- A **sequential circuit** consists of a *feedback path*, and employs some *memory elements*.




Sequential circuit = Combinational logic + Memory Elements

Introduction

- There are two types of sequential circuits:
 - ❖ *synchronous*: outputs change only at specific time
 - ❖ *asynchronous*: outputs change at any time
- *Multivibrator*: a class of sequential circuits. They can be:
 - ❖ *bistable* (2 stable states)
 - ❖ *monostable* or *one-shot* (1 stable state)
 - ❖ *astable* (no stable state)
- Bistable logic devices: *latches* and *flip-flops*.
- Latches and flip-flops differ in the method used for changing their state.

Memory Elements

 - **Memory element:** a device which can remember value indefinitely, or change value on command from its inputs.



- **Characteristic table:**


Command (at time t)	$Q(t)$	$Q(t+1)$
Set	X	1
Reset	X	0
Memorise / No Change	0	0
	1	1

$Q(t)$: current state


$Q(t+1)$ or Q^+ : next state

Memory Elements

 - Memory element with clock. Flip-flops are memory elements that change state on clock signals.



- Clock is usually a square wave.

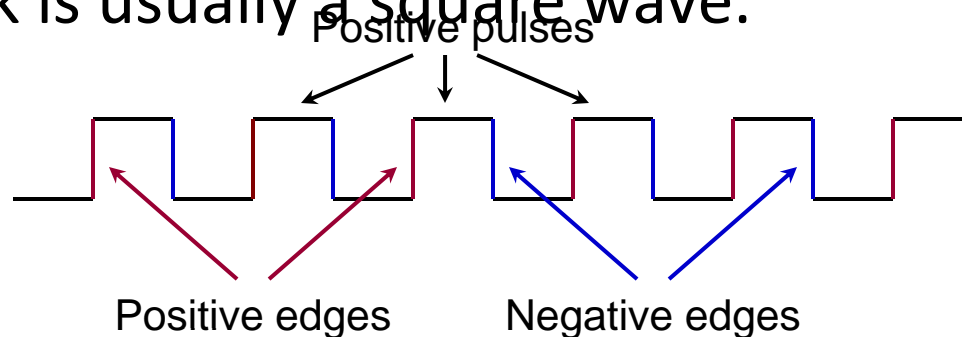

Memory Elements

- Two types of triggering/activation:
 - ❖ pulse-triggered
 - ❖ edge-triggered
- Pulse-triggered
 - ❖ latches
 - ❖ ON = 1, OFF = 0
- Edge-triggered
 - ❖ flip-flops
 - ❖ positive edge-triggered (ON = from 0 to 1; OFF = other time)
 - ❖ negative edge-triggered (ON = from 1 to 0; OFF = other time)

S-R Latch

- *Complementary* outputs: Q and Q' .
- When Q is HIGH, the latch is in *SET* state.
- When Q is LOW, the latch is in *RESET* state.
- For *active-HIGH input S-R latch* (also known as NOR gate latch),
 - R =HIGH (and S =LOW) \Rightarrow RESET state
 - S =HIGH (and R =LOW) \Rightarrow SET state
 - both inputs LOW \Rightarrow no change
 - both inputs HIGH \Rightarrow Q and Q' both LOW (invalid)!


S-R Latch

- For *active-LOW input S'-R' latch* (also known as NAND gate latch),
 - $R'=LOW$ (and $S'=HIGH$) \Leftrightarrow RESET state
 - $S'=LOW$ (and $R'=HIGH$) \Leftrightarrow SET state
 - both inputs HIGH \Leftrightarrow no change
 - both inputs LOW \Leftrightarrow Q and Q' both HIGH (invalid)!
- Drawback of S-R latch: invalid condition exists and must be avoided.

S-R Latch


- Characteristics table for active-high input S-R latch:

S	R	Q	Q'	
0	0	NC	NC	No change. Latch remained in present state.
1	0	1	0	Latch SET.
0	1	0	1	Latch RESET.
1	1	0	0	Invalid condition.

 


- Characteristics table for active-low input S'-R' latch:

S'	R'	Q	Q'	
1	1	NC	NC	No change. Latch remained in present state.
0	1	1	0	Latch SET.
1	0	0	1	Latch RESET.
0	0	1	1	Invalid condition.

 


S-R Latch

Active-HIGH input S-R latch


 


Active-LOW input S'-R' latch

 

Gated S-R Latch

  - S-R latch + *enable input (EN)* and 2 NAND gates → *gated S-R latch*.



Gated S-R Latch

- Outputs change (if necessary) only when EN is HIGH.
- Under what condition does the invalid state occur?
- Characteristic table:

$EN=1$

$Q(t)$	S	R	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	indeterminate


S	R	$Q(t+1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	indeterminate	

$$Q(t+1) = S + R'.Q$$

$$S.R = 0$$

Gated D Latch

 - Make R input equal to S' \rightarrow *gated D latch*.
- D latch eliminates the undesirable condition of invalid state in the S - R latch.



Gated D Latch

- When EN is HIGH,
 - ❖ $D=HIGH \rightarrow$ latch is SET
 - ❖ $D=LOW \rightarrow$ latch is RESET
- Hence when EN is HIGH, Q 'follows' the D (data) input.
- Characteristic table:

EN	D	$Q(t+1)$	
1	0	0	Reset
1	1	1	Set
0	X	$Q(t)$	No change


When $EN=1$, $Q(t+1) = D$

Latch Circuits: Not Suitable

- Latch circuits are not suitable in synchronous logic circuits.
- When the enable signal is active, the excitation inputs are gated directly to the output Q. Thus, any change in the excitation input immediately causes a change in the latch output.
- The problem is solved by using a special timing control signal called a *clock* to restrict the times at which the states of the memory elements may change.
- This leads us to the edge-triggered memory elements called *flip-flops*.


Edge-Triggered Flip-flops

 - *Flip-flops*: synchronous bistable devices
- Output changes state at a specified point on a triggering input called the *clock*.
- Change state either at the *positive edge* (rising edge) or at the *negative edge* (*falling edge*) of the clock signal.




Edge-Triggered Flip-flops

 - S-R, D and J-K edge-triggered flip-flops. Note the “>” symbol at the clock input.



Positive edge-triggered flip-flops

 

Negative edge-triggered flip-flops

S-R Flip-flop

- **S-R flip-flop**: on the triggering edge of the clock pulse,
 - ❖ $S=HIGH$ (and $R=LOW$) \Rightarrow SET state
 - ❖ $R=HIGH$ (and $S=LOW$) \Rightarrow RESET state
 - ❖ both inputs LOW \Rightarrow no change
 - ❖ both inputs $HIGH$ \Rightarrow invalid
- Characteristic table of positive edge-triggered S-R flip-flop:

S	R	CLK	$Q(t+1)$	Comments
0	0	X	$Q(t)$	No change
0	1	\uparrow	0	Reset
1	0	\uparrow	1	Set
1	1	\uparrow	?	Invalid

X = irrelevant (“don’t care”)




\uparrow = clock transition LOW to HIGH

S-R Flip-flop



- It comprises 3 parts:
 - ❖ a basic *NAND latch*
 - ❖ a *pulse-steering* circuit
 - ❖ a *pulse transition detector* (or *edge detector*) circuit
- The **pulse transition detector** detects a rising (or falling) edge and produces a very *short-duration spike*.

S-R Flip-flop

The pulse transition detector.

   


Positive-going transition
(rising edge)

  

Negative-going transition
(falling edge)

D Flip-flop

 - **D flip-flop**: single input D (data)
 - ❖ $D=HIGH \Rightarrow$ SET state
 - ❖ $D=LOW \Rightarrow$ RESET state
- Q follows D at the clock edge.
- Convert S-R flip-flop into a D flip-flop: add an inverter.




A positive edge-triggered D flip-flop formed with an S-R flip-flop.

D	CLK	$Q(t+1)$	Comments
1	↑	1	Set
0	↑	0	Reset

↑ = clock transition LOW to HIGH

D Flip-flop

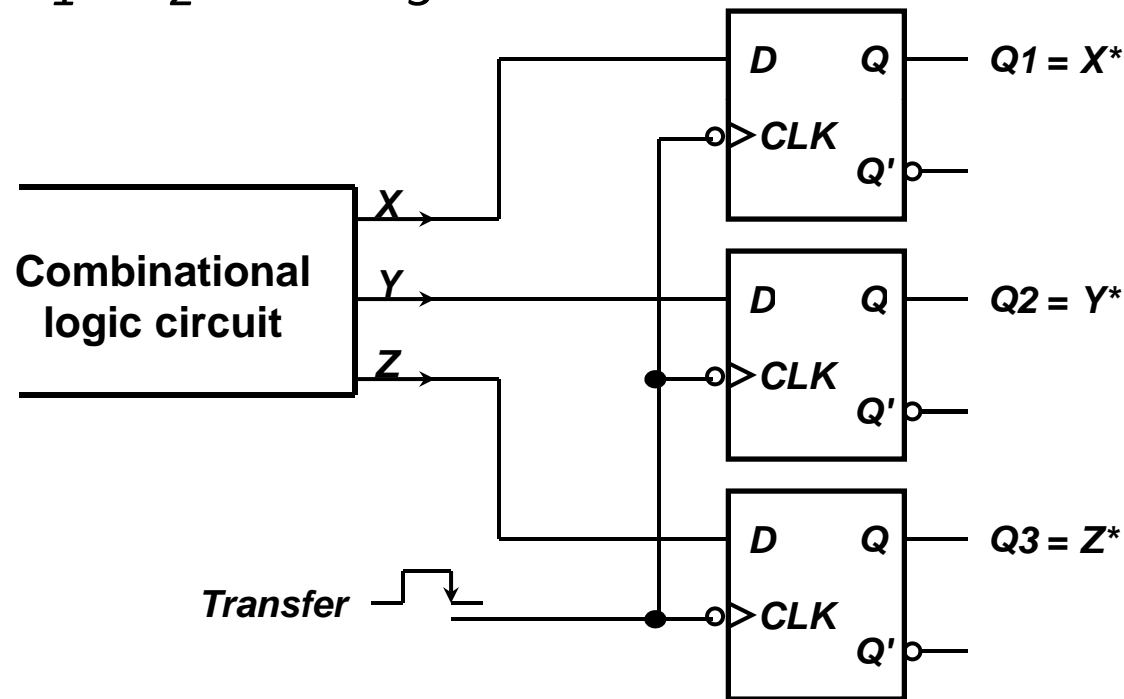- Application: *Parallel data transfer*.
To transfer logic-circuit outputs X , Y , Z to flip-flops Q_1 , Q_2 and Q_3 for storage.




* After occurrence of negative-going transition

J-K Flip-flop

- J-K flip-flop: Q and Q' are fed back to the pulse-steering NAND gates.
- No invalid state.
- Include a *toggle* state.
 - ❖ $J=\text{HIGH}$ (and $K=\text{LOW}$) \Leftrightarrow SET state
 - ❖ $K=\text{HIGH}$ (and $J=\text{LOW}$) \Leftrightarrow RESET state
 - ❖ both inputs LOW \Leftrightarrow no change
 - ❖ both inputs HIGH \Leftrightarrow toggle

J-K Flip-flop

- J-K flip-flop.

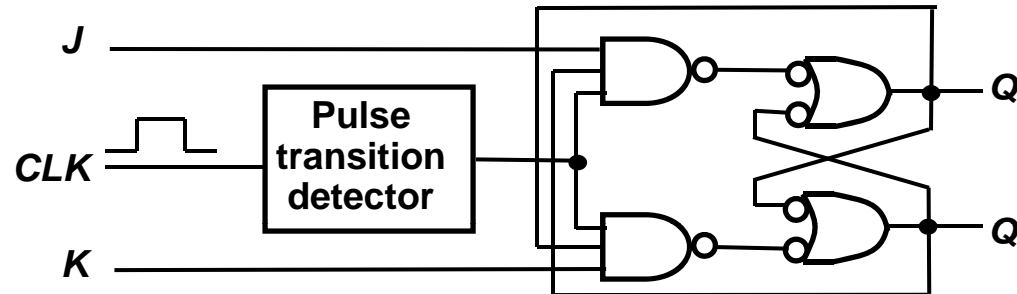

- Characteristic table.


J	K	CLK	$Q(t+1)$	Comments
0	0	↑	$Q(t)$	No change
0	1	↑	0	Reset
1	0	↑	1	Set
1	1	↑	$Q(t)'$	Toggle

$$Q(t+1) = J \cdot Q' + K' \cdot Q$$

Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

T Flip-flop

 - **T flip-flop**: single-input version of the J-K flip flop, formed by tying both inputs together.



- **Characteristic table.**


T	CLK	$Q(t+1)$	Comments
0	↑	$Q(t)$	No change
1	↑	$Q(t)'$	Toggle

Q	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0


$$Q(t+1) = T \cdot Q' + T' \cdot Q$$

T Flip-flop

- Application: *Frequency division.*

 

Divide clock frequency by 2.

 

Divide clock frequency by 4.



- Application: *Counter* (to be covered in Lecture 13.)

Asynchronous Inputs

- S-R, D and J-K inputs are synchronous inputs, as data on these inputs are transferred to the flip-flop's output only on the triggered edge of the clock pulse.
- **Asynchronous** inputs affect the state of the flip-flop independent of the clock; example: *preset (PRE)* and *clear (CLR)* [or *direct set (SD)* and *direct reset (RD)*]
- When $PRE=HIGH$, Q is immediately set to HIGH.
- When $CLR=HIGH$, Q is immediately cleared to LOW.
- Flip-flop in normal operation mode when both PRE and CLR are LOW.





Asynchronous Inputs

  - A J-K flip-flop with active-LOW preset and clear inputs.



Types of Flip-flops

    - SR flip-flop (Set, Reset)
- T flip-flop (Toggle)
- D flip-flop (Delay)
- JK flip-flop



Excitation Tables

Previous State -> Present State	S	R
0 -> 0	0	X
0 -> 1	1	0
1 -> 0	0	1
1 -> 1	X	0

Previous State -> Present State	T
0 -> 0	0
0 -> 1	1
1 -> 0	1
1 -> 1	0


Excitation Tables

Previous State -> Present State	D
0 -> 0	0
0 -> 1	1
1 -> 0	0
1 -> 1	1


Previous State -> Present State	J	K
0 -> 0	0	X
0 -> 1	1	X
1 -> 0	X	1
1 -> 1	X	0

Timing Diagrams

	S	R
0->0	0	X
0->1	1	0
1->0	0	1
1->1	X	0

 


	T
0->0	0
0->1	1
1->0	1
1->1	0

 


Timing Diagrams

	D
0->0	0
0->1	1
1->0	0
1->1	1

 

	J	K
0->0	0	X
0->1	1	X
1->0	X	1
1->1	X	0

 

Converting Flip-flops

- Use T flip-flop to implement D flip-flop

D	Q+
0	0
1	1

D\Q+	0	1
0	0	0
1	1	1


D\Q+	0	1
0	0	1
1	1	0

T	Q+
0	Q
1	Q'

$$\mathbf{T = DQ' + D'Q}$$

Converting flip-flops

 - Use T flip-flop to implement D flip-flop



Converting Flip-flops

- Use T flip-flop to implement JK flip-flop

T	Q+
0	Q
1	Q'

JK\Q+	0	1
00	0	1
01	0	0
11	1	0
10	1	1


JK\Q+	0	1
00	0	0
01	0	1
11	1	1
10	1	0

J	K	Q+
0	0	Q
0	1	0
1	0	1
1	1	Q'

$$\mathbf{T = JQ' + KQ}$$


Converting flip-flops

 - Use T flip-flop to implement JK flip-flop




Registers

 - Sample data using clock
- Hold data between clock cycles
- Computation (and delay) occurs between registers




Timing Methodologies (cont'd)

 - Definition of terms
 - setup time: minimum time before the clocking event by which the input must be stable (T_{su})
 - hold time: minimum time after the clocking event until which the input must remain stable (T_h)




 there is a timing "window" around the clocking event during which the input must remain stable and unchanged in order to be recognized



Typical timing specifications

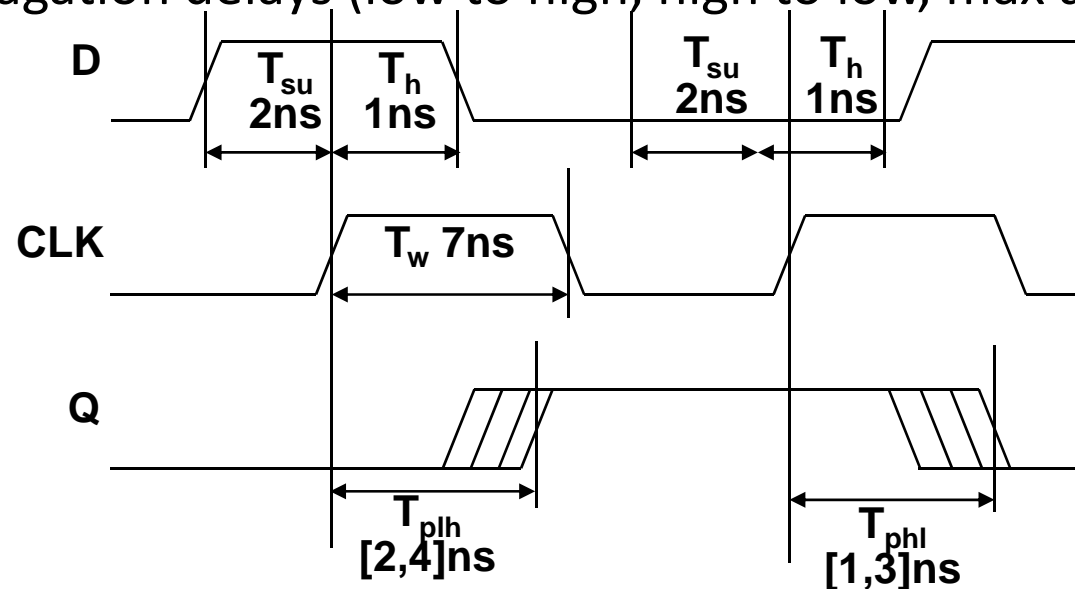
- Positive edge-triggered D flip-flop
 - setup and hold times
 - minimum clock width
 - propagation delays (low to high, high to low, max and typical)



**all measurements are made from the clocking event that is,
the rising edge of the clock**

System Clock Frequency

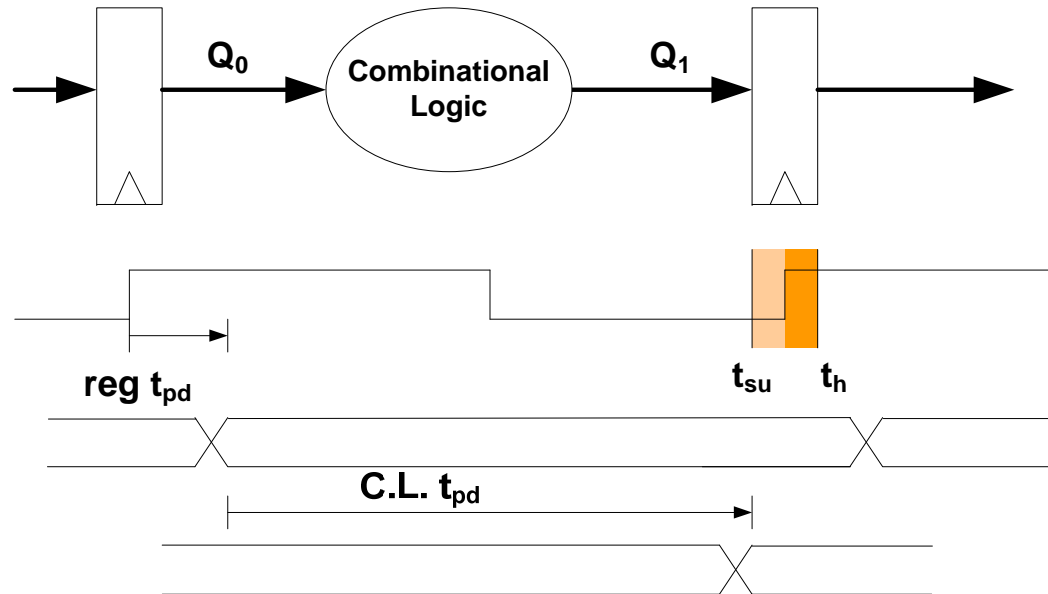
- Register transfer must fit into one clock cycle
 - $\text{reg } t_{pd} + \text{C.L. } t_{pd} + \text{reg } t_{su} < T_{clk}$
 - Use maximum delays
 - Find the “critical path”
 - Longest register-register delay



Sequential Logic

Short Paths

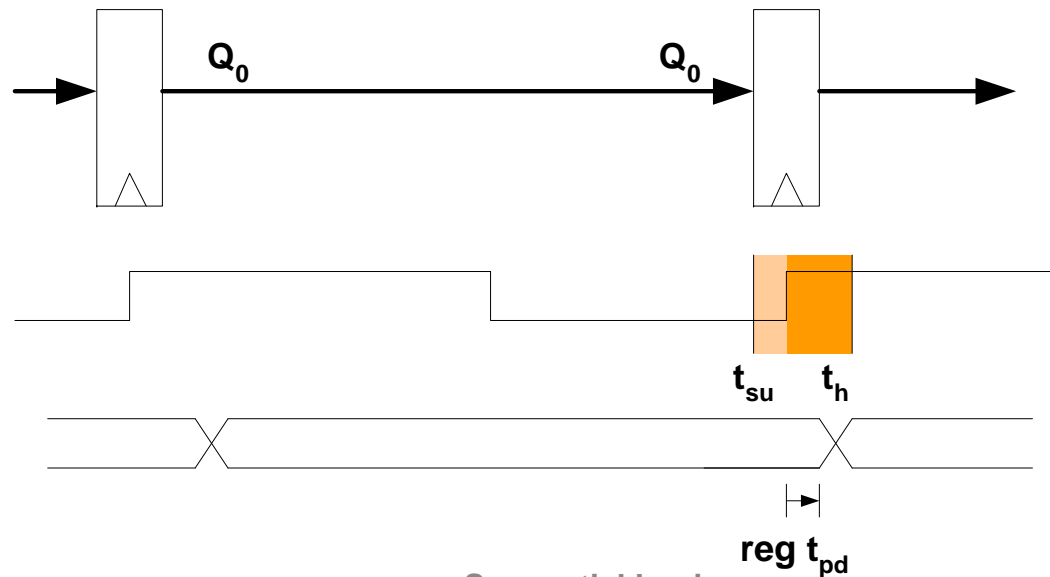
- Can a path have too little delay?
 - Yes: Hold time can be violated
 - Unless $t_{pd} > t_h$
 - Use min delay (contamination delay)
- Fortunately, most registers have hold time = 0
 - But there can still be a problem! Clock skew...



Sequential Logic


Clock Skew

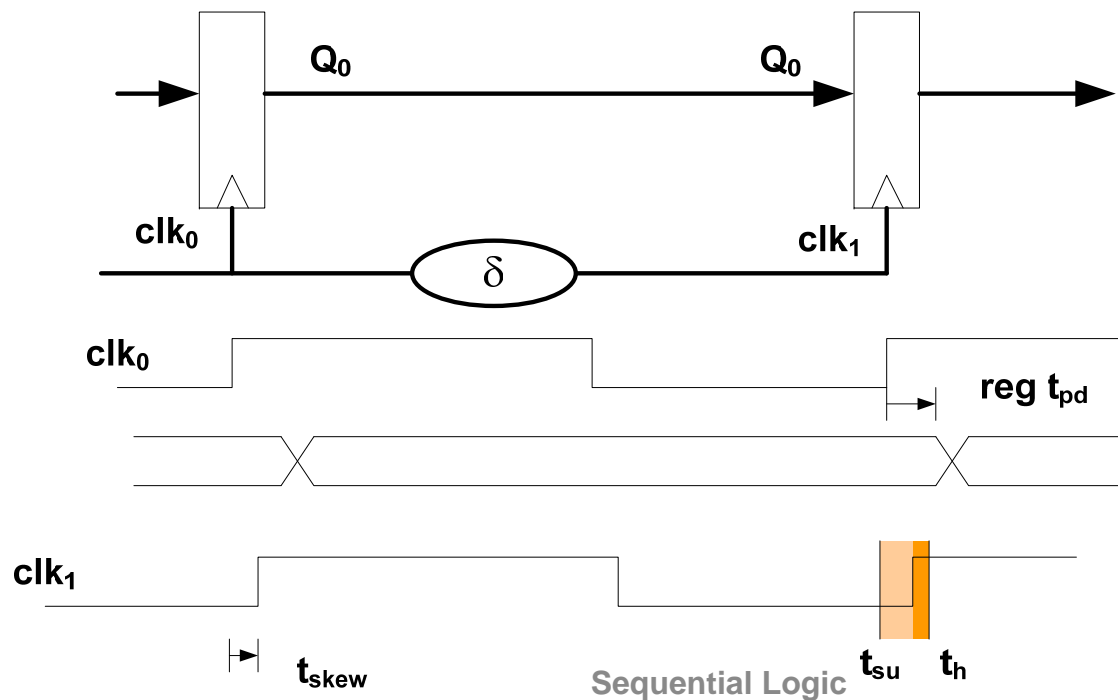- Cannot make clock arrive at registers at the same time
- If skew > 0 :
 - $t_{pd} > t_h + t_{skew}$
 - Clock skew can cause system failure
 - Can you fix this after you've fabbed the chip?




Clock Skew

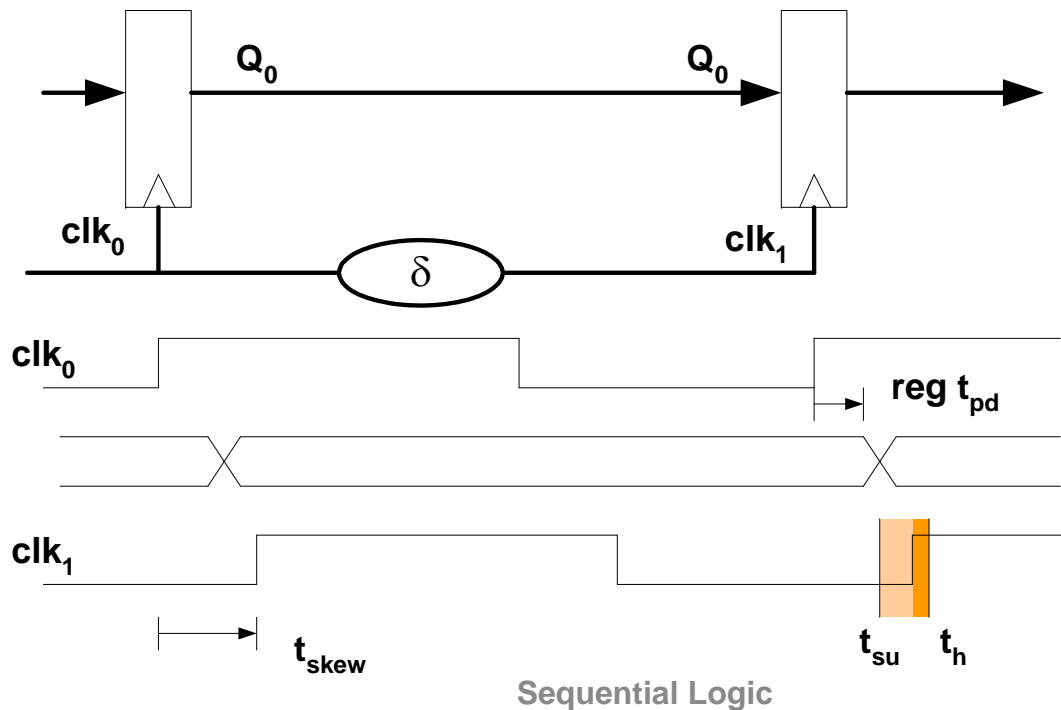- Cannot make clock arrive at registers at the same time
- If skew > 0 :
 - $t_{pd} > t_h + t_{skew}$
 - Clock skew can cause system failure
 - Can you fix this after you've fabbed the chip?



Clock Skew


- If skew < 0:
 - $t_{clk} > reg\ t_{pd} + CL\ t_{pd} + reg\ t_{SU} + |t_{skew}|$
 - Can you fix this after fab?

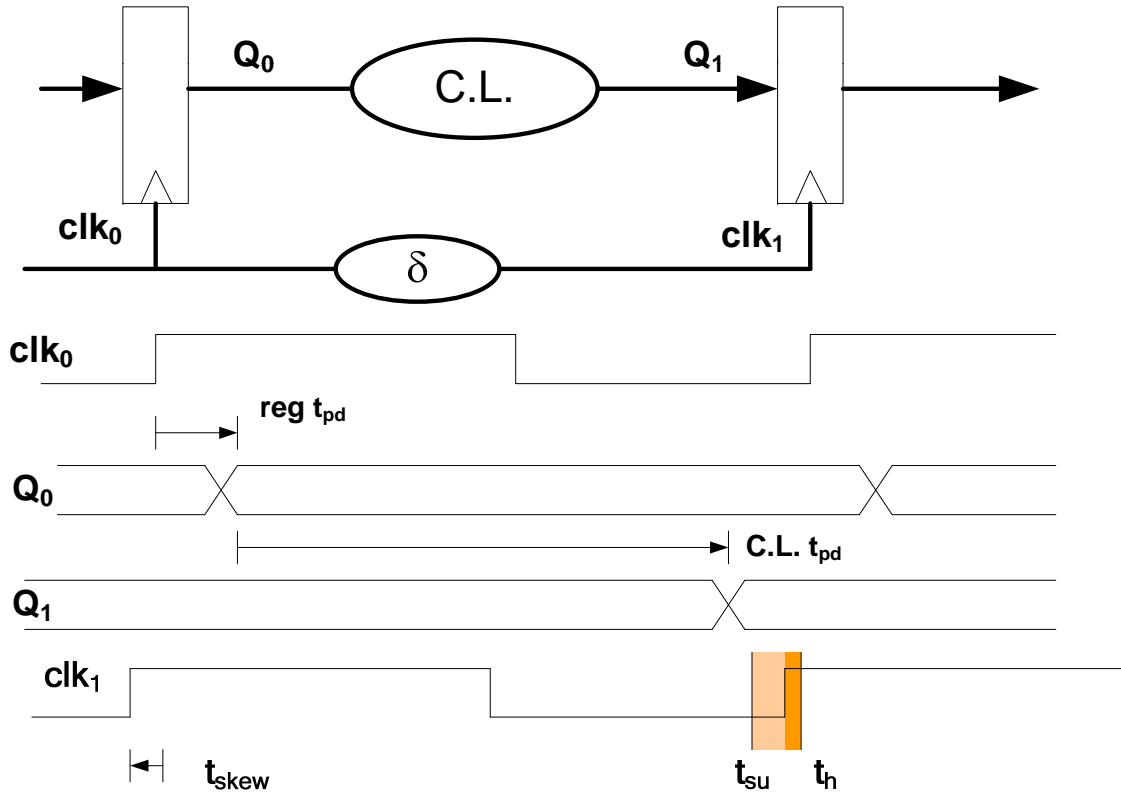

Sequential Logic

Clock Skew

- If skew < 0 :
 - $t_{\text{clk}} > \text{reg } t_{\text{pd}} + \text{C.L. } t_{\text{pd}} + \text{reg } t_{\text{SU}} + |t_{\text{skew}}|$
 - Can you fix this after fab?

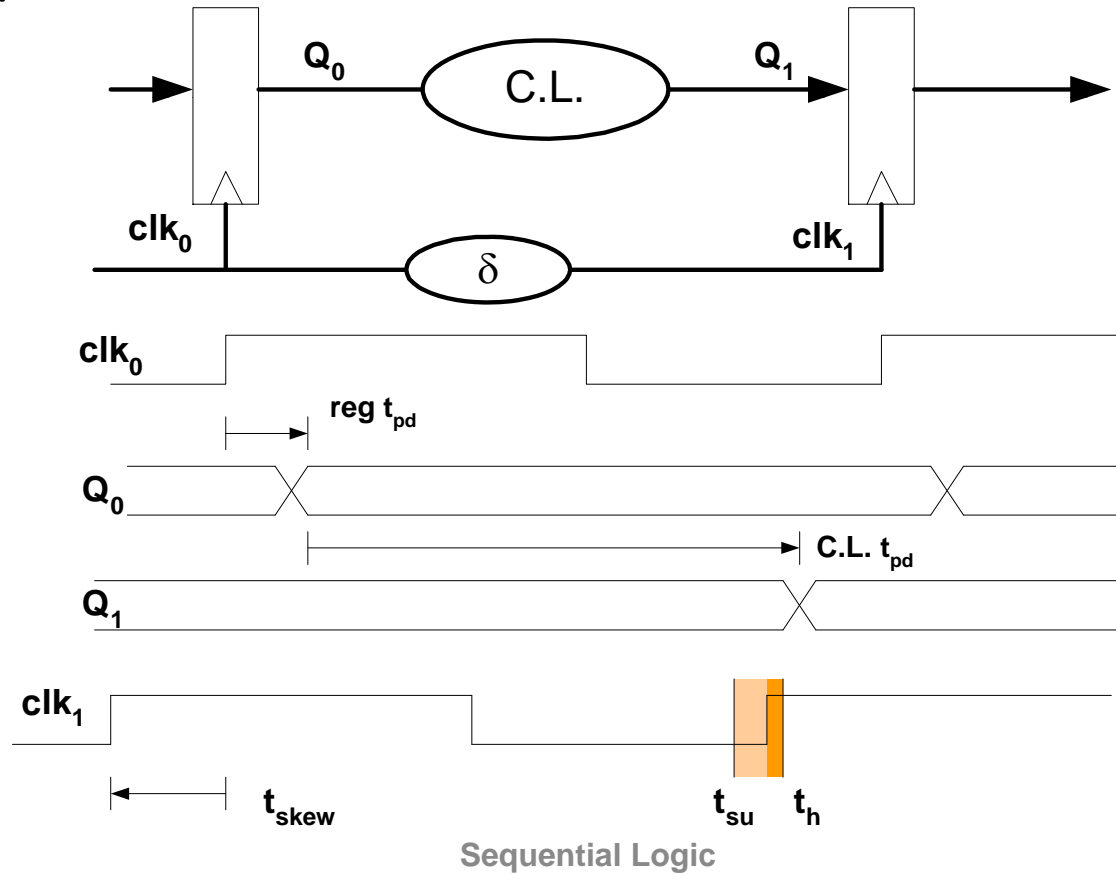


Clock Skew

- Correct behavior assumes that all storage elements sample at exactly the same time
- Not possible in real systems:
 - clock driven from some central location
 - different wire delay to different points in the circuit
- Problems arise if skew is of the same order as FF contamination delay
- Gets worse as systems get faster (wires don't improve as fast)
 - 1) distribute clock signals against the data flow
 - 2) wire carrying the clock between two communicating components should be as short as possible
 - 3) try to make all wires from the clock generator be the same length
=> clock tree

Nasty Example

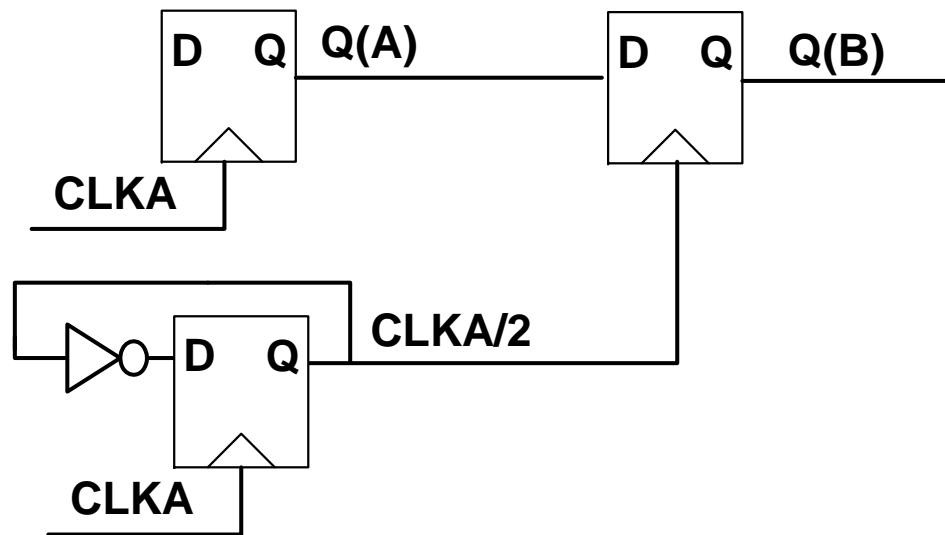
- What can go wrong?
- How can you fix it?




Other Types of Latches and Flip-Flops

- D-FF is ubiquitous
 - simplest design technique, minimizes number of wires
preferred in PLDs and FPGAs
good choice for data storage register
edge-triggered has most straightforward timing constraints
- Historically J-K FF was popular
 - versatile building block, often requires less total logic
 - two inputs require more wiring and logic
 - can always be implemented using D-FF
- Level-sensitive latches in special circumstances
 - popular in VLSI because they can be made very small (4 T)
 - fundamental building block of all other flip-flop types
 - two latches make a D-FF
- Preset and clear inputs are highly desirable
 - System reset


Comparison of latches and flip-flops

 

positive
edge-triggered
flip-flop

 

 
transparent, flow-through
(level-sensitive)
latch



behavior is the same unless input changes
while the clock is high



What About External Inputs?

 - Internal signals are OK
 - Can only change when clock changes
- External signals can change at any time
 - Asynchronous inputs
 - Truly asynchronous
 - Produced by a different clock
- This means register may sample a signal that is changing
 - Violates setup/hold time
 - What happens?




Sequential Logic

Sampling external inputs

 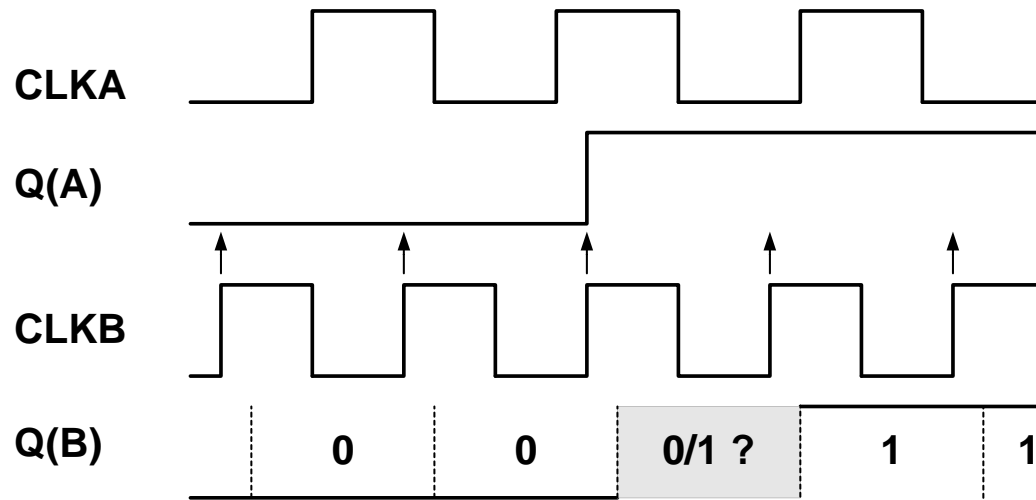


Synchronization failure

 - Occurs when FF input changes close to clock edge
 - the FF may enter a metastable state – neither a logic 0 nor 1 –
 - it may stay in this state an indefinite amount of time
 - this is not likely in practice but has some probability



 **small, but non-zero probability
that the FF output will get stuck
in an in-between state**



**oscilloscope traces demonstrating
synchronizer failure and eventual
decay to steady state**

Calculating probability of failure

- For a single synchronizer


$$\text{Mean-Time Between Failure (MTBF)} = \exp (t_r / \tau) / (T_0 \times f_c \times f_a)$$

where a failure occurs if metastability persists beyond time t_r

- t_r is the resolution time - extra time in clock period for settling
 - $T_{\text{clk}} - (t_{\text{pd}} + T_{\text{CL}} + t_{\text{setup}})$
- f_c is the frequency of the FF clock
- f_a is the number of asynchronous input changes per second applied to the FF
- T_0 and τ are constants that depend on the FF's electrical characteristics (e.g., gain or steepness of curve)
 - example values are $T_0 = 1\text{ms}$ and $\tau = 30\text{ps}$
(sensitive to temperature, voltage, cosmic rays, etc.).
- Must add probabilities from all synchronizers in system
 $1/\text{MTBF}_{\text{system}} = \sum 1/\text{MTBF}_{\text{synch}}$

Xilinx Measurements

 
XC2VP4 Metastable Recovery
~300MHz Clock, 50MHz Data



Sequential Logic

Xilinx Measurements

 
**Metastable Progress
2002 vs 1996
~100MHz Clock, 1 MHz Data**



Sequential Logic


What does this circuit do?

- What's wrong with this?

 

What does this circuit do?


- How much better is this?

 

- Can you do better?


Guarding against synchronization failure

 - Give the register time to decide
 - Probability of failure cannot be reduced to 0, but it can be reduced
- *Slow down the system clock?*
- *Use very fast technology for synchronizer -> quicker decision?*
- *Cascade two synchronizers?*




Stretching the Resolution Time

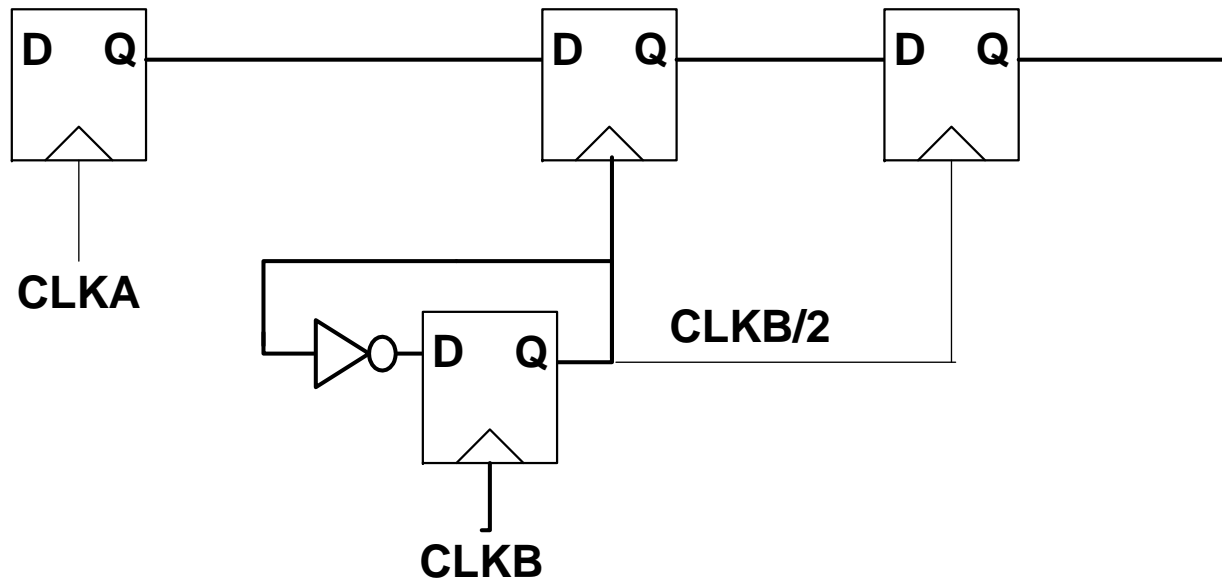- Also slows the sample rate and transfer rate




Sampling Rate

 - How fast does your sample clock need to be?



Sampling Rate

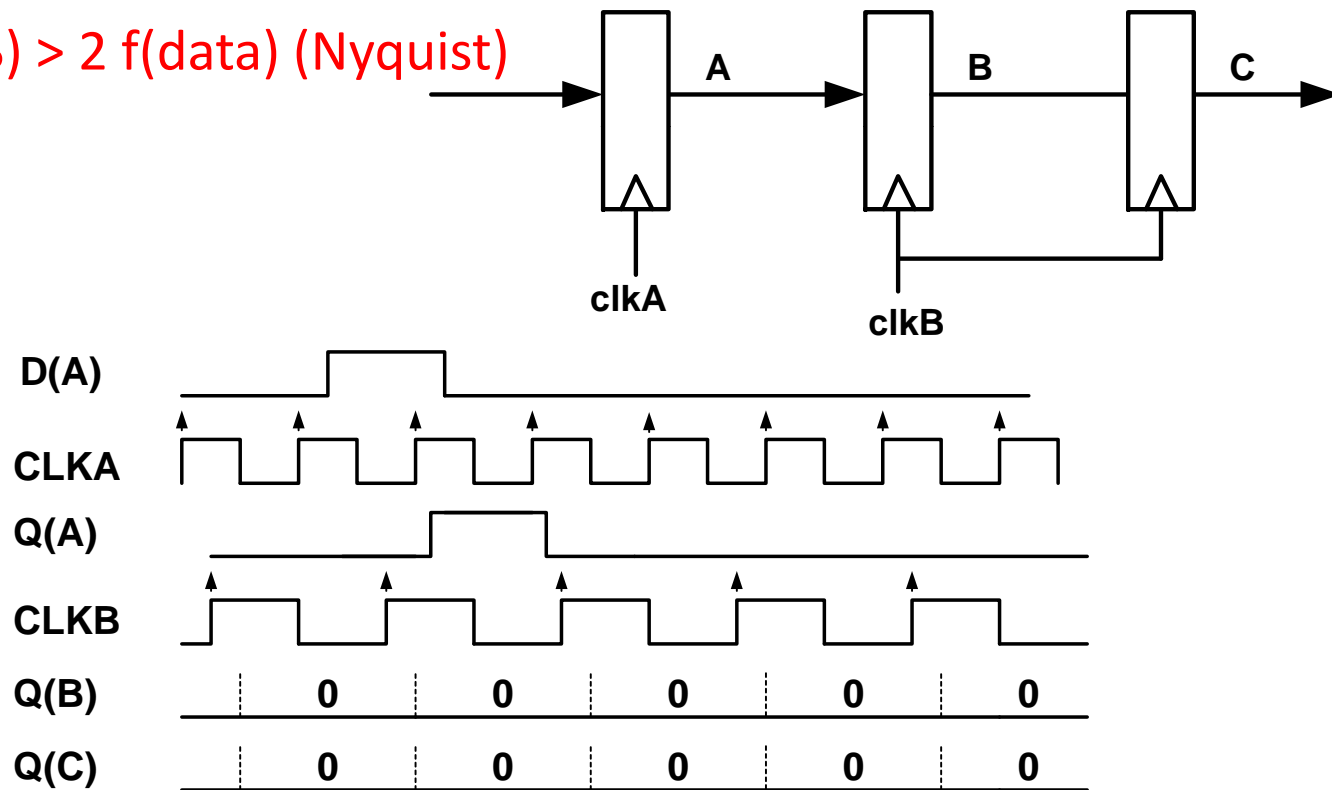- How fast does your sample clock need to be?
 - $f(\text{clkB}) > f(\text{clkA})$
 - $f(\text{clkB}) > 2 f(\text{data})$ (Nyquist)




Sampling Rate

- What if sample clock can't go faster?
- If input clock is not available, no solution(?)
- If input clock is available (e.g. video codec)


Increasing sample rate

 - The problem is the **relative** sample rate
 - Slow down the input clock!




Another Problem with Asynchronous inputs

 - What goes wrong here? (Hint: it's not a metastability thing)
- What is the fix?




More Asynchronous inputs

 - What is the problem?
- What is the fix?




Important Rule!

 - Exactly one register makes the synchronizing decision




More Asynchronous inputs

 - Can we input asynchronous data values with several bits?



More Asynchronous inputs

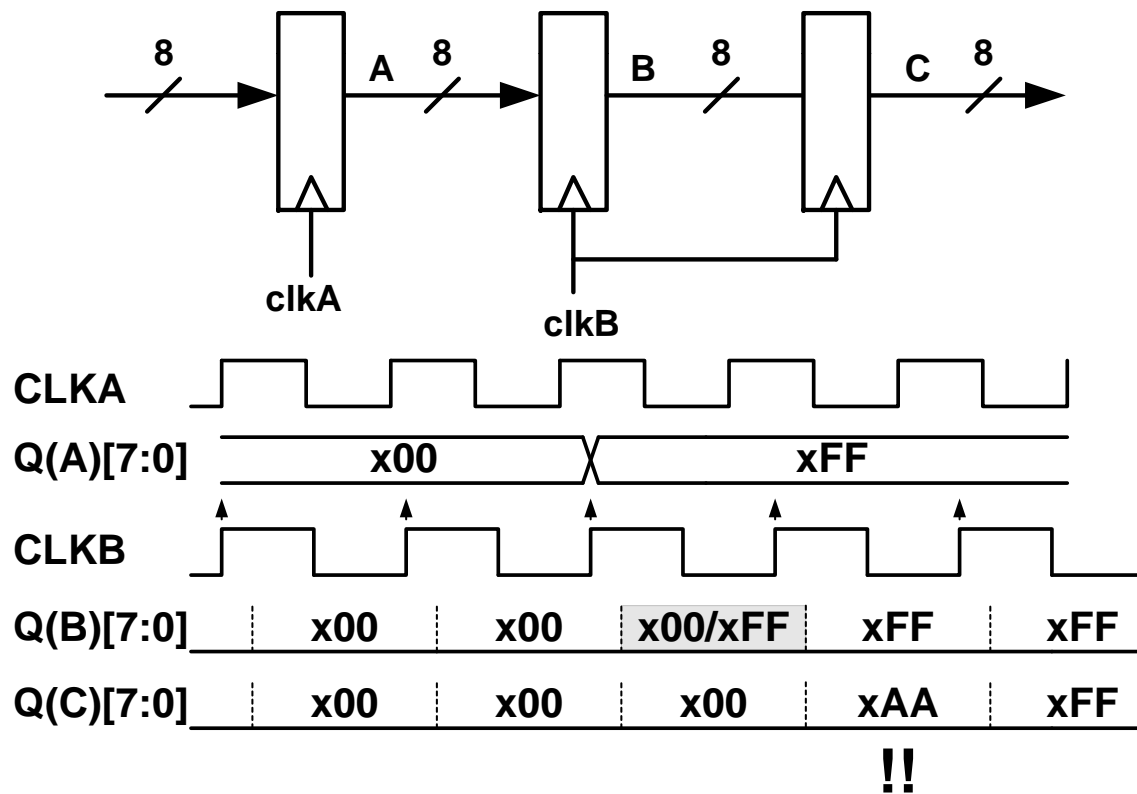- How can we input asynchronous data values with several bits?




What Went Wrong?

- Each bit has a different delay
 - Wire lengths differ
 - Gate thresholds differ
 - Driver speeds are different
 - Register delays are different
 - Rise vs. Fall times
 - Clock skews to register bits
- Bottom line – “data skew” is inevitable
 - aka Bus Skew
 - Longer wires => More skew
- What is the solution??


Sending Multiple Data Bits

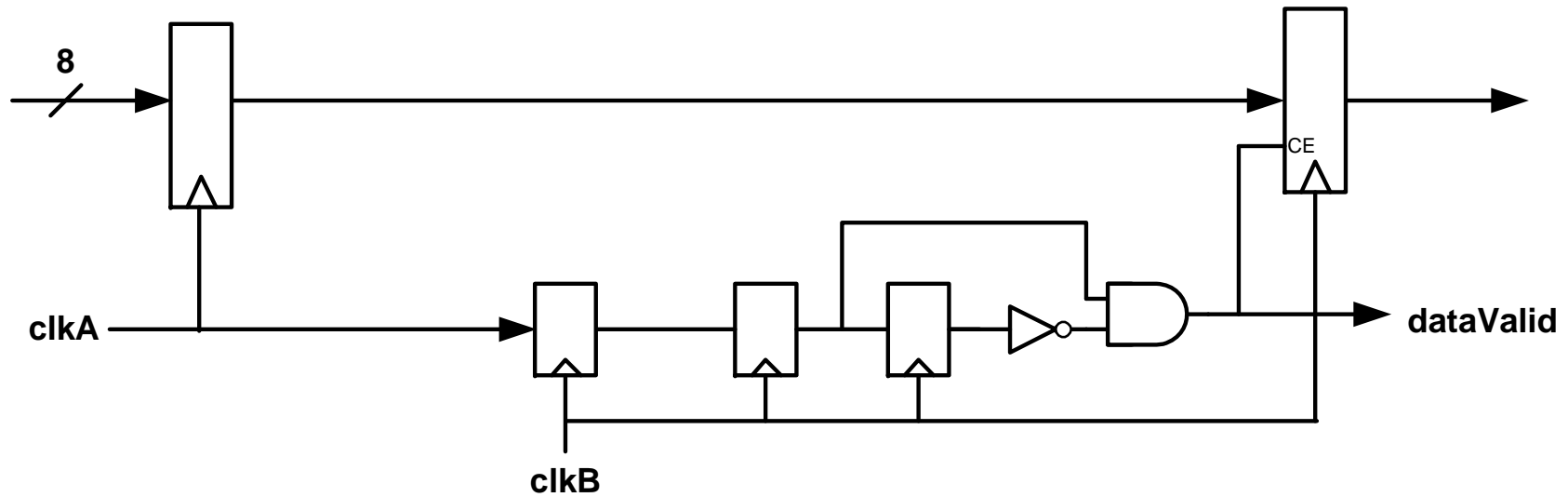- Must send a “clock” with the data
 - Waits until data is stable
 - De-skewing delay
- **$f(\text{clkB}) > 2 f(\text{clkA})$**




Sending Multiple Data Bits

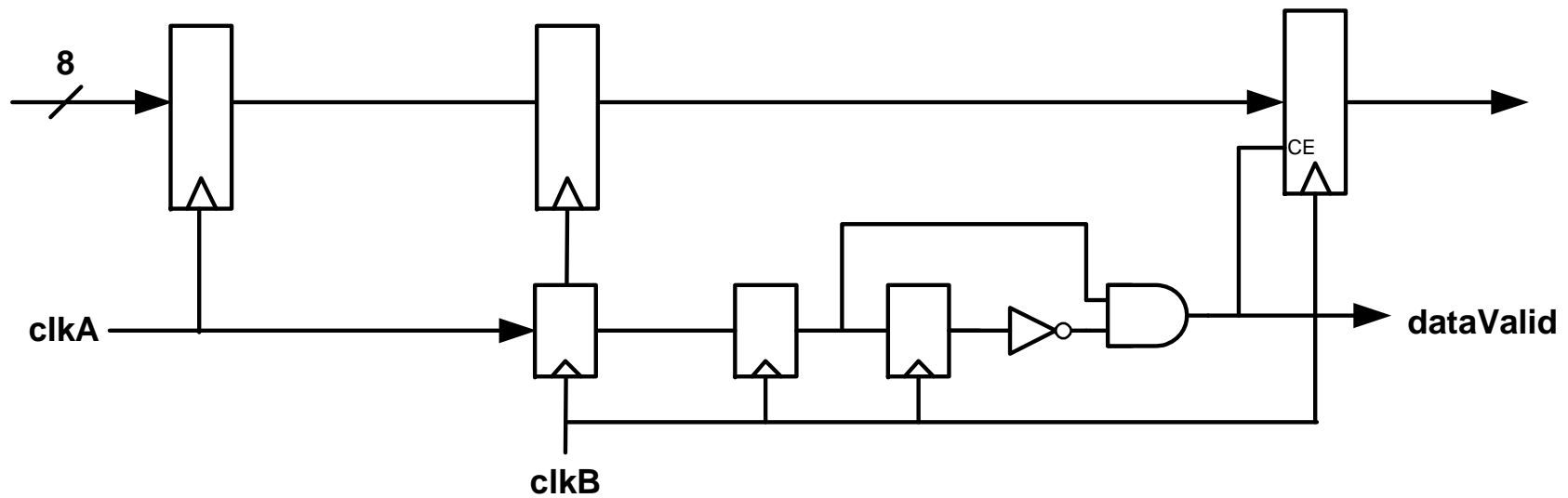- Balancing path delays . . .
- What's wrong with this solution?
- What's the right way to do it?




Sending Multiple Data Bits

- The right way to do it . . .

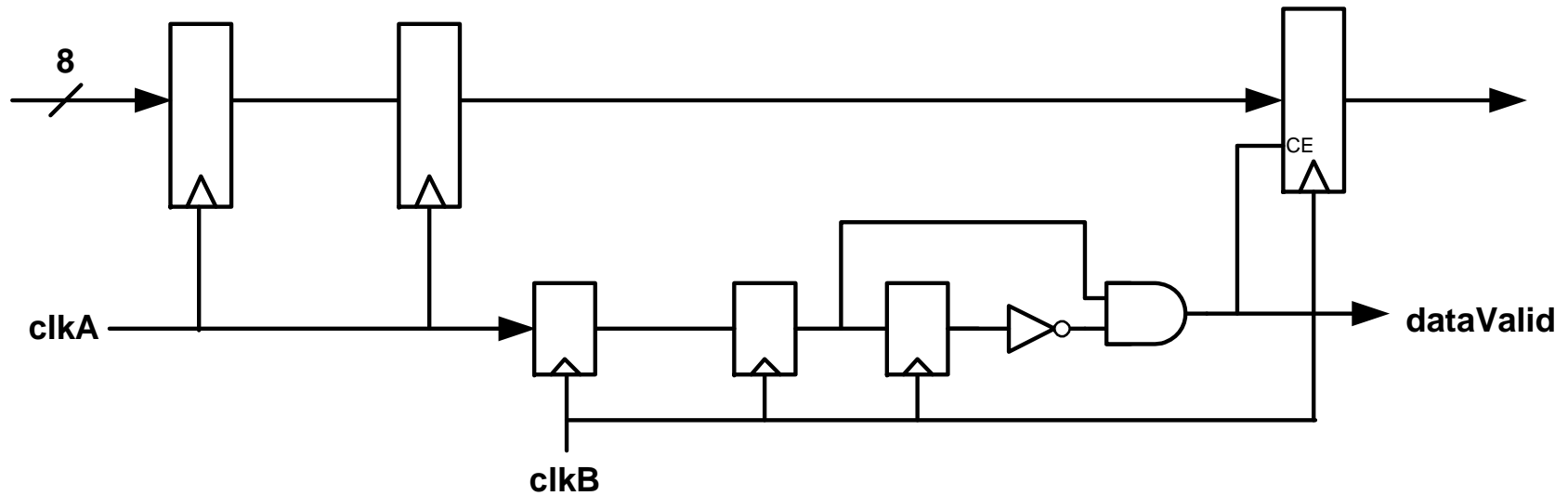

Sending Multiple Data Bits

- Slightly different alternative . . .

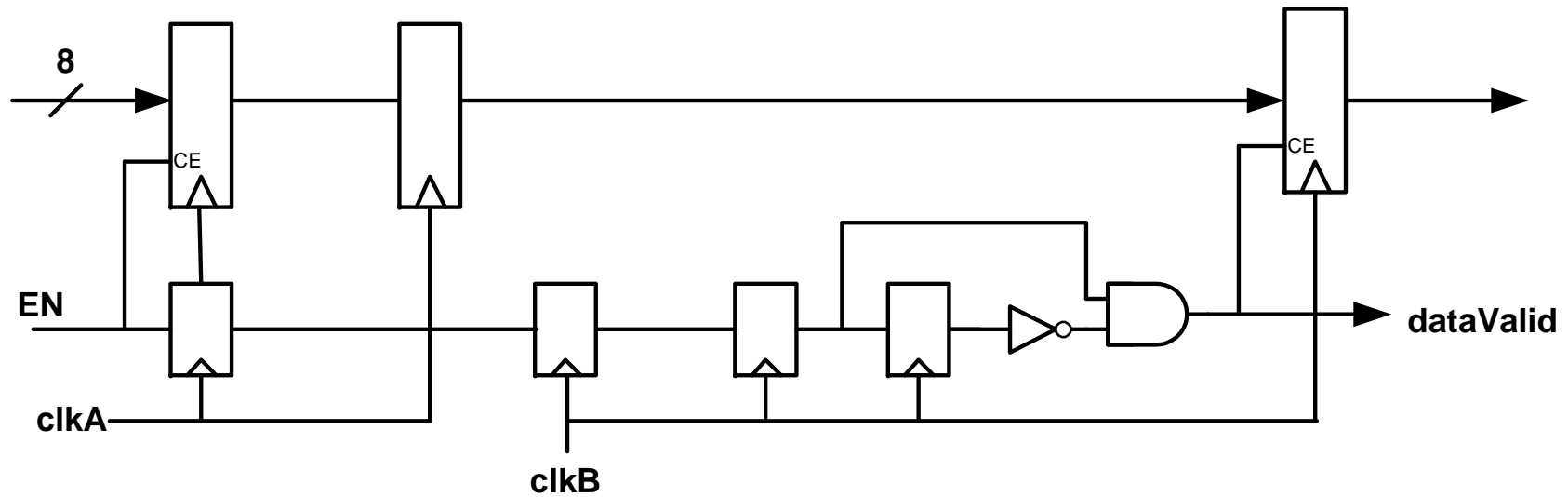

Sequential Logic Counters and Registers

Counters

- [Introduction: Counters](#)
- [Asynchronous \(Ripple\) Counters](#)
- [Asynchronous Counters with MOD number \$< 2^n\$](#)
- [Asynchronous Down Counters](#)
- [Cascading Asynchronous Counters](#)

Lecture 13: Sequential Logic Counters and Registers

- Synchronous (Parallel) Counters
- Up/Down Synchronous Counters
- Designing Synchronous Counters
- Decoding A Counter
- Counters with Parallel Load

Lecture 13: Sequential Logic Counters and Registers

Registers

- Introduction: Registers
 - ❖ Simple Registers
 - ❖ Registers with Parallel Load
- Using Registers to implement Sequential Circuits
- Shift Registers
 - ❖ Serial In/Serial Out Shift Registers
 - ❖ Serial In/Parallel Out Shift Registers
 - ❖ Parallel In/Serial Out Shift Registers
 - ❖ Parallel In/Parallel Out Shift Registers

Lecture 13: Sequential Logic Counters and Registers

- Bidirectional Shift Registers
- An Application – Serial Addition
- Shift Register Counters
 - ❖ Ring Counters
 - ❖ Johnson Counters
- Random-Access Memory (RAM)

Introduction: Counters



- **Counters** are circuits that cycle through a specified number of states.
- Two types of counters:
 - ❖ synchronous (parallel) counters
 - ❖ asynchronous (ripple) counters
- Ripple counters allow some flip-flop outputs to be used as a source of clock for other flip-flops.
- Synchronous counters apply the same clock to all flip-flops.

Asynchronous (Ripple) Counters

- **Asynchronous counters:** the flip-flops do not change states at exactly the same time as they do not have a common clock pulse.
- Also known as **ripple counters**, as the input clock pulse “ripples” through the counter – cumulative delay is a drawback.
- n flip-flops \rightarrow a MOD (modulus) 2^n counter. (Note: A MOD- x counter cycles through x states.)
- Output of the last flip-flop (MSB) divides the input clock frequency by the MOD number of the counter, hence a counter is also a *frequency divider*.

Asynchronous (Ripple) Counters

  - Example: 2-bit ripple binary counter.
- Output of one flip-flop is connected to the clock input of the next more-significant flip-flop.




Timing diagram

00 → 01 → 10 → 11 → 00 ...


Asynchronous (Ripple) Counters

- Example: 3-bit ripple binary counter.

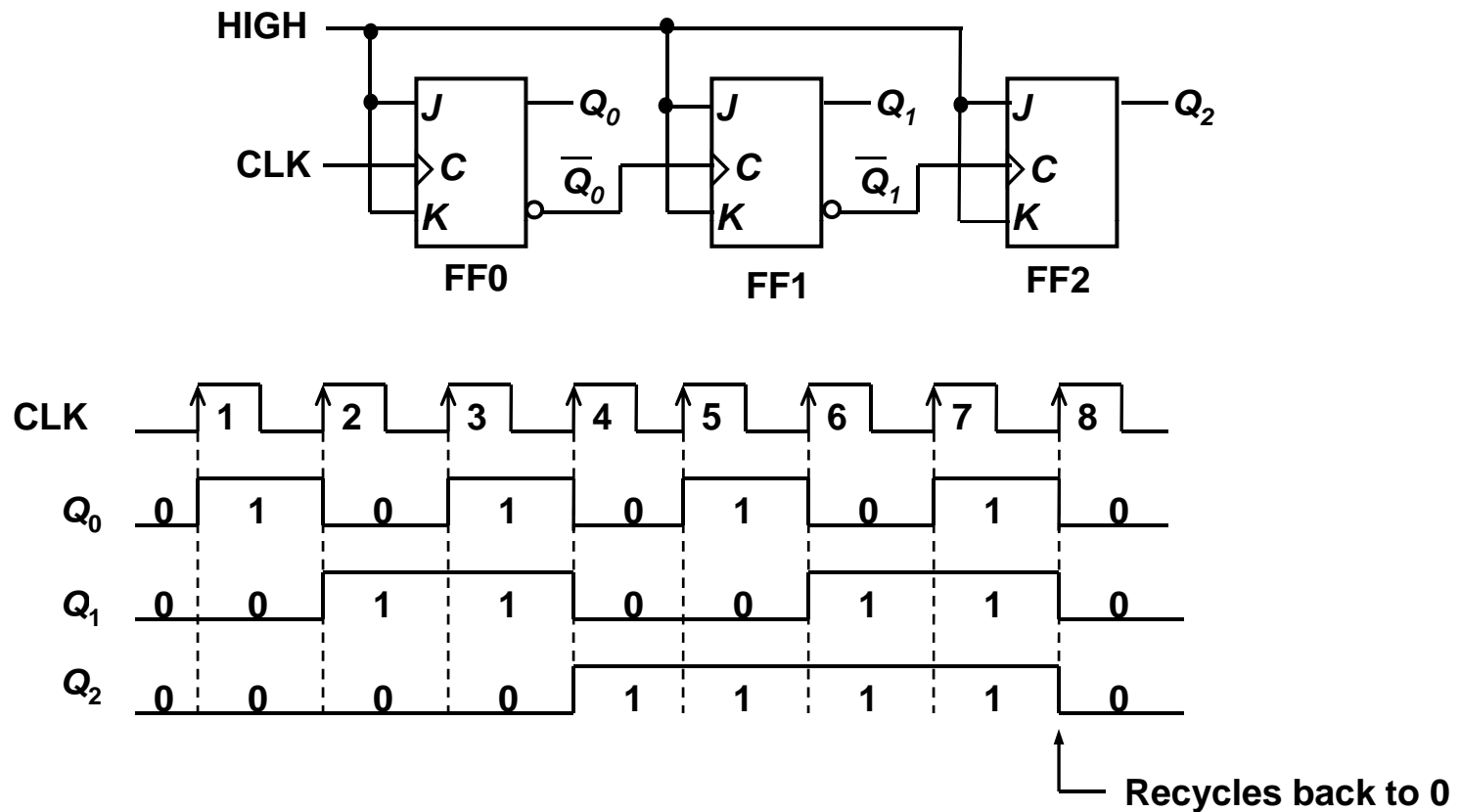



Asynchronous (Ripple) Counters

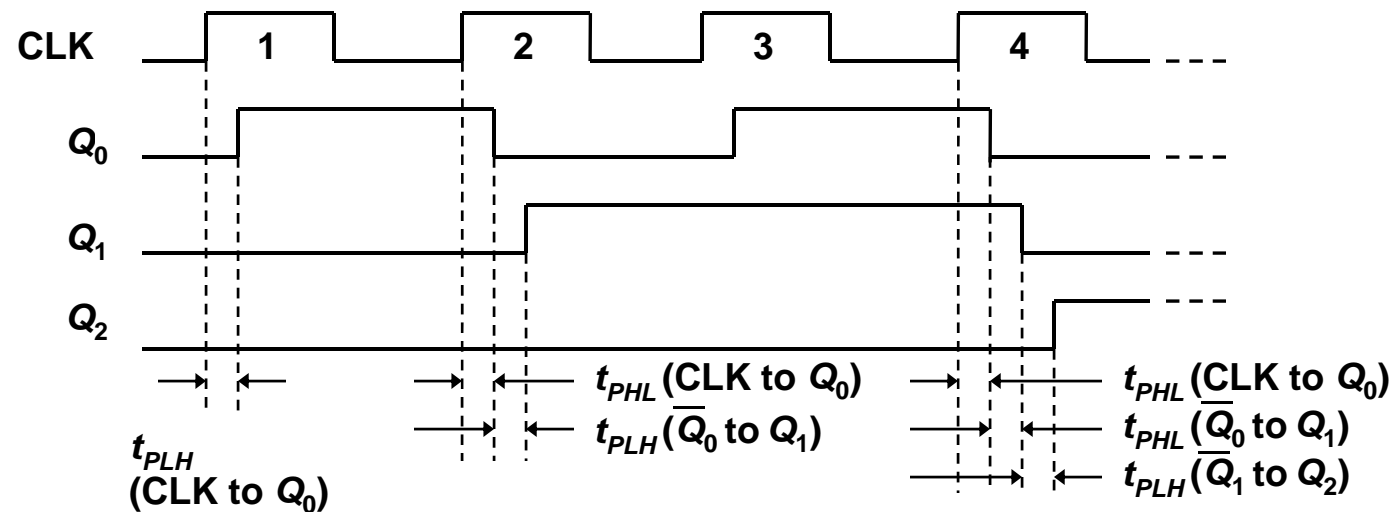- Propagation delays in an asynchronous (ripple-clocked) binary counter.
- If the accumulated delay is greater than the clock pulse, some counter states may be misrepresented!




Asynchronous (Ripple) Counters

  - Example: 4-bit ripple binary counter (negative-edge triggered).




Asyn. Counters with MOD no. $< 2^n$

 - States may be skipped resulting in a **truncated sequence**.
- Technique: force counter to *recycle before going through all of the states* in the binary sequence.
- Example: Given the following circuit, determine the counting sequence (and hence the modulus no.)




Asyn. Counters with MOD no. $< 2^n$

- Example (cont'd):

 

All J, K inputs are 1 (HIGH).


 


MOD-6 counter produced by clearing (a MOD-8 binary counter) when count of six (110) occurs.

Asynchronous Counters with MOD number $< 2^n$


Asyn. Counters with MOD no. $< 2^n$

  - Example (cont'd): Counting sequence of circuit (in CBA order).




Asyn. Counters with MOD no. $< 2^n$

 - *Exercise:* How to construct an asynchronous MOD-5 counter? MOD-7 counter? MOD-12 counter?
- *Question:* The following is a MOD-? counter?





Asyn. Counters with MOD no. $< 2^n$

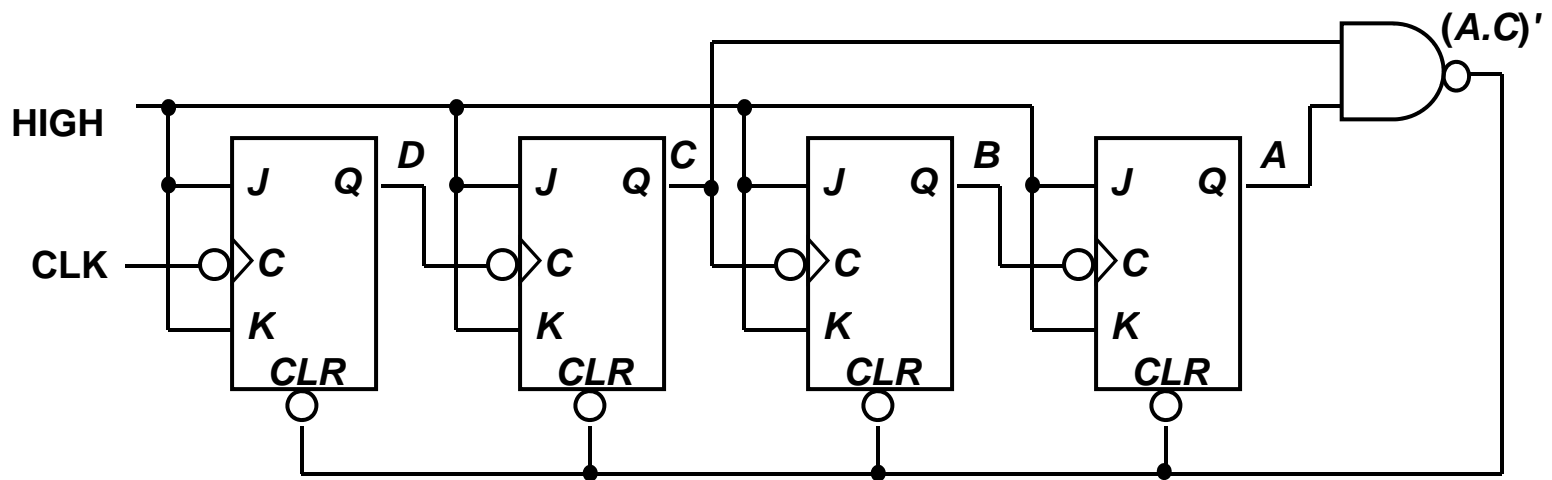- **Decade counters** (or **BCD counters**) are counters with 10 states (modulus-10) in their sequence. They are commonly used in daily life (e.g.: utility meters, odometers, etc.).
- Design an asynchronous decade counter.




Asyn. Counters with MOD no. $< 2^n$

  - Asynchronous decade/BCD counter (cont'd).




Asynchronous Down Counters

 - So far we are dealing with *up counters*. *Down counters*, on the other hand, count downward from a maximum value to zero, and repeat.
- Example: A 3-bit binary (MOD- 2^3) down counter.




Asynchronous Down Counters

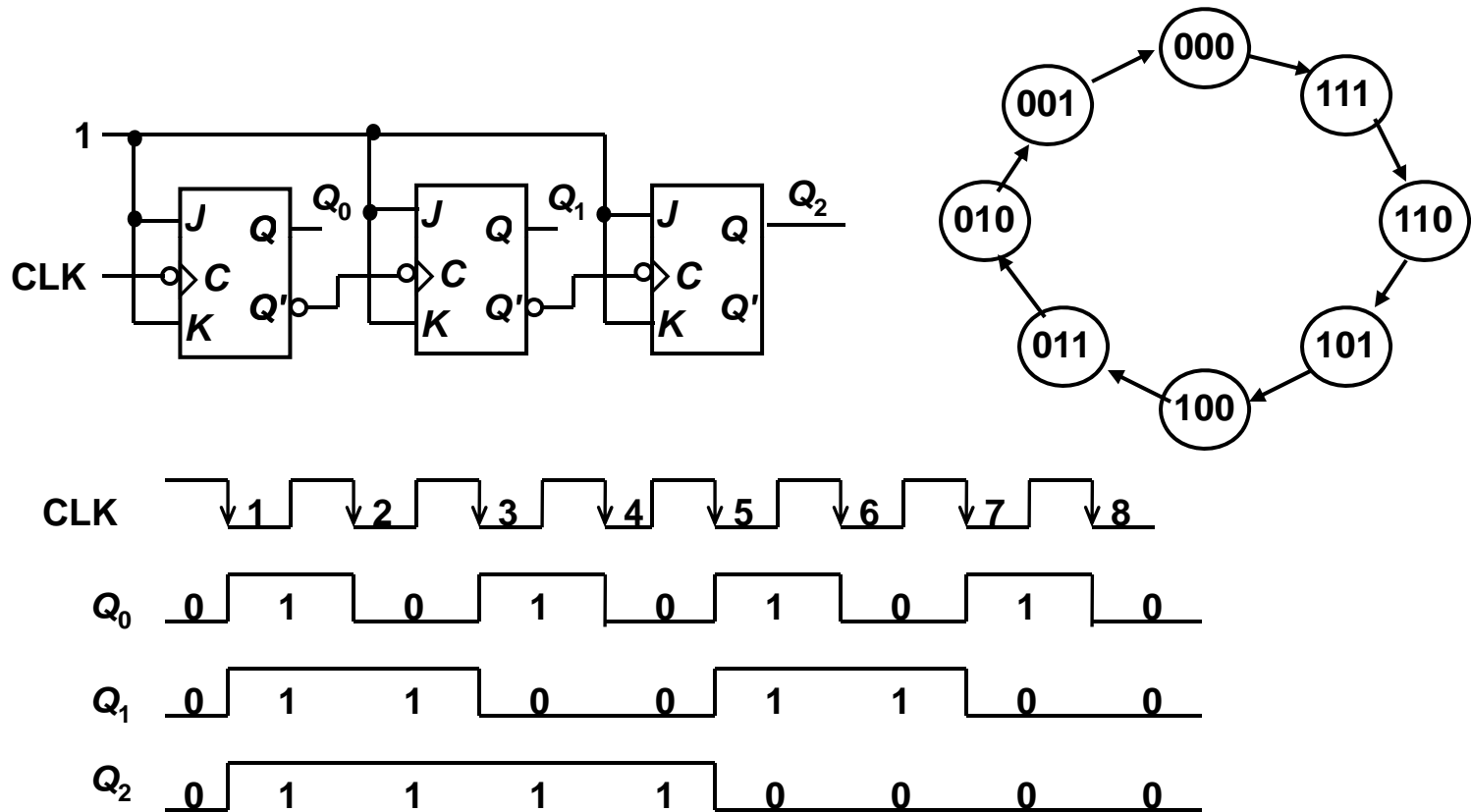- Example: A 3-bit binary (MOD-8) down counter.




Cascading Asynchronous Counters

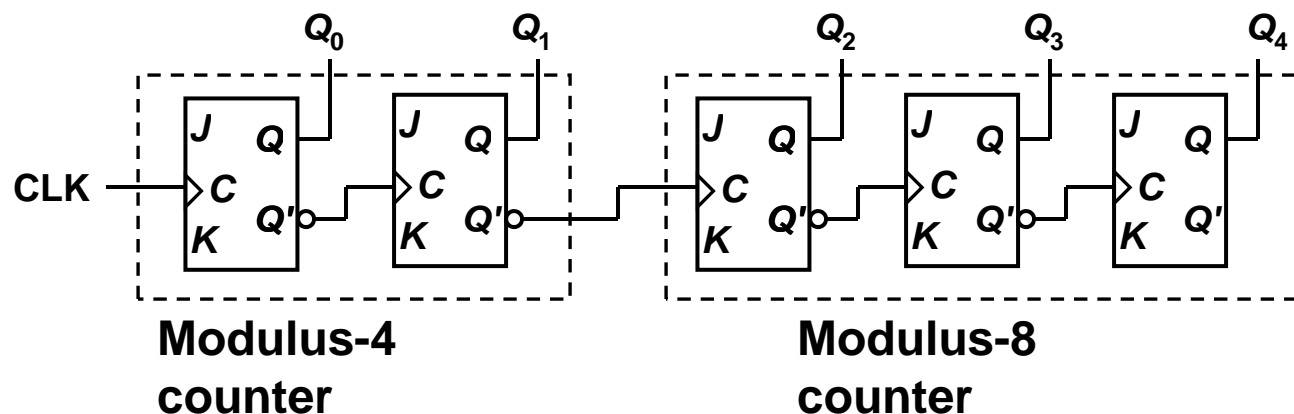- Larger asynchronous (ripple) counter can be constructed by cascading smaller ripple counters.
- Connect last-stage output of one counter to the clock input of next counter so as to achieve higher-modulus operation.
- Example: A modulus-32 ripple counter constructed from a modulus-4 counter and a modulus-8 counter.



Cascading Asynchronous Counters

 
- Example: A 6-bit binary counter (counts from 0 to 63) constructed from two 3-bit counters.



A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	0
0	0	0	0	0	1
0	0	0	:	:	:
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	0	1
:	:	:	:	:	:

Cascading Asynchronous Counters

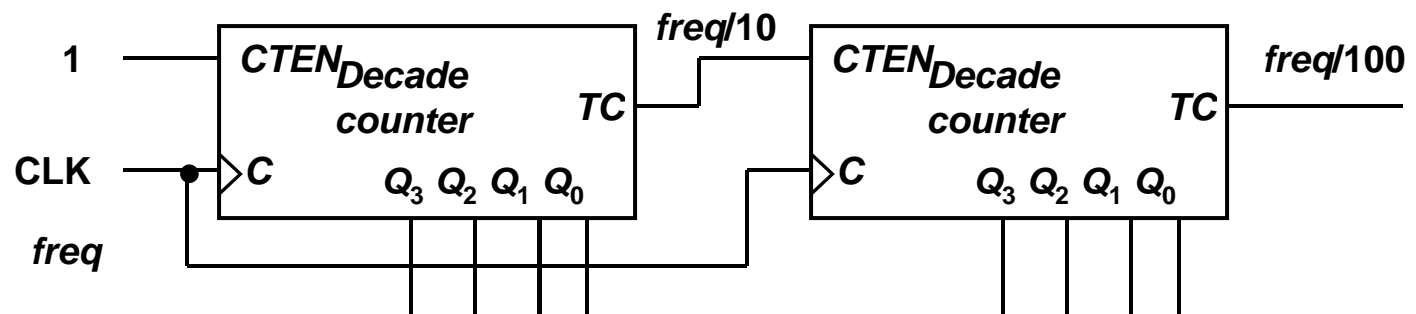
- If counter is not a binary counter, requires additional output.
- Example: A modulus-100 counter using two decade counters.



$TC = 1$ when counter recycles to 0000

Synchronous (Parallel) Counters

 - **Synchronous (parallel) counters:** the flip-flops are clocked at the same time by a common clock pulse.
- We can design these counters using the sequential logic design process (covered in Lecture #12).
- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).



Present state		Next state		Flip-flop inputs	
A_1	A_0	A_1^+	A_0^+	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1


Synchronous (Parallel) Counters

- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).

Present state		Next state		Flip-flop inputs	
A_1	A_0	A_1^+	A_0^+	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

$$TA_1 = A_0$$


$$TA_0 = 1$$

 

Synchronous (Parallel) Counters

- Example: 3-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J, K inputs).

Present state			Next state			Flip-flop inputs		
A_2	A_1	A_0	A_2^+	A_1^+	A_0^+	TA_2	TA_1	TA_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

 


Synchronous (Parallel) Counters

- Example: 3-bit synchronous binary counter (cont'd).

$$TA_2 = A_1.A_0$$

$$TA_1 = A_0 TA_0 = 1$$

 

Synchronous (Parallel) Counters

- Note that in a binary counter, the n^{th} bit (shown underlined) is always complemented whenever

$$\underline{0}11\dots11 \rightarrow \underline{1}00\dots00$$

$$\text{or } \underline{1}11\dots11 \rightarrow \underline{0}00\dots00$$

- Hence, X_n is complemented whenever

$$X_{n-1}X_{n-2} \dots X_1X_0 = 11\dots11.$$

- As a result, if T flip-flops are used, then

$$TX_n = X_{n-1} \cdot X_{n-2} \cdot \dots \cdot X_1 \cdot X_0$$

Synchronous (Parallel) Counters


- Example: 4-bit synchronous binary counter.

$$TA_3 = A_2 \cdot A_1 \cdot A_0$$

$$TA_2 = A_1 \cdot A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

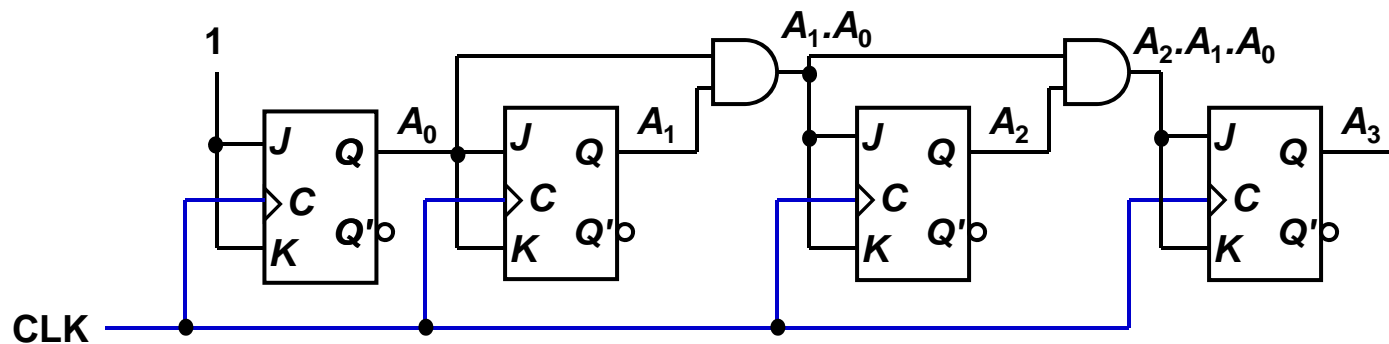

Synchronous (Parallel) Counters

- Example: Synchronous decade/BCD counter.

Clock pulse	Q_3	Q_2	Q_1	Q_0
Initially	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10 (recycle)	0	0	0	0

$$T_0 = 1$$

$$T_1 = Q_3' \cdot Q_0$$

$$T_2 = Q_1 \cdot Q_0$$

$$T_3 = Q_2 \cdot Q_1 \cdot Q_0 + Q_3 \cdot Q_0$$

Synchronous (Parallel) Counters


- Example: Synchronous decade/BCD counter (cont'd).

$$T_0 = 1$$

$$T_1 = Q_3' \cdot Q_0$$

$$T_2 = Q_1 \cdot Q_0$$
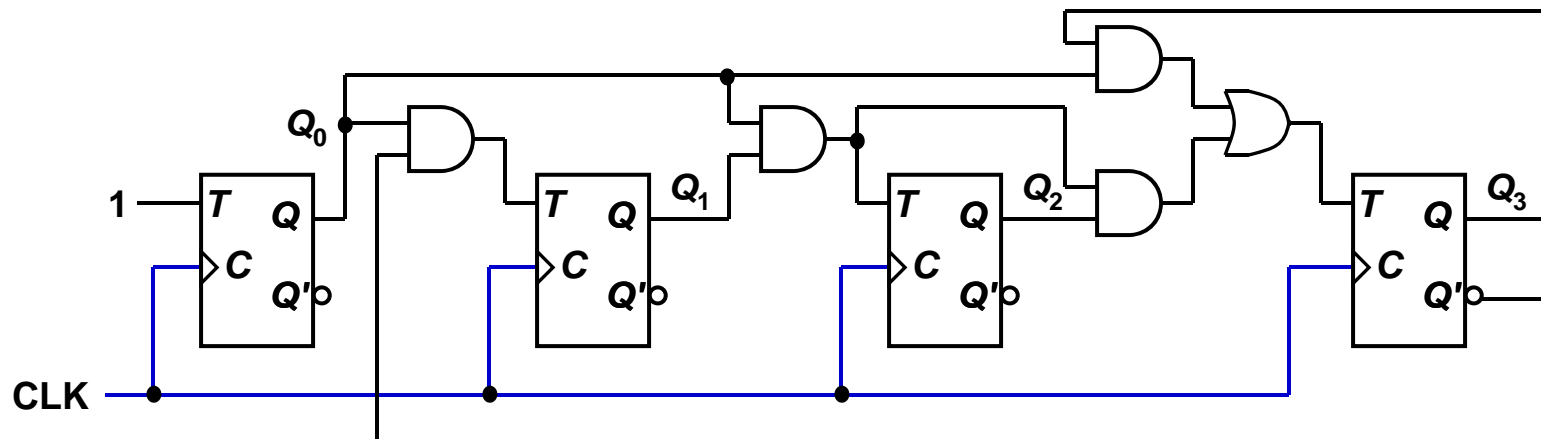
$$T_3 = Q_2 \cdot Q_1 \cdot Q_0 + Q_3 \cdot Q_0$$



Up/Down Synchronous Counters

- **Up/down synchronous counter:** a *bidirectional* counter that is capable of counting either up or down.
- An input (control) line $\overline{Up/Down}$ (or simply *Up*) specifies the direction of counting.
 - ❖ $\overline{Up/Down} = 1 \rightarrow$ Count upward
 - ❖ $\overline{Up/Down} = 0 \rightarrow$ Count downward

Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter.

Clock pulse	<i>Up</i>	Q_2	Q_1	Q_0	<i>Down</i>
0		0	0	0	
1		0	0	1	
2		0	1	0	
3		0	1	1	
4		1	0	0	
5		1	0	1	
6		1	1	0	
7		1	1	1	

$$TQ_0 = 1$$

$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$

$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$

Up counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0$$

$$TQ_2 = Q_0 \cdot Q_1$$

Down counter

counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0'$$

$$TQ_2 = Q_0' \cdot Q_1'$$


Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter (cont'd).

$$TQ_0 = 1$$


$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$
 
$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$



Designing Synchronous Counters

 - Covered in Lecture #12.
- Example: A 3-bit Gray code counter (using JK flip-flops).



Present state			Next state			Flip-flop inputs					
Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+	JQ_2	KQ_2	JQ_1	KQ_1	JQ_0	KQ_0
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	1	0	X	1	X	X	0
0	1	0	1	1	0	1	X	X	0	0	X
0	1	1	0	1	0	0	X	X	0	X	1
1	0	0	0	0	0	X	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	1	0	1	X	0	X	1	X	0

Designing Synchronous Counters

- 3-bit Gray code counter: flip-flop inputs.

		$Q_1 Q_0$			
		00	01	11	10
Q_2	0				1
	1	X	X	X	X

$JQ_2 = Q_1 \cdot Q_0'$

		$Q_1 Q_0$			
		00	01	11	10
Q_2	0		1	X	X
	1			X	X

$JQ_1 = Q_2' \cdot Q_0$

		$Q_1 Q_0$			
		00	01	11	10
Q_2	0	1	X	X	
	1		X	X	1

$JQ_0 = Q_2 \cdot Q_1 + Q_2' \cdot Q_1'$
 $= (Q_2 \oplus Q_1)'$

		$Q_1 Q_0$			
		00	01	11	10
Q_2	0	X	X	X	X
	1	1			

$KQ_2 = Q_1' \cdot Q_0'$

		$Q_1 Q_0$			
		00	01	11	10
Q_2	0	X	X		
	1	X	X	1	

$KQ_1 = Q_2 \cdot Q_0$

		$Q_1 Q_0$			
		00	01	11	10
Q_2	0	X		1	X
	1	X	1		X

$KQ_0 = Q_2 \cdot Q_1' + Q_2' \cdot Q_1$
 $= Q_2 \oplus Q_1$


Designing Synchronous Counters

- 3-bit Gray code counter: logic diagram.

$$JQ_2 = Q_1 \cdot Q_0'$$
$$KQ_2 = Q_1' \cdot Q_0'$$

$$JQ_1 = Q_2' \cdot Q_0$$
$$KQ_1 = Q_2 \cdot Q_0$$
 
$$JQ_0 = (Q_2 \oplus Q_1)'$$
$$KQ_0 = Q_2 \oplus Q_1$$




Decoding A Counter

- **Decoding a counter** involves determining which state in the sequence the counter is in.
- Differentiate between *active-HIGH* and *active-LOW* decoding.
- Active-HIGH decoding: output HIGH if the counter is in the state concerned.
- Active-LOW decoding: output LOW if the counter is in the state concerned.


Decoding A Counter

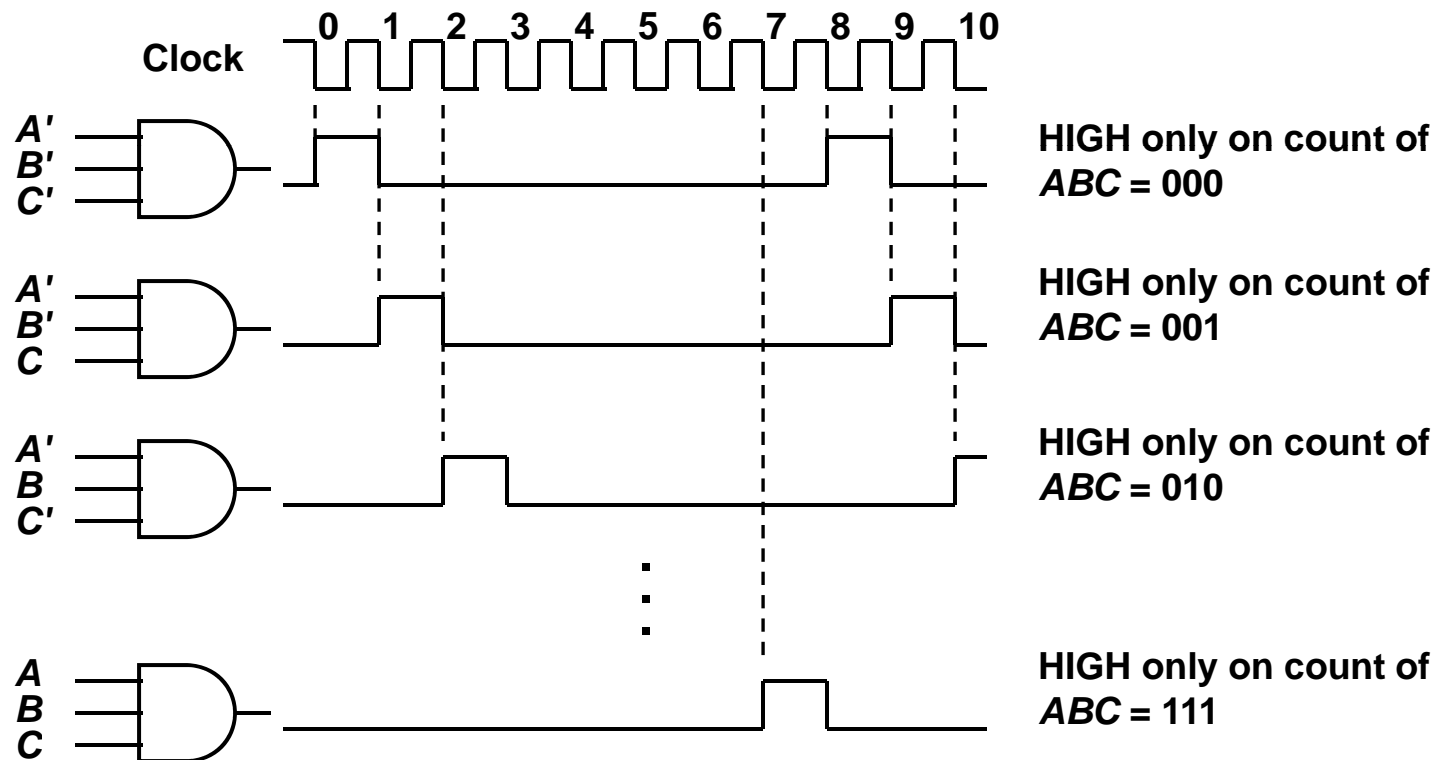- Example: MOD-8 ripple counter (active-HIGH decoding).




Decoding A Counter

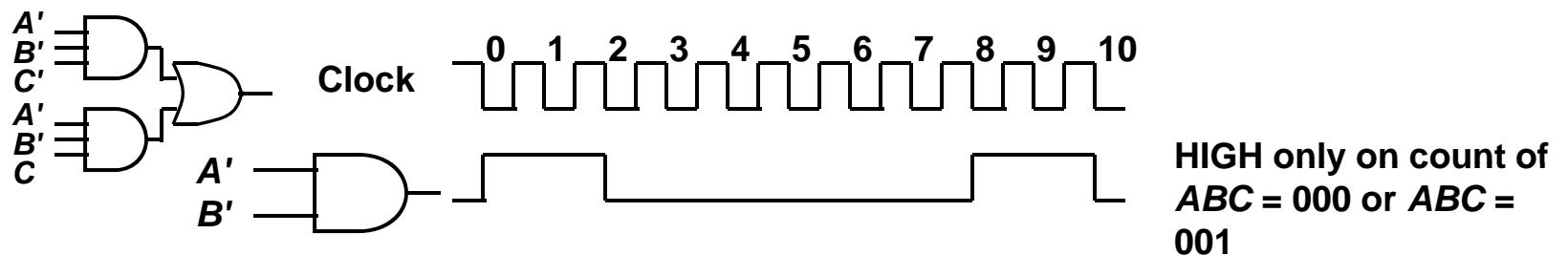- Example: To detect that a MOD-8 counter is in state 0 (000) or state 1 (001).



 - **Example: To detect that a MOD-8 counter is in the odd states (states 1, 3, 5 or 7), simply use C.**







Counters with Parallel Load

- Counters could be augmented with parallel load capability for the following purposes:
 - ❖ To start at a different state
 - ❖ To count a different sequence
 - ❖ As more sophisticated register with increment/decrement functionality.

Counters with Parallel Load

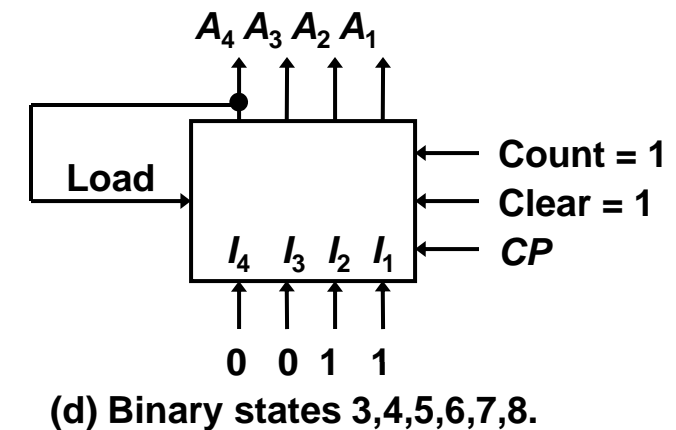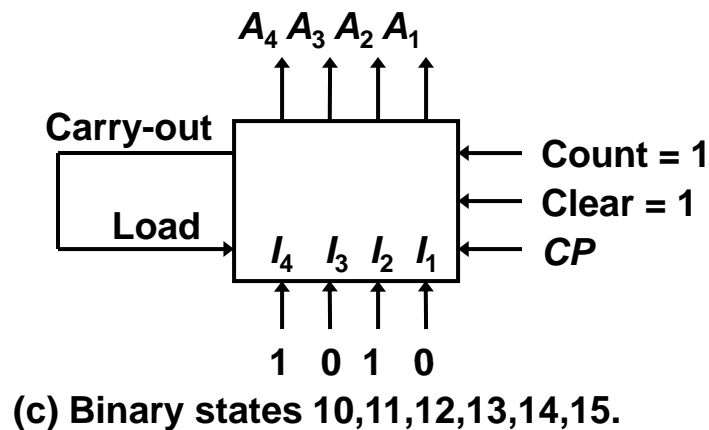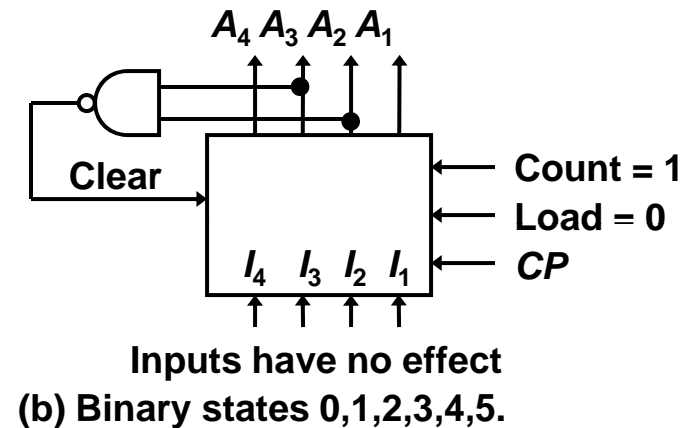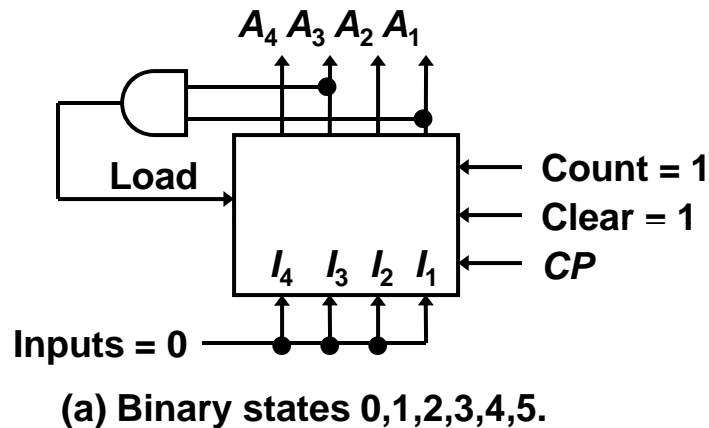
- Different ways of getting a MOD-6 counter:



Counters with Parallel Load

- 4-bit counter with parallel load.

Clear	CP	Load	Count	Function
0	X	X	X	Clear to 0
1	X	0	0	No change
1	↑	1	X	Load inputs
1	↑	0	1	Next state

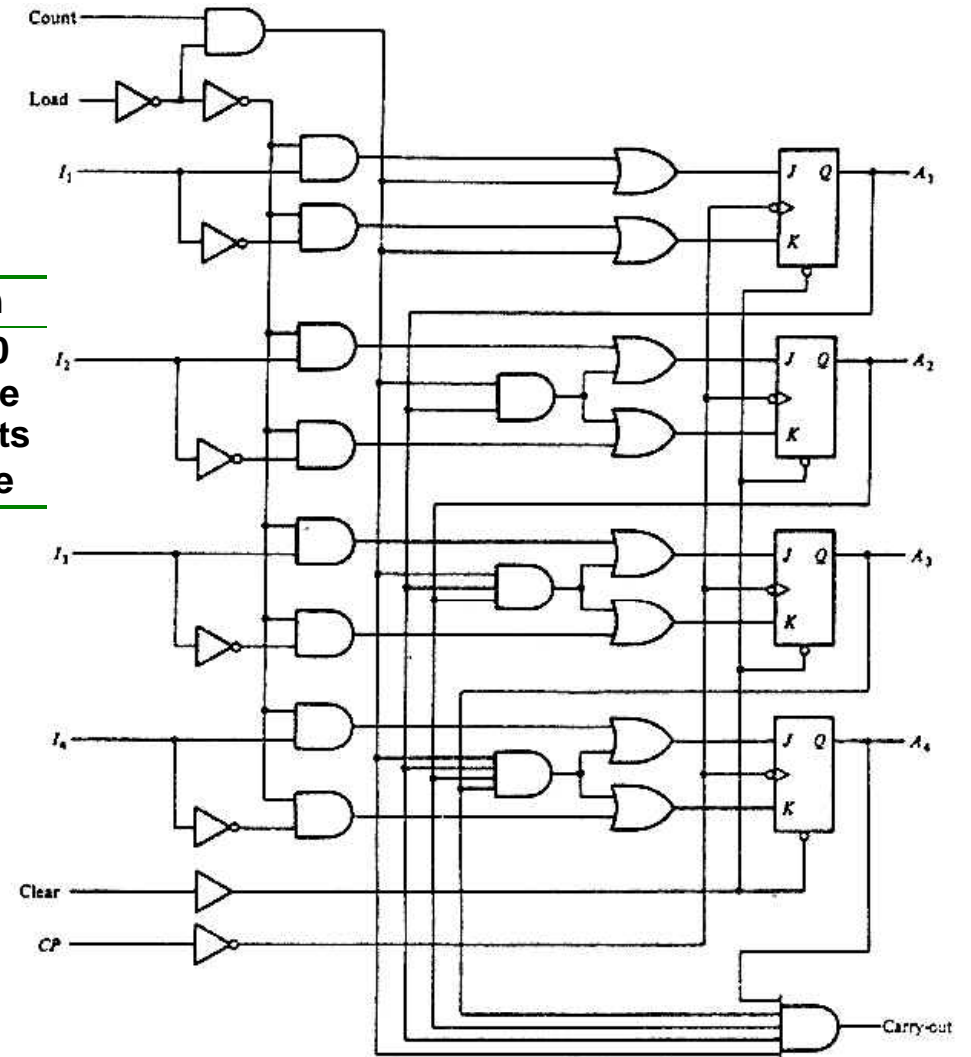


Introduction: Registers

- An *n-bit register* has a group of n flip-flops and some logic gates and is capable of storing n bits of information.
- The flip-flops store the information while the gates control when and how new information is transferred into the register.
- Some functions of register:
 - ❖ retrieve data from register
 - ❖ store/load new data into register (serial or parallel)
 - ❖ shift the data within register (left or right)

Simple Registers

 
- No external gates.
- Example: A 4-bit register. A new 4-bit data is loaded every clock cycle.



Registers With Parallel Load

- Instead of loading the register at every clock pulse, we may want to control when to load.
- *Loading* a register: transfer new information into the register. Requires a *load* control input.
- *Parallel loading*: all bits are loaded simultaneously.


Registers With Parallel Load

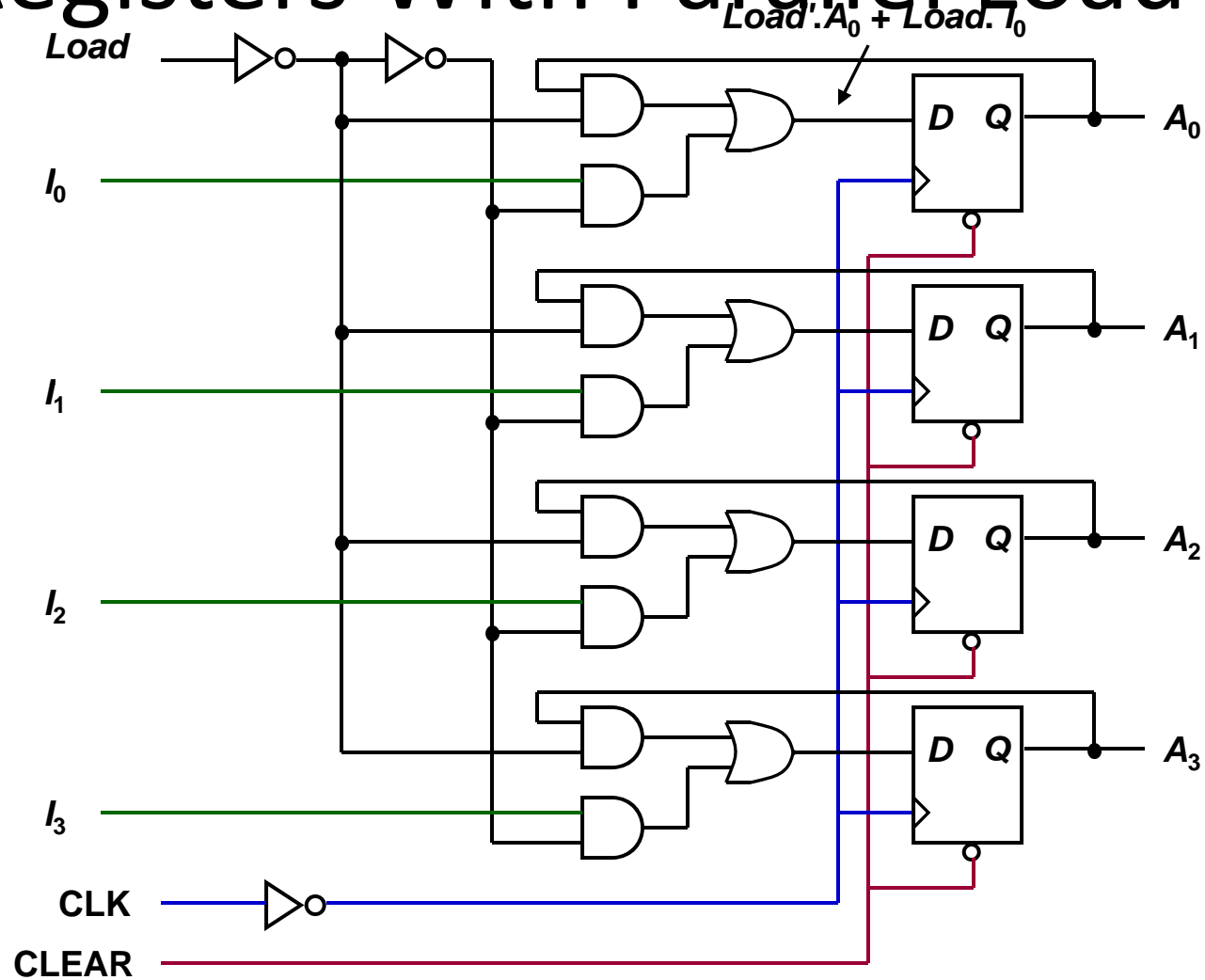

Registers With Parallel Load

Using Registers to implement Sequential Circuits

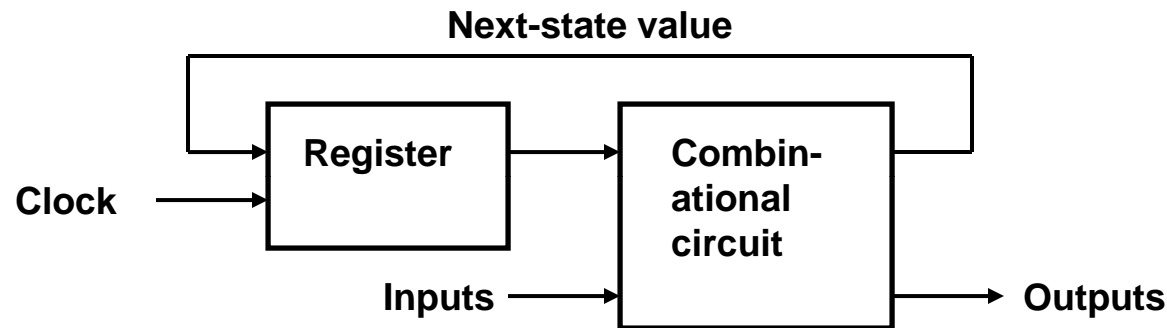- A sequential circuit may consist of a *register* (memory) and a *combinational circuit*.



- **The external inputs and present states of the register determine the next states of the register and the external outputs, through the combinational circuit.**
- **The combinational circuit may be implemented by any of the methods covered in *MSI components and Programmable Logic Devices*.**

Using Registers to implement Sequential Circuits


■ Example 1:

$$A_1^+ = \sum m(4,6) = A_1 \cdot x'$$

$$A_2^+ = \sum m(1,2,5,6) = A_2 \cdot x' + A_2' \cdot x = A_2 \oplus x$$

$$y = \sum m(3,7) = A_2 \cdot x$$

Present state		Input x	Next State		Output y
A_1	A_2		A_1^+	A_2^+	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1

 


Using Registers to implement Sequential Circuits

- Example 2: Repeat example 1, but use a ROM.

Address			Outputs		
1	2	3	1	2	3
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1

ROM truth
table

 


Shift Registers


- Another function of a register, besides storage, is to provide for *data movements*.
- Each *stage* (flip-flop) in a shift register represents one bit of storage, and the shifting capability of a register permits the movement of data from stage to stage within the register, or into or out of the register upon application of clock pulses.

Shift Registers

 
- Basic data movement in shift registers (four bits are used for illustration).




(a) Serial in/shift right/serial out

 


(b) Serial in/shift left/serial out

 


(c) Parallel in/serial out

 


(d) Serial in/parallel out

 

(e) Parallel in / parallel out

 


(f) Rotate right

 

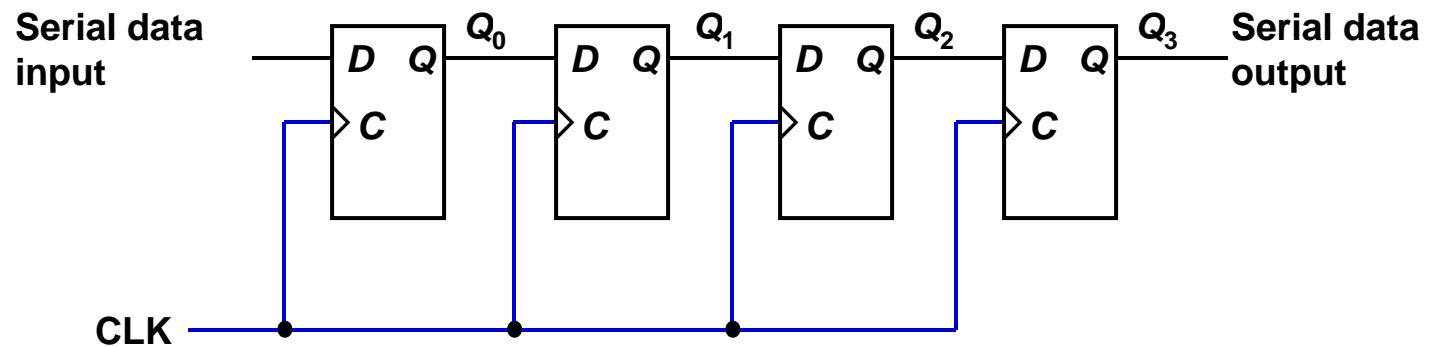(g) Rotate left


Serial In/Serial Out Shift Registers

- Accepts data serially – one bit at a time – and also produces output serially.



Serial In/Serial Out Shift Registers

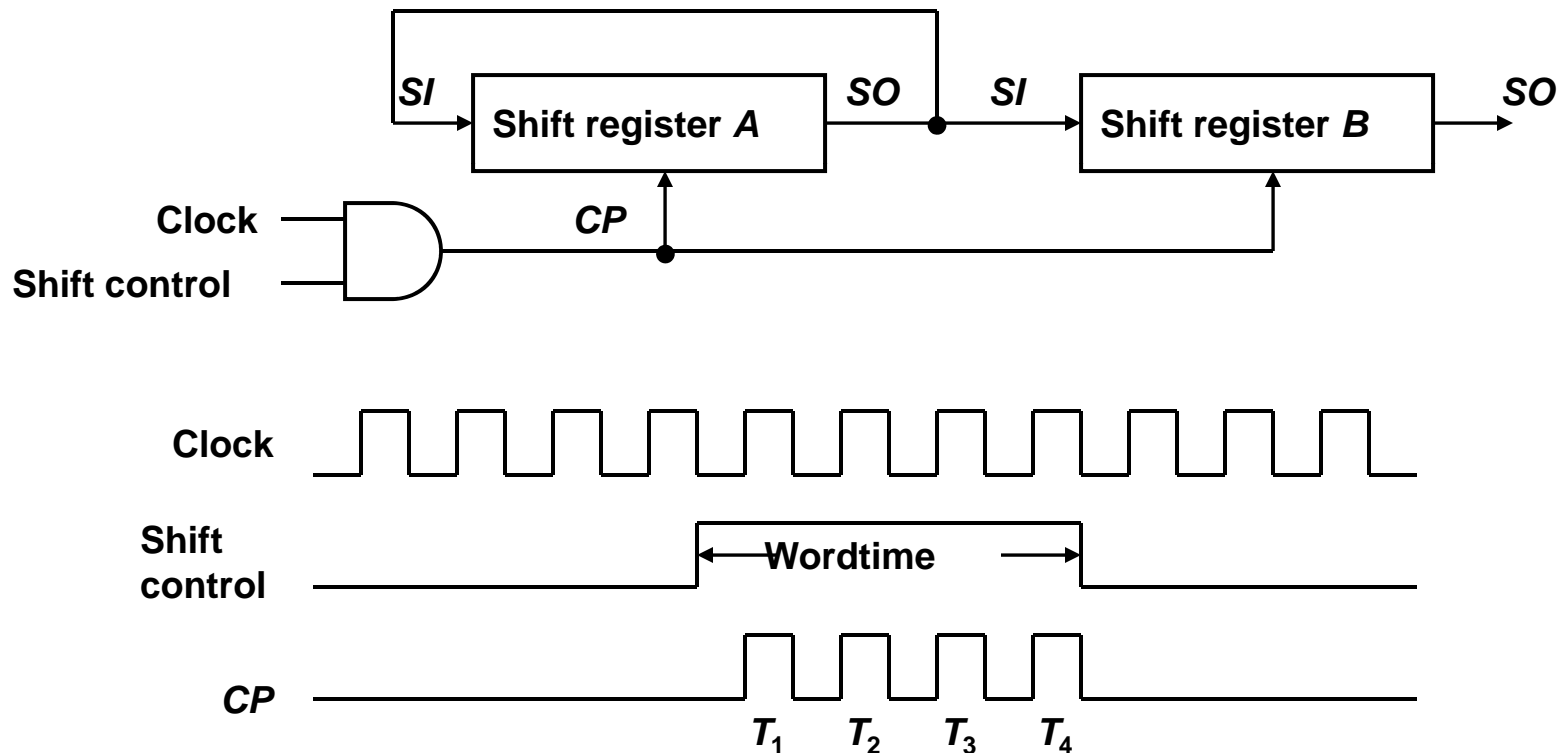- Application: Serial transfer of data from one register to another.





Serial In/Serial Out Shift Registers

- Serial-transfer example.

Timing Pulse	Shift register A	Shift register B	Serial output of B
Initial value	1 0 1 1	0 0 1 0	0
After T_1	1 1 0 1	1 0 0 1	1
After T_2	1 1 1 0	1 1 0 0	0
After T_3	0 1 1 1	0 1 1 0	0
After T_4	1 0 1 1	1 0 1 1	1


Serial In/Parallel Out Shift Registers

  - Accepts data serially.
- Outputs of all stages are available simultaneously.




Parallel In/Serial Out Shift Registers

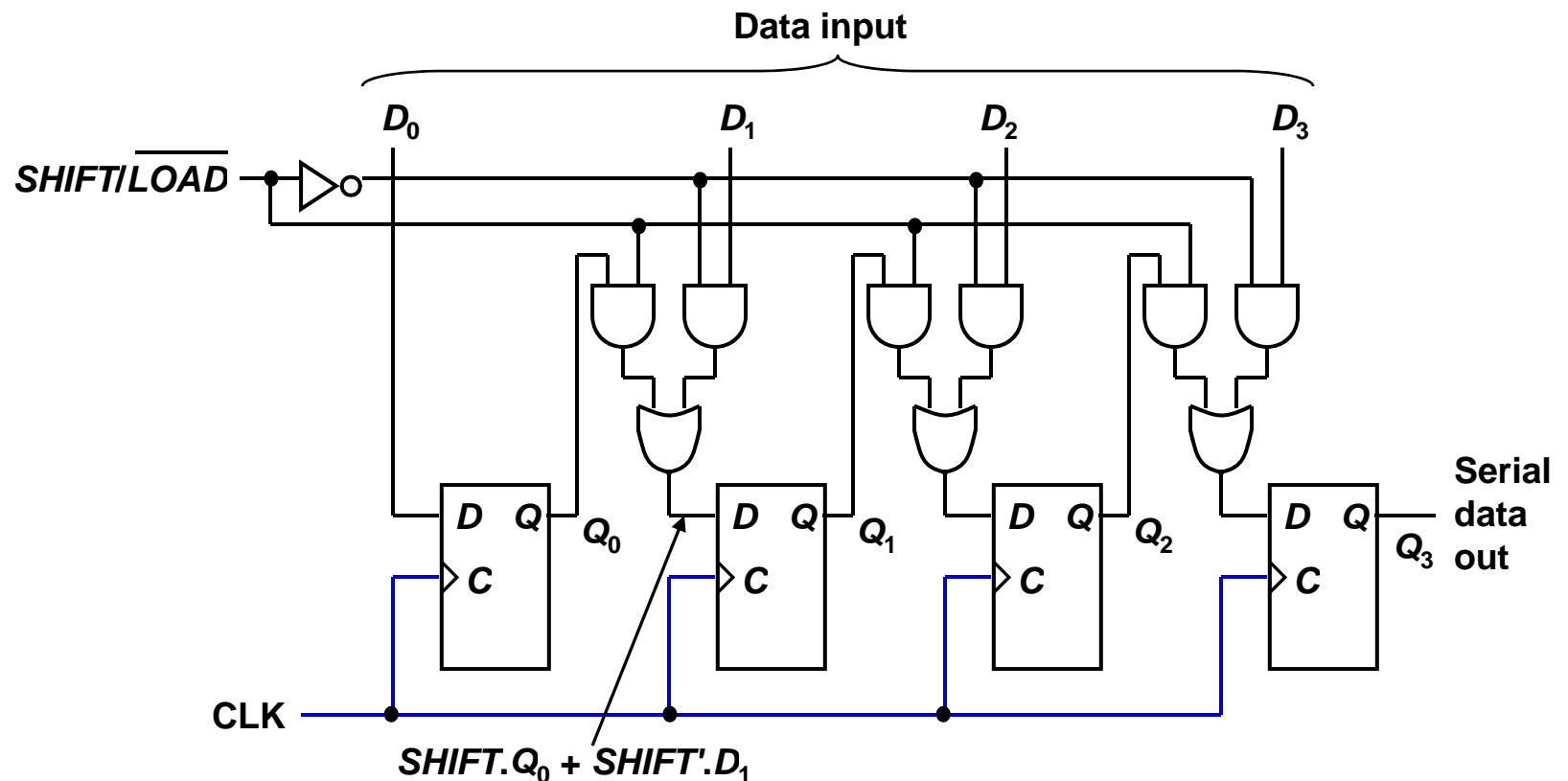- Bits are entered simultaneously, but output is serial.



Parallel In/Serial Out Shift Registers

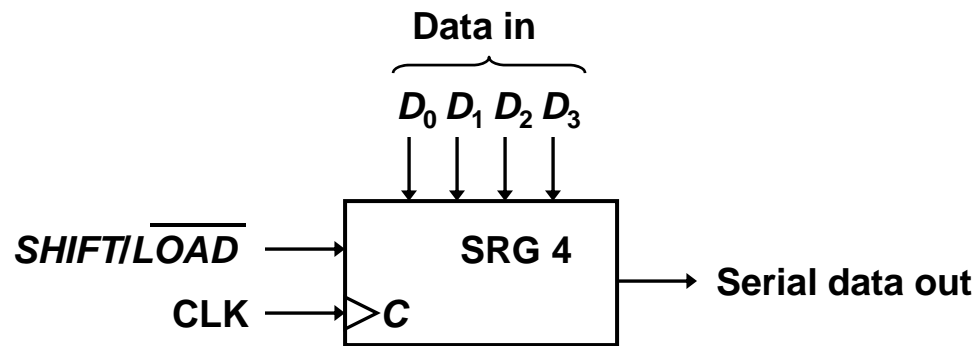
- Bits are entered simultaneously, but output is serial.



Logic symbol


Parallel In/Parallel Out Shift Registers

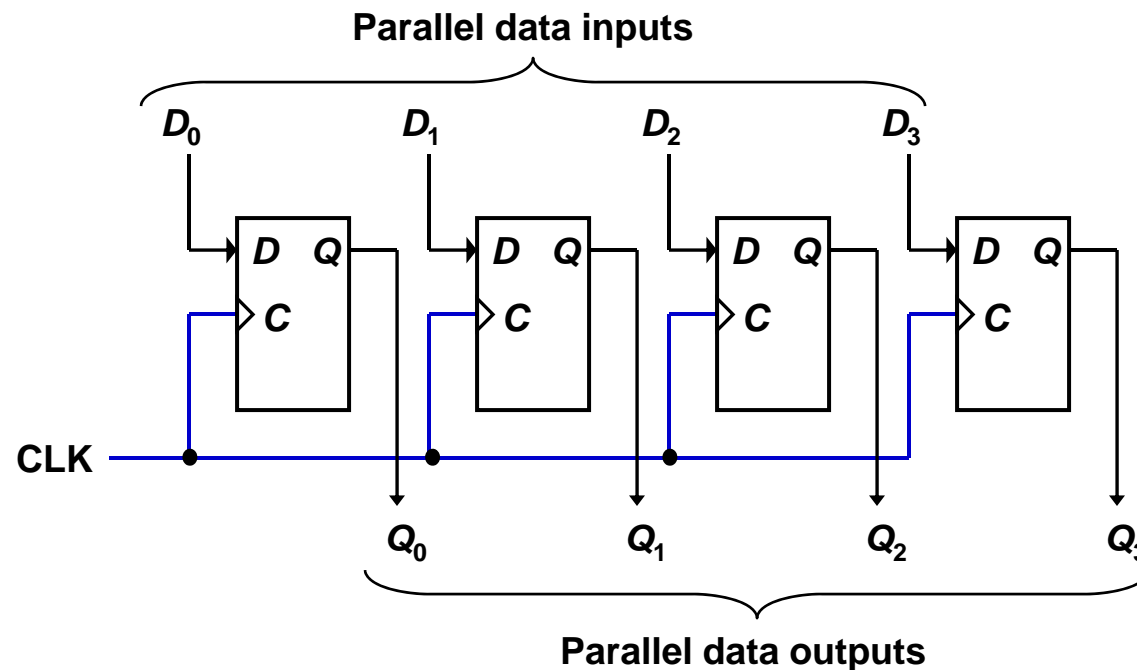- Simultaneous input and output of all data bits.




Bidirectional Shift Registers

 - Data can be shifted either left or right, using a control line $\overline{RIGHT/LEFT}$ (or simply $RIGHT$) to indicate the direction.



Bidirectional Shift Registers

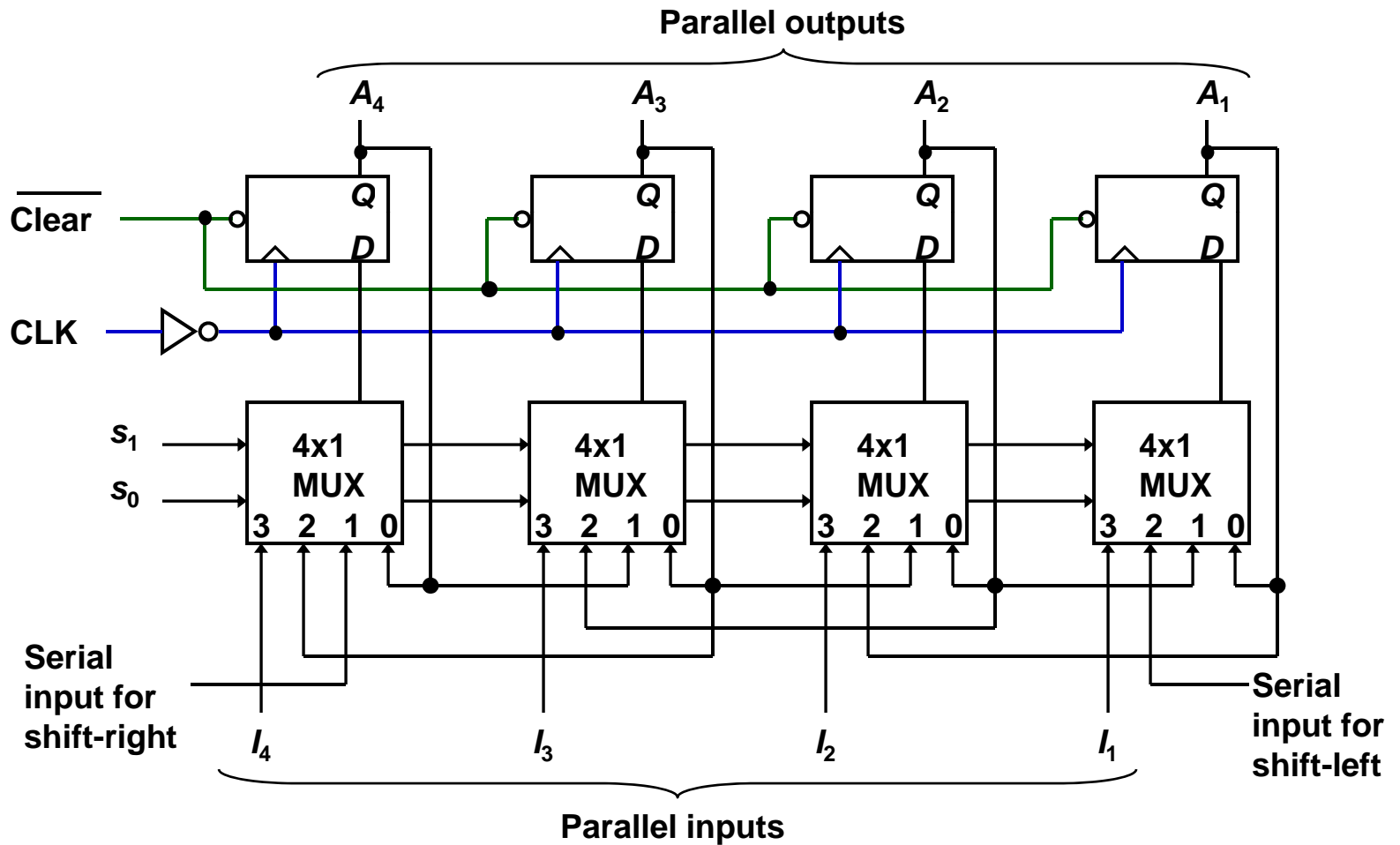- 4-bit bidirectional shift register with parallel load.




Bidirectional Shift Registers

- 4-bit bidirectional shift register with parallel load.

<i>Mode Control</i>		<i>Register Operation</i>
<i>s₁</i>	<i>s₀</i>	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

An Application – Serial Addition

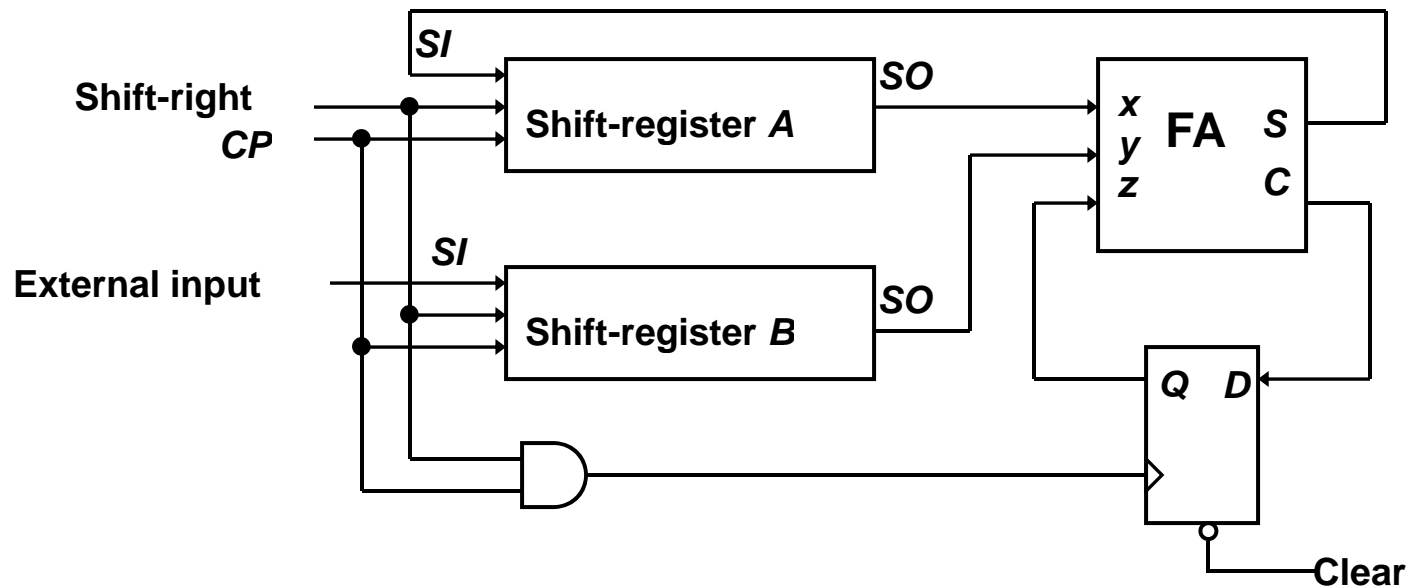- Most operations in digital computers are done in parallel. Serial operations are slower but require less equipment.
- A serial adder is shown below. $A \leftarrow A + B$.



An Application – Serial Addition

- $A = 0100$; $B = 0111$. $A + B = 1011$ is stored in A after 4 clock pulses.

Initial:	A: 0 1 0 0 B: 0 1 1 1	Q: <u>0</u>
Step 1: $0 + 1 + 0$ S = 1 , C = 0	A: 1 0 1 0 B: x 0 1 1	Q: <u>0</u>
Step 2: $0 + 1 + 0$ S = 1 , C = 0	A: 1 1 0 1 B: x x 0 1	Q: <u>0</u>
Step 3: $1 + 1 + 0$ S = 0 , C = 1	A: 0 1 1 0 B: x x x 0	Q: <u>1</u>
Step 4: $0 + 0 + 1$ S = 1 , C = 0	A: 1 0 1 1 B: x x x x	Q: <u>0</u>

Shift Register Counters


- **Shift register counter**: a shift register with the serial output connected back to the serial input.
- They are classified as counters because they give a specified sequence of states.
- Two common types: the *Johnson counter* and the *Ring counter*.

Ring Counters


- One flip-flop (stage) for each state in the sequence.
- The output of the last stage is connected to the D input of the first stage.
- An n -bit ring counter cycles through n states.
- No decoding gates are required, as there is an output that corresponds to every state the counter is in.

Ring Counters

- Example: A 6-bit (MOD-6) ring counter.

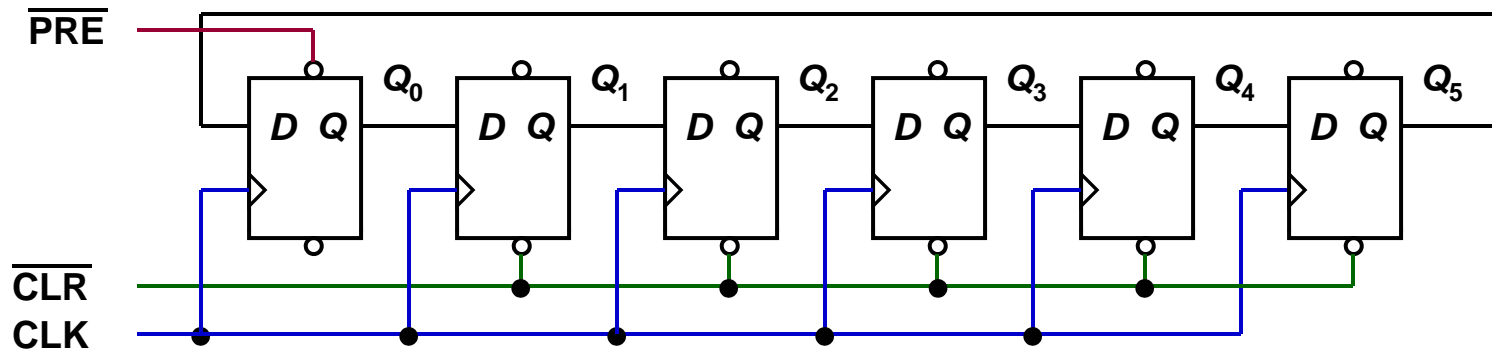

Clock	Q ₀	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅
0	1	0	0	0	0	0
1	0	1	0	0	0	0
2	0	0	1	0	0	0
3	0	0	0	1	0	0
4	0	0	0	0	1	0
5	0	0	0	0	0	1

 


Johnson Counters


- The complement of the output of the last stage is connected back to the D input of the first stage.
- Also called the *twisted-ring counter*.
- Require fewer flip-flops than ring counters but more flip-flops than binary counters.
- An n -bit Johnson counter cycles through $2n$ states.
- Require more decoding circuitry than ring counter but less than binary counters.

Johnson Counters

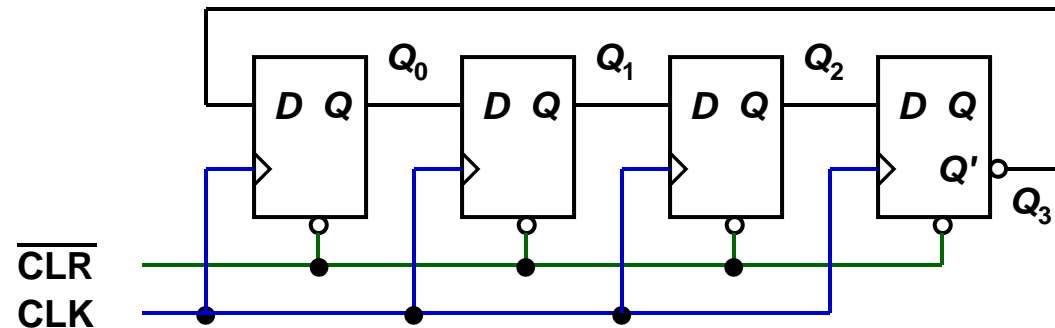- Example: A 4-bit (MOD-8) Johnson counter.





Clock	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

 

Johnson Counters

- Decoding logic for a 4-bit Johnson counter.

Clock	A	B	C	D	Decoding
0	0	0	0	0	$A'.D'$
1	1	0	0	0	$A.B'$
2	1	1	0	0	$B.C'$
3	1	1	1	0	$C.D'$
4	1	1	1	1	$A.D$
5	0	1	1	1	$A'.B$
6	0	0	1	1	$B'.C$
7	0	0	0	1	$C'.D$

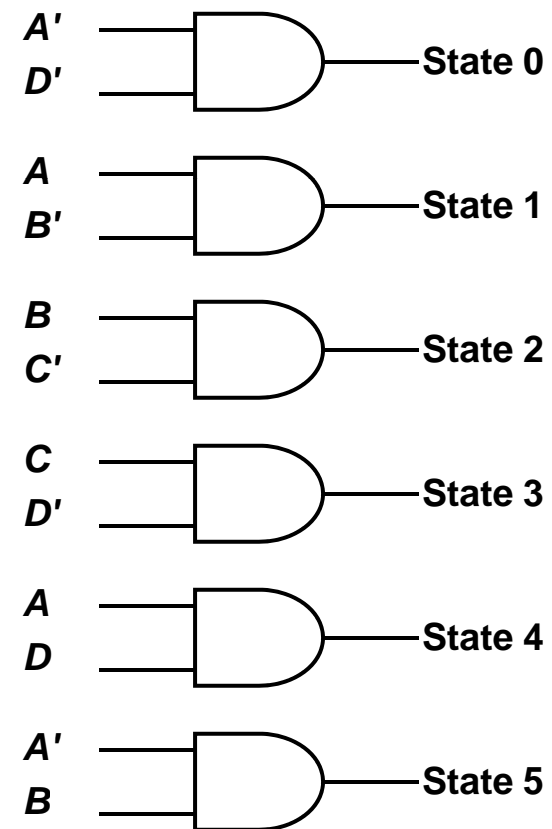 


Random Access Memory (RAM)

- A memory unit stores binary information in groups of bits called *words*.
- The data consists of n lines (for n -bit words). **Data input lines** provide the information to be stored (*written*) into the memory, while **data output lines** carry the information out (*read*) from the memory.
- The **address** consists of k lines which specify which word (among the 2^k words available) to be selected for reading or writing.
- The control lines *Read* and *Write* (usually combined into a single control line *Read/Write*) specifies the direction of transfer of the data.

Random Access Memory (RAM)

- Block diagram of a memory unit:

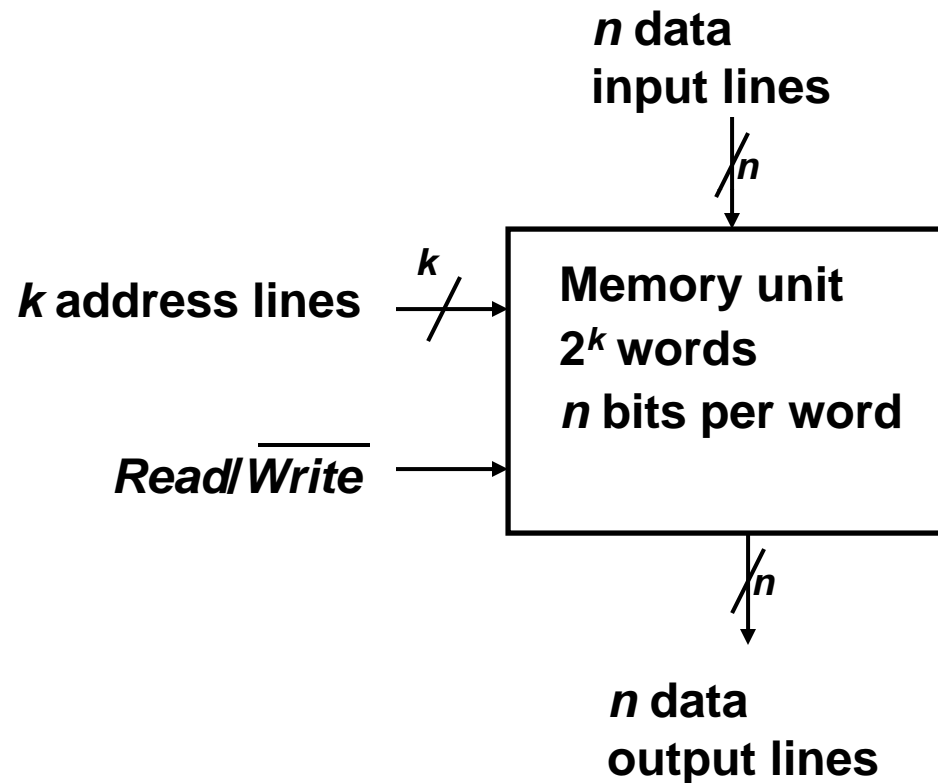

Random Access Memory (RAM)

- Content of a 1024 x 16-bit memory:

Memory address		Memory content
binary	decimal	
000000000	0	1011010111011101
000000001	1	1010000110000110
000000010	2	0010011101110001
:	:	:
:	:	:
111111101	1021	1110010101010010
111111110	1022	0011111010101110
111111111	1023	1011000110010101

Random Access Memory (RAM)

- The **Write** operation:
 - ❖ Transfers the address of the desired word to the address lines
 - ❖ Transfers the data bits (the word) to be stored in memory to the data input lines
 - ❖ Activates the *Write* control line (set $\overline{Read/Write}$ to 0)
- The **Read** operation:
 - ❖ Transfers the address of the desired word to the address lines
 - ❖ Activates the *Read* control line (set $\overline{Read/Write}$ to 1)

Random Access Memory (RAM)


- The Read/Write operation:

Memory Enable	<i>Read/Write</i>	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word


- **Two types of RAM: Static and dynamic.**
 - ❖ Static RAMs use flip-flops as the memory cells.
 - ❖ Dynamic RAMs use capacitor charges to represent data. Though simpler in circuitry, they have to be constantly refreshed.

Random Access Memory (RAM)

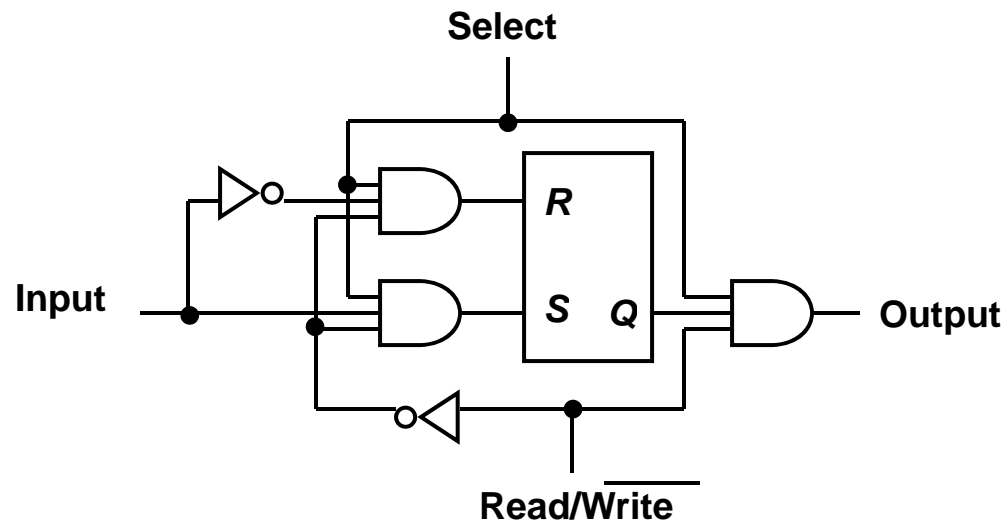- A single memory cell of the static RAM has the following logic and block diagrams.




**Logic
diagram**

 

**Block
diagram**


Random Access Memory (RAM)

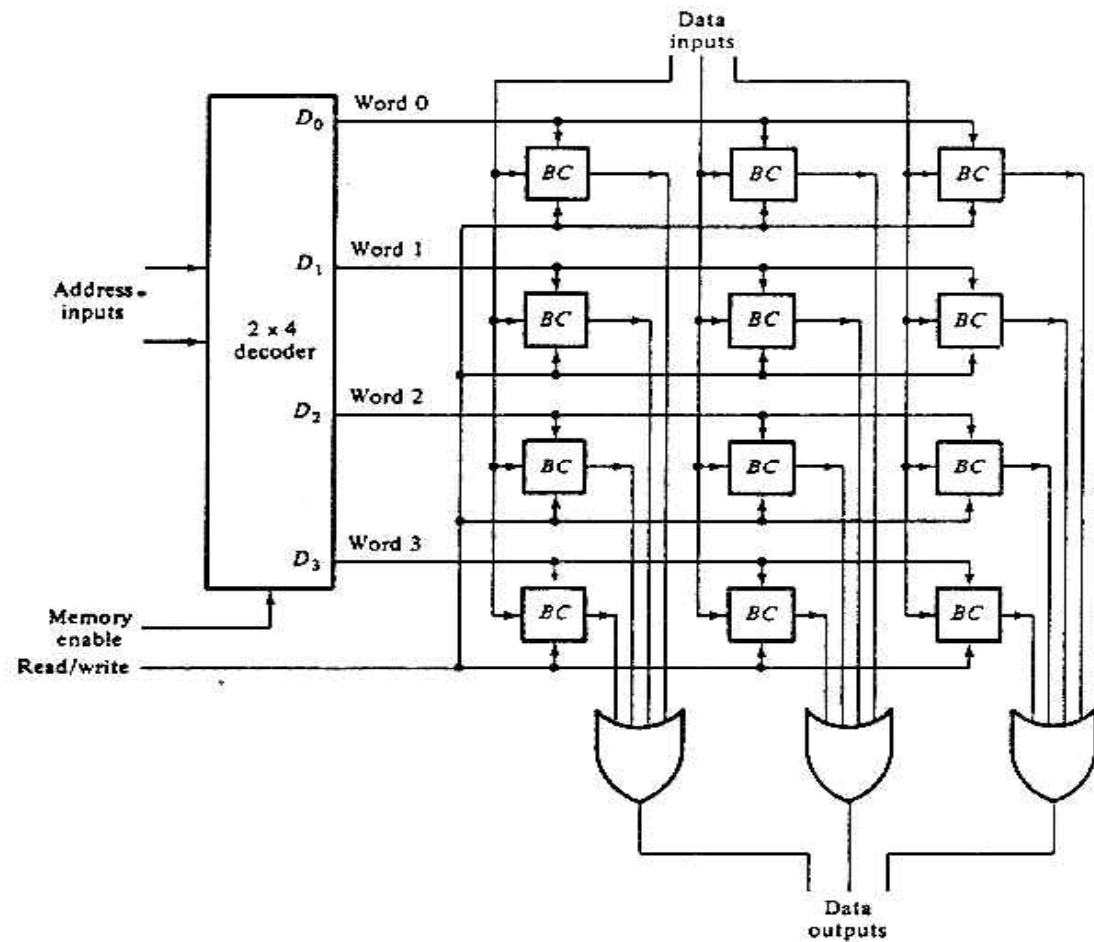- Logic construction of a 4 x 3 RAM (with decoder and OR gates).




Random Access Memory (RAM)

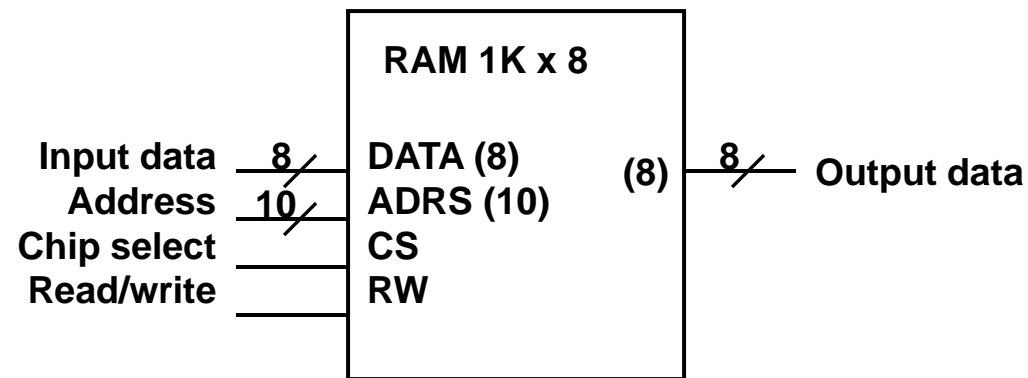- An array of RAM chips: memory chips are combined to form larger memory.
- A 1K x 8-bit RAM chip:



Block diagram of a 1K x 8 RAM chip

Random Access Memory (RAM)

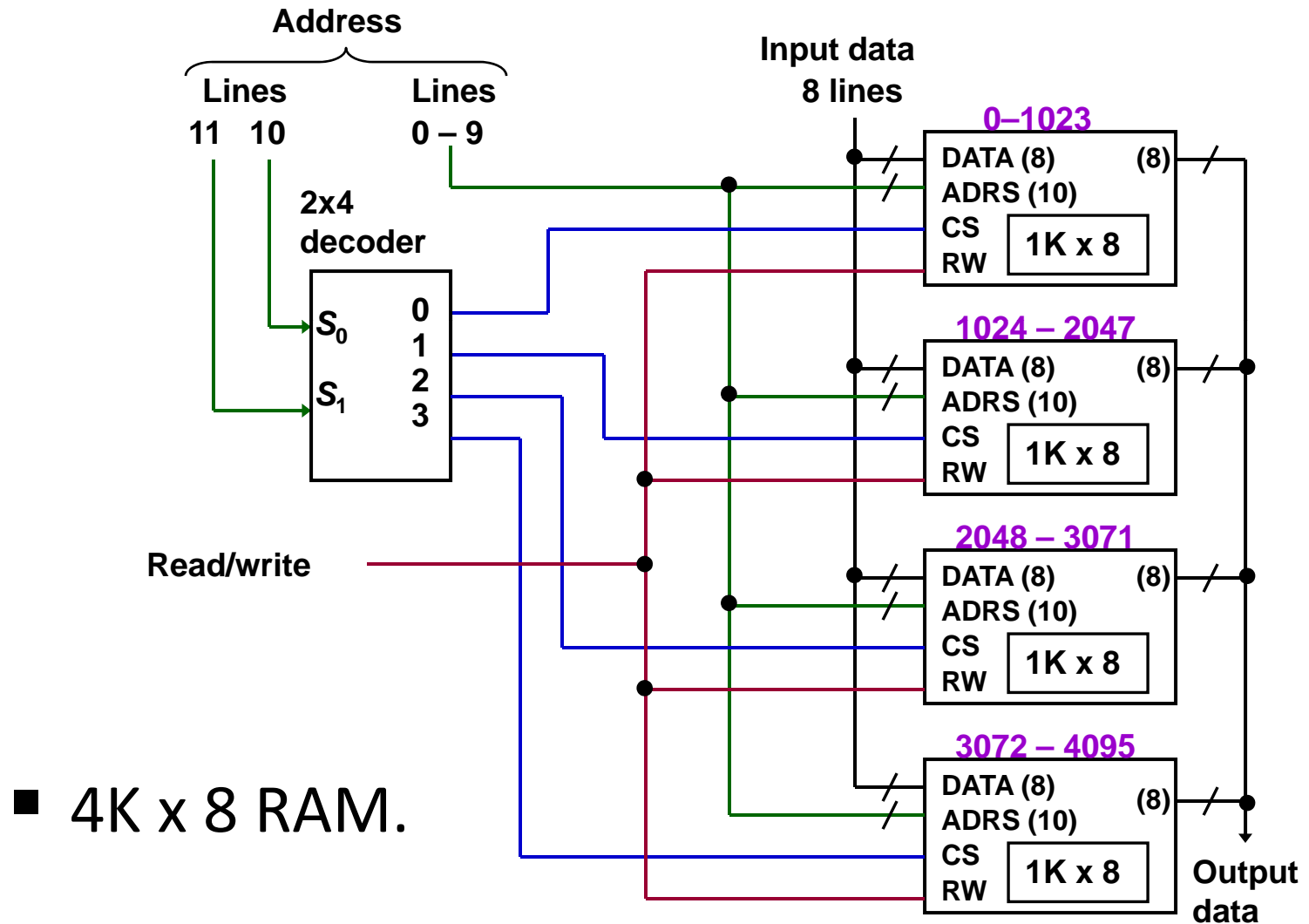

End of segment