


ELECTRONICS SYSTEM DESIGN

SECTION-4

MULTI INPUT SYSTEM CONTROLLER DESIGN AND PLDs

Programmable Logic Organization

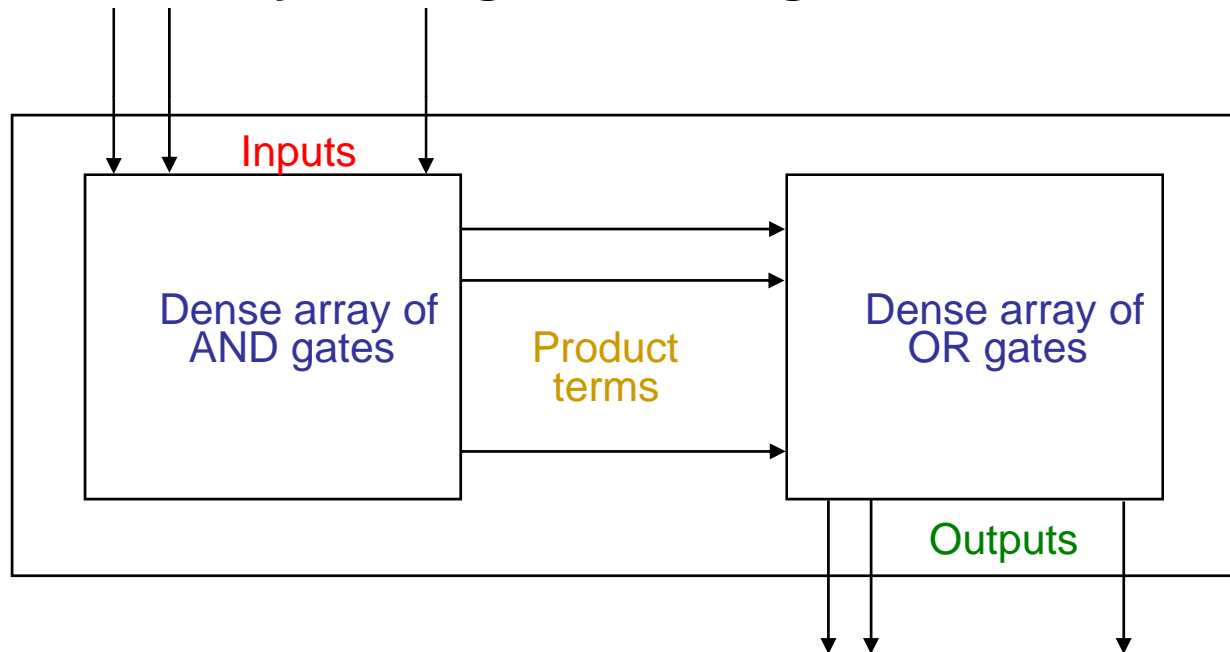- Pre-fabricated building block of many AND/OR gates (or NOR, NAND)
- "Personalized" by making or breaking connections among the gates



Programmable Array Block Diagram for Sum of Products Form

Basic Programmable Logic Organizations

- Depending on which of the AND/OR logic arrays is programmable, we have three basic organizations

ORGANIZATION	AND ARRAY	OR ARRAY
PAL	PROG.	FIXED
PROM	FIXED	PROG.
PLA	PROG.	PROG.

PLA Logic Implementation

Key to Success: Shared Product Terms

Equations

Example:

$$F_0 = A + \bar{B}\bar{C}$$

$$F_1 = A\bar{C} + AB$$

$$F_2 = \bar{B}\bar{C} + AB$$

$$F_3 = \bar{B}C + A$$

Personality Matrix

Product term	Inputs			Outputs			
	A	B	C	F ₀	F ₁	F ₂	F ₃
AB	1	1	-	0	①	①	0
$\bar{B}C$	-	0	1	0	0	0	1
$A\bar{C}$	1	-	0	0	1	0	0
$\bar{B}\bar{C}$	-	0	0	①	0	①	0
A	1	-	-	①	0	0	①

Reuse of terms

Input Side:


1 = asserted in term
 0 = negated in term
 - = does not participate

Output Side:

1 = term connected to output
 0 = no connection to output

PLA Logic Implementation


Example Continued - Unprogrammed device

 

All possible connections are available
before programming

PLA Logic Implementation

*Example Continued -
Programmed part*

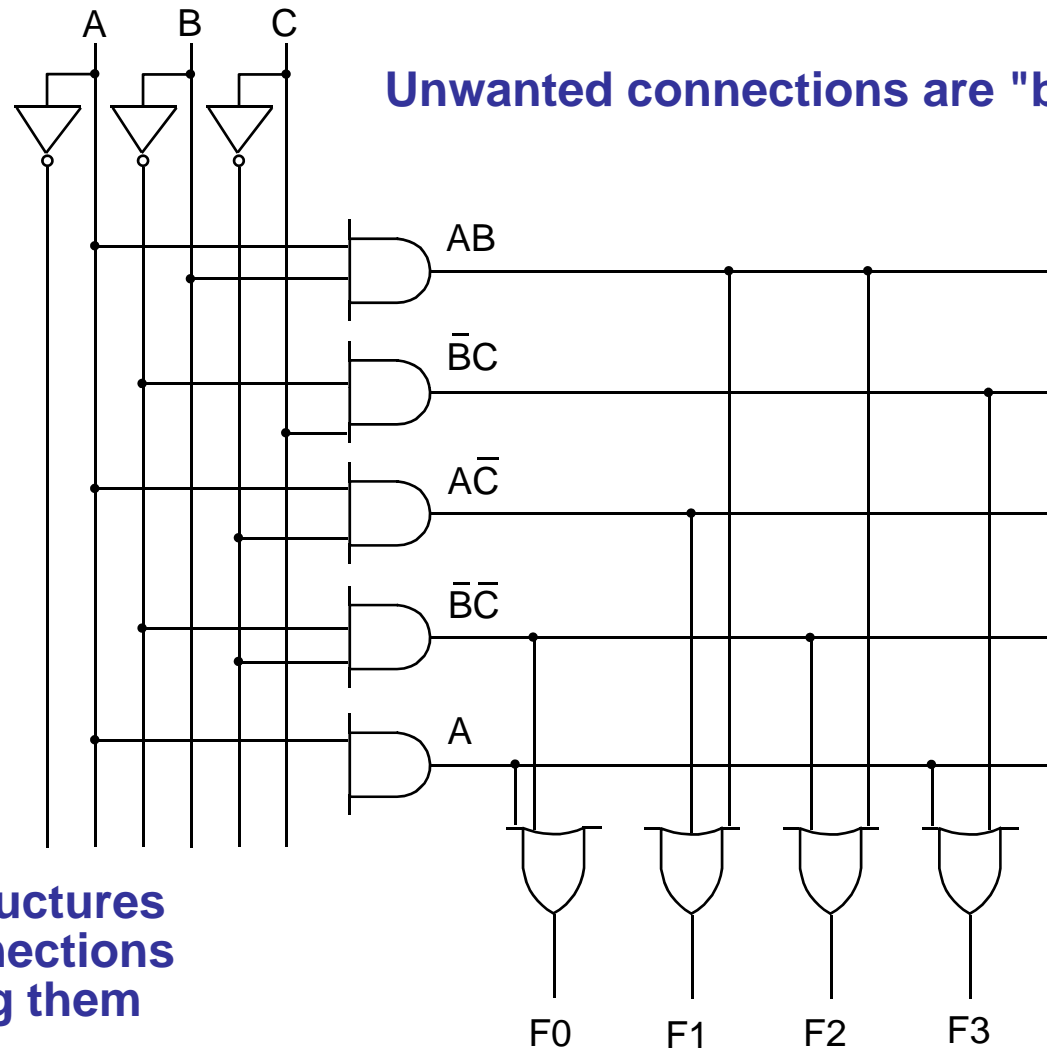

Unwanted connections are "blown"

Note: some array structures work by making connections rather than breaking them

PLA Logic Implementation

Alternative representation


Short-hand notation
so we don't have to
draw all the wires!

X at junction indicates
a connection

Notation for implementing

$$F0 = A B + \bar{A} \bar{B}$$

$$F1 = C \bar{D} + \bar{C} D$$

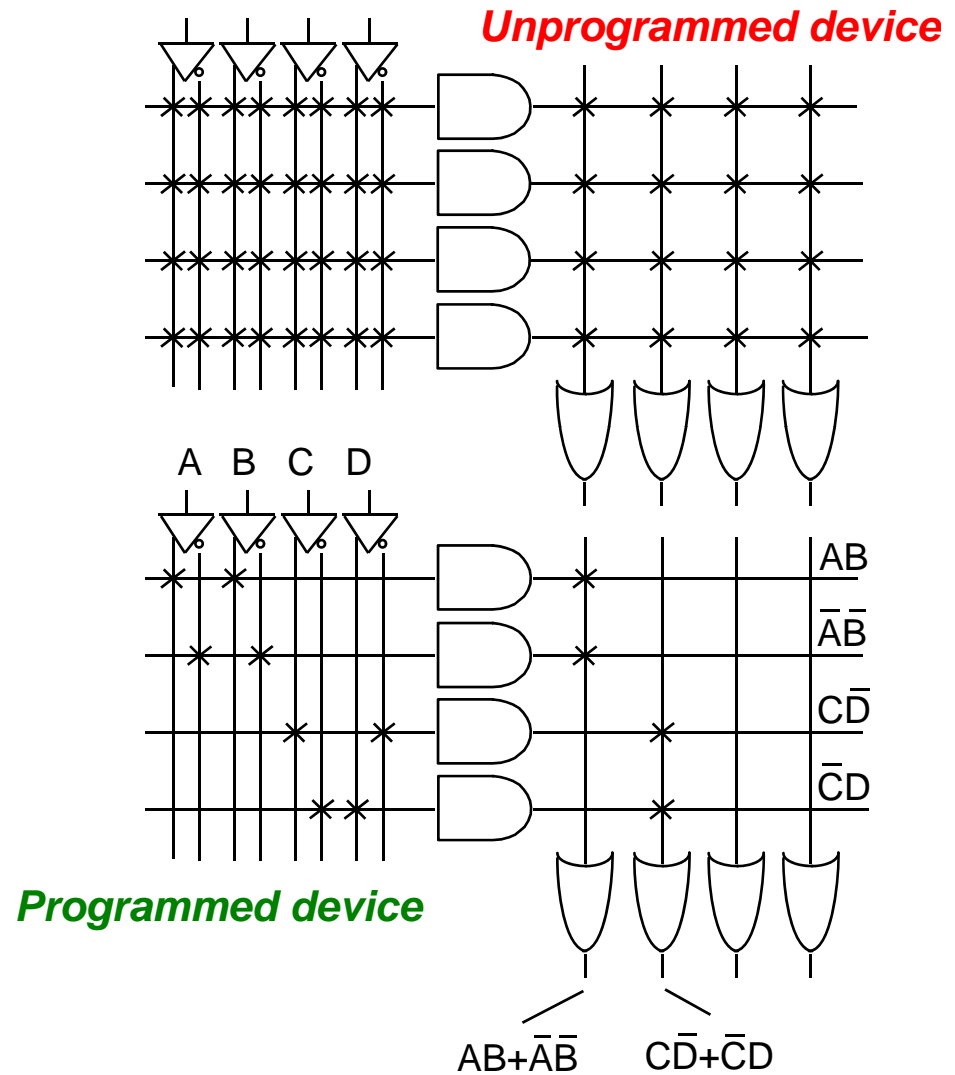

PLA Logic Implementation

Design Example

Multiple functions of A, B, C

$$F1 = A B C$$


$$F2 = A + B + C$$

$$F3 = \overline{A B C}$$

$$F4 = \overline{A + B + C}$$

$$F5 = A \oplus B \oplus C$$


$$F6 = \overline{A \oplus B \oplus C}$$

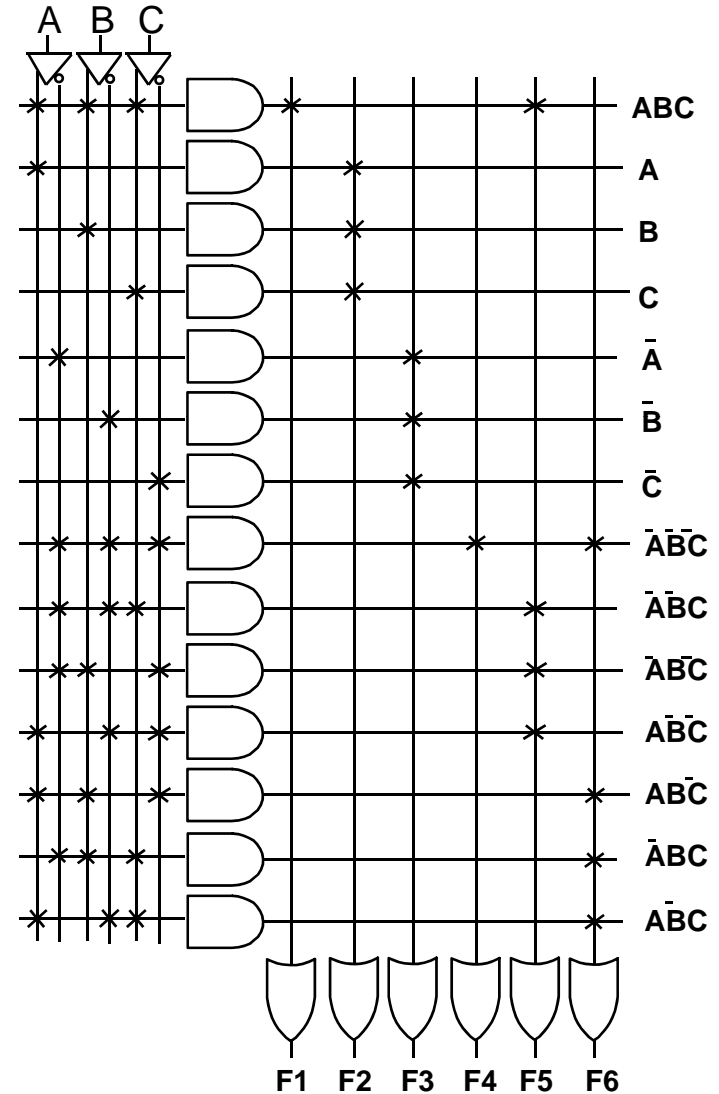

PALs and PLAs

What is difference between Programmable Array Logic (PAL) and Programmable Logic Array (PLA)?

 **PAL concept — implemented by Monolithic Memories
AND array is programmable, OR array is fixed at fabrication**



A given column of the OR array has access to only a subset of the possible product terms

PLA concept — Both AND and OR arrays are programmable

PALs and PLAs

- Of the two organizations the PLA is the most flexible
 - One PLA can implement a huge range of logic functions
 - BUT many pins; large package, higher cost
- PALs are more restricted / you trade number of OR terms vs number of outputs
 - Many device variations needed
 - Each device is cheaper than a PLA


PAL Logic Implementation

Design Example: BCD to Gray Code Converter


K-maps

Truth Table


A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

 


K-map for W

 

K-map for X

 

K-map for Y

 

K-map for Z

Minimized Functions:

$$W = A + B D + B C$$

$$X = B \bar{C}$$

$$Y = \bar{B} + \bar{C}$$

$$Z = \bar{A} \bar{B} \bar{C} D + B C D + A D + B \bar{C} D$$

PAL Logic Implementation

Programmed PAL:

Minimized Functions:


$$W = A + \overline{B}D + BC$$

$$X = B\overline{C}$$

$$Y = \overline{B} + \overline{C}$$


$$Z = \overline{A}\overline{B}\overline{C}D + B\overline{C}D + A\overline{D} + \overline{B}\overline{C}D$$

4 product terms per each OR gate

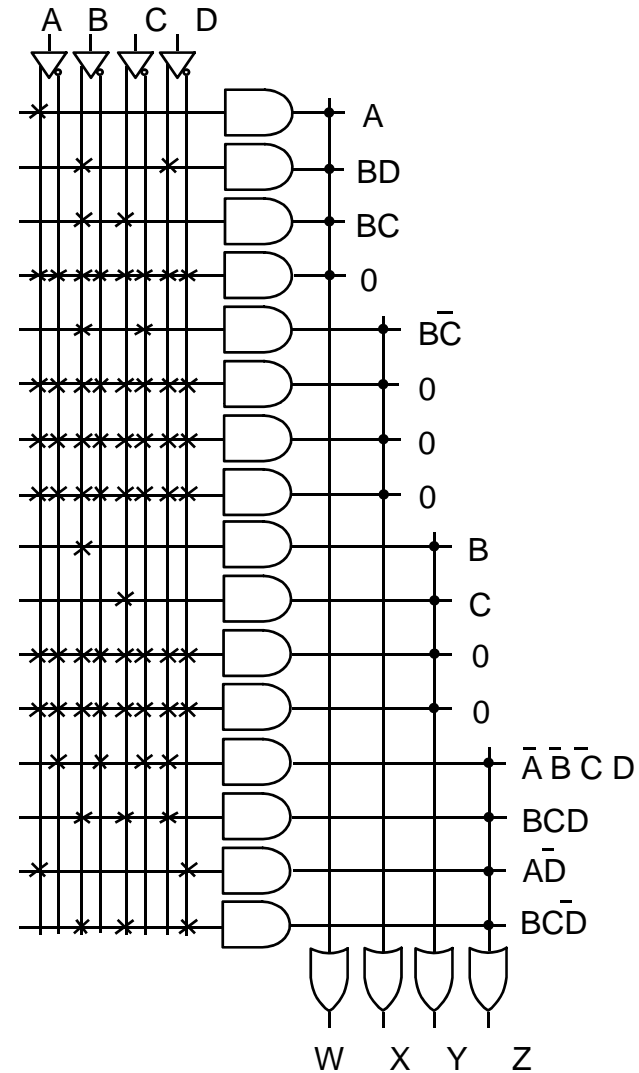

PAL Logic Implementation





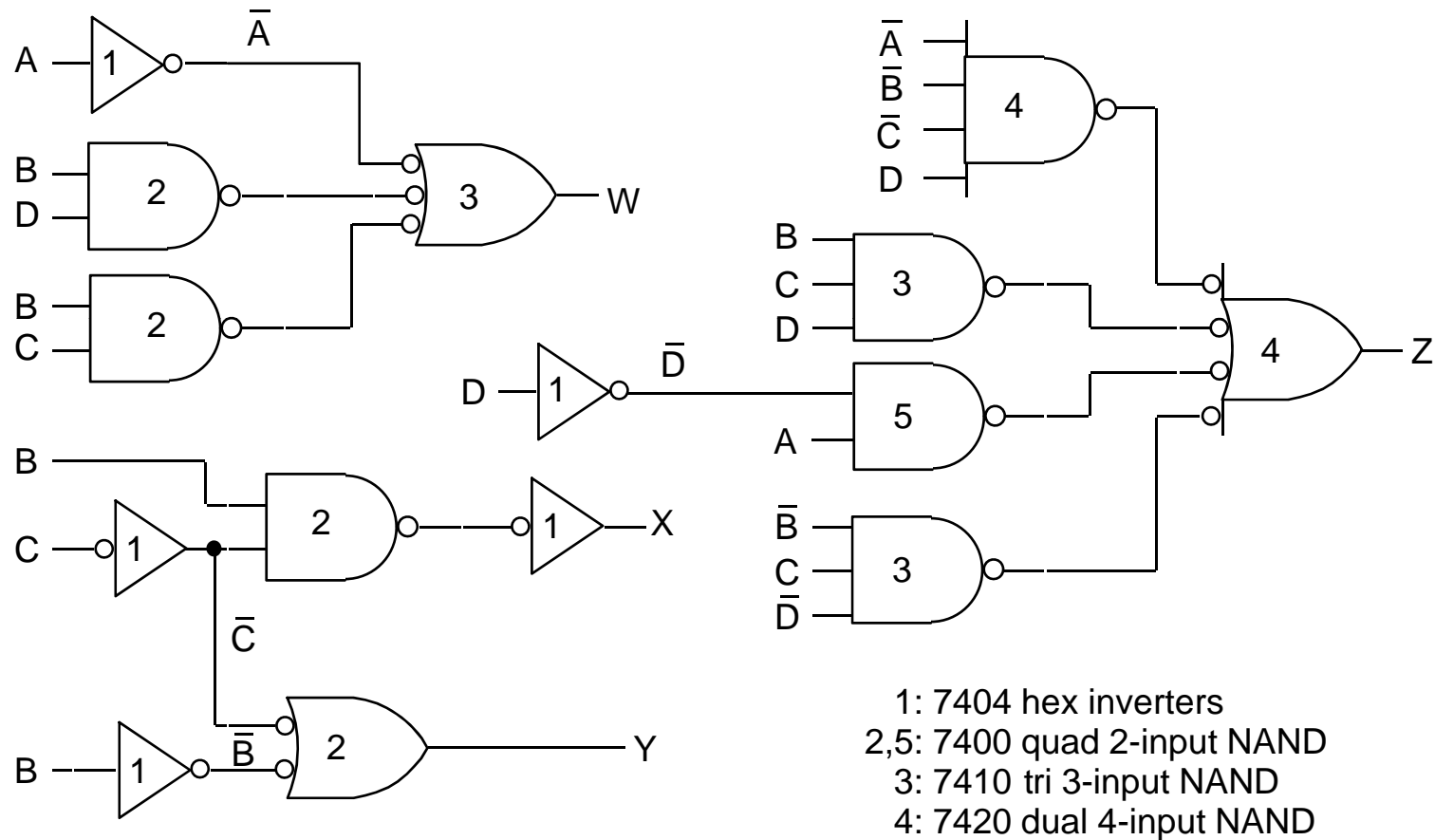
Code Converter Discrete Gate Implementation




4 SSI Packages vs. 1 PLA/PAL Package!

PLA Logic Implementation

Another Example: Magnitude Comparator

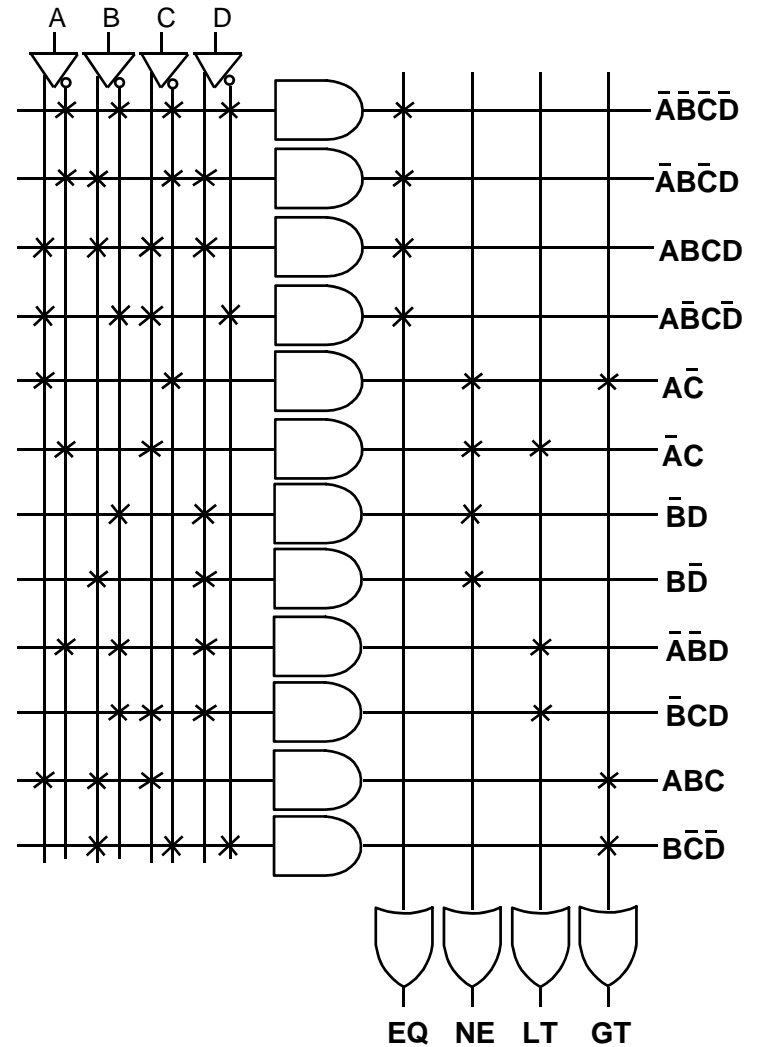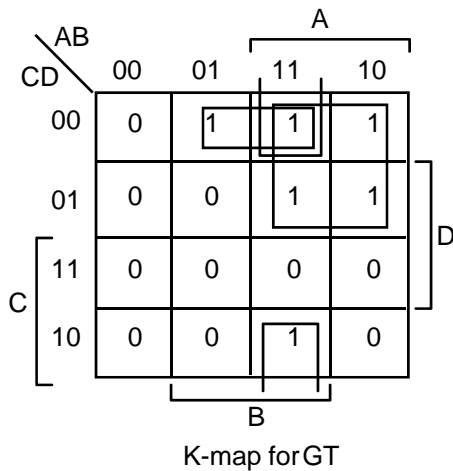 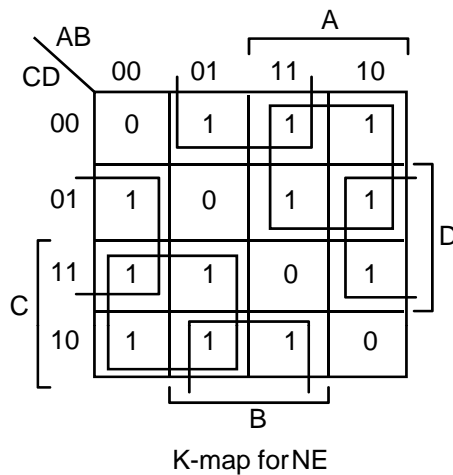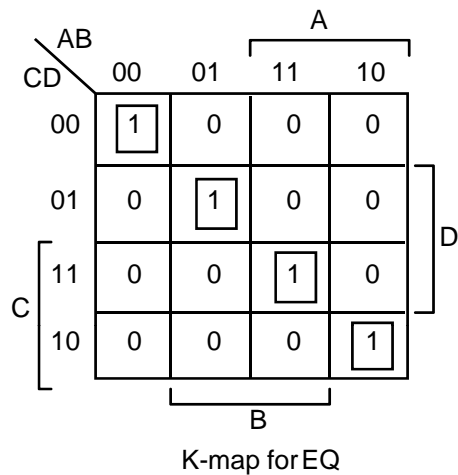

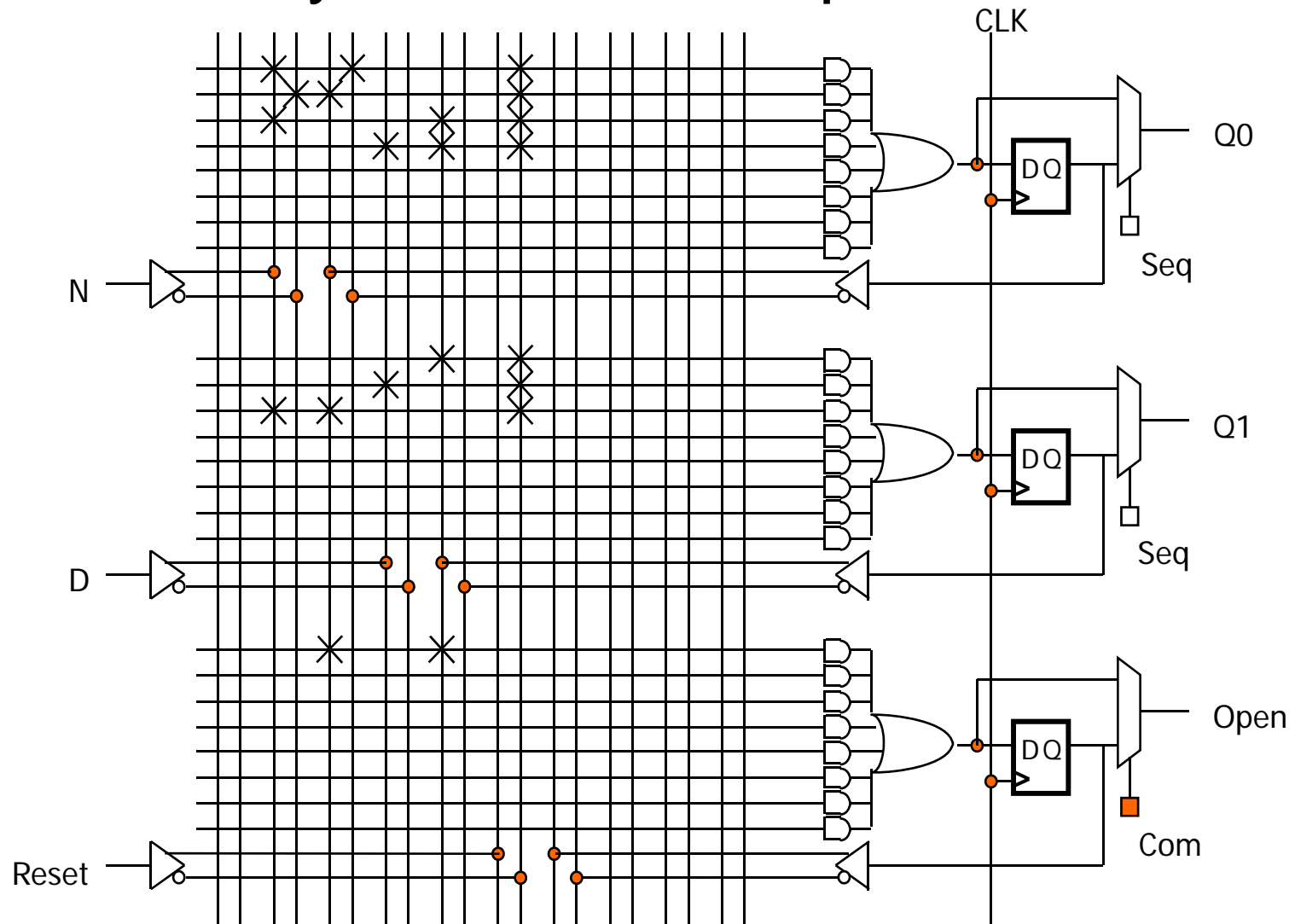
Another Variation: Synchronous vs. Asynchronous Outputs



Complex Programmable Logic Devices

- Complex PLDs typically combine PAL combinational logic with FFs
 - Organized into logic blocks
 - Fixed OR array size
 - Combinational or registered output
 - Some pins are inputs only
- Usually enough logic for simple counters, state machines, decoders, etc.
- e.g. GAL22V10, GAL16V8, etc.


GAL CPLD

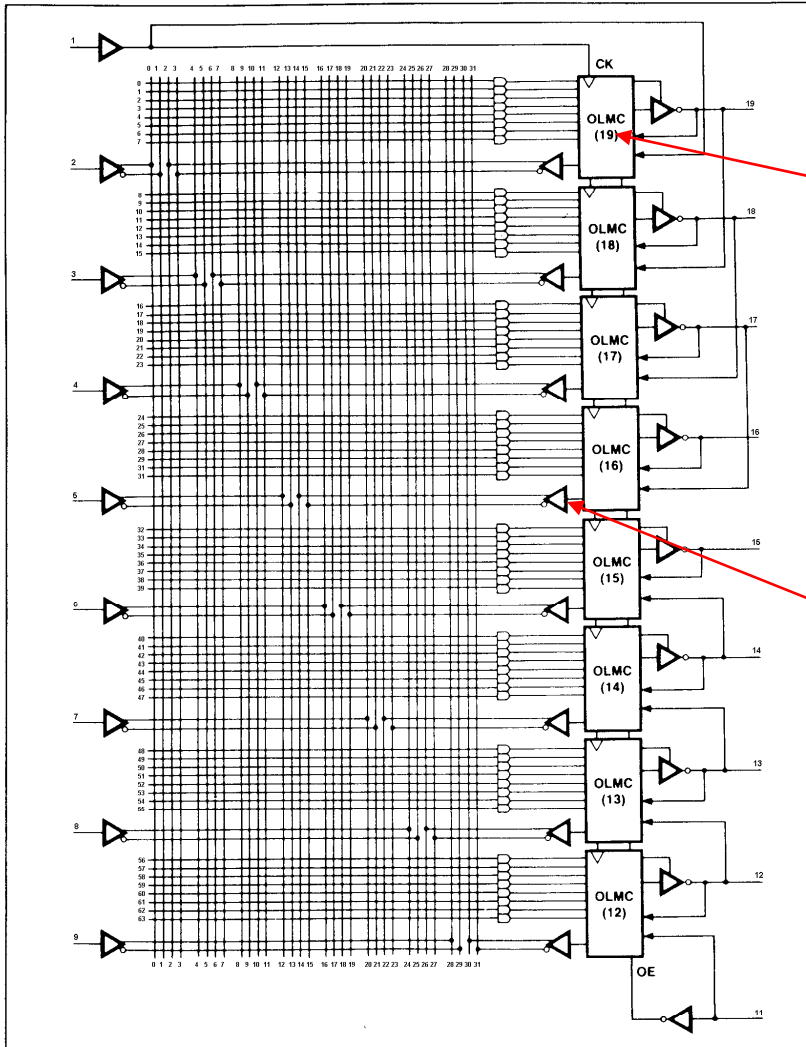

OLMC (Output Logic MacroCell) has OR, FF, output multiplexer and I/O control logic.

Note that OLMC output is fed back to input matrix for use in other OLMCs.


GAL22V10 OLMC Structure

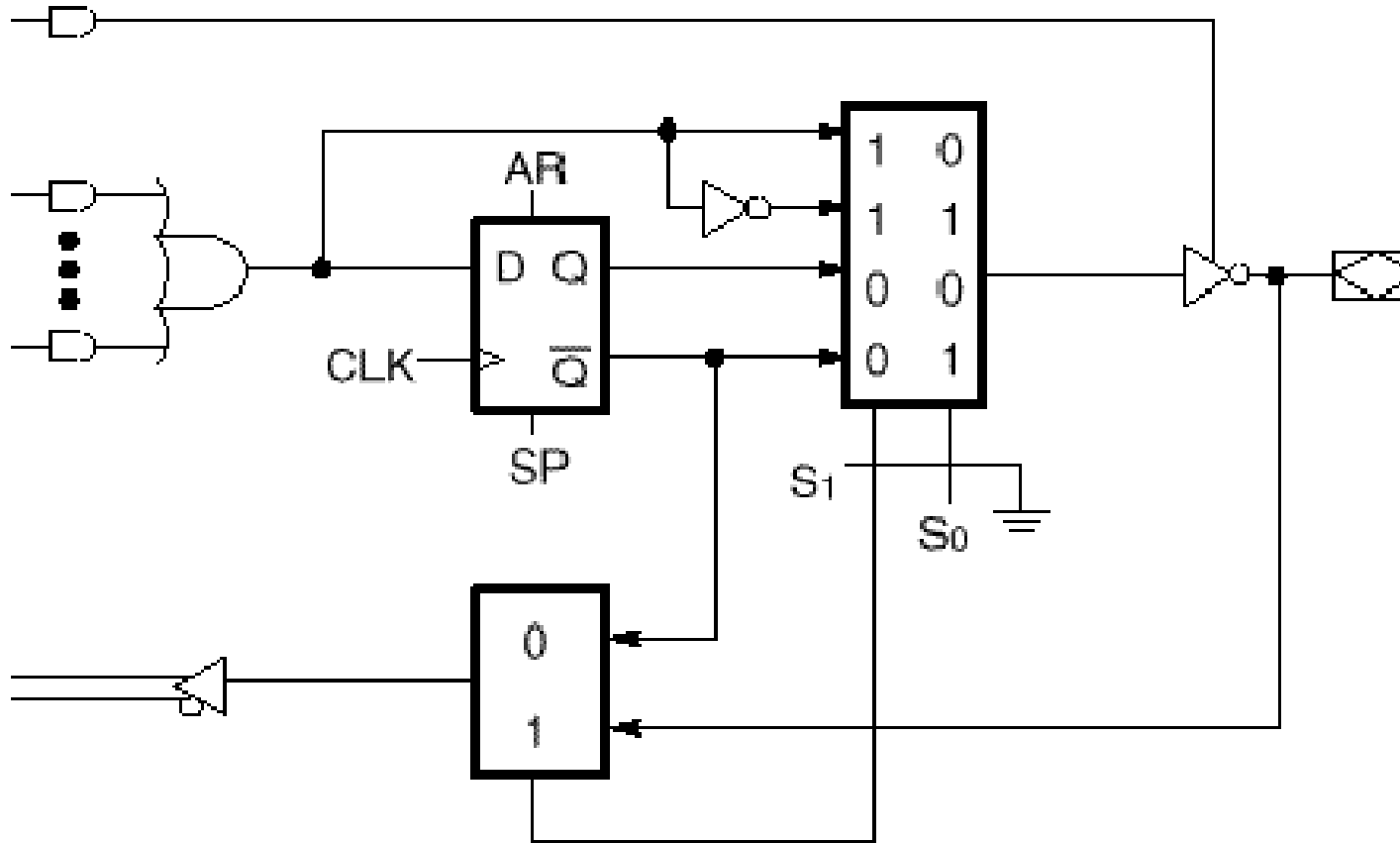

PAL22V10 OLMC Configuration Modes

- Registered Mode: active (low, high): Q' is feedback as input only, no dedicated input in this mode
- Combinational Mode: active (low, high) can feedback comb. Output (high, low) and/or dedicated input

GAL16V8 OLMC Structure

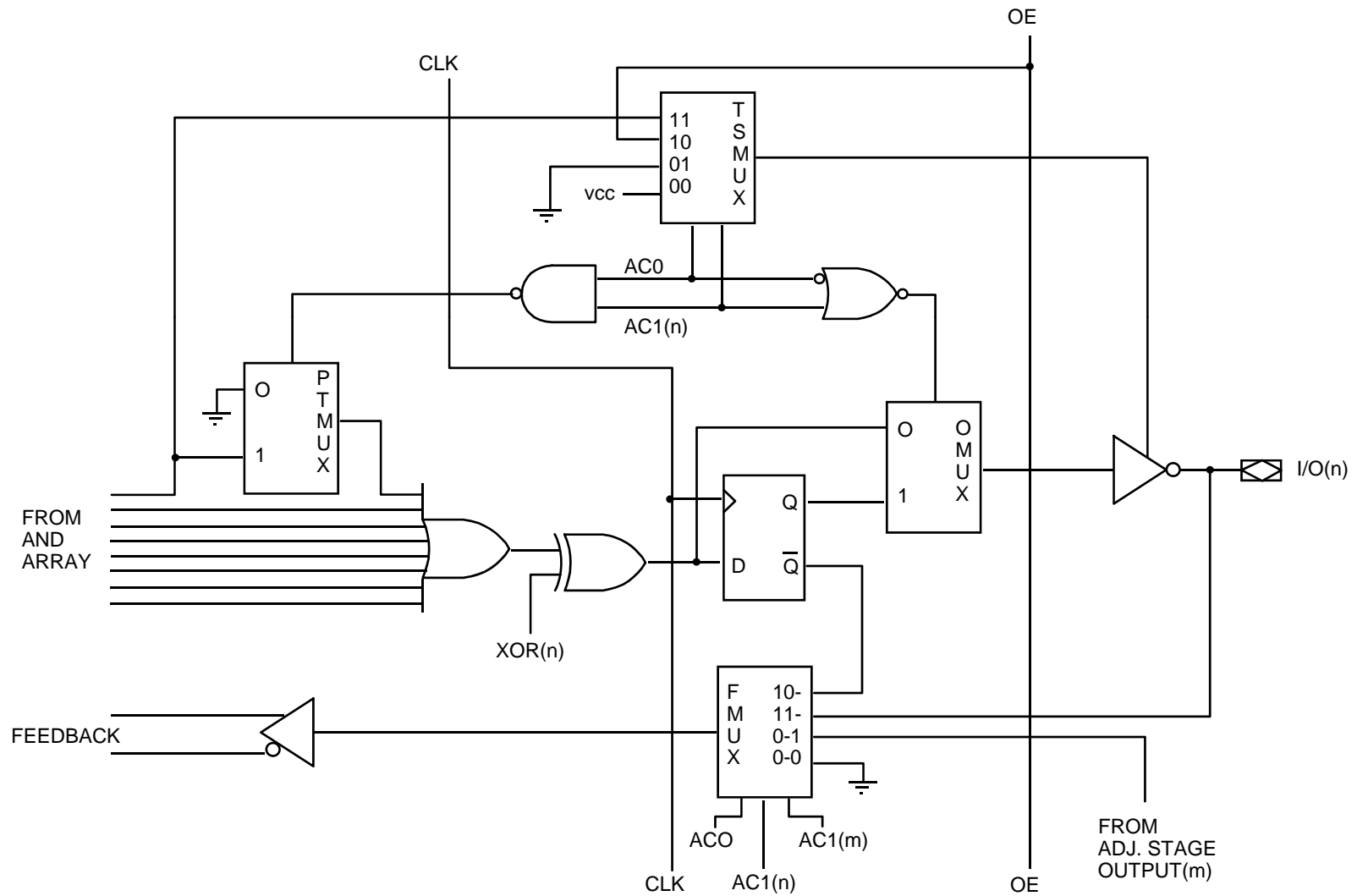

PAL16V8 OLMC

Configuration Modes

Simple mode (combinational output)

- combinational output

- combinational output with feedback

- dedicated input

Complex mode

- combinational output, with feedback

- combinational input from another OLMC

Registered mode: active (low, high): Q' is feedback as input (no dedicated input)

Field Programmable Gate Arrays (FPGAs)

- FPGAs have much more logic than CPLDs
 - 2K to >10M equivalent gates
 - Requires different architecture
 - FPGAs can be RAM-based or Flash-based
 - RAM FPGAs must be programmed at power-on
 - External memory needed for programming data
 - May be dynamically reconfigured
 - Flash FPGAs store program data in non-volatile memory
 - Reprogramming is more difficult
 - Holds configuration when power is off

FPGA Structure

- Typical organization in 2-D array
 - Configurable logic blocks (CLBs) contain functional logic (could be similar to PAL22V10)
 - Combinational functions plus FFs
 - Complexity varies by device
 - CLB interconnect is either local or long line
 - CLBs have connections to local neighbors
 - Horizontal and vertical channels use for long distance
 - Channel intersections have switch matrix
 - IOBs (I/O logic Blocks) connect to pins
 - Usually have some additional C.L./FF in block

Field-Programmable Gate Arrays structure

- Logic blocks
 - To implement combinational and sequential logic
- Interconnect
 - Wires to connect inputs and outputs to logic blocks
- I/O blocks
 - Special logic blocks at periphery of device for external connections
- Key questions:
 - How to make logic blocks programmable?
 - How to connect the wires?
 - *After the chip has been fabbed*
 - HW problems: 7-19, 7-20, 7-22, 7-23, 7-26 due 22/9/07

