

Basic circuit Concept

SHEET RESISTANCE R_s

 


TABLE 4.1 Typical sheet resistances R_s of MOS layers for 5 μm^* , and Orbit 2 μm^* and 1.2 μm^* technologies

Layer	R_s ohm per square		
	5 μm	Orbit	Orbit 1.2 μm
Metal	0.03	0.04	0.04
Diffusion (or active)**	10→50	20→45	20→45
Silicide	2→4	—	—
Polysilicon	15→100	15→30	15→30
n-transistor channel	$10^{4\dagger}$	$2 \times 10^{4\dagger}$	$2 \times 10^{4\dagger}$
p-transistor channel	$2.5 \times 10^{4\dagger}$	$4.5 \times 10^{4\dagger}$	$4.5 \times 10^{4\dagger}$

AREA CAPACITANCES OF LAYERS

- it will be apparent that conducting layers are separated from the substrate and each other by insulating (dielectric) layers,
- thus parallel plate capacitive effects must be present and must be allowed for.
- For any layer, knowing the dielectric (silicon dioxide) thickness, we can calculate area capacitance as follows:

$$C = \frac{\epsilon_0 \epsilon_{ins} A}{D} \text{ farads}$$


TABLE 4.2 Typical area capacitance values for MOS circuits

<i>Capacitance</i>	<i>Value in pF × 10⁻⁴/μm² (Relative values in brackets)</i>					
	<i>5 μm</i>		<i>2 μm</i>		<i>1.2 μm</i>	
Gate to channel	4	(1.0)	8	(1.0)	16	(1.0)
Diffusion (active)	1	(0.25)	1.75	(0.22)	3.75	(0.23)
Polysilicon* to substrate	0.4	(0.1)	0.6	(0.075)	0.6	(0.038)
Metal 1 to substrate	0.3	(0.075)	0.33	(0.04)	0.33	(0.02)
Metal 2 to substrate	0.2	(0.05)	0.17	(0.02)	0.17	(0.01)
Metal 2 to metal 1	0.4	(0.1)	0.5	(0.06)	0.5	(0.03)
Metal 2 to polysilicon	0.3	(0.075)	0.3	(0.038)	0.3	(0.018)

THE DELAY UNIT τ

Since the transition point of an inverter or gate is $0.5 V_{DD}$ • *which is close to $0.63 V_{DD}$* • it appears to be common practice to use transit time and time constant (as defined for the delay unit t) interchangeably and 'stray' capacitances are usually allowed for by doubling (or more) the theoretical values calculated.

INVERTER DELAYS

 


$$T_d = (1 + Z_{p.u.}/Z_{p.d.})\tau$$

Thus, the inverter pair delay for inverters having 4:1 ratio is 5τ .

However, a single 4:1 inverter exhibits undesirable asymmetric delays since the delay in turning on is, for example, τ , while the corresponding delay in turning off is 4τ . Quite obviously, the asymmetry is worse when considering an inverter with an 8:1 ratio.

Super Buffers

 


considering a positive going logic transition V_{in} at the input, it will be seen that the inverter formed by T_1 and T_2 is turned on and, thus, the gate of T_3 is pulled down toward 0 volt with a small delay. Thus, T_3 is cut off while T_4

(the gate of which is also connected to V_{in}) is turned on and the output is pulled down quickly.

Now consider the opposite transition: when V_{in} drops to 0 volt, then the gate of T_3 is allowed to rise quickly to V_{DD} . Thus, as T_4 is also turned off by V_{in} , T_3 is made to conduct

PROPAGATION DELAYS

 

the overall delay increases rapidly as n increases and in practice no more than four pass transistors should be normally connected in series. However, this number can be exceeded if a buffer is inserted between each group of four pass transistors or if relatively long time delays are acceptable.