

# Electromechanical Systems & Actuators

## DC MACHINES

These slides are the contributions of: Dr. A. Gastli, Dr. A. Al-Badi, and Dr. Amer Al-Hinai

### DC Machines

#### LEARNING GOALS

##### Introduction

- Application of DC Machine
- Advantages & Disadvantages of DC Machine

##### Construction of DC Machine

- Field System
- Armature
- Commutator
- Brush

##### Principle of Operation

- Faraday's Law
- Armature Voltage & Developed Torque

##### Classification of DC Machine

- Permanent Magnet
- Self-Excited
- Separately-Excited

##### DC Machine Representation

##### Magnetization Curve (Saturation)

##### DC Motor & Generator Equations

##### Power Flow & Efficiency

##### Torque-Speed Characteristics

##### Starting of DC Machine

## Introduction

- ◆ Most of the electrical machine in service are AC type.
- ◆ DC machine are of considerable industrial importance.
- ◆ DC machine mainly used as DC motors and the DC generators are rarely used.
- ◆ DC motors provides a fine control of the speed which can not be attained by AC motors.
- ◆ DC motors can developed rated torque at all speeds from standstill to rated speed.
- ◆ Developed torque at standstill is many times greater than the torque developed by an AC motor of equal power and speed rating.

## Application of DC Machines

- ◆ The d.c. machine can operate as either a motor or a generator, at present its use as a generator is limited because of the widespread use of ac power.
- ◆ Large d.c. motors are used in machine tools, printing presses, fans, pumps, cranes, paper mill, traction, textile mills and so forth.
- ◆ Small d.c. machines (fractional horsepower rating) are used primarily as control device-such as tachogenerators for speed sensing and servomotors for position and tracking.

## Application of DC Machines




Paper Mills



Steel Mills



Mining

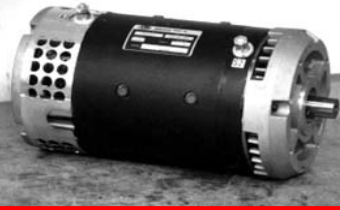

DC Motor



Oil Rigs



Robots



Machine Tools



Petrochemical

## Advantages & Disadvantages Of D.C. Motors

### Advantages

- High starting torque
- Rapid acceleration and deceleration.
- Speed can be easily controlled over wide speed range.
- Used in tough jobs (traction motors, electric trains, electric cars,....)
- Built in wide range of sizes.

### Disadvantages


- Needs regular maintenance
- Cannot be used in explosive area
- High cost

# Introduction

## Electric Machine




## Electromechanical Energy Conversion

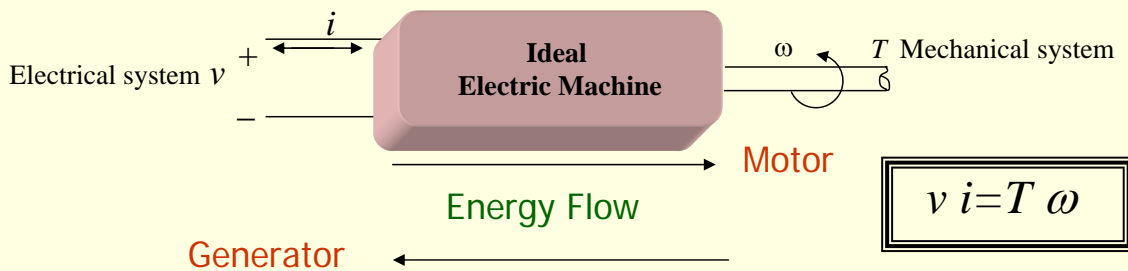


# Construction of DC Machine

## Parts of a DC Machine

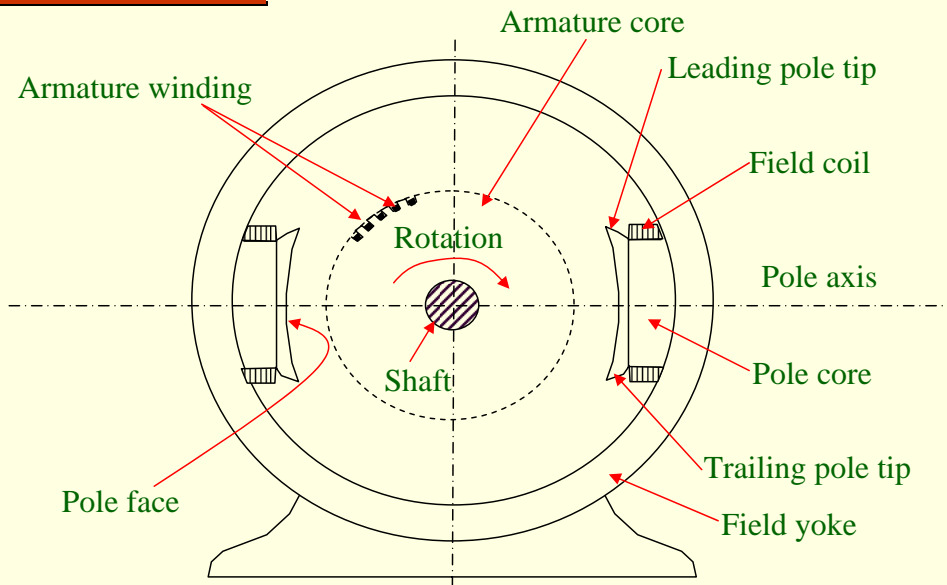

# Construction of DC Machine

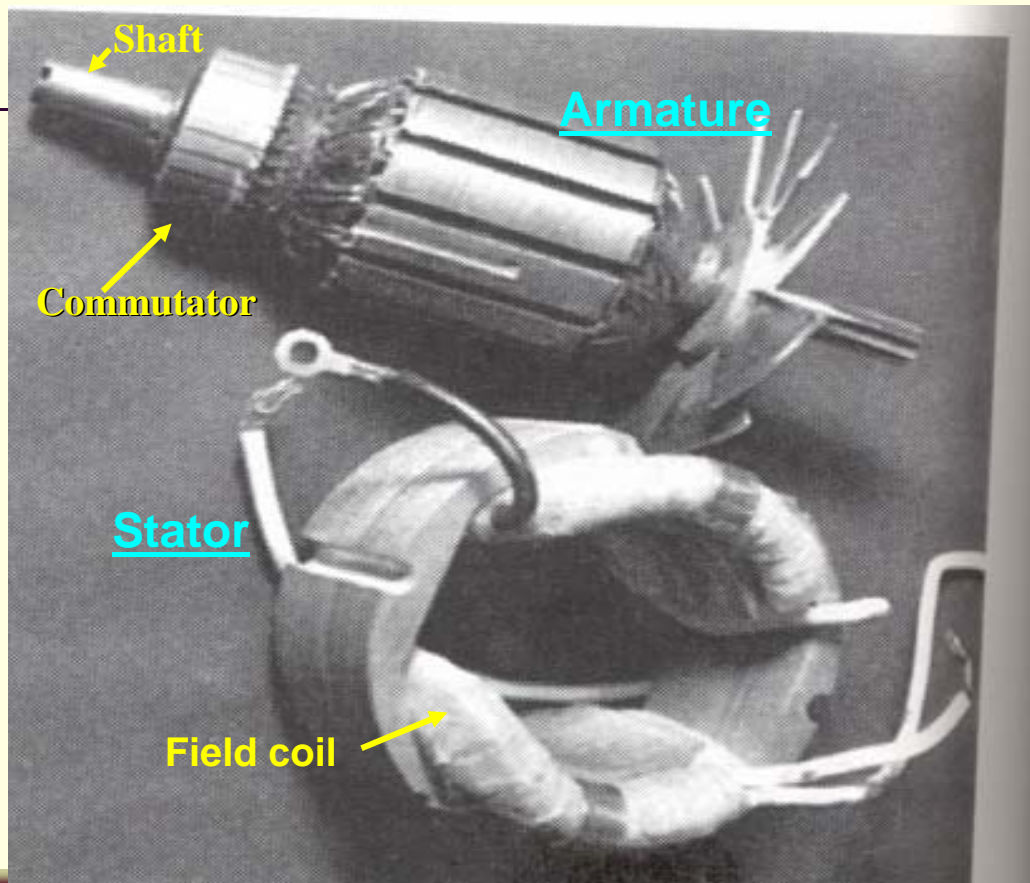

## Construction of DC Machine: Field System


The field system is to produce uniform magnetic field within which the armature rotates. This consists of Yoke or frame: Acts as a mechanical support of the machine



*2000HP DC Motor field System*
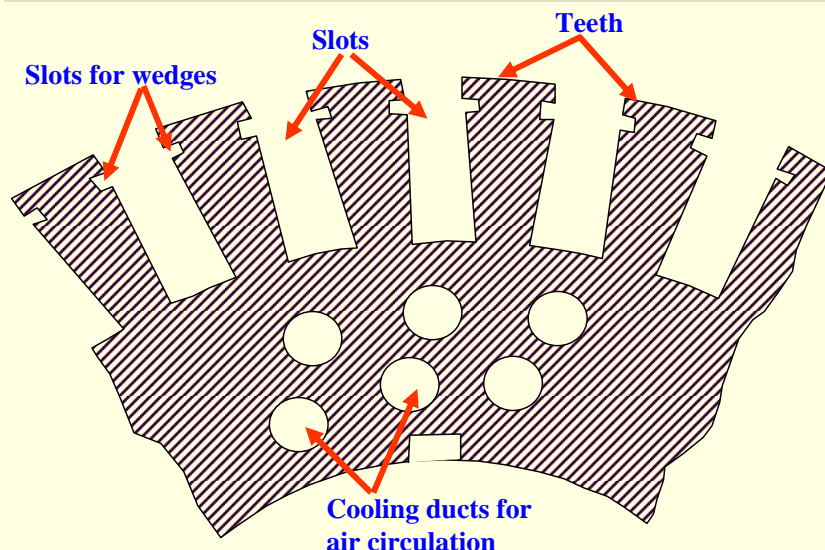
## Construction of DC Machine: Armature

The rotor or the armature core, which carries the rotor or armature winding, is made of sheet-steel laminations. The laminations are stacked together to form a cylindrical structure




The armature coils that make the armature winding are located in the slots

Non-conducting slot liners are wedged in between the coil and the slot walls for protection from abrasion, electrical insulation and mechanical support

*Portion of an armature lamination of a dc machine showing slots and teeth*



## Construction of DC Machine: Armature

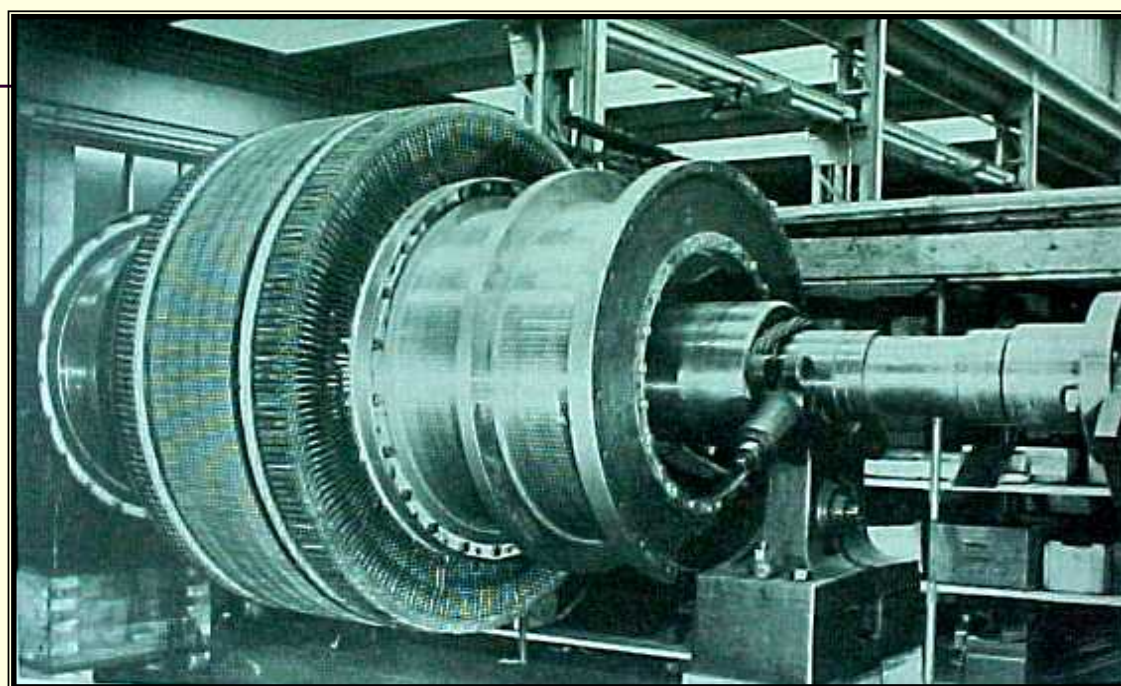

*Armature of a DC Machine*
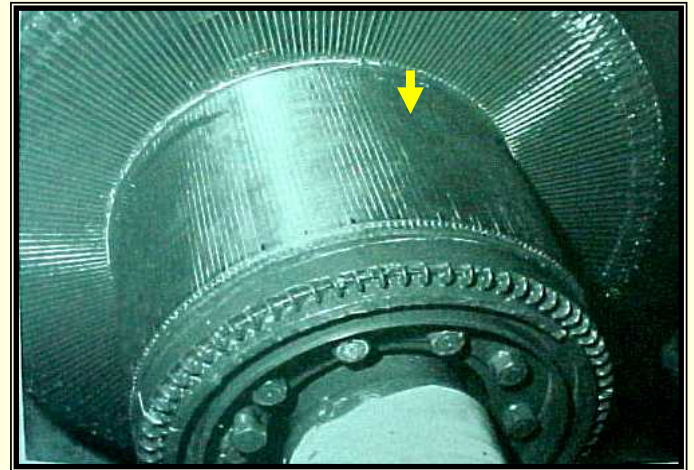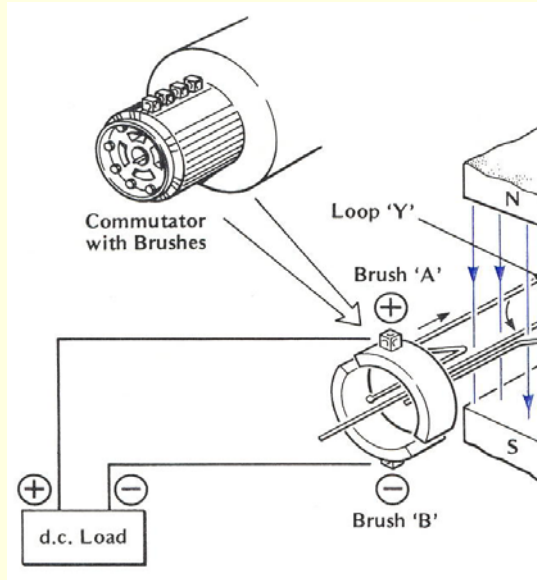
## Construction of DC Machine: Commutator


**Commutator:** is a mechanical rectifier, which converts the alternating voltage generated in the armature winding into direct voltage across the brush. It is made of copper segments insulated from each other by mica and mounted on the shaft of the machine. The armature windings are connected to the commutator segments.



*Commutator*

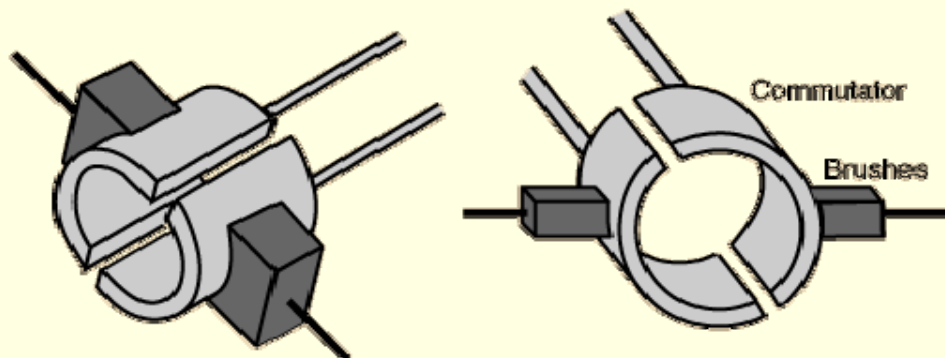
## Construction of DC Machine: Brush

The purpose of the brush is to ensure electrical connections between the rotating commutator and stationary external load circuit. It is made of carbon and rest on the commutator.




*Commutator and Brushes*
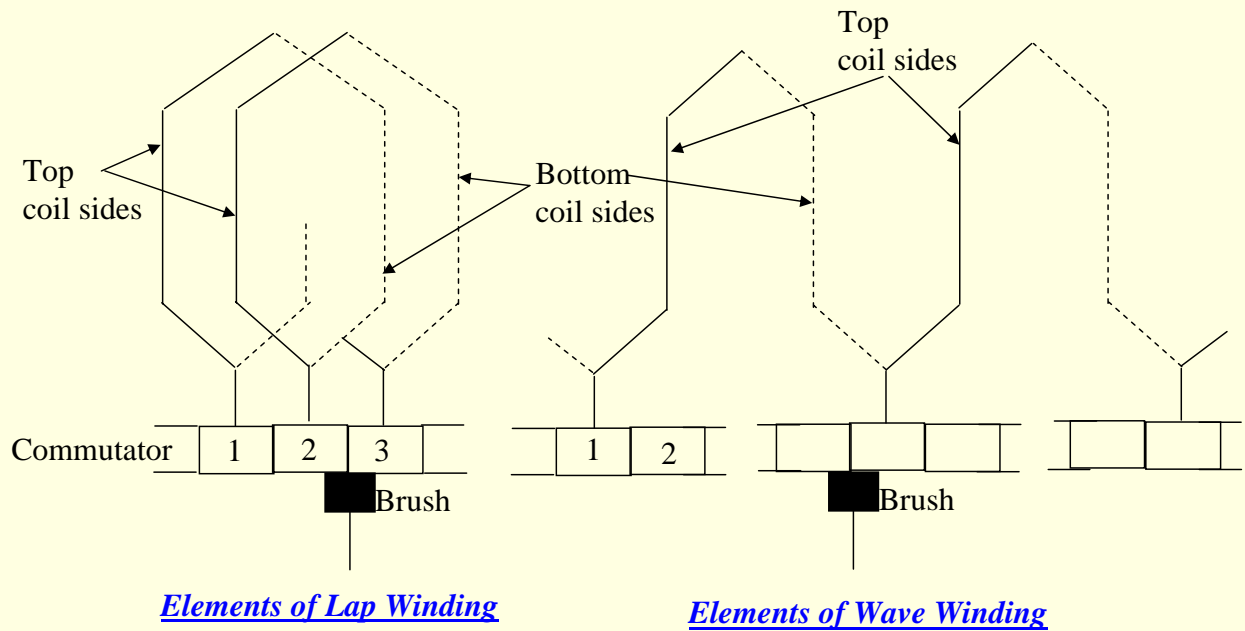
# Construction of DC Machine: Armature Winding



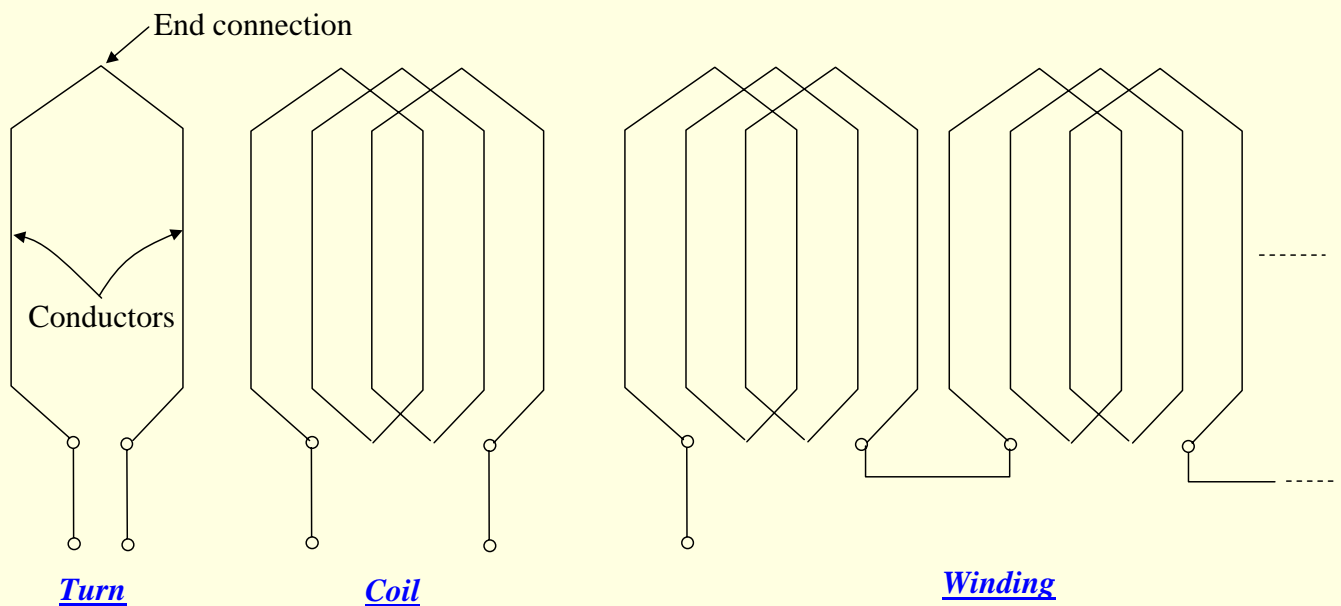
# Construction of DC Machine: Armature Winding






# Construction of DC Machine: Armature Winding

## Lap Winding

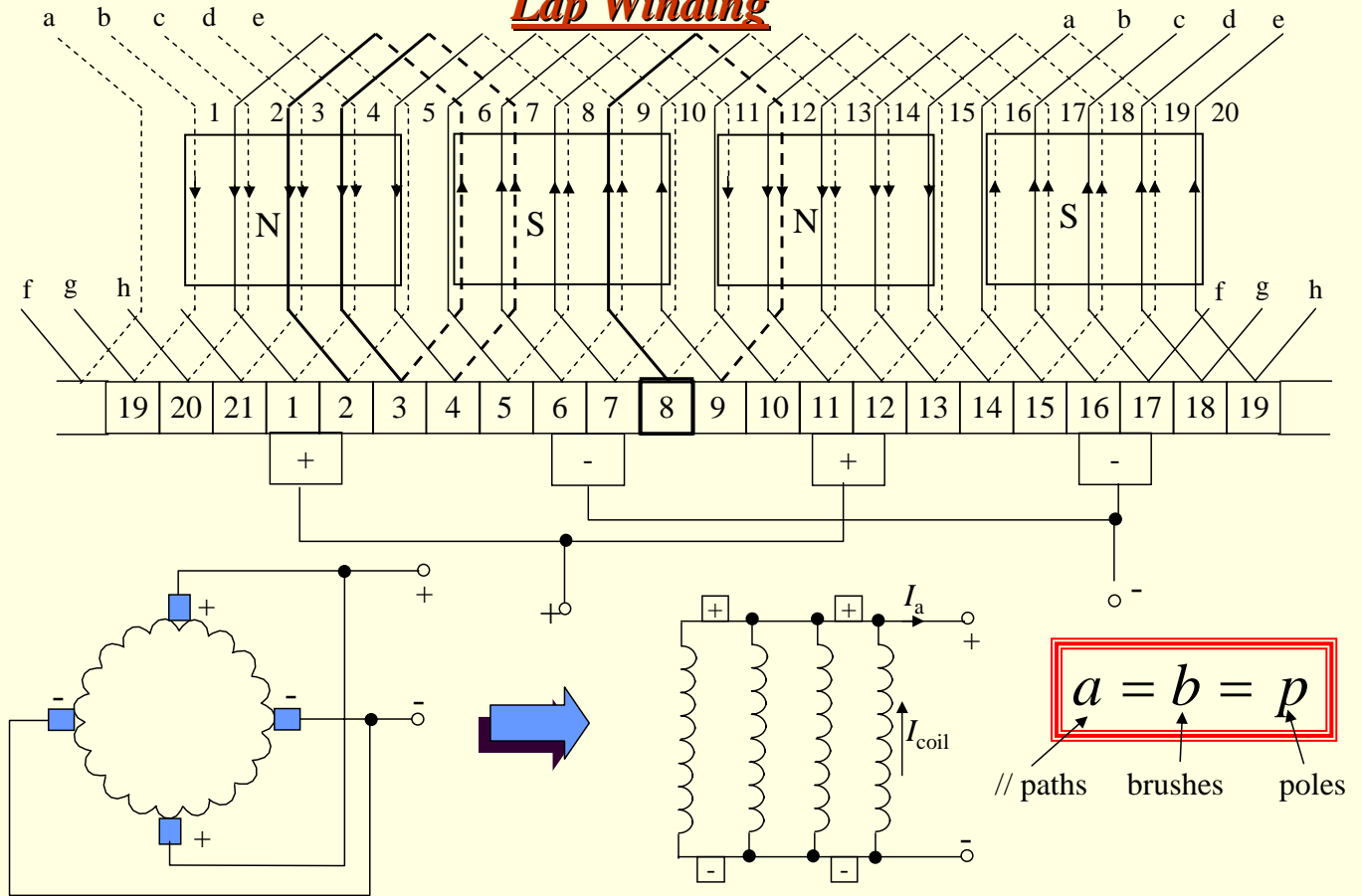

# Construction of DC Machine: Armature Winding

## Wave Winding

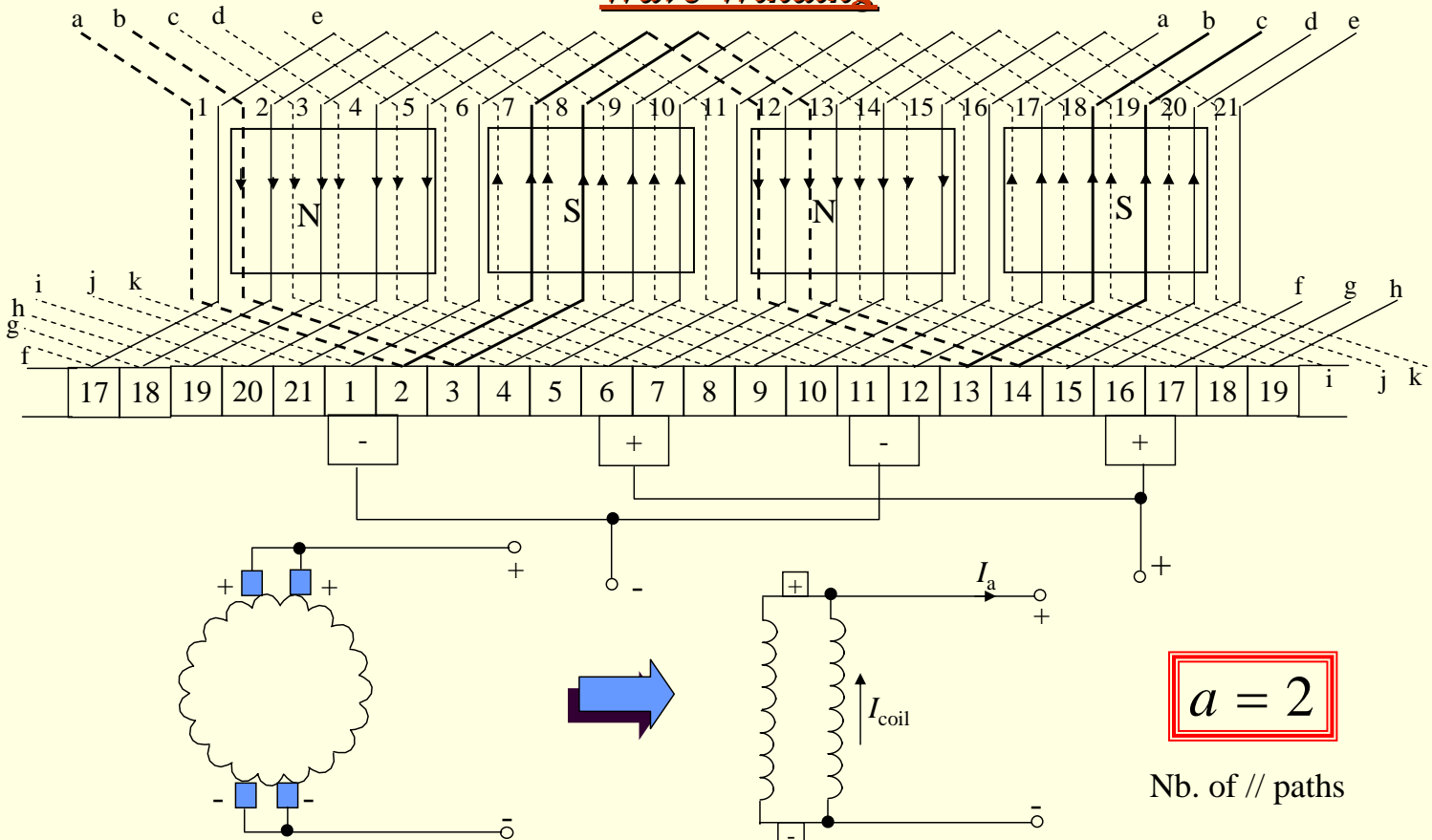


Nb. of // paths

# Principle of Operation
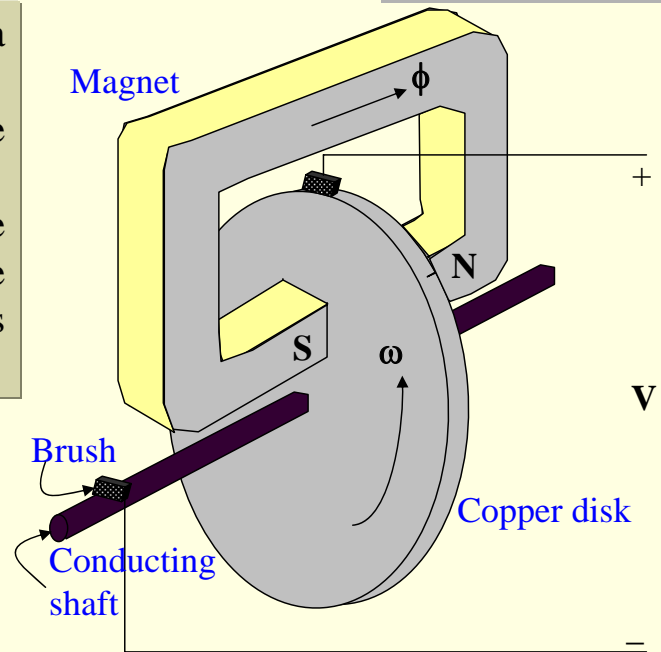
## The Faraday Disk and Faraday's Law

An emf is induced in a circuit placed in a magnetic field if either:

- the magnetic flux linking the circuit is time varying
- or there is a relative motion between the circuit and the magnetic field such that the conductors comprising the circuit cut a cross the magnetic flux lines.



- 1<sup>st</sup> form of the law is the basis of transformers.
- 2<sup>nd</sup> form is the basic principle of operation of electric generators.

# Principle of Operation

## The right-hand rule and generator action

Velocity,  $u$

Flux density,  $B$

emf,  $e$


$$\Phi = B \cdot A$$

$$\Phi = B \cdot l \cdot s$$

$$e = \frac{d\Phi}{dt} = \frac{dB \cdot l \cdot s}{dt}$$


$$e = B \cdot l \cdot \frac{ds}{dt}, u = \frac{ds}{dt}$$

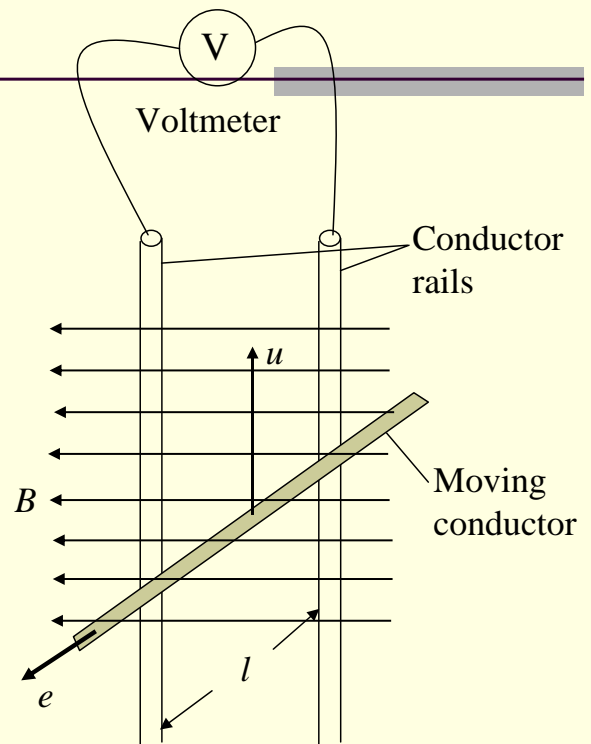Faraday's law or flux cutting rule  $\rightarrow e = Blu$




# Principle of Operation

## Without Commutator

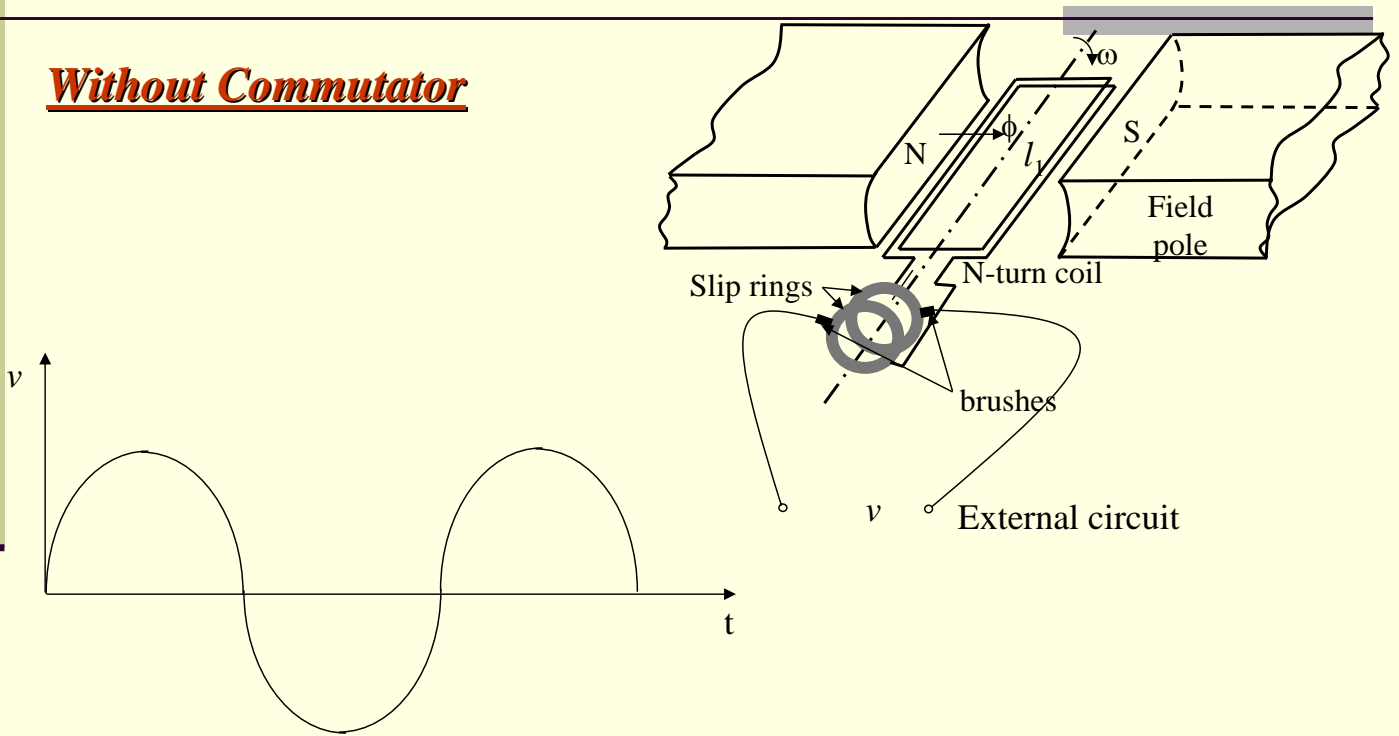


# Principle of Operation

## With Commutator

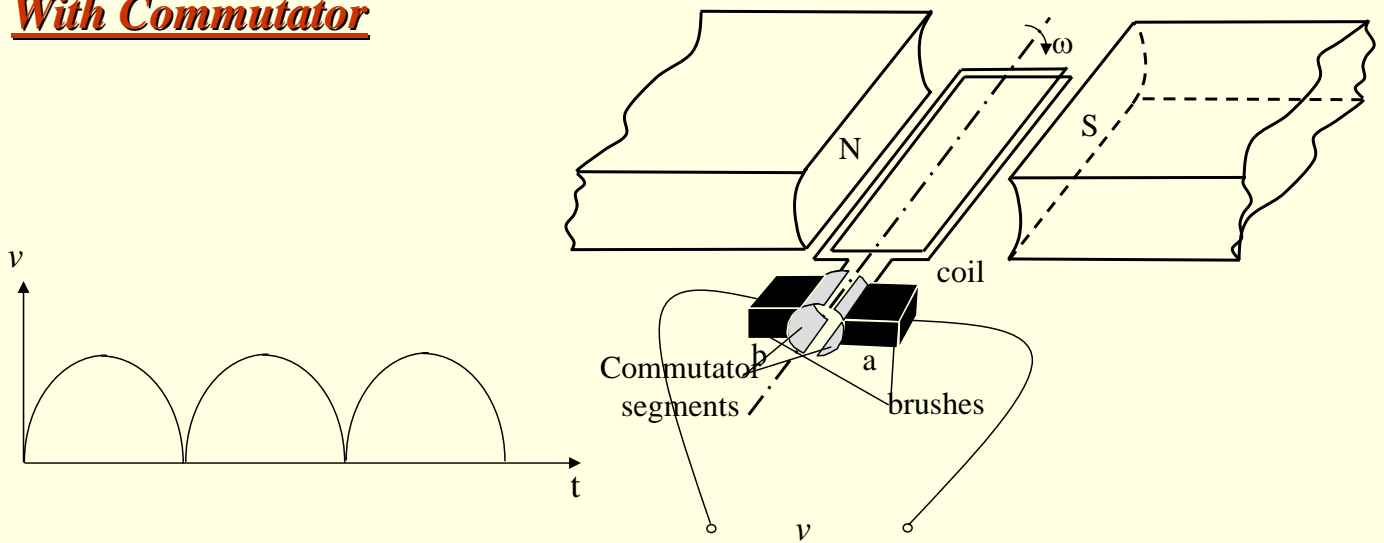

# Single-Phase Full wave Rectifier

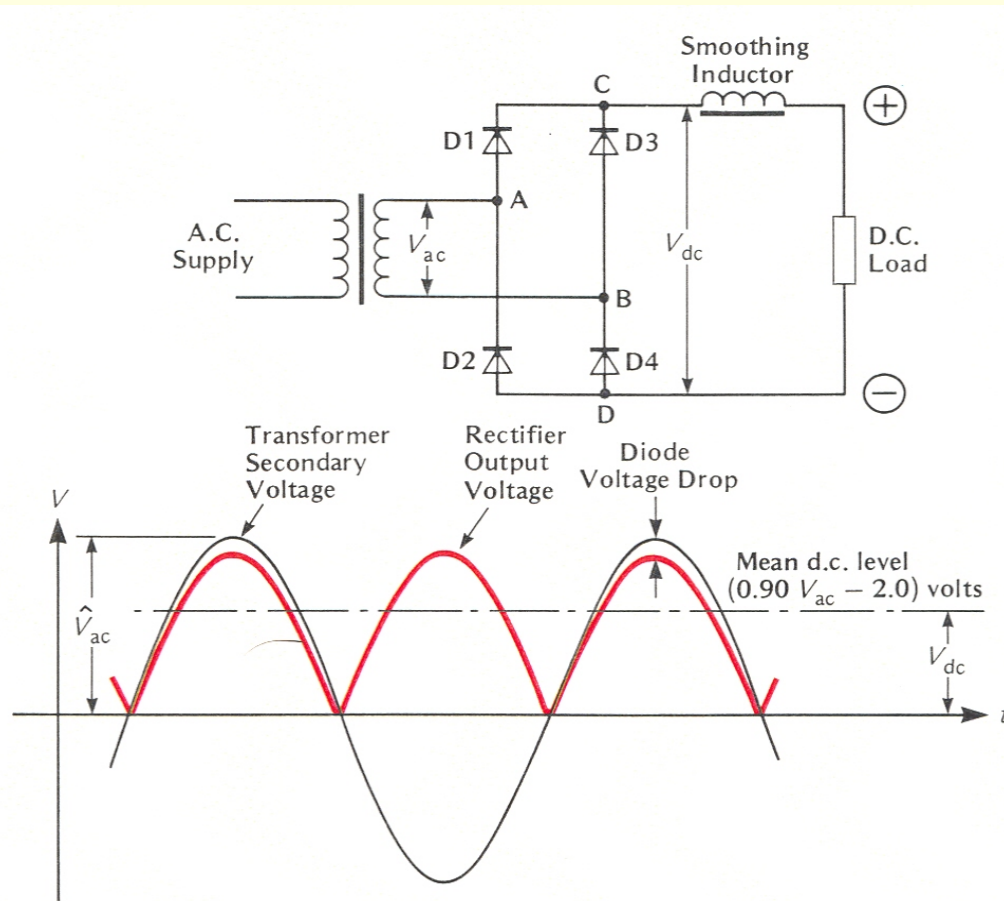

Dr. Adel Gastli



23

# Multi-Pole Machines

If  $p$  is the number of poles, then  $p/2$  cycles of variation of the flux are encountered every complete mechanical rotation.

$$\text{One pole pitch} = 180^\circ \text{ ed} = \frac{360^\circ \text{ md}}{p}$$
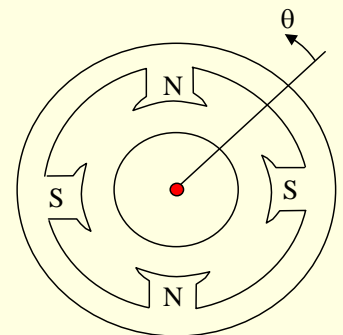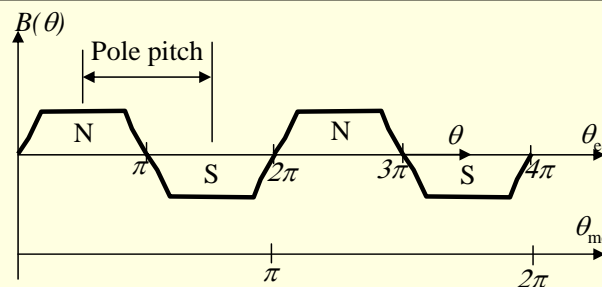
$$\theta_{ed} = \frac{p}{2} \theta_{md}$$



$\theta_{ed}$  : electrical degrees or angular measure in cycles  
 $\theta_{md}$  : mechanical degrees or angular measure in space

Dr. Adel Gastli

MCTE3210: Electromechanical Systems & Actuators

24

## Principle of Operation: Armature Voltage

$$Emf_{conductor} = \frac{\text{Flux / Re v.}}{\text{time / Re v.}} = \frac{p \cdot \Phi}{(60 / N_m)} = \frac{p \cdot \Phi \cdot N_m}{60}$$

$$Emf_{Total} = \frac{Emf_{conductor}}{\text{Number of conductor / path}}$$

$$Emf_{Total} = \left( \frac{p \cdot \Phi \cdot N_m}{60} \right) / \left( \frac{Z}{a} \right) = \frac{p \cdot \Phi \cdot Z \cdot N_m}{60 a}$$

where

$p$  = number of poles

$Z$  = total number of armature conductors

$a$  = number of parallel paths, 2 for wave and  $p$  for lap.

$\Phi$  = flux per pole (Weber)

$N_m$  = speed of the motor in the revolutions per minute (rpm)

time of 1 revolution =  $60/N_m$  (sec)

## Principle of Operation: Armature Voltage

$$\text{Let } \omega_m = \frac{2 \cdot \pi \cdot N_m}{60} \Rightarrow N_m = \frac{\omega_m \cdot 60}{2 \cdot \pi}$$

$\omega_m$  = speed of the motor in radians per second

$$Emf_{Total} = \frac{p \cdot \Phi \cdot Z}{60 a} \cdot \frac{\omega_m \cdot 60}{2 \cdot \pi} = \frac{p \cdot \Phi \cdot Z \cdot \omega_m}{2 \cdot \pi \cdot a}$$

$$Emf_{Total} = K_a \cdot \Phi \cdot \omega_m$$

$K_a$ : armature constant

$$K_a = \frac{p \cdot Z}{2 \cdot \pi \cdot a}$$

**Generated voltage** : generator operation  
**Back emf** : motor operation

# Developed (or Electromagnetic) Torque

Consider the turn shown in the following Figure.

$$\text{Area per pole } A = \frac{2\pi r l}{p}$$

$$\text{Flux density } B = \frac{\Phi}{A} = \frac{p \Phi}{2\pi r l}$$


$$\text{Current / conductor is } I_c = \frac{I_a}{a}$$

$$\text{The force on a conductor is } f_c = B l \frac{I_a}{a}$$


$$\text{The torque developed by a conductor is } T_c = f_c r = B l \frac{I_a}{a} r = \frac{\Phi p I_a}{2\pi a}$$

The total torque developed is

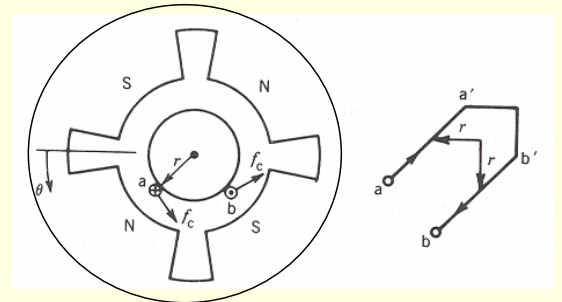
$$T_e = \frac{Zp \Phi I_a}{2\pi a} = K_a \Phi I_a = \frac{E_a I_a}{\omega_m}$$



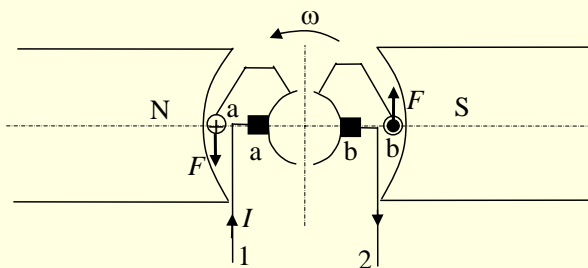
# Production of Unidirectional Torque and Operation of an Elementary



Position of conductor a under N-pole

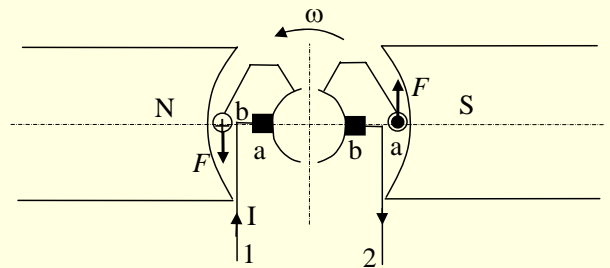


Position of conductor a under S-pole

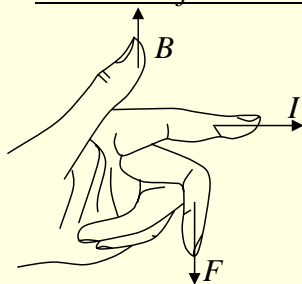


Left-hand rule

With this configuration the torque is unidirectional and independent of conductor position


# Classification of DC Machine

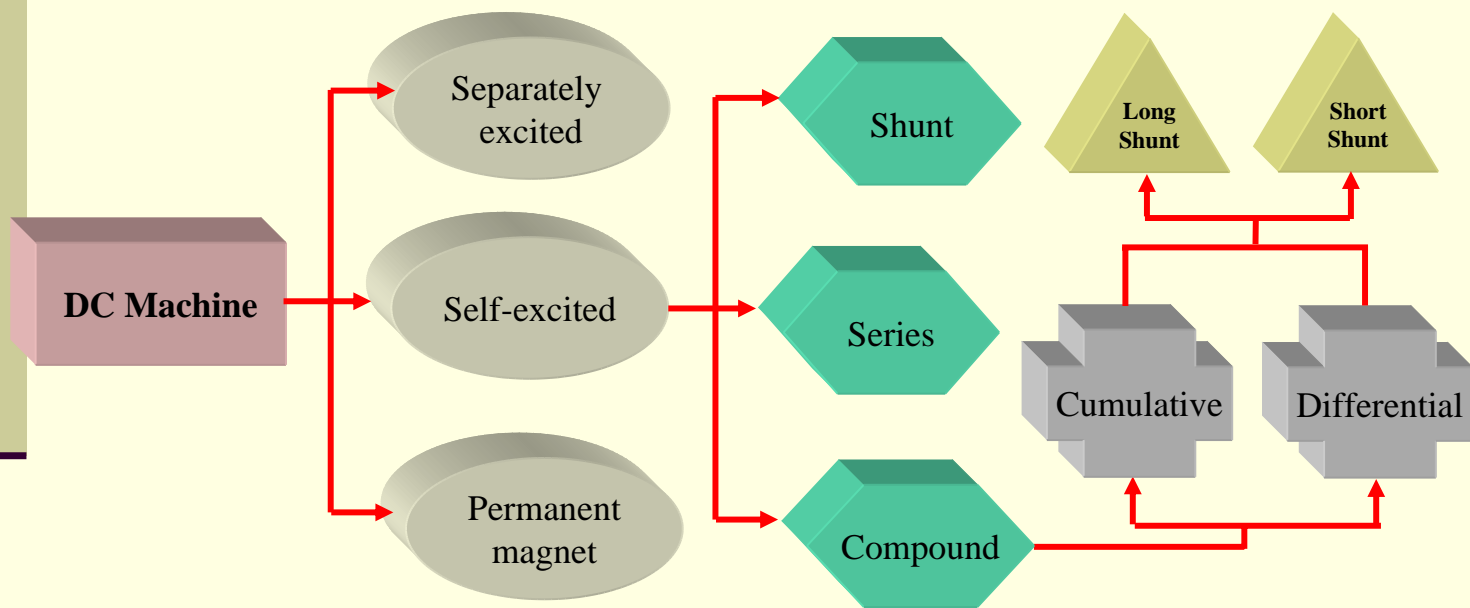


# Classification of DC Machine

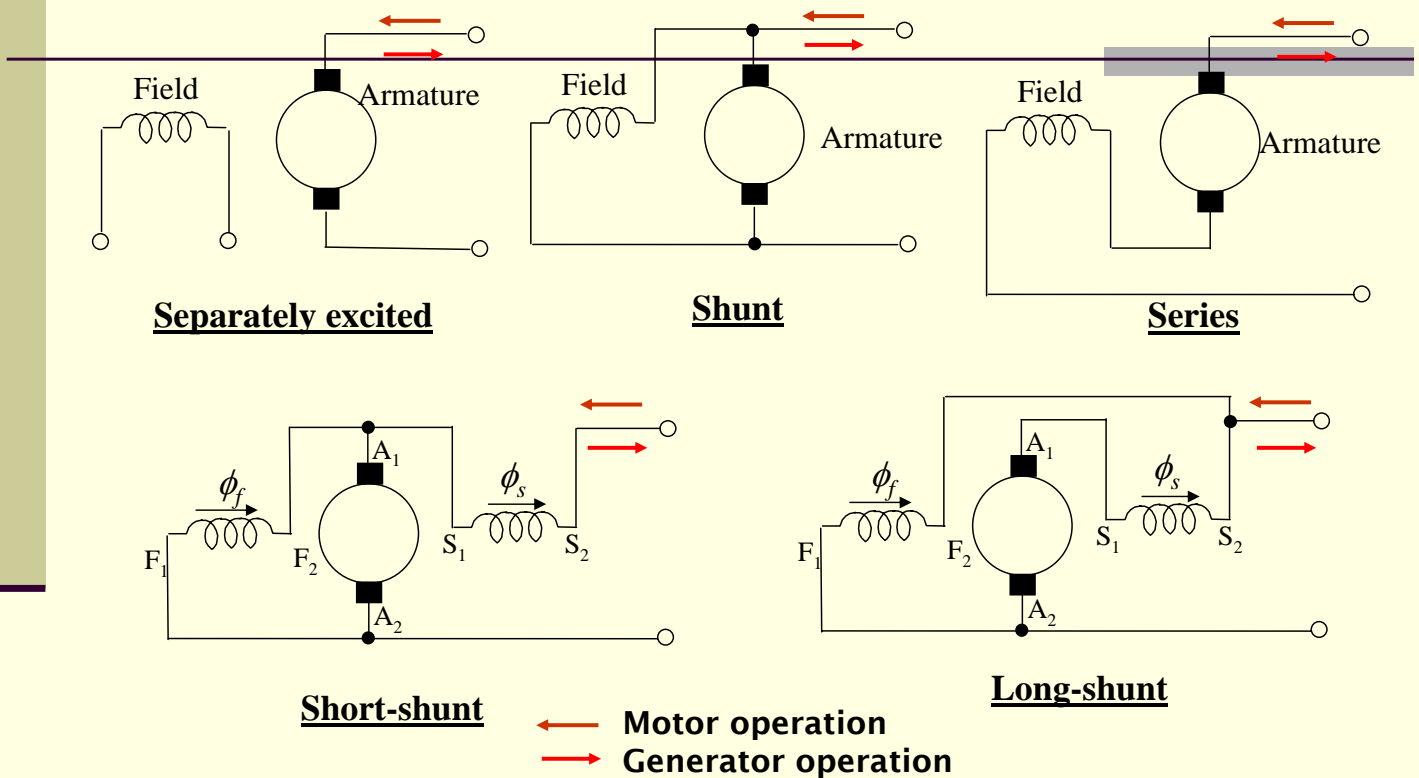

# Classification of DC Machine

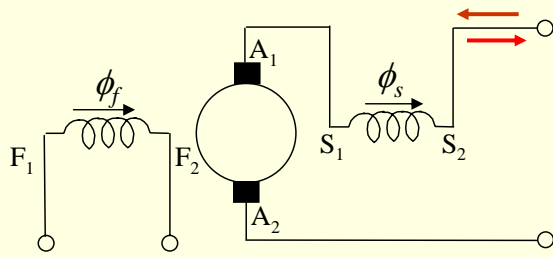

**Cumulative compound**




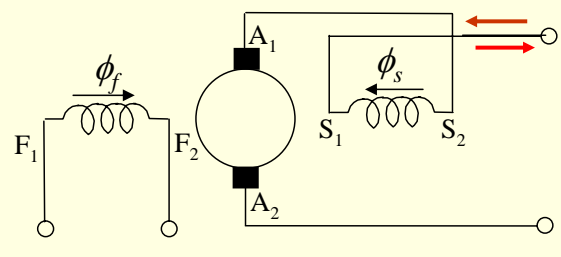


**Differential compound**

← Motor operation  
 → Generator operation
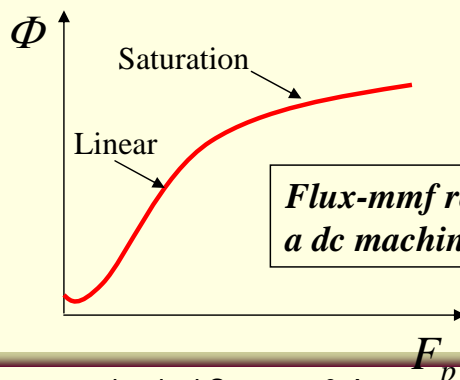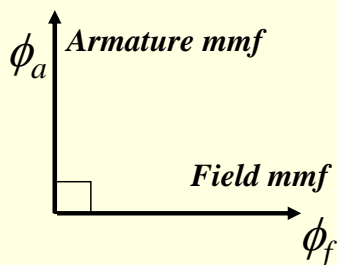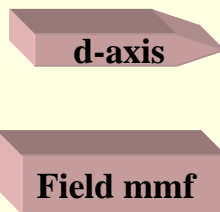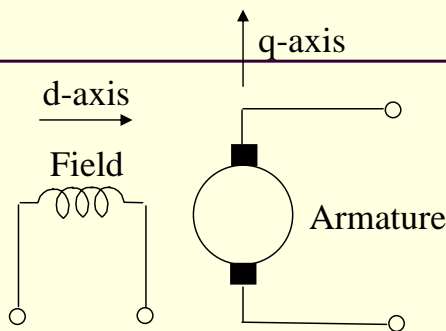
# DC Machine Representation


The mmf's produced by the field circuit and the armature circuit are in quadrature.



*Flux-mmf relation in a dc machine*


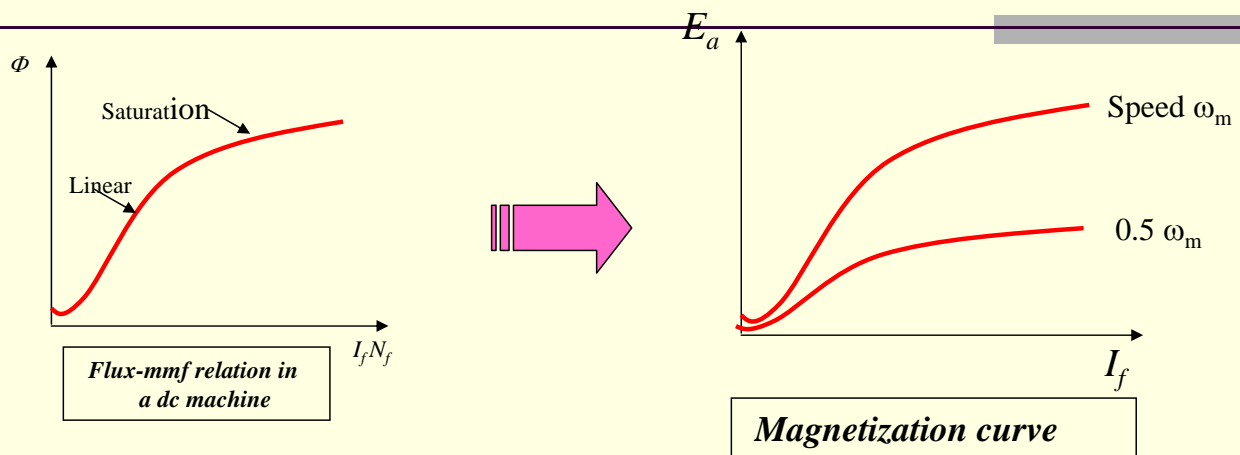
# Magnetization (or Saturation) Curve of a DC Machine




The magnetizing curve is obtained experimentally by rotating the the dc machine at a given speed and measuring the open-circuit armature terminal voltage as the current in the field winding is changed.

**Magnetization Curve**

Represents the saturation level in the magnetic system of the dc machine for various values of *excitation mmf*.

## Dc Motors Equations

### Separately Excited DC Motor

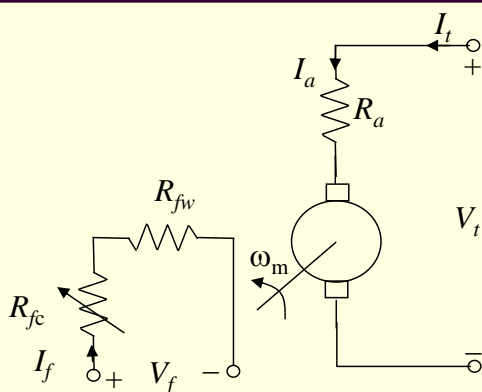

$$V_f = R_f I_f$$

$$E_a = V_t - I_a R_a$$

$$E_a = K_a \Phi \omega_m$$

$$T_e = K_a \Phi I_a$$

- $R_{fw}$ : resistance of field winding.
- $R_{fc}$ : resistance of control rheostat used in field circuit.
- $R_f = R_{fw} + R_{fc}$ : total field resistance
- $R_a$ : resistance of armature circuit, including the effect of brushes. Sometimes  $R_a$  is shown as the resistance of armature winding alone; the brush-contact voltage drop is considered separately and is usually assumed to be about 2V.

# Dc Motors Equations


## Shunt or Self-Excited DC Motor

$$V_f = R_f I_f = V_t$$

$$E_a = V_t - I_a R_a$$


$$E_a = K_a \Phi \omega_m, \quad T_e = K_a \Phi I_a$$

$$V_t = I_t R_L, \quad I_a = I_t - I_f$$

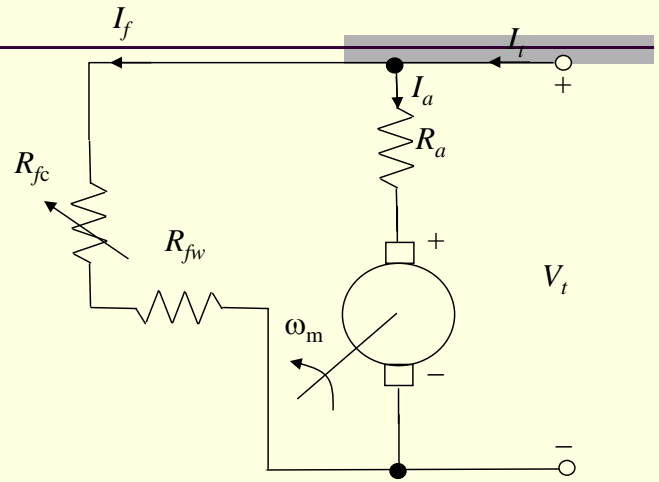

# Dc Generator Equations

## Separately Excited DC Generator

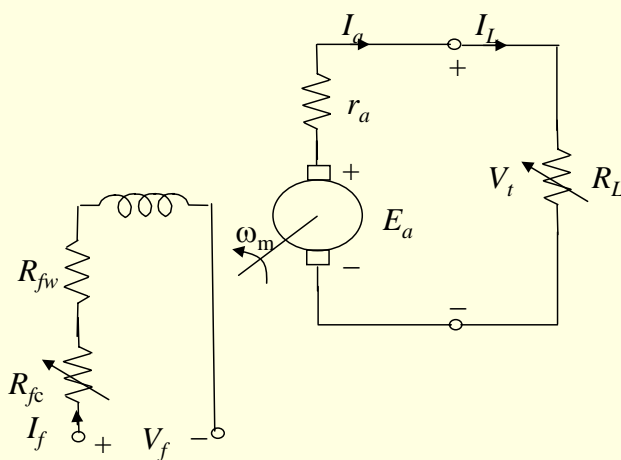

$$V_f = (R_{fw} + R_{fc}) I_f = R_f I_f$$

$$E_a = V_t + I_a r_a$$

$$E_a = K_a \Phi \omega_m$$


$$V_t = I_L R_L$$

$$I_a = I_L$$

# Dc Generator Equations

## Self-Excited DC Generators

### 1. Shunt generator

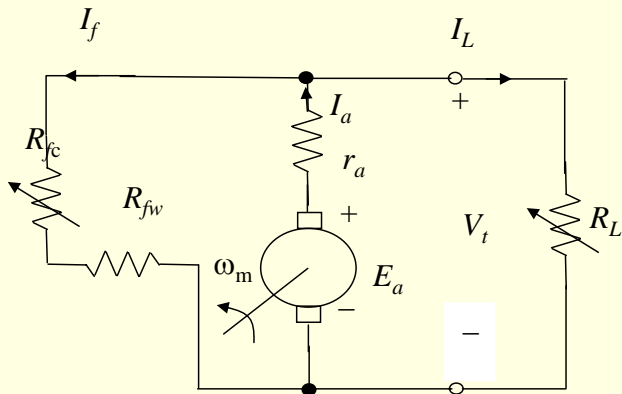

$$V_f = R_f I_f = V_t$$

$$E_a = V_t + I_a r_a$$


$$E_a = K_a \Phi \omega_m$$

$$V_t = I_L R_L$$

$$I_a = I_L + I_f$$

# Dc Generator Equations

### 2. Series Generator

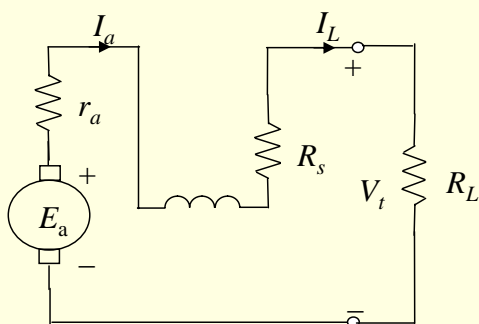


$$V_t = E_a - I_a (r_a + R_s)$$

$$I_L = I_a = I_f$$

$$E_a = K_a \Phi_s \omega_m$$

# Dc Generator Equations

## 3. Compound DC Generator

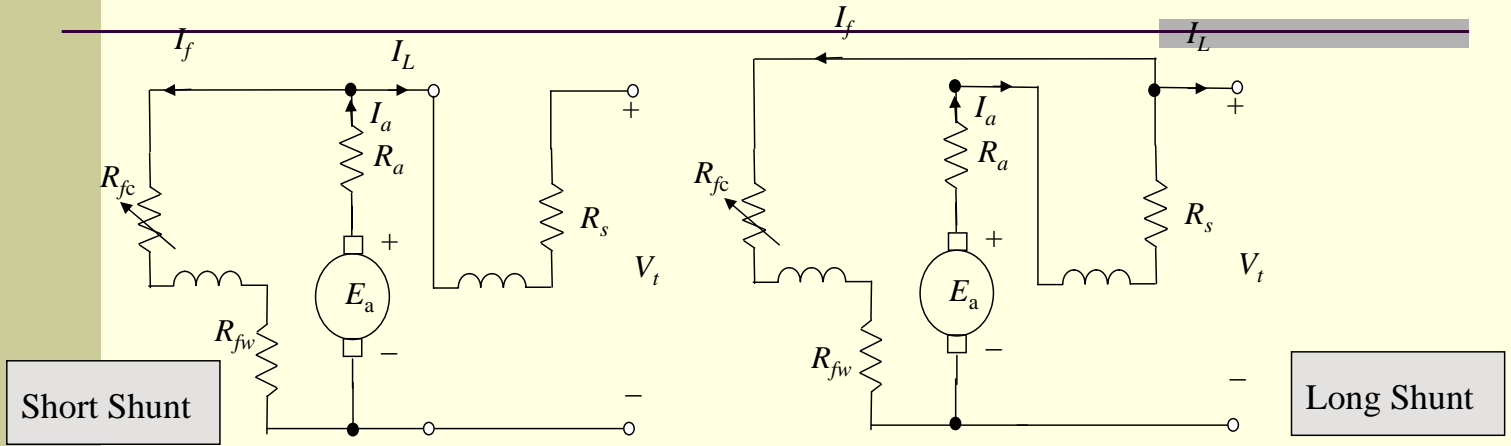

$$V_t = E_a - I_a R_a - I_L R_s$$

$$I_L = I_a - I_f$$

$$I_f = \frac{E_a - I_a R_a}{R_{fw} + R_{fc}}$$

$$E_a = K_a (\Phi_{sh} \pm \Phi_s) \omega_m$$

$$E_a = K_a (\Phi_{sh} \pm \Phi_s) \omega_m$$

**Cumulative**

**Differential**

$$V_t = E_a - I_a (R_a + R_s)$$



$$I_L = I_a - I_f$$

$$I_f = \frac{V_t}{R_{fw} + R_{fc}}$$

$$E_a = K_a (\Phi_{sh} \pm \Phi_s) \omega_m$$

## Power Flow and Efficiency

### DC Generators

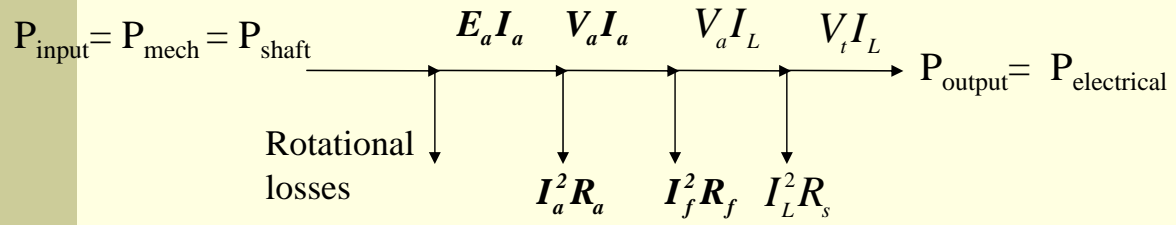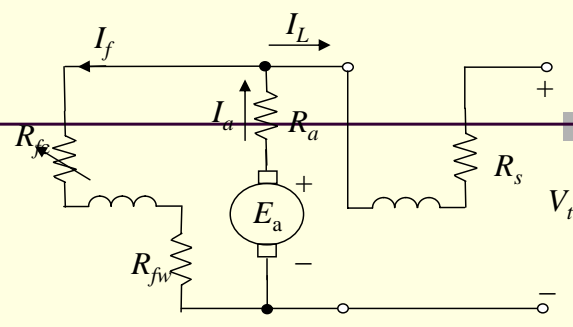



$$\eta = \frac{P_{output}}{P_{input}} = \frac{P_{output}}{P_{output} + Losses}$$

$$\eta = \frac{V_t I_L}{V_t I_L + \sum I^2 R + Rotational Losses}$$

$$\eta = \frac{V_t I_L}{E_a I_a + Rotational Losses}$$

# Power Flow and Efficiency

## DC Motors

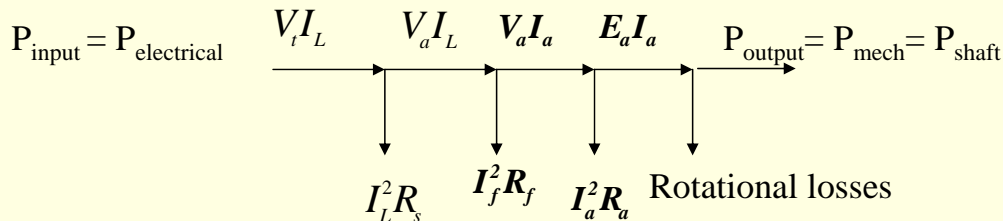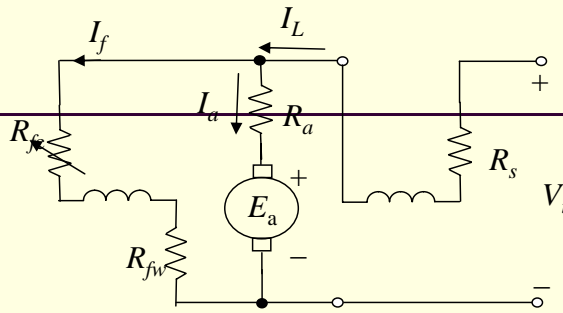

$$\eta = \frac{P_{output}}{P_{input}} = \frac{P_{input} - \text{Losses}}{P_{input}}$$

$$\eta = \frac{V_t I_L - \sum I^2 R - \text{Rotational Losses}}{V_t I_L}$$

$$\eta = \frac{E_a I_a - \text{Rotational Losses}}{V_t I_L}$$

# Torque-Speed Characteristics



## Separately excited & Shunt motors

( $\Phi$  is independent of the load torque)

$$\left. \begin{aligned} V_t &= E_a + I_a r_a \\ E_a &= K_a \Phi \omega_m \end{aligned} \right\} \omega_m = \frac{V_t - I_a r_a}{K_a \Phi}$$

$$T = K_a \Phi I_a$$

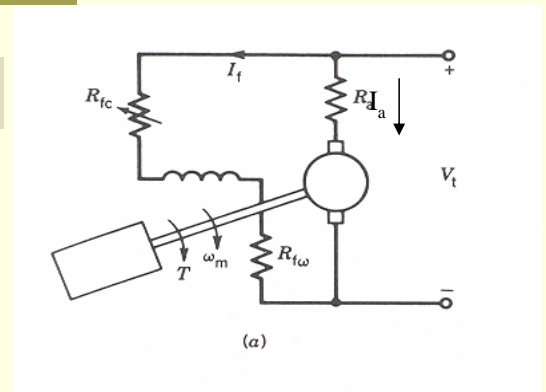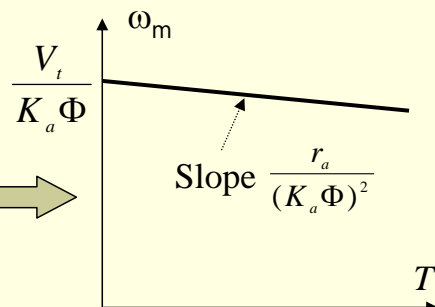Therefore, 
$$\omega_m = \frac{V_t}{K_a \Phi} - \frac{r_a}{(K_a \Phi)^2} T$$



# Torque-Speed Characteristics

## Series motors

$$E_a = V_t - I_a (R_a + R_s)$$

$$E_a = K_a \phi \omega_m$$



Neglecting saturation  $\phi = K_1 I_f = K_1 I_a$

$$E_a = K_a K_1 I_a \omega_m = K_s I_a \omega_m$$

$$\omega_m = \frac{V_t}{K_s I_a} - \frac{R_a + R_s}{K_s}$$

But  $T = K_a \phi I_a = K_a K_1 I_a^2 = K_s I_a^2$
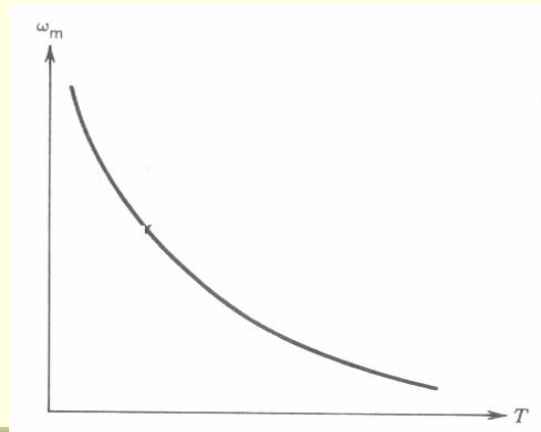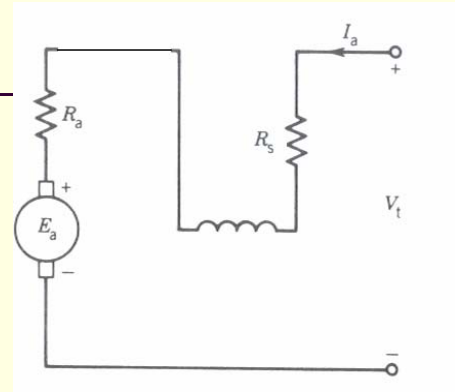
$$\therefore \omega_m = \frac{V_t}{\sqrt{K_s} \sqrt{T}} - \frac{R_a + R_s}{K_s} \quad \Rightarrow$$



# Torque-Speed Characteristics

## Compound motors

Cumulative Compound


$$AT_t = AT_{shunt} \pm AT_{series}$$

Differential Compound

$$\phi_t = \phi_{shunt} \pm \phi_{series}$$

$$\omega_m = \frac{V_t}{K_a \phi_t} - \frac{r_a}{(K_a \phi_t)^2} T$$

➔

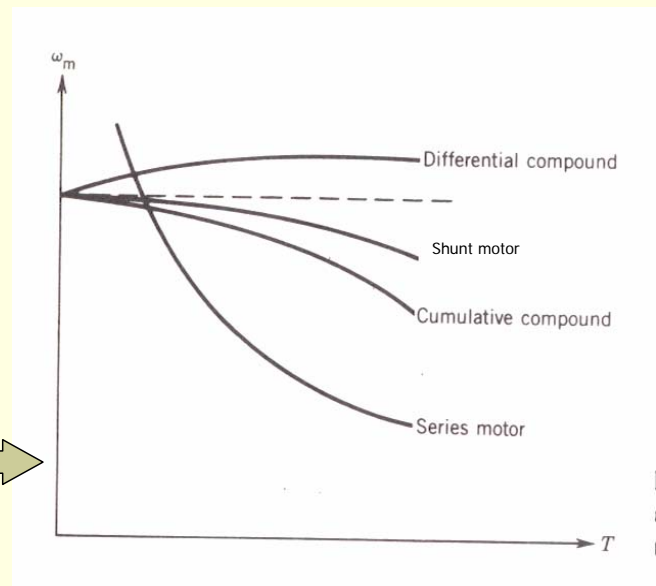

## Starting of DC Machine

If a d.c. motor is directly connected to a d.c. power supply, the starting current will be dangerously high.

$$I_a = \frac{V_t - E_a}{r_a} \quad \text{at starting} \quad \omega = 0 \rightarrow E_a = 0$$

$$\therefore I_a \Big|_{\text{Starting}} = \frac{V_t}{r_a}$$

Since  $r_a$  is small, the starting current is very large.

The starting current can be limited by the following methods:

- 1- Use a variable-voltage supply.
- 2- Insert an external resistance at start, as shown in the Figure.

