

NETWORK FUNCTION

TRANSIENT RESPONSE:

- Transient Response of RC, RL, and RLC Circuits to various excitation signals such as step, ramp, impulse and sinusoidal excitations using Laplace transform.


- NETWORK ANALYSIS is concerned with determining the response ,given the excitation and the network .
- IN NETWORK SYNTHESIS , the problem is to design the network given the excitation and the desired response

NETWORK ELEMENT



- ⦿ Resistor
- ⦿ Capacitor
- ⦿ Inductor

RESISITOR

- ◉ $V(t) = R i(t)$
- ◉ $i(t) = G V(t)$

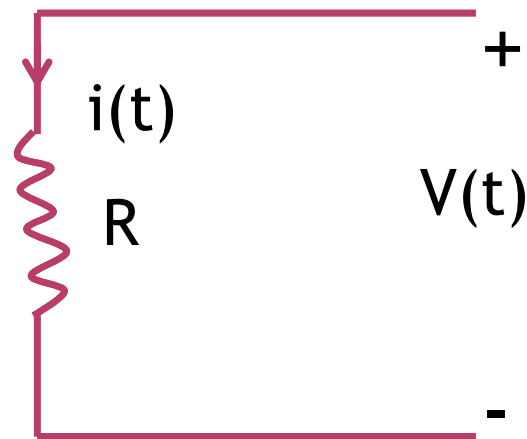

CAPACITOR

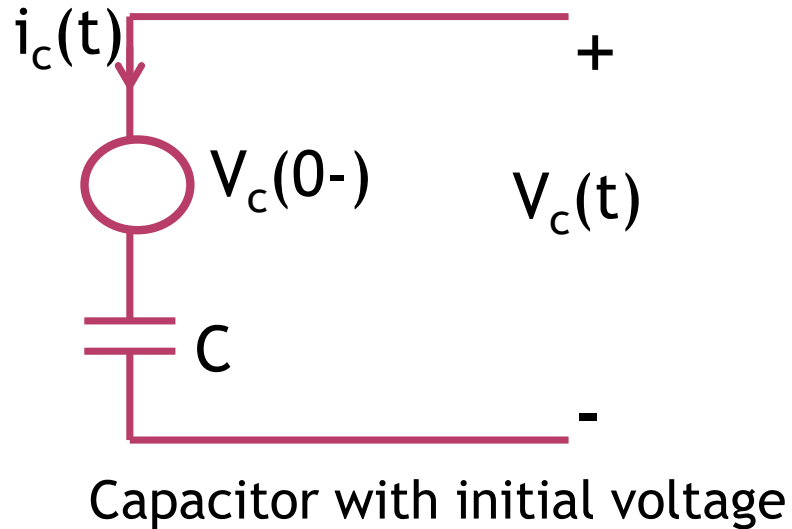
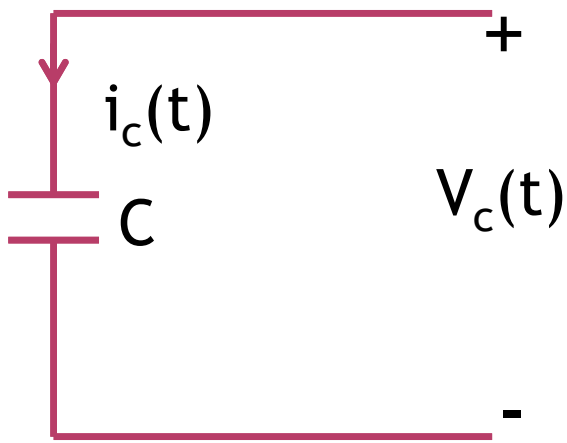


$$i_c(t) = C \frac{dV_c(t)}{dt}$$

$$i_c(t) = \frac{1}{C} \int_{0^-}^t i_c(t) dt + V_c(0^-)$$

$V_c(0^-)$ is the initial value of voltage across the capacitor just before the switching action

INDUCTOR

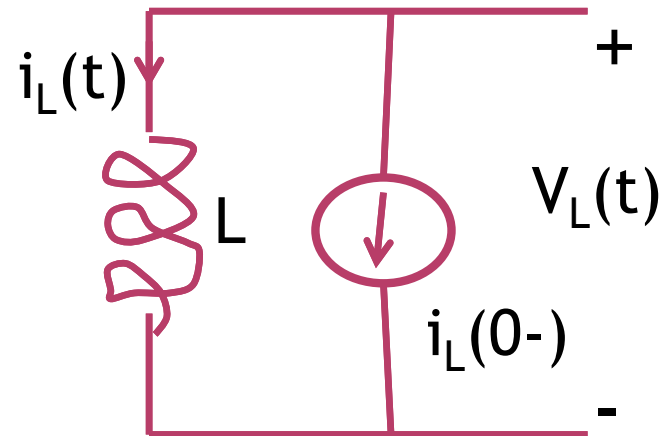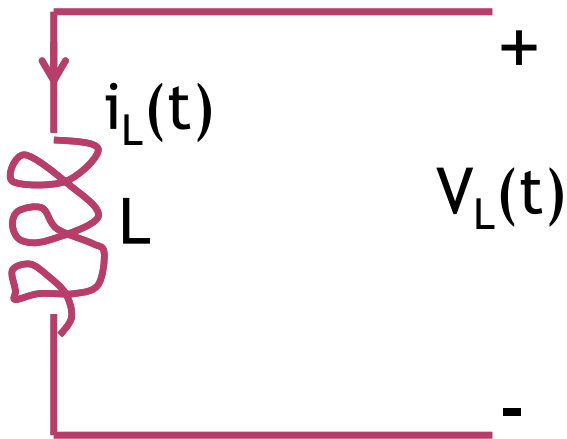

Inductor with initial Current

$$V_L(t) = L \frac{di_L(t)}{dt}$$

$$i_L(t) = \frac{1}{L} \int_{0^-}^t V_L(t) dt + i_L(0^-)$$

$i_L(0^-)$ is the initial value of current through the inductor just before the switching action

TRANSIENT RESPONSE:

- for t between 0 and T
- Means short living
- Value of voltage and current during the transient period are known as the transient responses
- Part of the total time response that goes to zero as time become large.

STEADY STATE RESPONSE

- Value of voltage and current after the transient has died out are known as steady state response
- Part of total time response which remains after the transient has passed
- Total response of a network is the sum of the transient response and a steady state response

ZERO INPUT RESPONSE

- Value of voltage and current that result from initial conditions when the excitation (input) is zero


ZERO STATE RESPONSE

- Value of voltage and current for an excitation which is applied when all initial condition are zero
- Also called rest or initially relaxed network


STEP AND IMPULSE RESPONSE

- The value of voltage and current for the excitation signal $U(t)$ and $\delta(t)$ when all condition are zero.


Types of Circuit Excitation

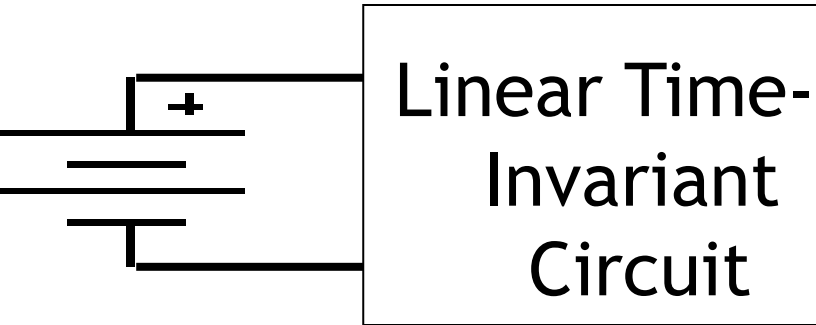

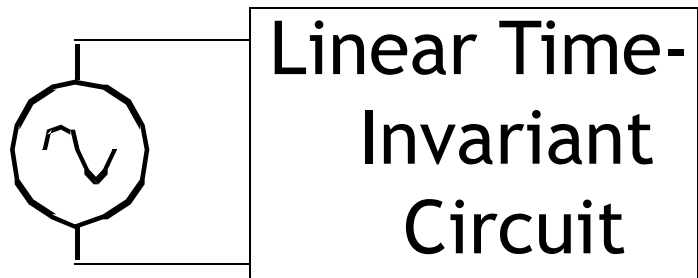
**Steady-State Excitation
(DC Steady-State)**



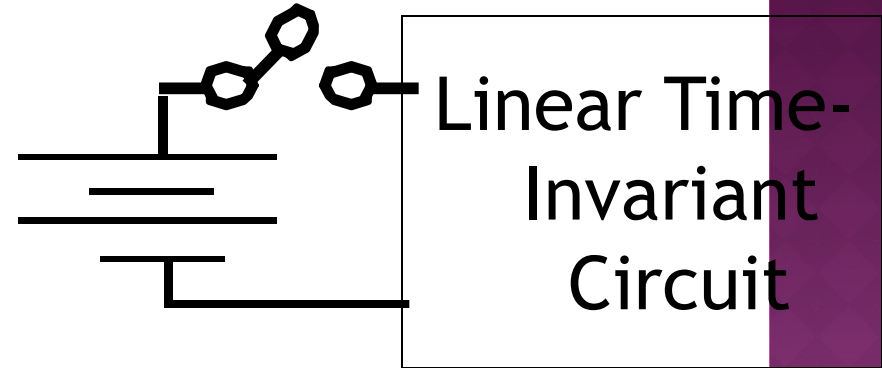**Sinusoidal (Single-Frequency) Excitation
→ AC Steady-State**





OR

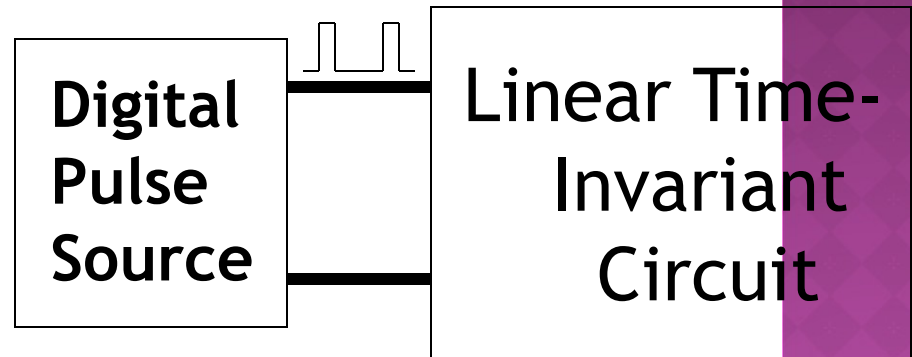

Transient Excitation


FIRST-ORDER CIRCUITS

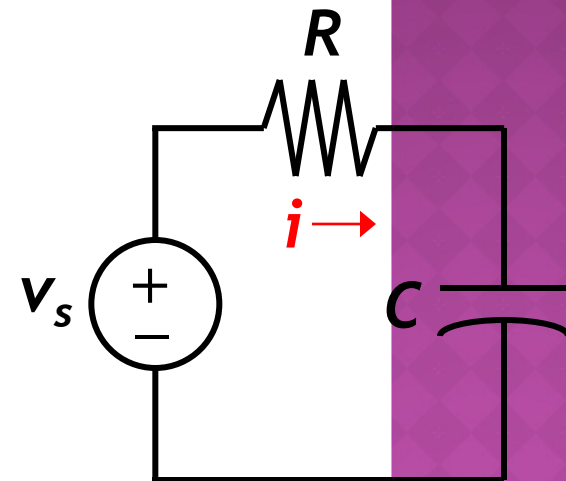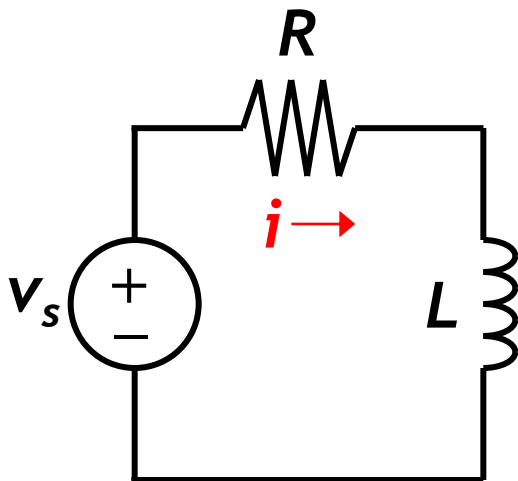- ⊙ A circuit that contains only sources, resistors and an inductor is called an *RL circuit*.
- ⊙ A circuit that contains only sources, resistors and a capacitor is called an *RC circuit*.
- ⊙ RL and RC circuits are called first-order circuits because their voltages and currents are described by first-order differential equations.



REVIEW (CONCEPTUAL)

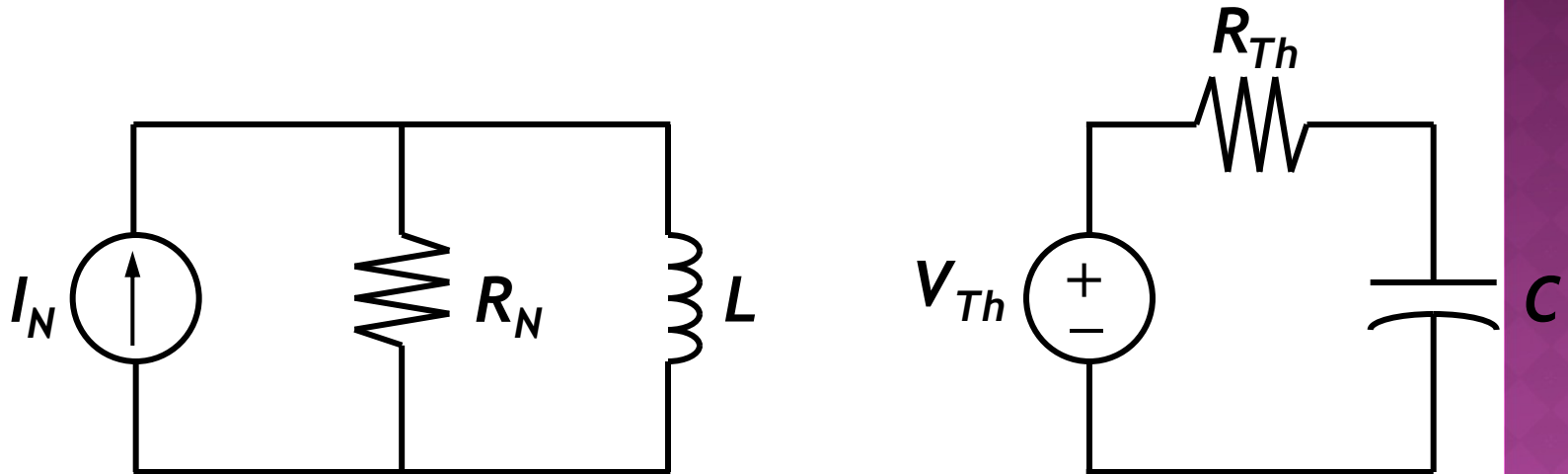- Any first-order circuit can be reduced to a Thévenin (or Norton) equivalent connected to either a single equivalent inductor or capacitor.



- In steady state, an inductor behaves like a short circuit
- In steady state, a capacitor behaves like an open circuit

- ⦿ The *natural response* of an RL or RC circuit is its behavior (*i.e.*, current and voltage) when stored energy in the inductor or capacitor is released to the resistive part of the network (containing no independent sources).
- ⦿ The *step response* of an RL or RC circuit is its behavior when a voltage or current source **step** is applied to the circuit, or immediately after a switch state is changed.